

$$- \mathcal{L}^{-1} \left[ \frac{1}{s} \times \frac{1/\beta}{1 + s/\omega_p'} \right]$$

$$\mathcal{L} \left[ \int_0^t f(t) \right] = \frac{1}{s} \mathcal{L} f(t)$$


$$\mathcal{L}^{-1} \left[ \frac{1/\beta}{1 + s/\omega_p'} \right] = \mathcal{L}^{-1} \left[ \frac{\omega_p'/\beta}{s + \omega_p'} \right]$$

$\downarrow$   
 $A_0 \beta \omega_p$

$$= \frac{\omega_p'}{\beta} e^{-\omega_p' t}$$

$$\int_0^t \frac{\omega_p'}{\beta} e^{-\omega_p' t} dt = \left[ \frac{\omega_p'}{\beta} \left( -\frac{1}{\omega_p'} \right) e^{-\omega_p' t} \right]_0^t$$
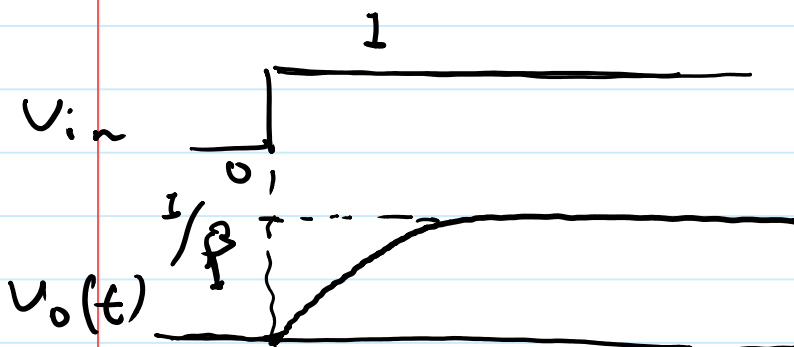
$$v_o(t) = \frac{1}{\beta} \left[ 1 - e^{-\omega_p' t} \right]$$



time constant

$$\tau = \frac{1}{\omega_p'}$$

if  $\beta < 0$  or -ve


Pole  $w_p'$  is shift to R.H.P and system becomes unstable

Conclusion

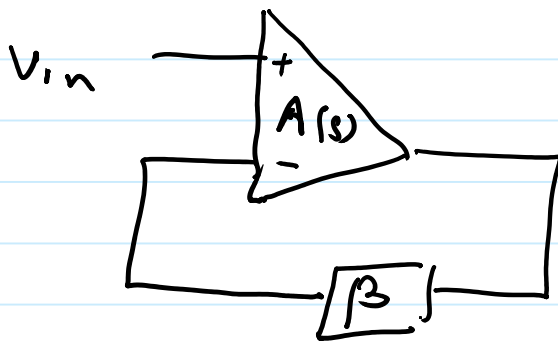
1. Stability of a negative feedback system can be analyzed using loop gain transfer function

$$H(s) = \frac{A}{1 + A\beta}$$

Loop Gain =  $A\beta$   
or open loop gain




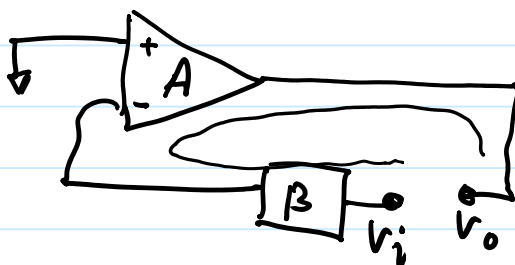In order to find Loop gain T.F. we need to break the feedback and set  $V_{in} = 0$



$$\frac{V_o(s)}{V_i(s)} = H_{LG}(s) = -\beta A(s)$$

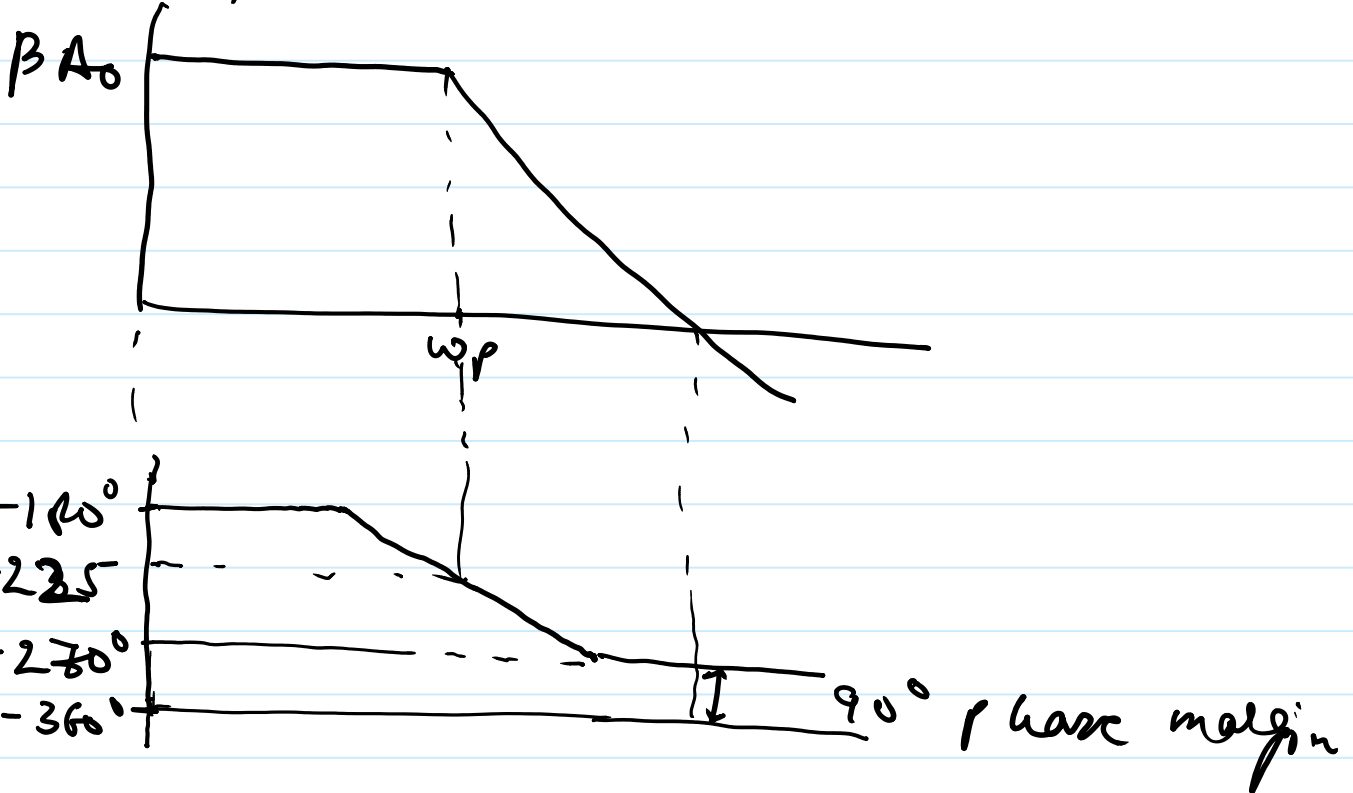
Once we get the L.C T.F. we plot magnitude and Phase response and find the Phase margin



Phase margin is the distance to  $180^\circ$  additional phase shift or distance to  $360^\circ$  total phase shift.

we also use gain margin for stability  
 Gain at 180° phase shift.

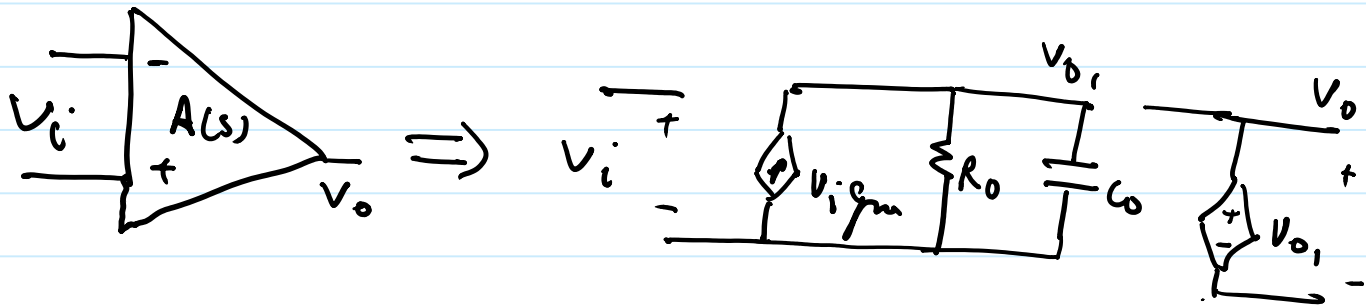- First order system with negative feedback is inherently stable as long as  $\beta > 0$



first order or single stage model of op-amp.

$$A_0 = g_m R_o$$

$g_m$  &  $R_o$  comes from transistor.




Transistor have some limitations on  $g_m R_o$  and usually single stage can't achieve  $> 100$

or 400B

most of the applications require gain of  $> 60\text{dB}$  or  $1000$  which can't be achieved with single stage.

we need two stage amplifier

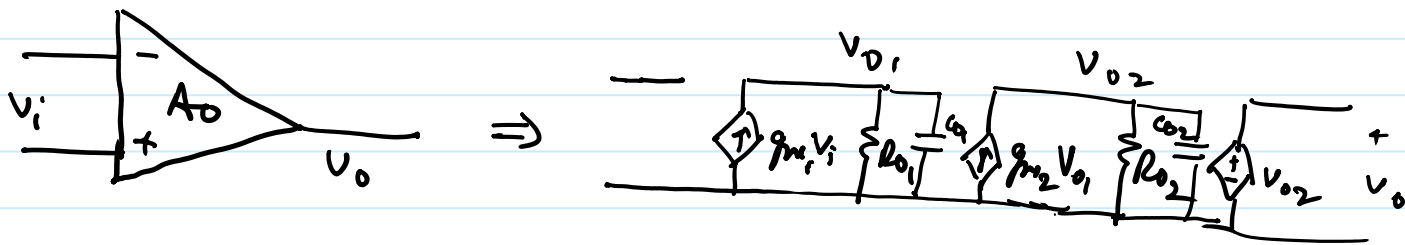

$$A_o = g_{m1} R_{o1} \cdot g_{m2} R_{o2}$$

$$g_{m1} R_{o1} = g_{m2} R_{o2} = 100$$

$$A_o = 10^4 = 80\text{dB}$$

capacitors  $C_{o1}$  &  $C_{o2}$  introduce two poles in op-amp

$$\omega_{p1} = \frac{1}{R_{o1} C_{o1}}, \quad \omega_{p2} = \frac{1}{R_{o2} C_{o2}}$$

$$A(s) = \frac{g_{m1} R_{o1} g_{m2} R_{o2}}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$