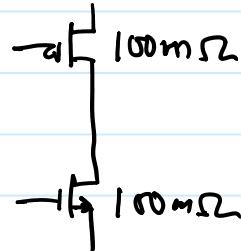



Segmented Power FETs

$P_{\text{sw}} = \frac{V^2}{R} f$


in PFM we reduce f_{sw} to get high η



segmented FET

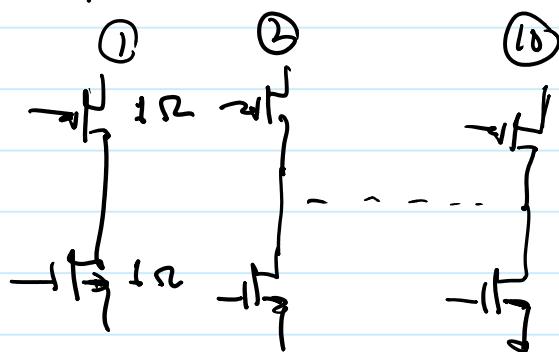


$N \rightarrow$ depend upon Z_{load}


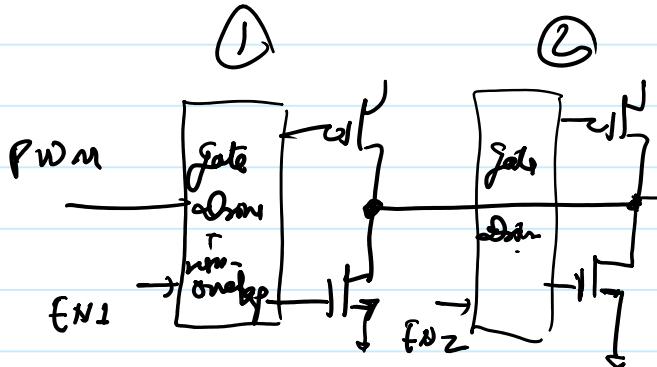


PSM and PFM Mode


PSM → Pulse Skip Mode

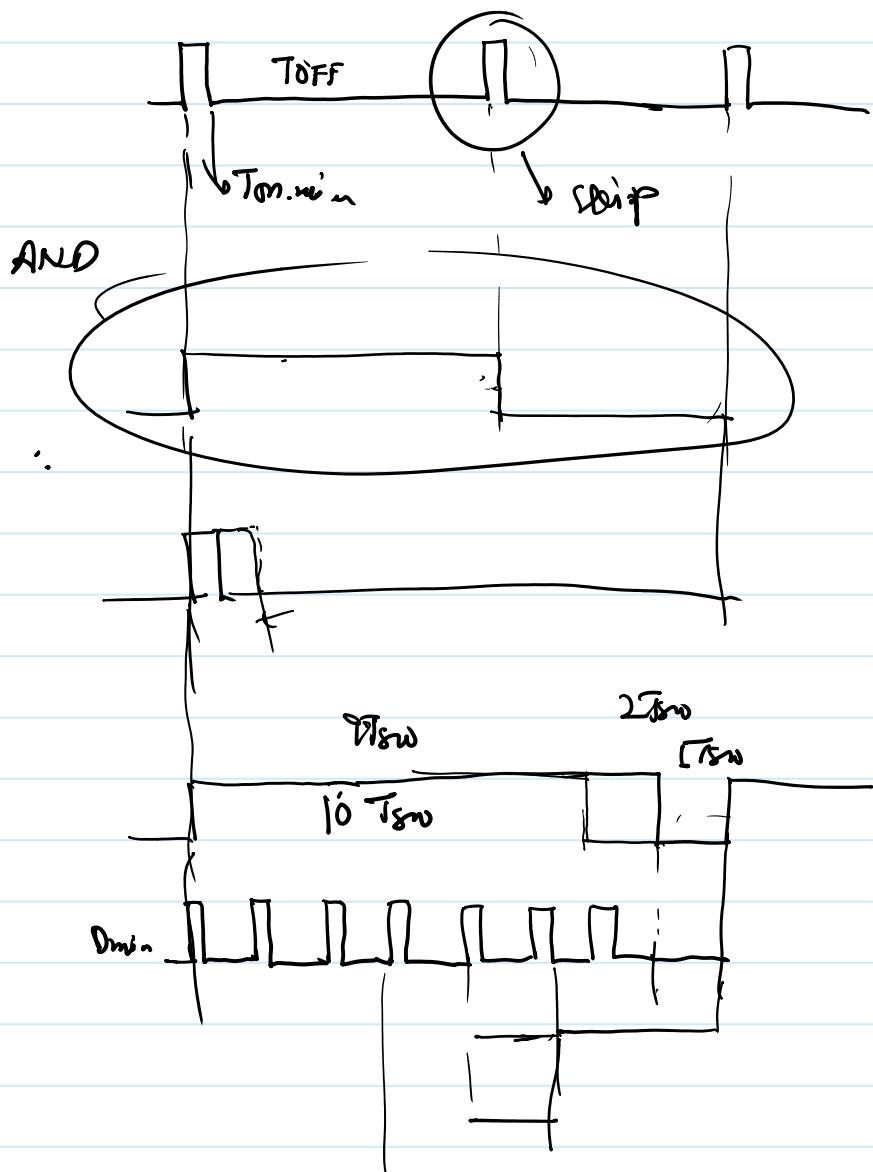

PFM Mode

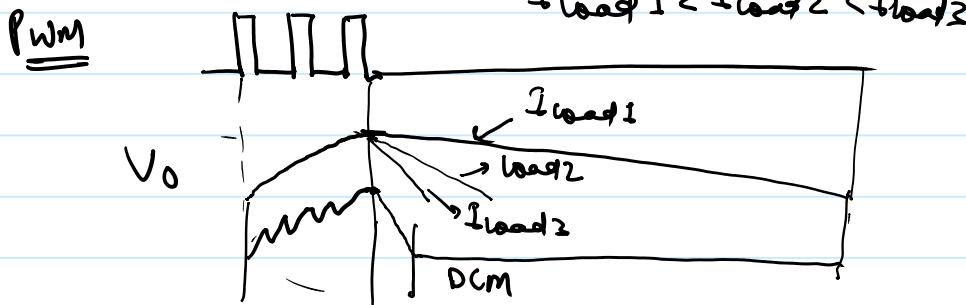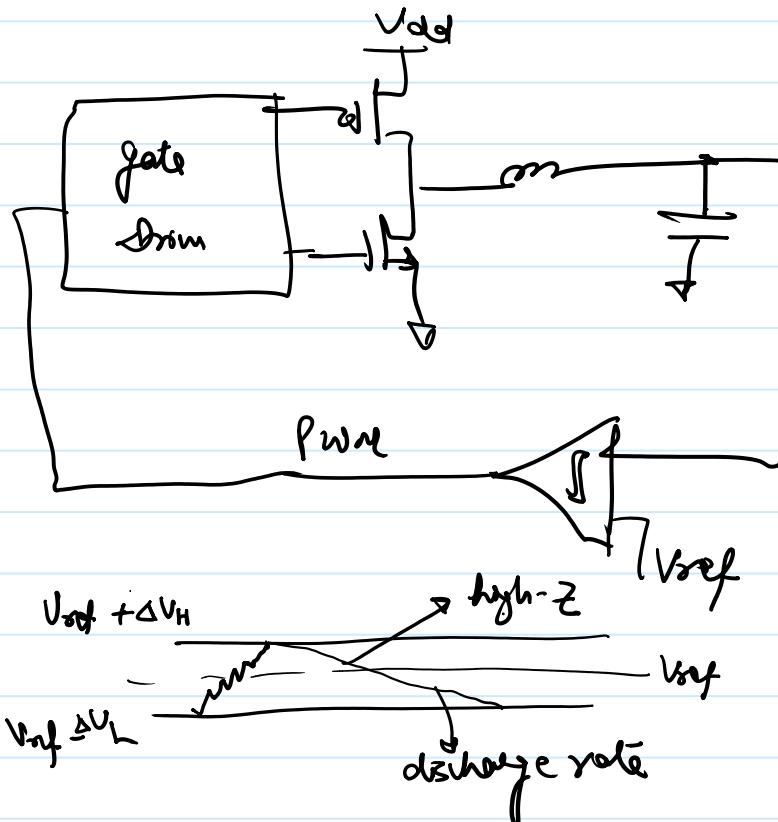


Exiting PFM Mode

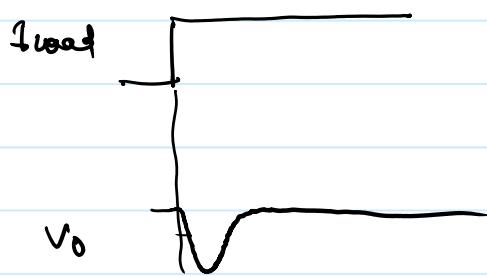

- ① V_o is regulated at slightly higher voltage (droop compensation)
 Exit PFM mode and enter PWM mode if $V_o < \beta V_{ref}$.
 or $V_{FB} < V_{REF}$

In PFM, regulate V_o at $V_o + \Delta V$

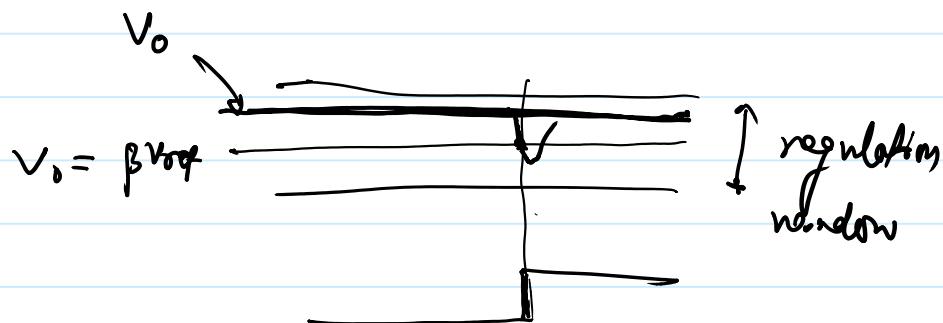

- ② Output of Zero cross comparator (ZCD) can also be used to exit PFM mode as converter will operate in CCM in case of high load.

