

EE2019: Analog Systems and Lab

Course summary

Aniruddhan S
Qadeer Ahmad Khan
Saurabh Saxena

<https://courses.iitm.ac.in>

Department of Electrical Engineering
Indian Institute of Technology, Madras
Chennai, 600036, India

26 April 2019


Time domain

- Step response
- Initial/final values and time-constants

Frequency domain




- Transfer function, poles and zeros
- Sinusoidal steady-state response; Bode plots

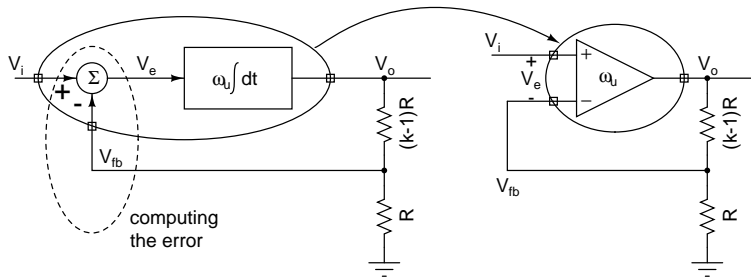Negative feedback amplifier and the opamp



- Infinite gain model
- Virtual short with negative feedback
- Finding opamp signs for negative feedback

Biasing opamp circuits

   

- Opamp saturation and offset
- Single and dual supply operation
- AC coupling

Opamp characteristics



August 2000

LF147/LF347

Wide Bandwidth Quad JFET Input Operational Amplifiers

General Description

The LF147 is a low cost, high speed quad JFET input operational amplifier with an internally trimmed input offset voltage (BI-FET II™ technology). The device requires a low

Features

- Internally trimmed offset voltage: 5 mV max
- Low input bias current: 50 pA
- Low input noise current: 0.01 pA/√Hz




DC Electrical Characteristics (Note 7)

Symbol	Parameter	Conditions	LF147			LF347B			LF347		Units	
			Min	Typ	Max	Min	Typ	Max	Min	Typ		Max
V_{OS}	Input Offset Voltage	$R_B=10\text{ k}\Omega$, $T_A=25^\circ\text{C}$ Over Temperature		1	5		3	5	5	10	mV	
					8			7		13	mV	
$\Delta V_{OS}/\Delta T$	Average TC of Input Offset Voltage	$R_B=10\text{ k}\Omega$		10			10		10		$\mu\text{V}/^\circ\text{C}$	
I_{OS}	Input Offset Current	$T_I=25^\circ\text{C}$, (Notes 7, 8) Over Temperature		25	100		25	100	25	100	pA	
					25			4		4	nA	
I_B	Input Bias Current	$T_I=25^\circ\text{C}$, (Notes 7, 8) Over Temperature		50	200		50	200	50	200	pA	
					50			8		8	nA	
R_{IN}	Input Resistance	$T_I=25^\circ\text{C}$		10^{12}			10^{12}		10^{12}		Ω	
A_{VOL}	Large Signal Voltage Gain	$V_S=\pm 15\text{V}$, $T_A=25^\circ\text{C}$ $V_O=\pm 10\text{V}$, $R_L=2\text{ k}\Omega$ Over Temperature	50	100		50	100		25	100	V/mV	
				25			25		15		V/mV	
V_O	Output Voltage Swing	$V_S=\pm 15\text{V}$, $R_L=10\text{ k}\Omega$	± 12	± 13.5		± 12	± 13.5		± 12	± 13.5	V	
V_{CM}	Input Common-Mode Voltage Range	$V_S=\pm 15\text{V}$	± 11	+15 -12		± 11	+15 -12		± 11	+15 -12	V	
CMRR	Common-Mode Rejection Ratio	$R_S\leq 10\text{ k}\Omega$	80	100		80	100		70	100	dB	
PSRR	Supply Voltage Rejection Ratio (Note 9)		80	100		80	100		70	100	dB	
I_S	Supply Current			7.2	11		7.2	11		7.2	11	mA

Source: www.ti.com/lit/ds/symlink/lf147.pdf





Stability of negative feedback circuits

   


- Stability criterion—Loop gain and phase margin
- Dominant pole compensation
- 2-stage Miller compensated opamp


Opamp examples: LM324, LF147

  

Open Loop Frequency Response

 


Bode Plot

 


Source: www.ti.com/lit/gpn/lm124, www.ti.com/lit/ds/symlink/lf147.pdf

- Passive RLC filters
- State-variable filter: Emulate equations of RLC filters using integrators
- Sallen-Key, Rauch filters, . . .


Filters

 


Series RLC lowpass filter

 


Parallel RLC bandpass filter

 

Opamp-RC biquadratic filter

 


Sallen-Key lowpass filter

 

Rauch lowpass filter

- LC resonant network compensated by a negative conductance
- Wien bridge oscillator
- Schmitt trigger oscillator

Data converters

 

Sampling

- Track and Hold (T/H), Sample and Hold (S/H)

Analog-to-digital conversion


- Flash ADC for high speed and low resolution
- SAR ADC for low speed and high resolution

Digital-to-analog conversion

- Resistor DAC: Resistor string, R-2R, binary weighted
- Binary weighted capacitor DAC (Suited for SAR ADCs)

Source: www.maximintegrated.com/en/app-notes/index.mvp/id/1080

DC-DC converters

 

$$L(s) = \frac{a}{sC_c R_c} \frac{V_s}{V_r} \frac{1}{s^2 LC + sL/R + 1}$$

Steady state $V_o = V_{ref}/a$

- DC-DC buck converter
- Average model from duty cycle to the output
- Voltage regulation loop and its stability

Acknowledgments: Army of TAs