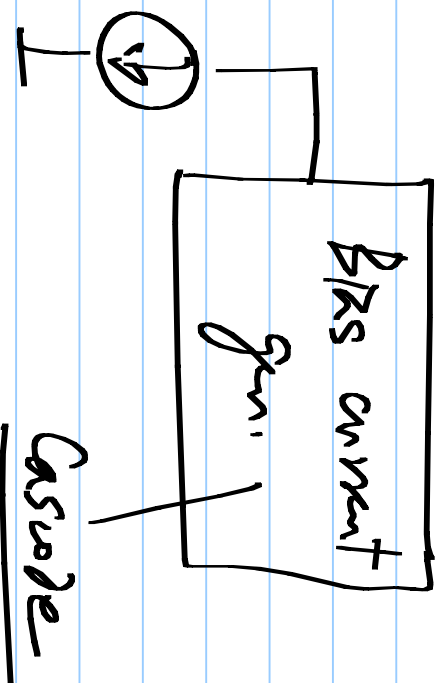



Lecture 19

29/2/2016


Cascode - Improves the output resistance
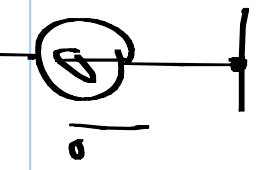
$$r_{ds} = \frac{1}{\lambda I_D} ; \lambda = \frac{k_n}{L} \quad \left[ \uparrow \rightarrow \text{increase } r_{ds} \right]$$





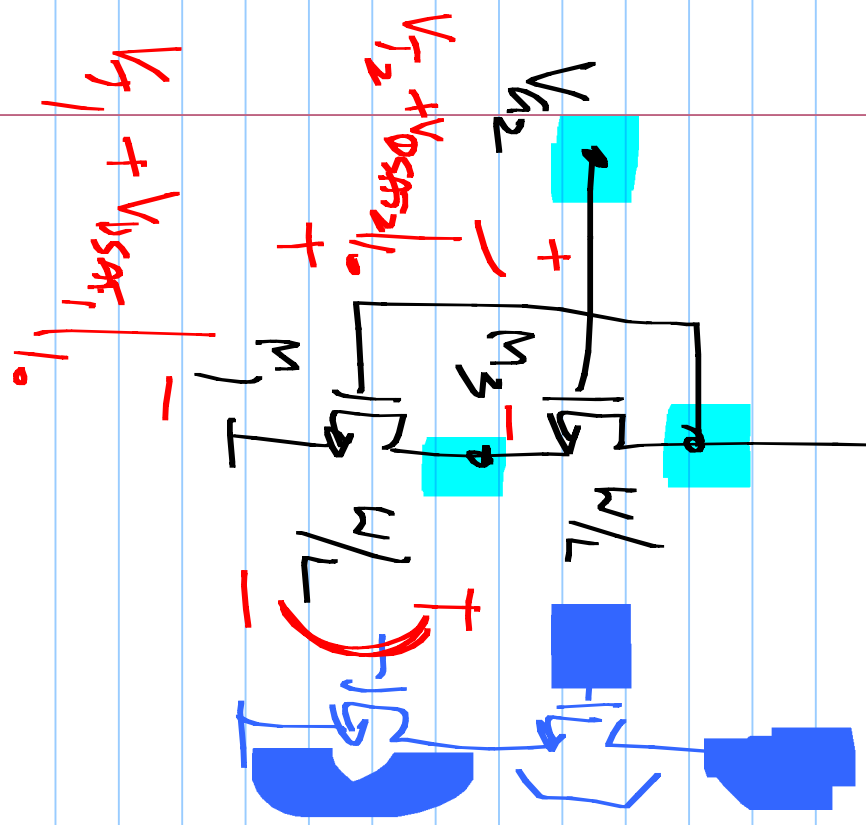$V_{A2}$  : both  $M_1, M_3$  are in -ve feedback




$I_{D1}, I_{D2}, I_{D3}, I_{D4}$   $M_n C_{ox}$   $2\mu + V_{DSAT}$

$$V_{A2} < V_T + V_{DSAT1} + V_{T2}$$


$$V_{A2} > V_{DSAT1} + V_{T2} + V_{DSAT2}$$

$$V_T + 2V_{DSAT}$$

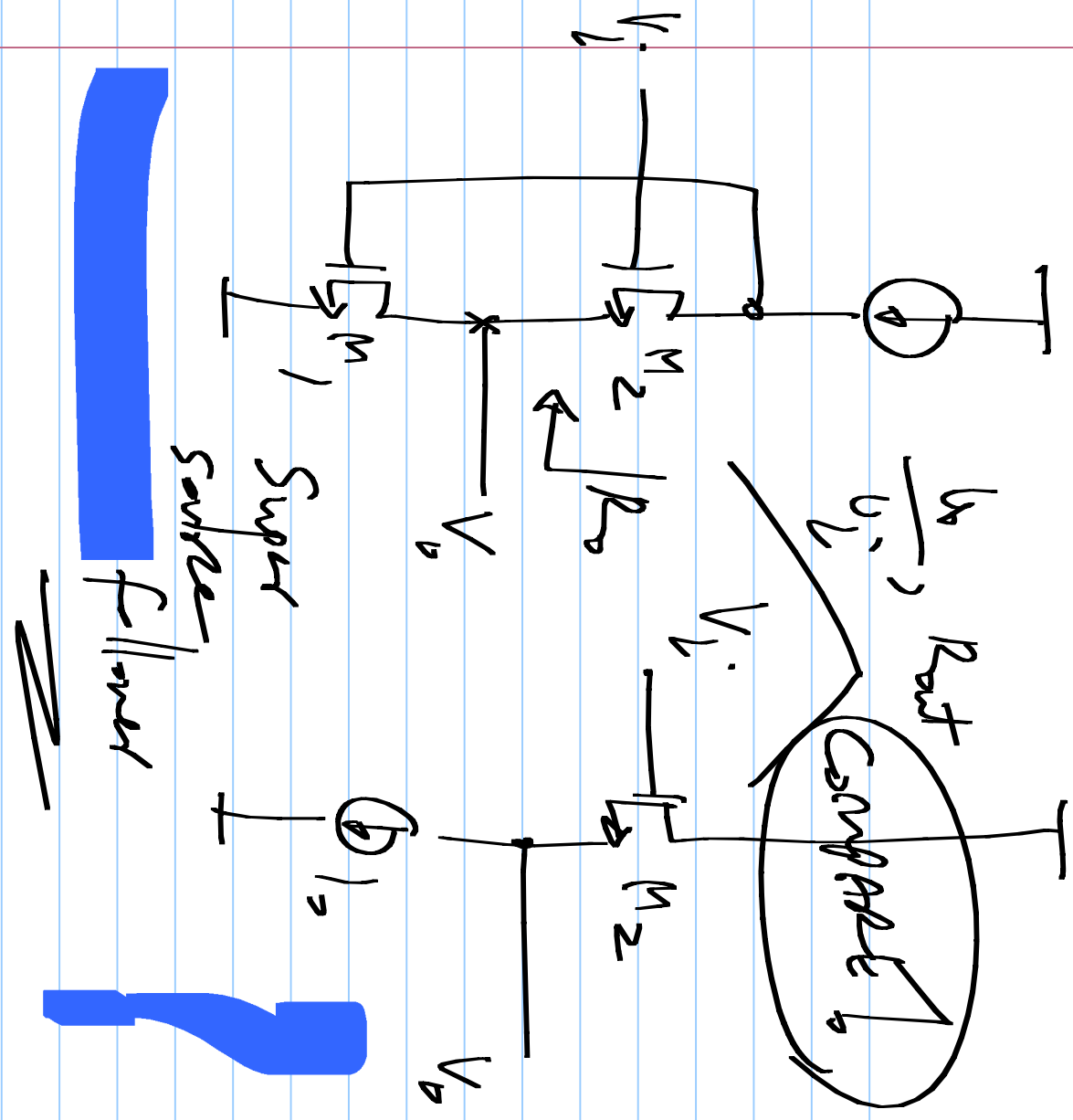

# Single stage opmp:

$$G_m = g_{m1}$$

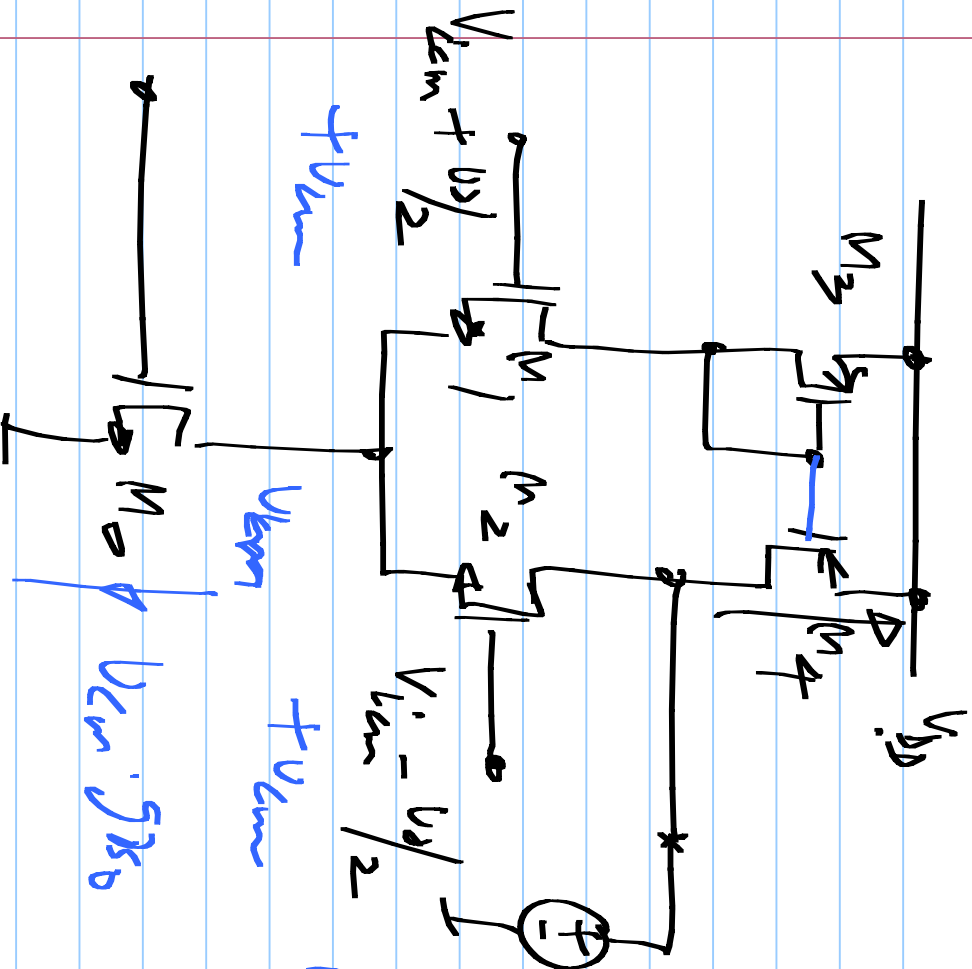

$$G_{out} = g_{m3} + g_{m2}$$

$$A_v =$$

$$\frac{g_{m1}}{g_{m3} + g_{m2}}$$


$$A_{cm} = \frac{g_{m5,6}}{2}$$


$$g_{m3}$$

$$g_{m2} V_{ds2} R_s + V_{ds2} + R_s$$

$$R_s = \frac{1}{g_{m1}}$$

~~$$2V_{ds2} + \frac{1}{g_{m1}}$$~~

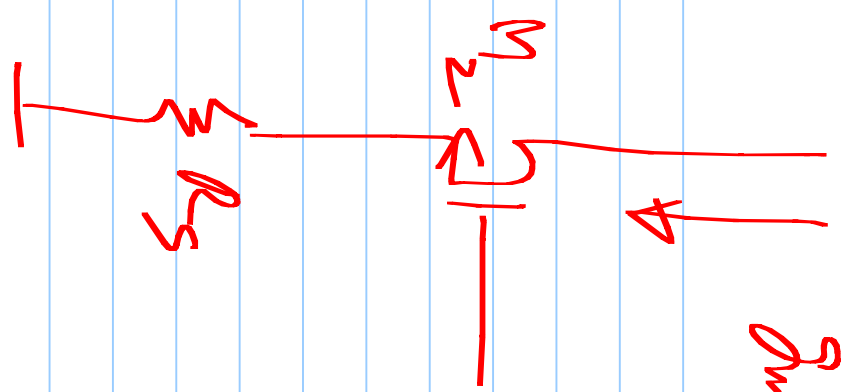

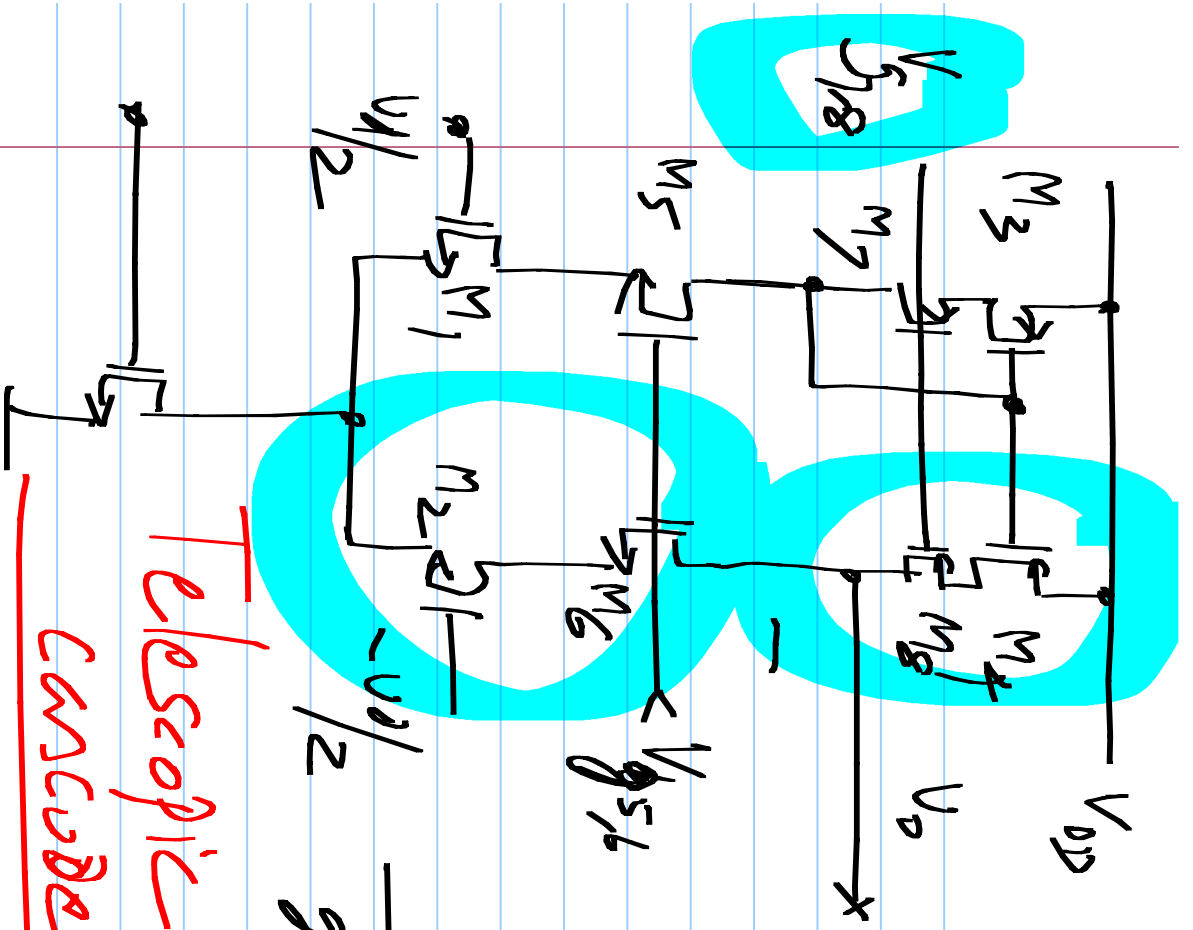


$$A_{v0} = \frac{V_o}{V_i} = \frac{g_{m1}}{g_{m5} + \frac{g_{m1} g_{m3} g_{m7}}{g_{m5}}}$$



$$g_{m3} \rightarrow \frac{g_{m3} \cdot g_{m7}}{g_{m7}}$$


$$\frac{g_{m1}}{g_{m5} + g_{m3}} \sim \frac{g_{m1}}{g_{m5}}$$

$$\left( \frac{g_{m1}}{g_{m5}} \right)^2$$

Telescopic  
Cascode

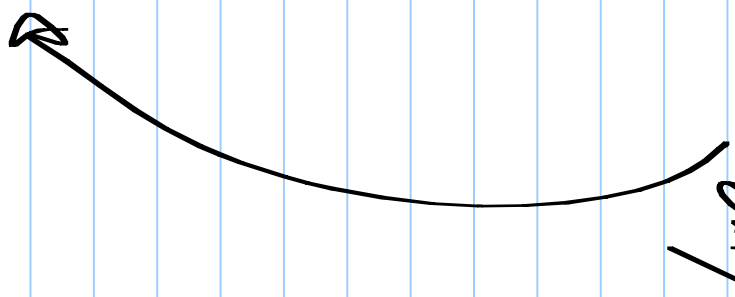

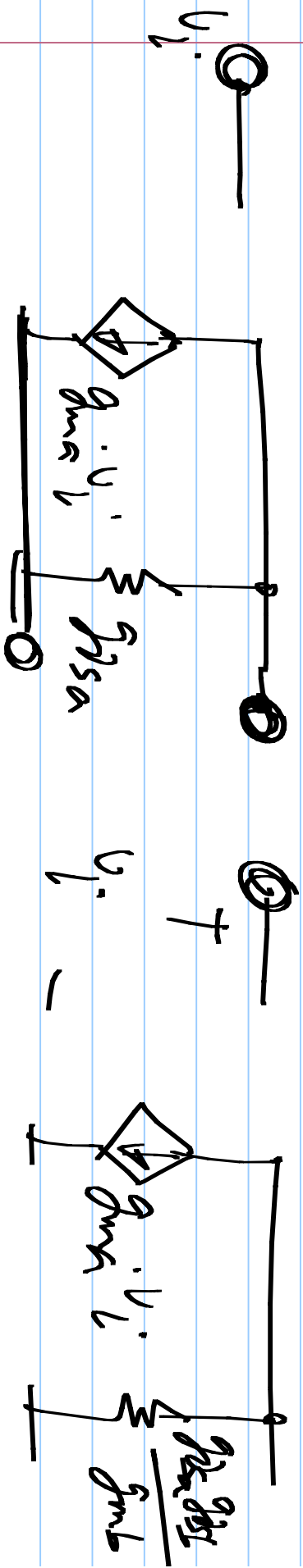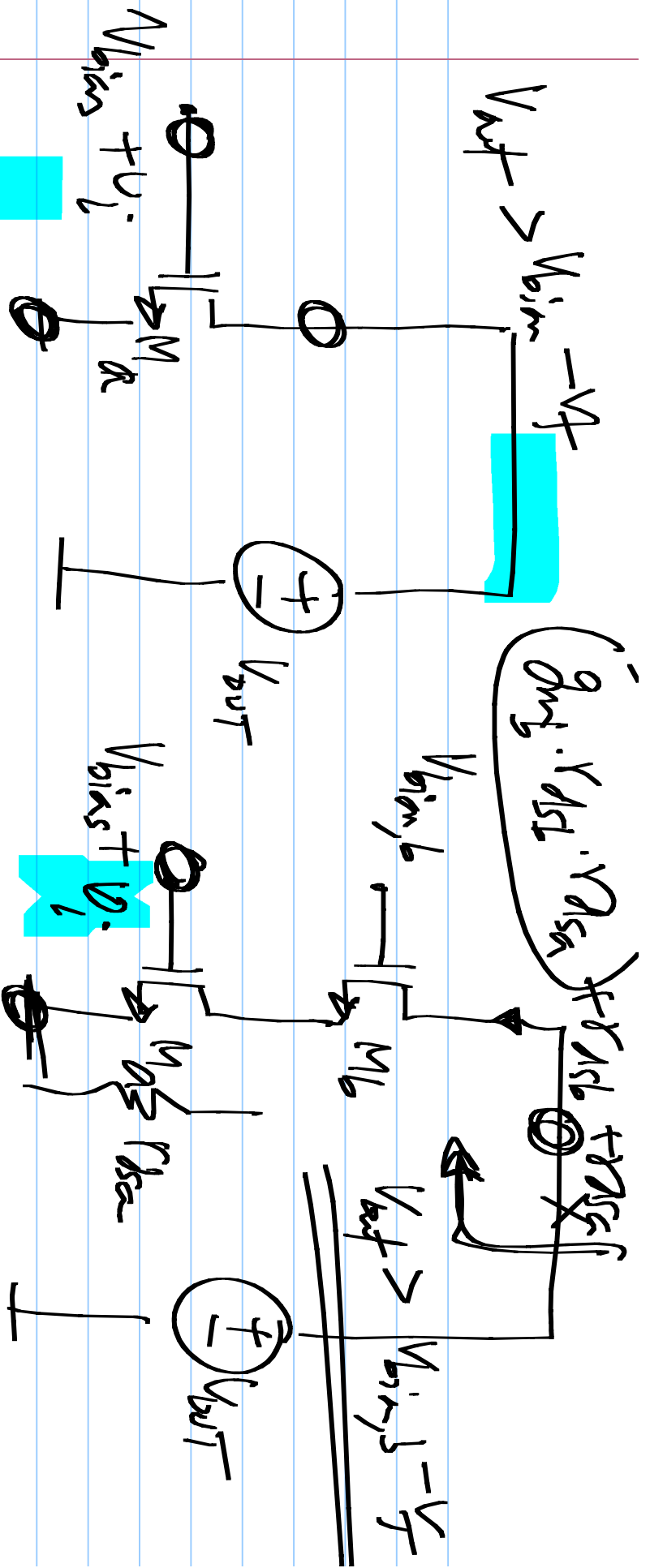

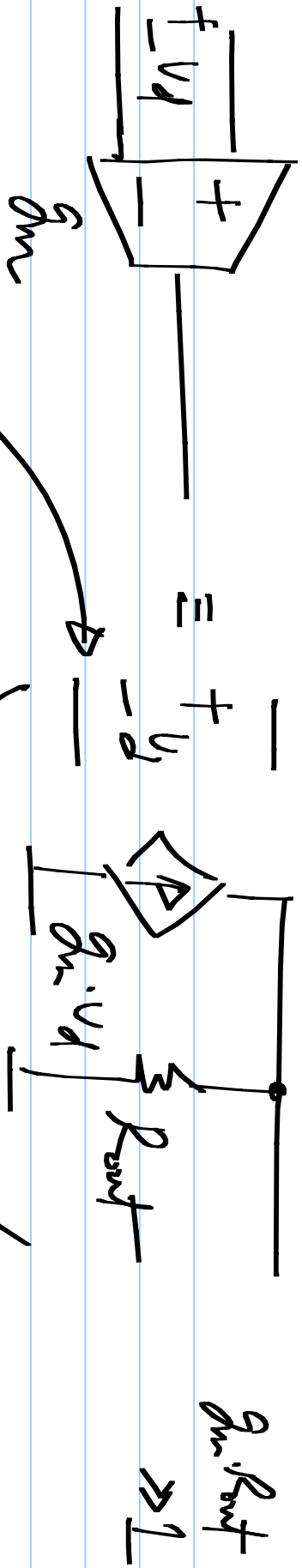

$V_i(t)$  Step response  $V_o(t)$

$\frac{V_o(s)}{V_i(s)}$  — Bode mag,  
 phase plots

