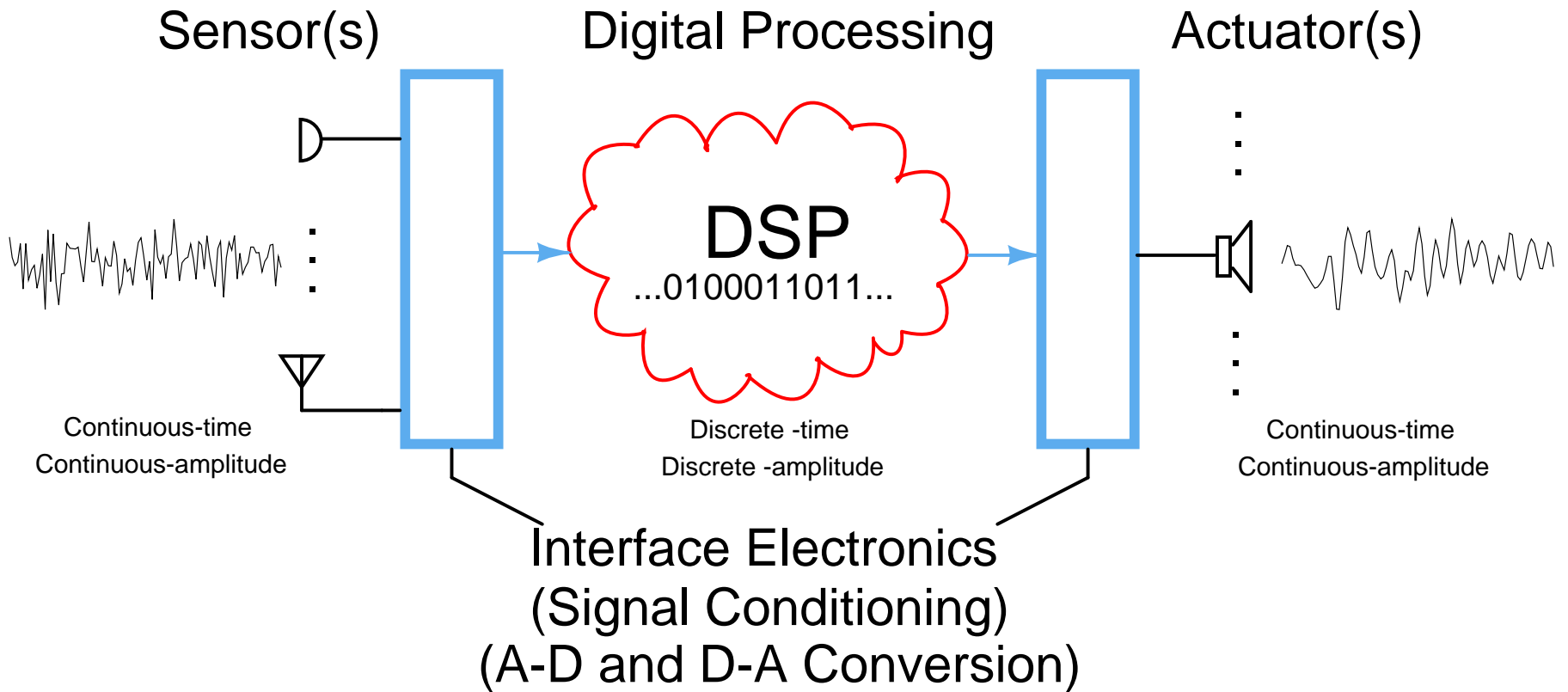


Digital and Analog Electronics for the Hobbyist

Electrofrolics
Shaastra 2010

Nagendra Krishnapura
Dept. of EE, IIT Madras
30th September 2010

Signal processing systems



Why digital?

Why digital?

- Digital levels less corrupted by noise
- Convenient storage
- Convenient signal processing

Why analog?

Why analog?

- Interface with the natural world
- Higher maximum speed of operation
- Analog to digital conversion
- Digital to analog conversion

Digital

Digital logic circuits

- Simple logic gates
- Complex logic gates
 - Encoders
 - Adders
- Storage elements
 - Latches
 - Flip flops
- Input and output interfaces


Digital logic-basic gates

- 7404 Inverter
- 7400(NAND), 7402(NOR)
- 7408(AND), 7432(OR)
- 7486: XOR gate

Digital logic-more complex blocks

- 74147: 10-Line to 4-Line Priority Encoder
- 74154: 4-Line to 16-Line Decoder
- 74273: 8 bit register with reset
- 7483: 4 bit full adder
- 7447 BCD to 7 segment decoder

Digital logic-encoder

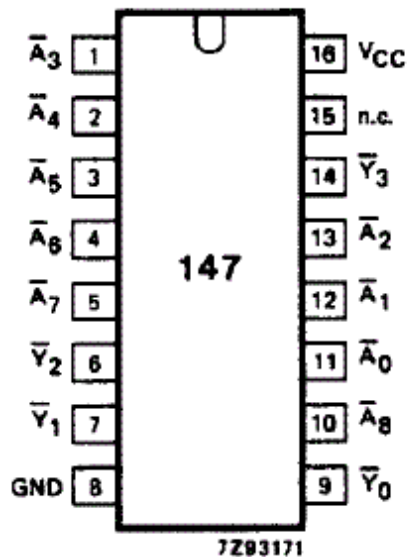

FUNCTION TABLE

INPUTS									OUTPUTS			
\bar{A}_0	\bar{A}_1	\bar{A}_2	\bar{A}_3	\bar{A}_4	\bar{A}_5	\bar{A}_6	\bar{A}_7	\bar{A}_8	\bar{Y}_3	\bar{Y}_2	\bar{Y}_1	\bar{Y}_0
H	H	H	H	H	H	H	H	H	H	H	H	H
X	X	X	X	X	X	X	X	L	L	H	H	L
X	X	X	X	X	X	X	L	H	L	H	L	H
X	X	X	X	X	X	L	H	H	H	L	L	H
X	X	X	X	L	H	H	H	H	H	L	H	L
X	X	L	H	H	H	H	H	H	H	H	L	L
X	L	H	H	H	H	H	H	H	H	H	L	H
L	H	H	H	H	H	H	H	H	H	H	H	L

Notes

1. H = HIGH voltage level
L = LOW voltage level
X = don't care

Figure reproduced from manufacturer's datasheet

Digital logic-adder (7483)


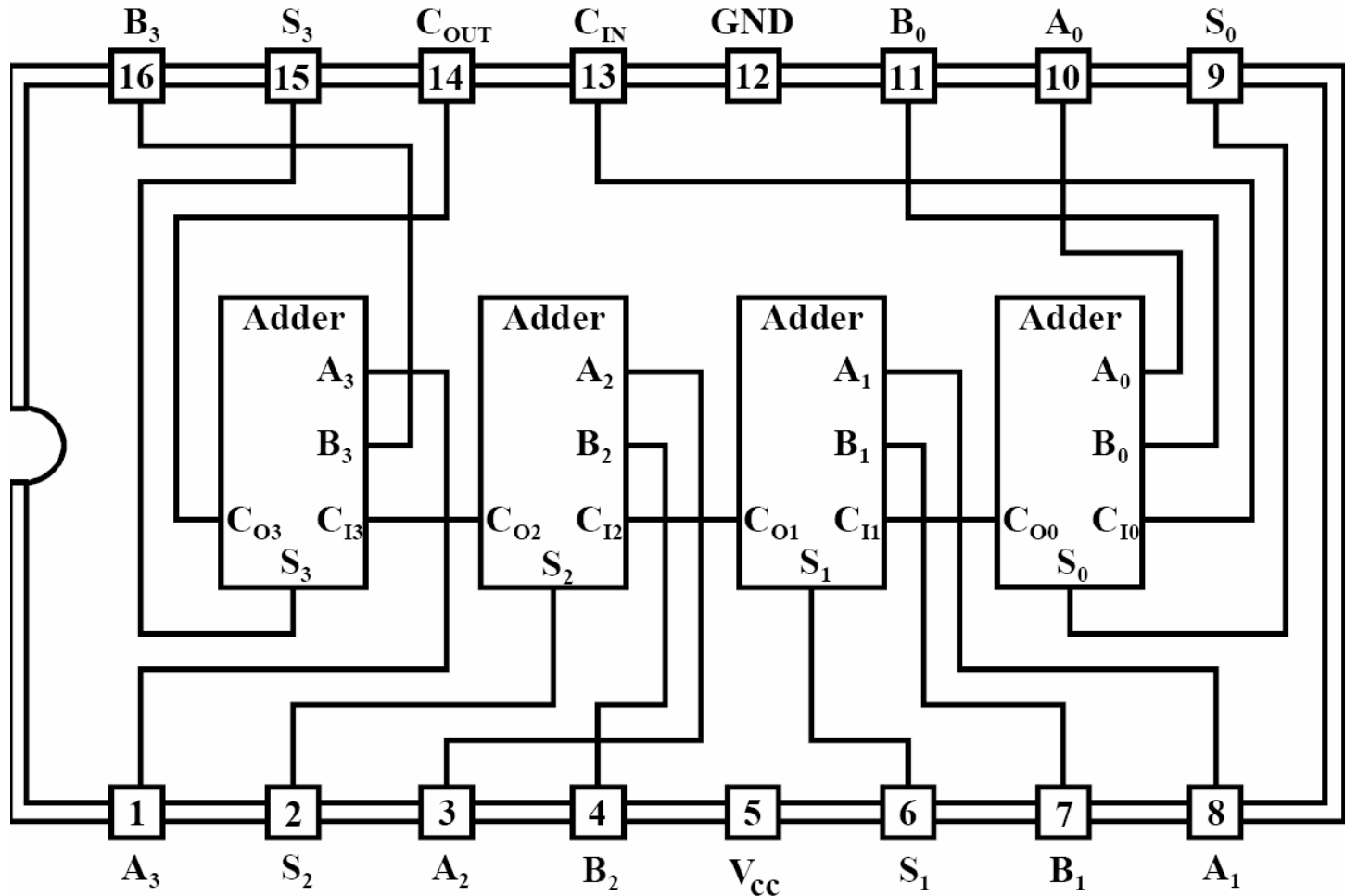


Figure reproduced from manufacturer's datasheet

Digital logic-storage

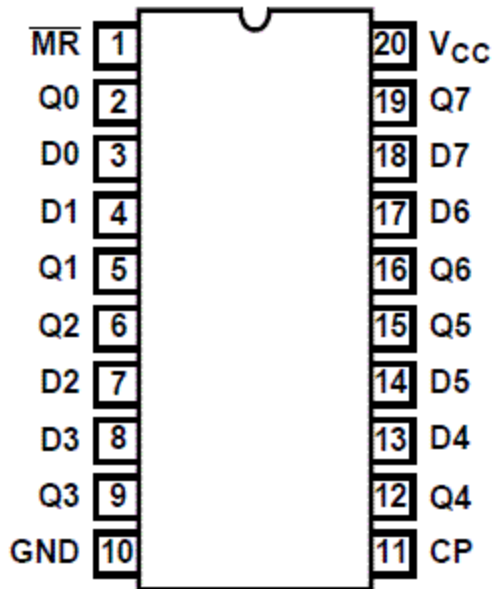





TRUTH TABLE

INPUTS			OUTPUT
RESET (MR)	CLOCK CP	DATA D _n	Q
L	X	X	L
H	↑	H	H
H	↑	L	L
H	L	X	Q ₀



NOTE: H = High Voltage Level, L = Low Voltage Level, X = Don't Care, ↑ = Transition from Low to High Level, Q₀ = Level Before the Indicated Steady-State Input Conditions Were Established.

Figure reproduced from manufacturer's datasheet



Human interface-input

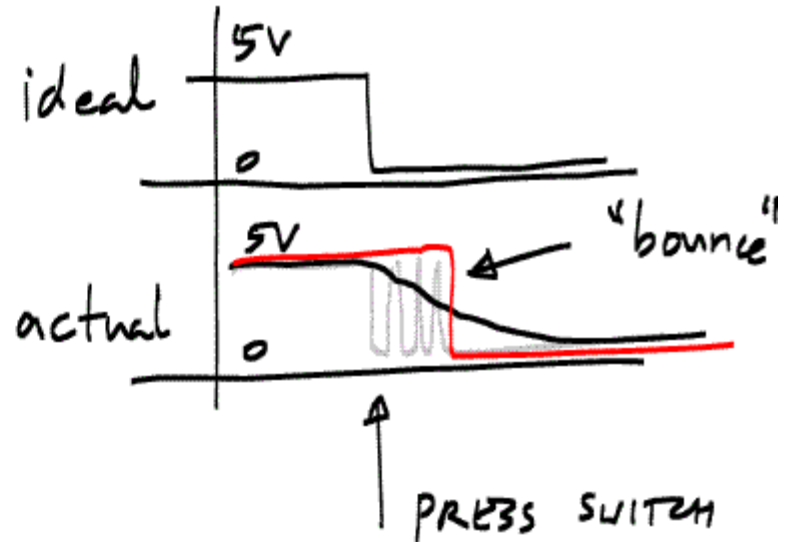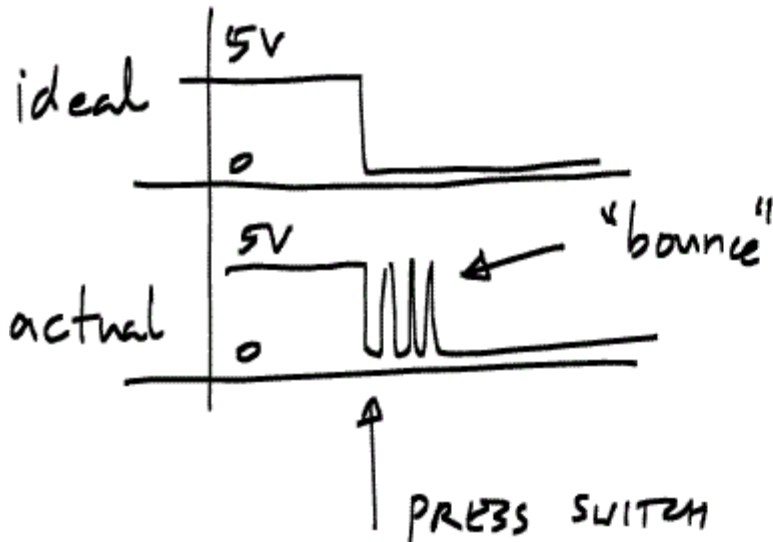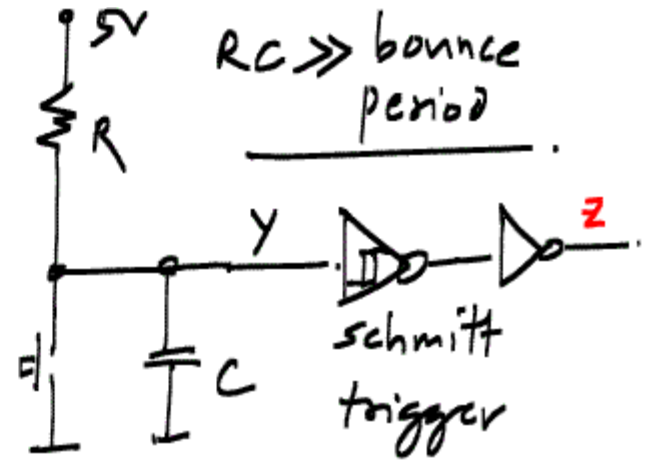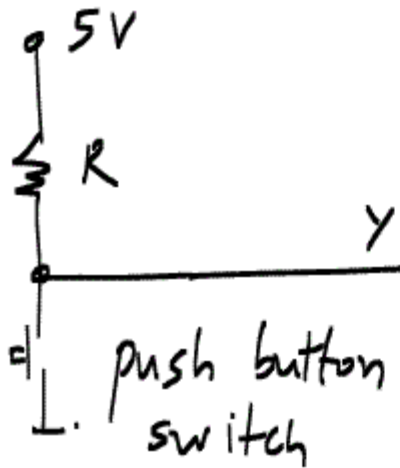

Human interface-input

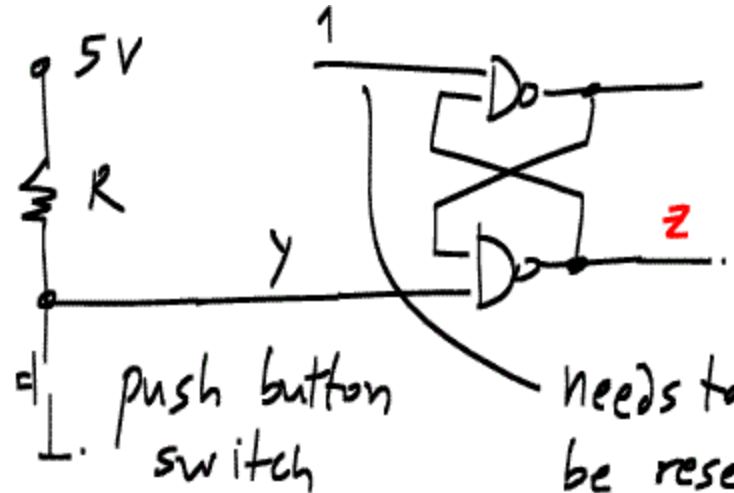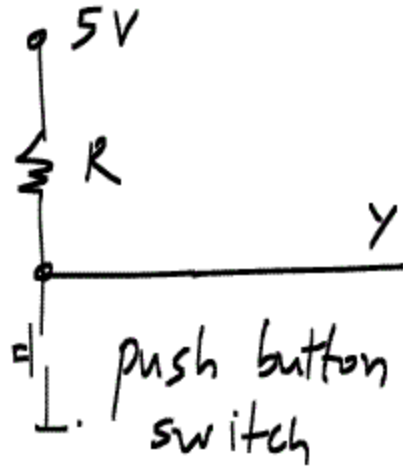


Needs to be reset before next key press

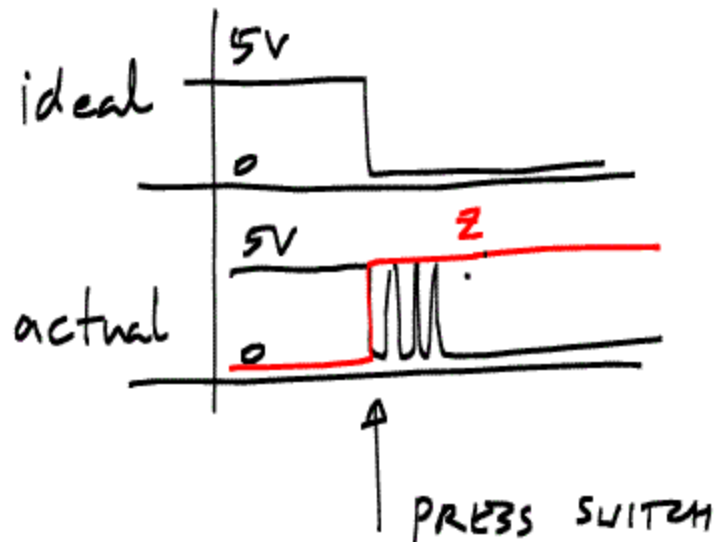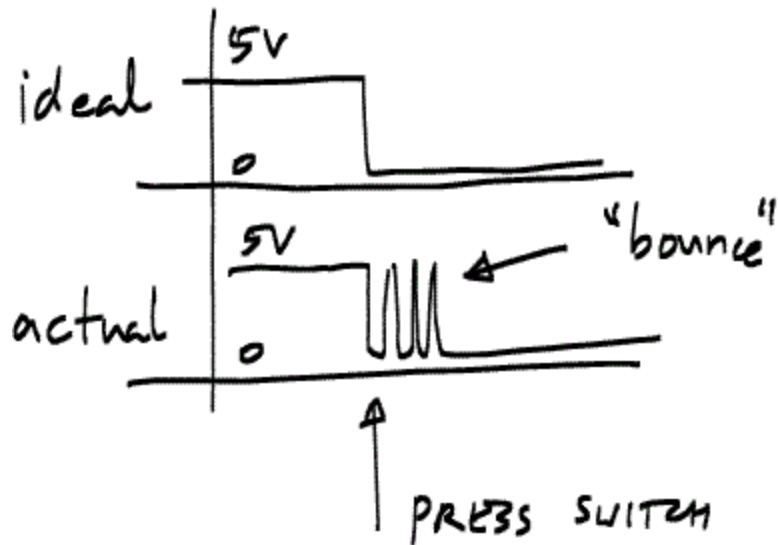



Human interface-output(display)



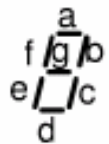
$V_F \sim 1.5 \dots 2V$
 $I_F \sim 1-10mA$;
 depends on the size



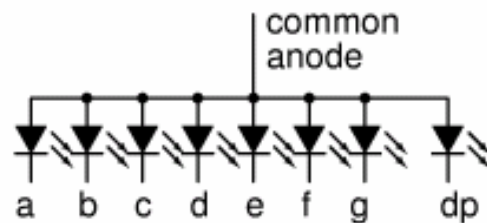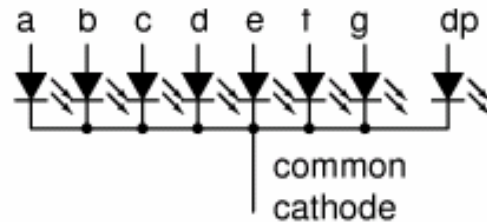
7 segment numeric display. may include decimal point



a) 7 segment display

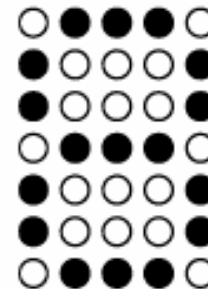


b) 5x7 array display

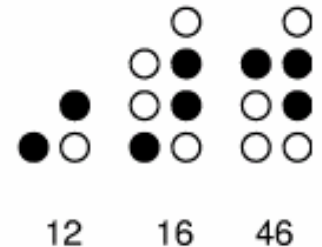

c) bcd display

- Display type: LED: bright / LCD: low power
- Interface type: 7 segment / dot matrix / anything else


Driving an LED

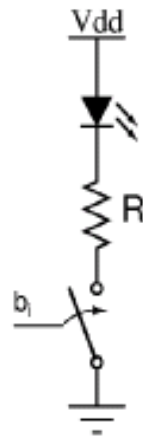


switch + current limiting resistor



current source drive

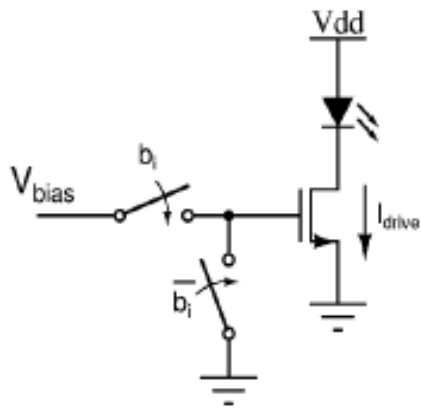


gate switching

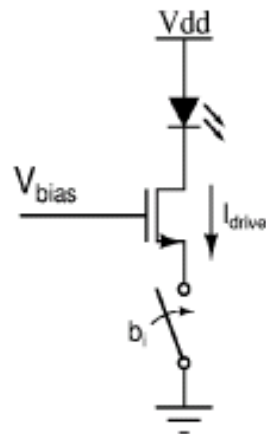


source switching

Driving a 7 segment display

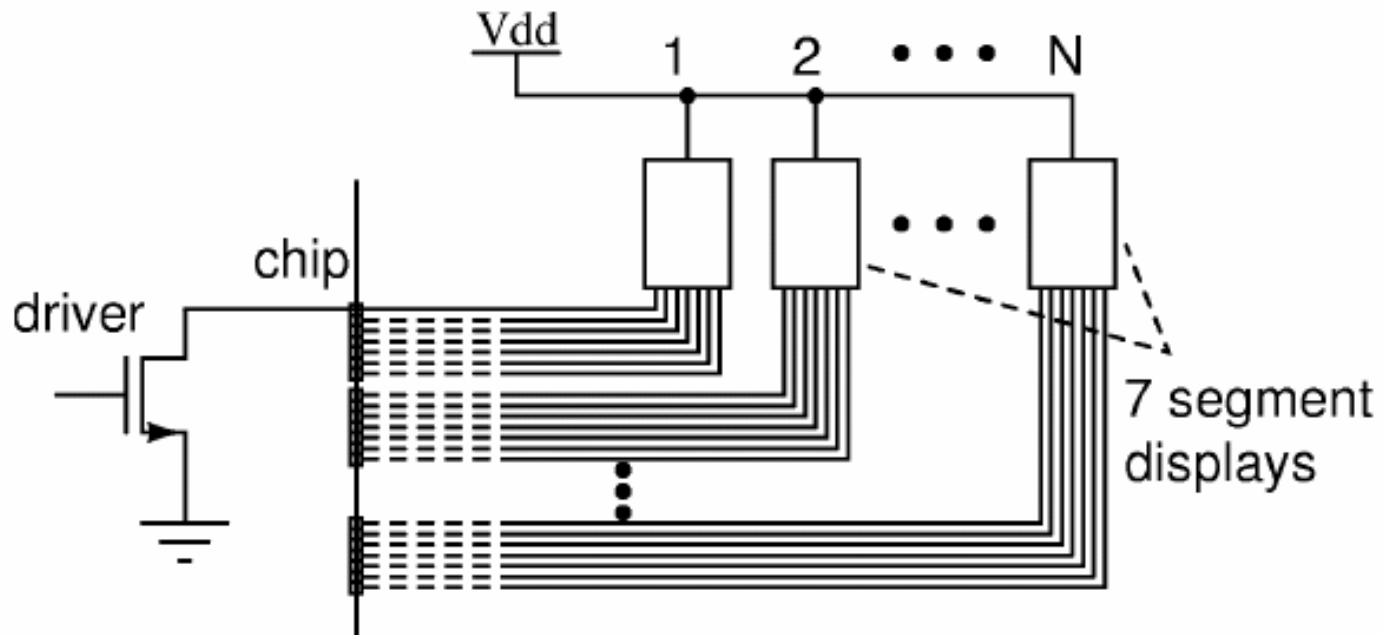

- Simple
- $7 \cdot N$ pins, drivers for N displays

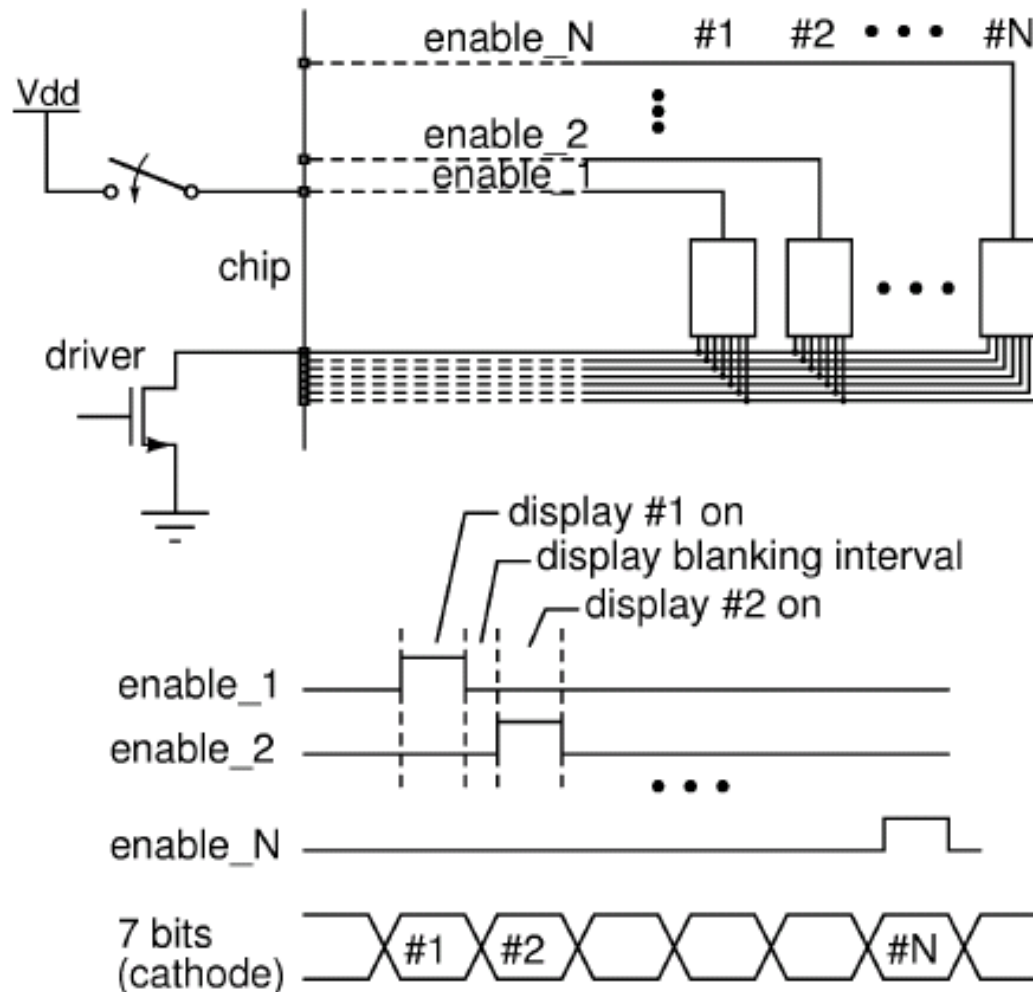Driving a 7 segment display: Multiplexing



Driving a 7 segment display: Multiplexing

- Cycle through N displays at a high rate \sim few kHz to result in a persistent display
- $N+7$ pins, drivers for N displays
- Display blanking to avoid wrong digit flickering. Enable only when digit input is stable
- Larger peak current ($\sim\sqrt{N}$) to preserve brightness
- Dot matrix displays: multiplexed row/column drivers


Analog

Analog circuit components


- Opamp
- CMOS inverter
- Transistors
- Diodes

Opamp

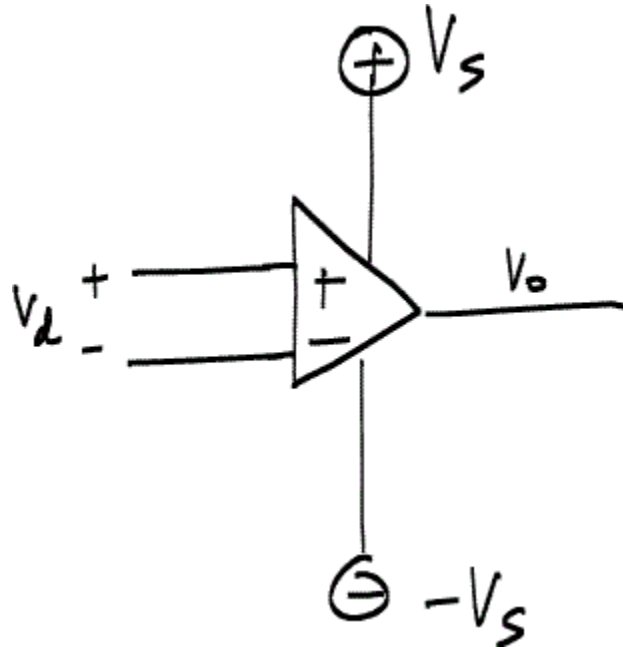- Provides a high gain
- Used to provide negative feedback
- $v_d=0$ in negative feedback




Opamp

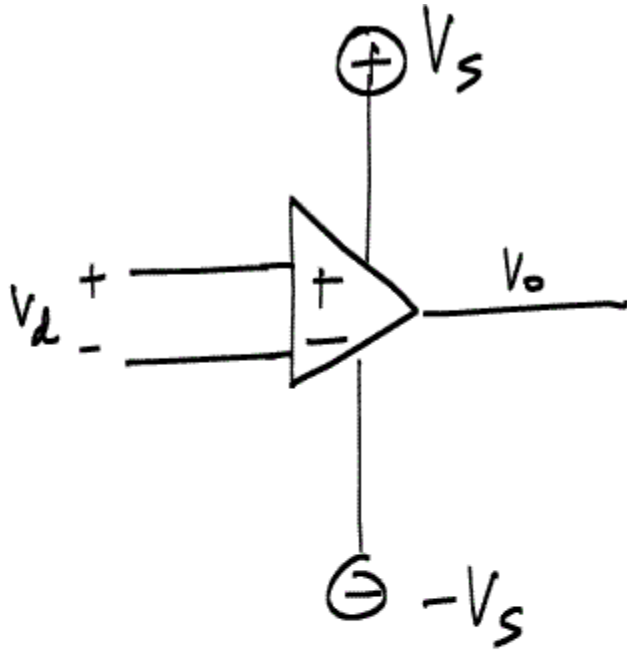

V_s : 6 - 20V
for typical opamps

- $\frac{v_o}{v_d}$: very large @ dc
- In negative feedback:
 $v_d \approx 0$


Opamp: LM741

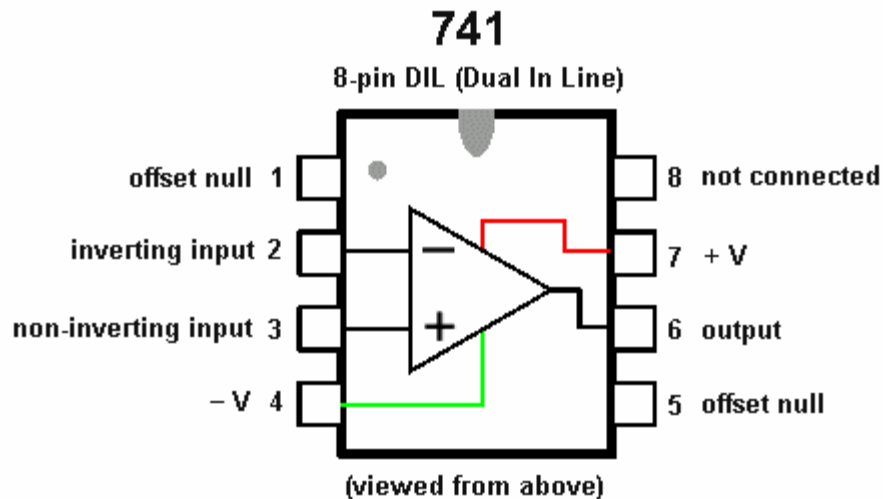

- Single opamp in a package
- 1MHz gain bandwidth product
- 1V/ μ s slew rate

Figure reproduced from manufacturer's datasheet


Opamp: LM324

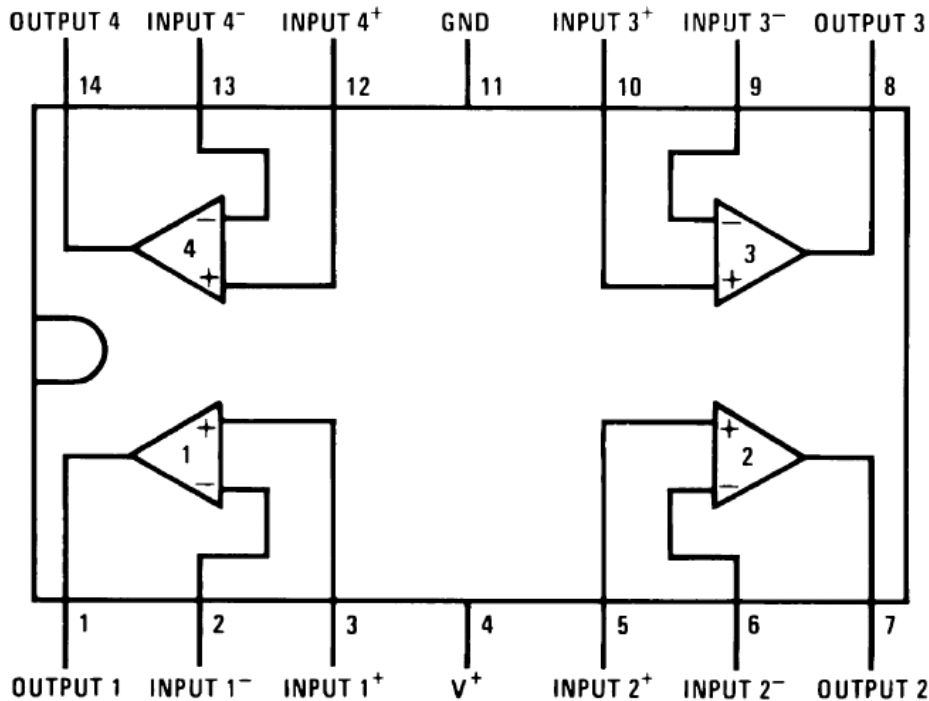

- 4 opamps in a package
- 1MHz gain bandwidth product
- 0.5V/ μ s slew rate

Figure reproduced from manufacturer's datasheet


Opamp: LF347

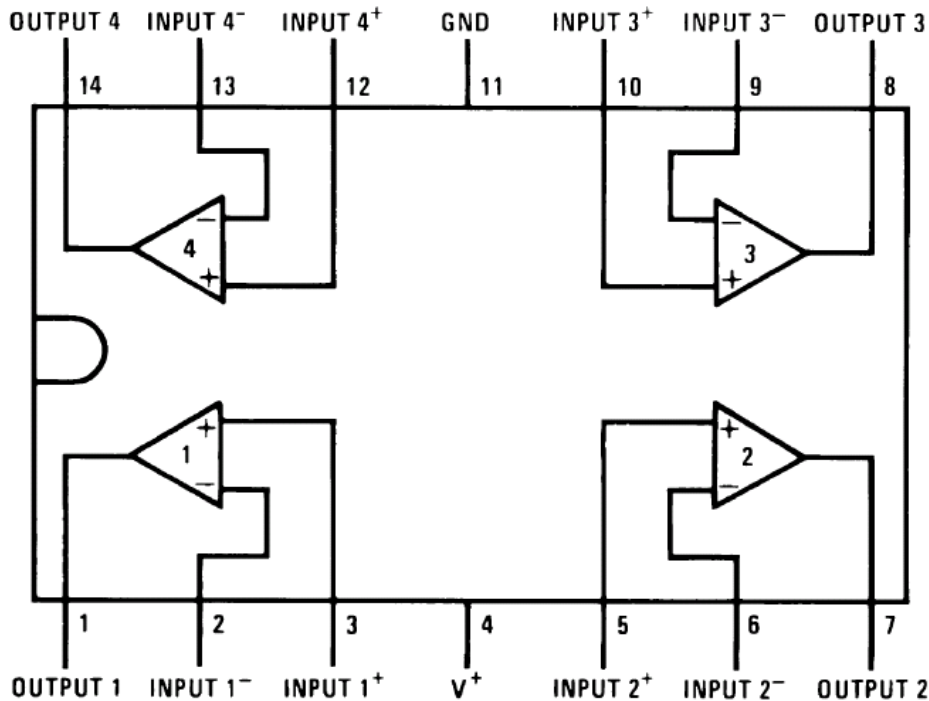


- 4 opamps in a package
- 4MHz gain bandwidth product
- 13V/ μ s slew rate
- **OUR CHOICE!**

Figure reproduced from manufacturer's datasheet

Opamp: Amplifiers

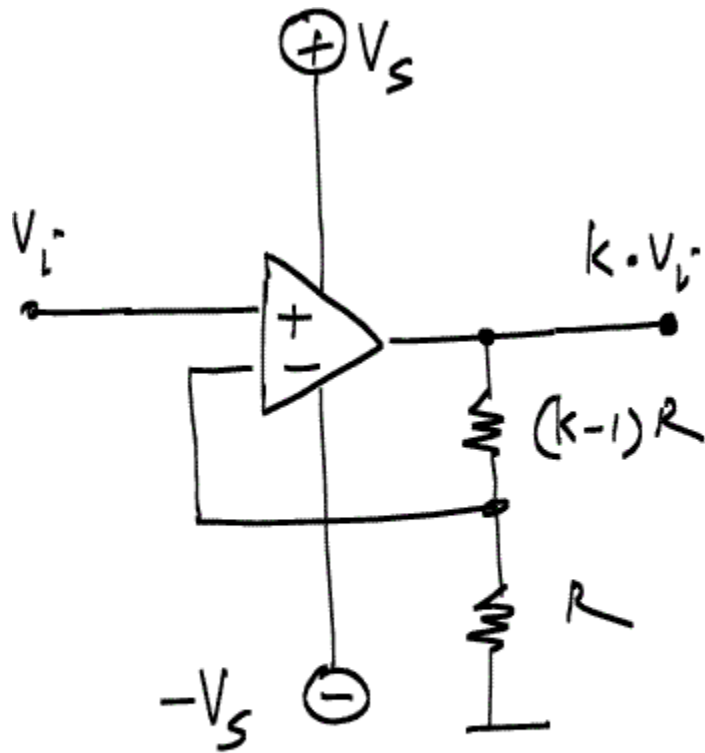


Non inverting amplifier

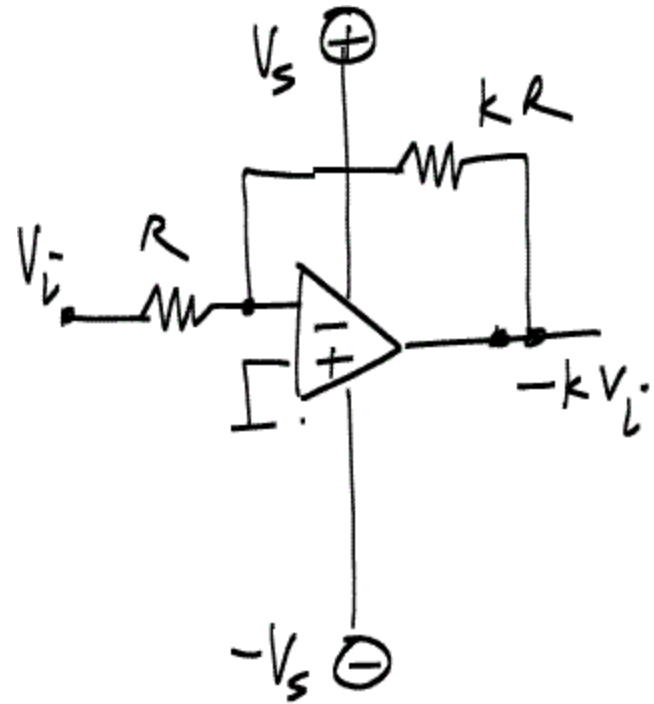



Inverting amplifier

$R \sim k\Omega$ to tens of $k\Omega$

Opamp: Adders

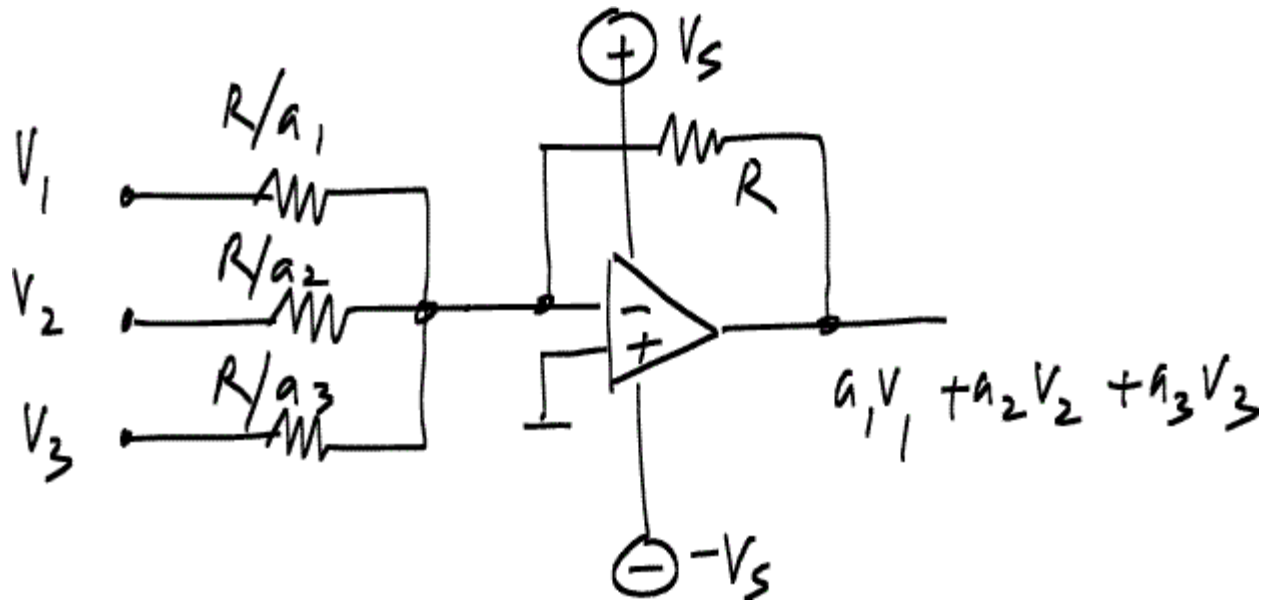


Opamp: Negative feedback

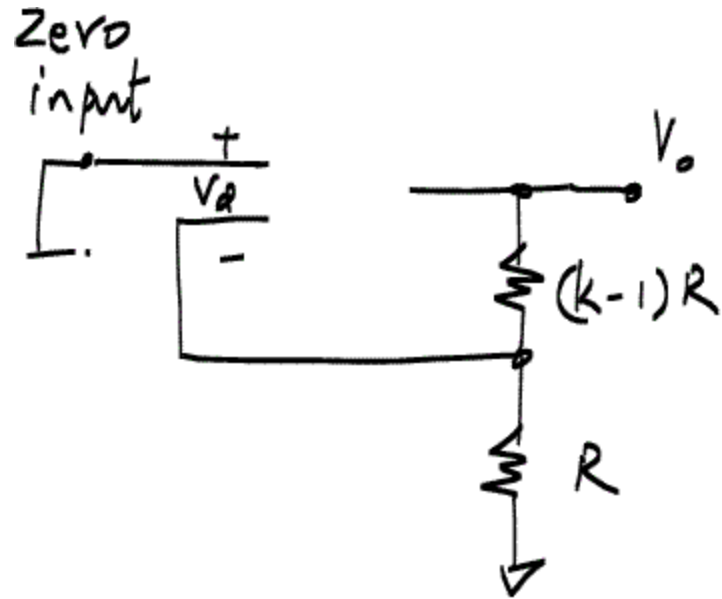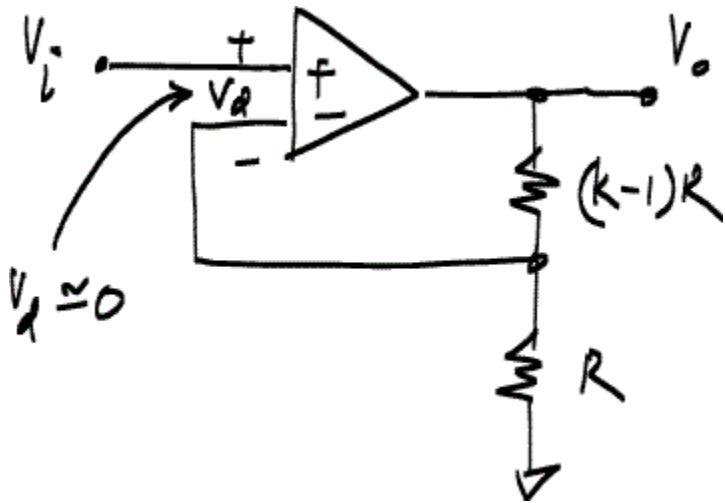


$$\frac{V_d}{V_o} = -\frac{1}{k} \text{ (negative)}$$

Opamp: Negative feedback

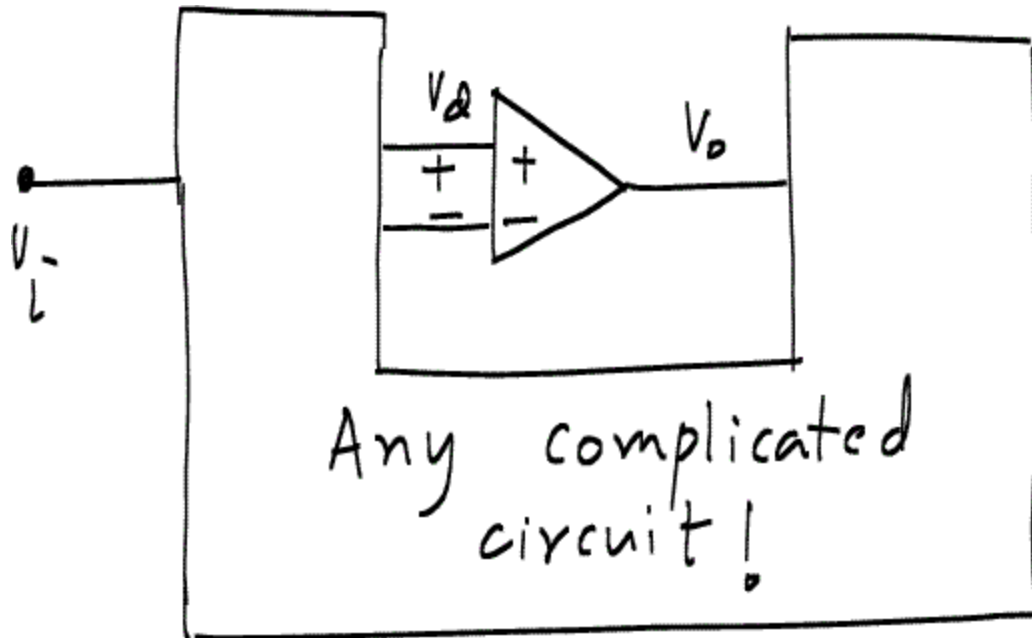


Opamp: Negative feedback

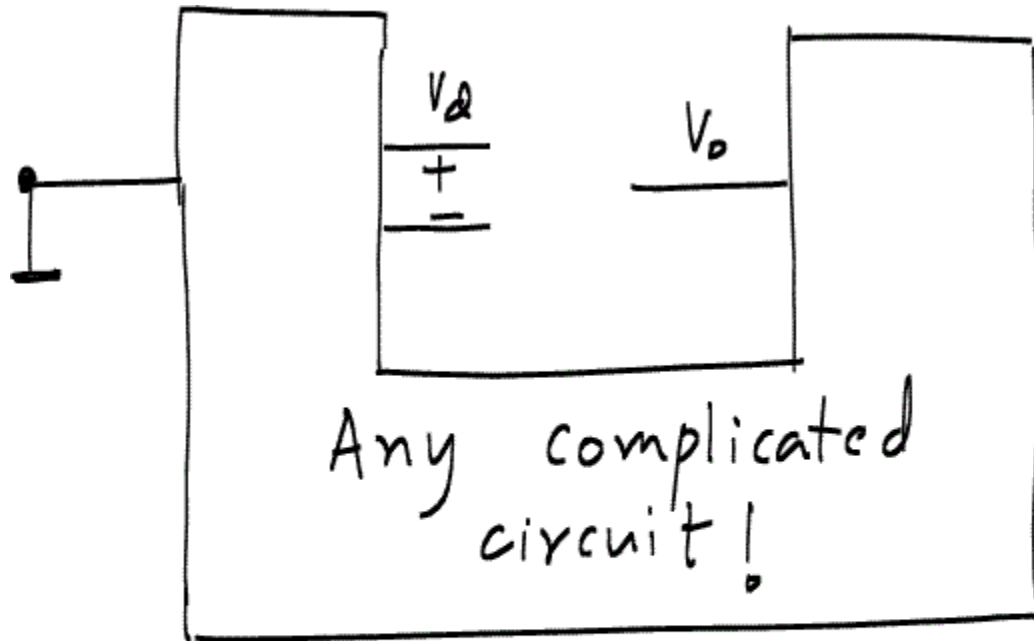


$\frac{V_d}{V_o}$ should be negative at dc
with the opamp removed

Opamp: Integrator??


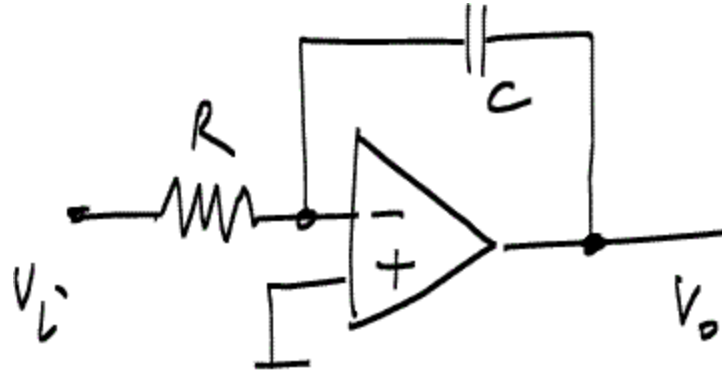


Doesn't work!

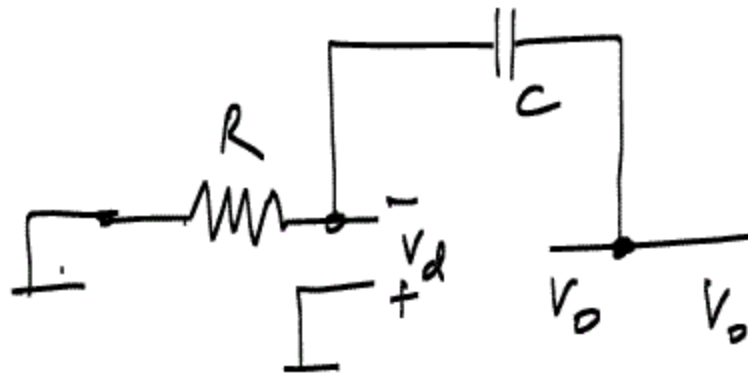


$$\frac{V_d}{V_o} = 0 \quad \text{at dc}$$

Opamp: Integrator??

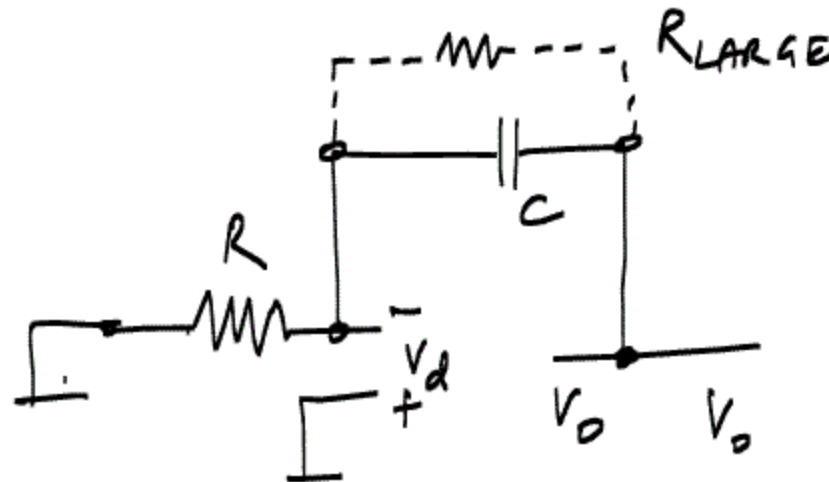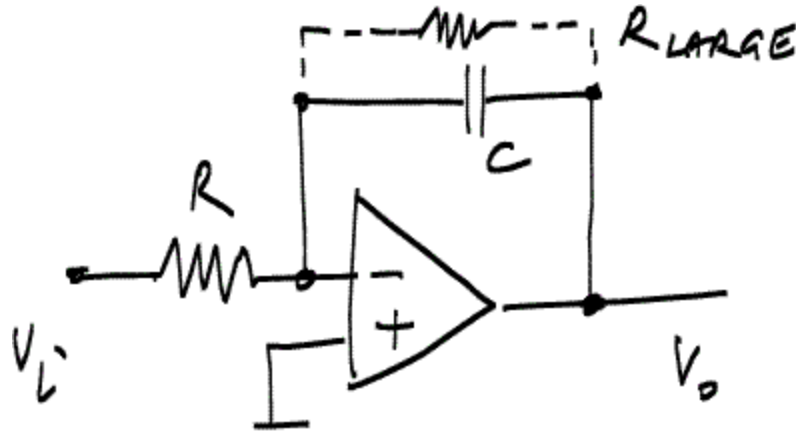

$$\frac{V_d}{V_o} = \frac{-R}{R + R_{LARGE}} \quad \text{at dc}$$


Opamp: Filters

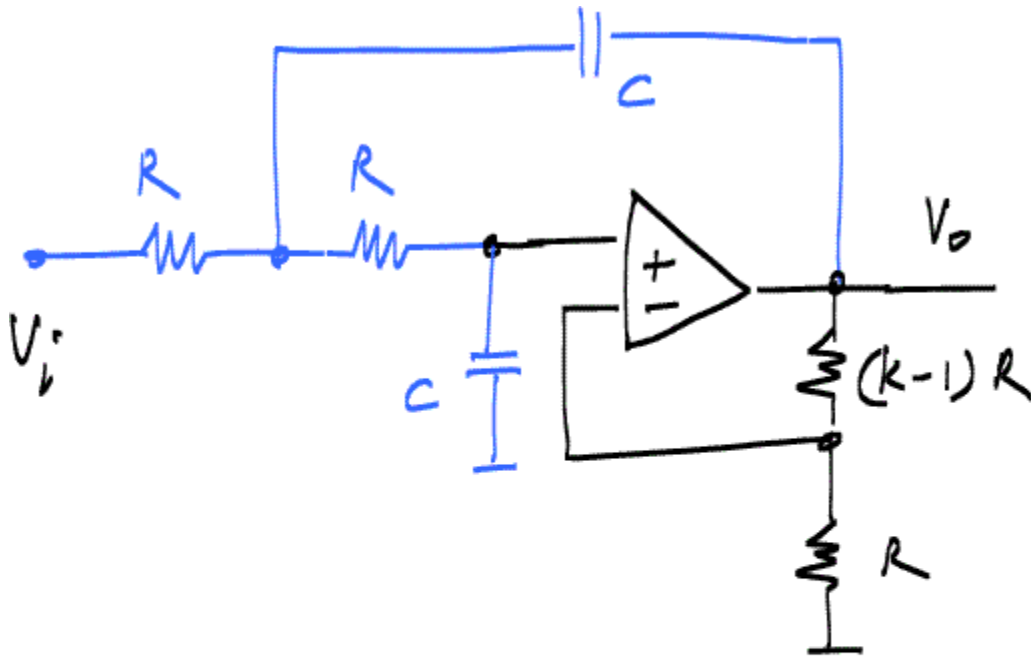




$$\frac{V_o}{V_i} = \frac{1}{(sCR)^2 + sCR(3-k) + 1}$$

$$3-k = \sqrt{2}$$

⇒ Maximally flat response

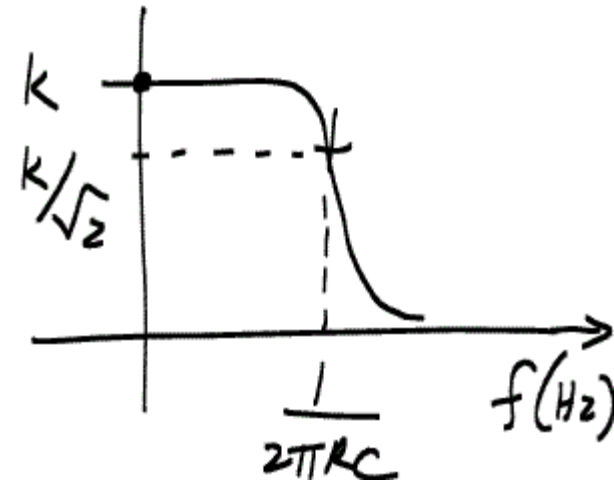


Opamp: Filters

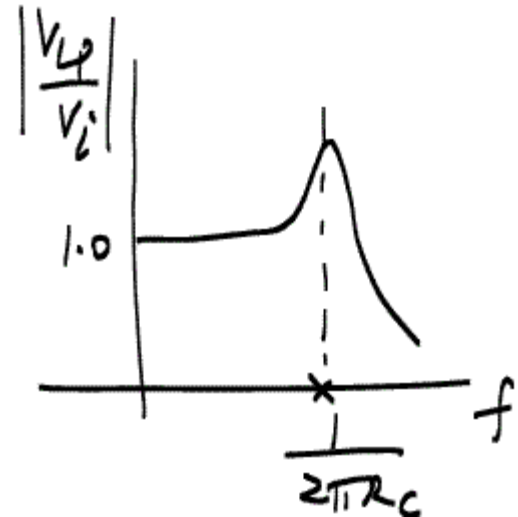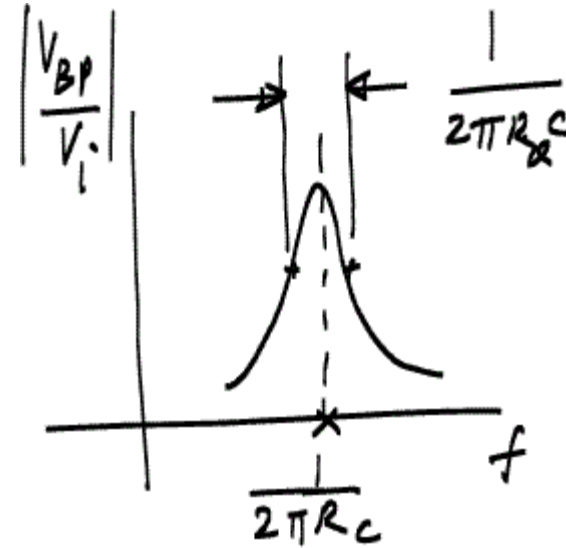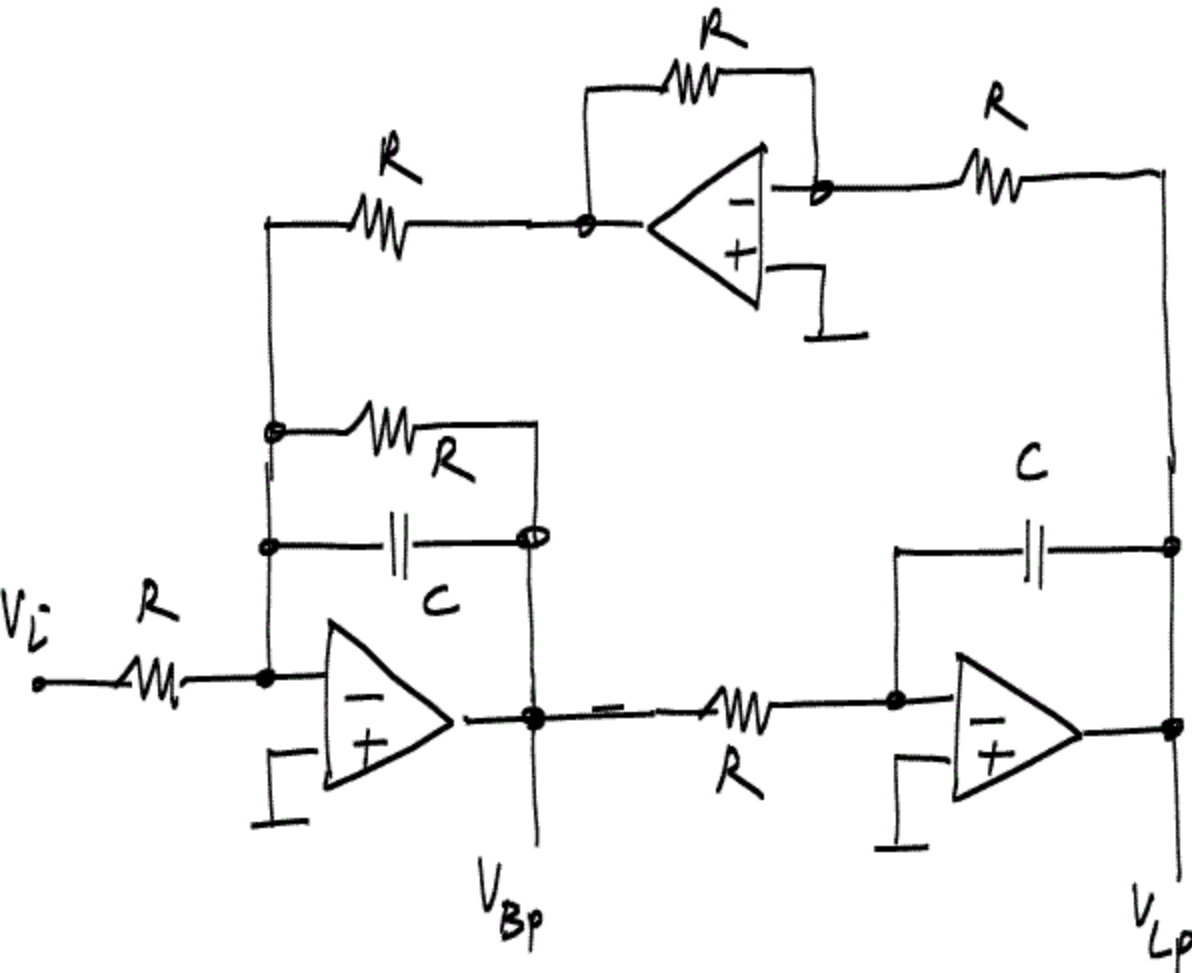

Opamp: Logarithmic amplifiers


Diode.

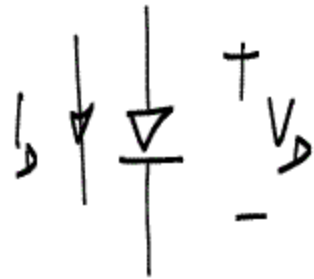

$$I_D \approx I_S \exp\left(\frac{V_D}{V_t}\right)$$

$$V_D \approx V_t \ln\left(\frac{I_D}{I_S}\right)$$

Bipolar transistor


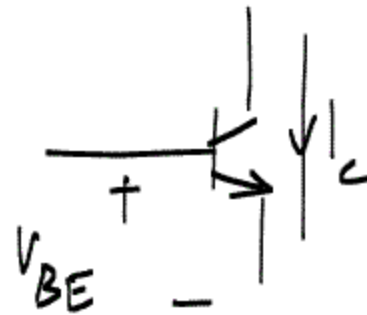


$$I_C \approx I_S \exp\left(\frac{V_{BE}}{V_t}\right)$$

$$V_{BE} \approx V_t \ln\left(\frac{I_C}{I_S}\right)$$

$$V_t = \frac{kT}{q} \approx 25.9 \text{ mV} @ \text{ R.T.}$$

Opamp: Logarithmic amplifiers

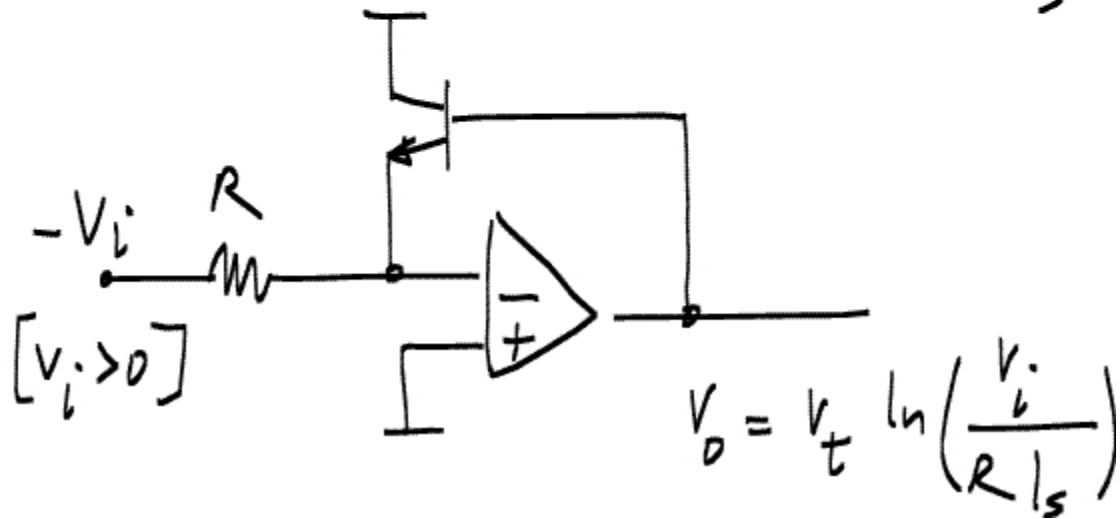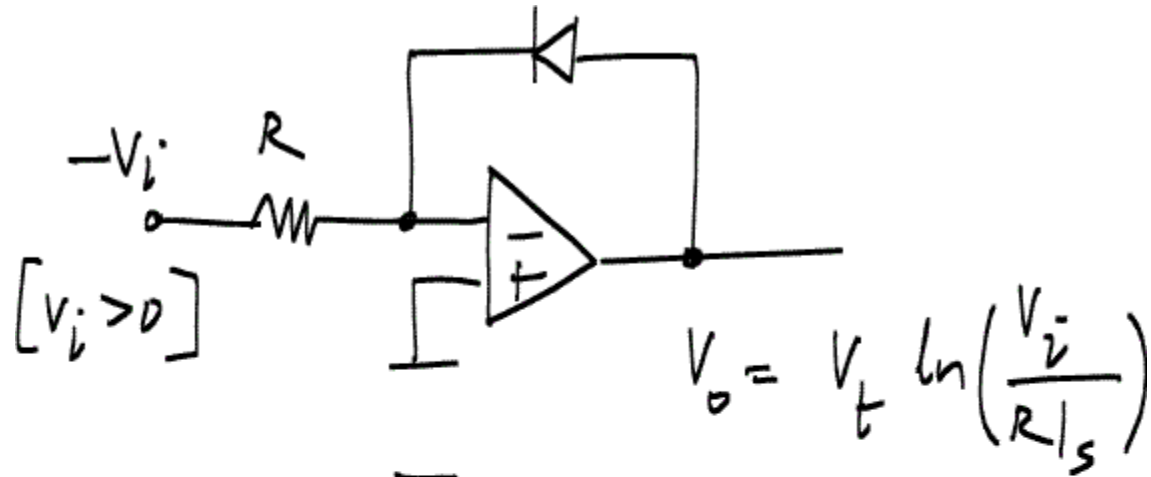


Opamp: Digital to analog converter

Digital input $D_{in} = b_3 b_2 b_1 b_0$

Analog output $V_{out} = \left(\frac{b_3}{2} + \frac{b_2}{4} + \frac{b_1}{8} + \frac{b_0}{16} \right) V_{ref}$

V_{ref} : Full scale voltage

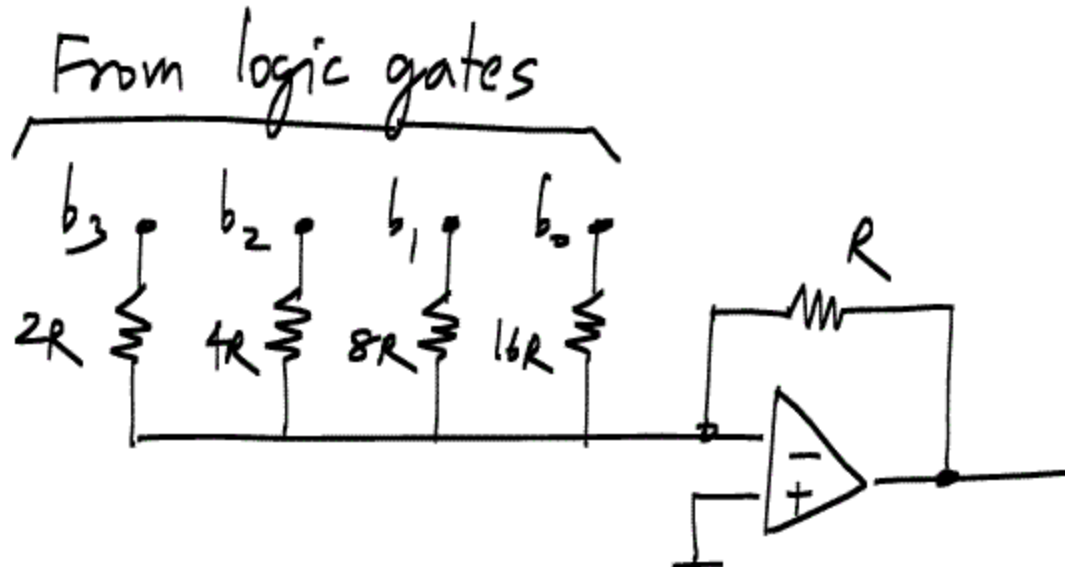


Opamp: Digital to analog converter


Digital input $D_{in} = b_3 b_2 b_1 b_0$

Analog output $V_{out} = \left(\frac{b_3}{2} + \frac{b_2}{4} + \frac{b_1}{8} + \frac{b_0}{16} \right) V_{ref}$


V_{ref} : Full scale voltage

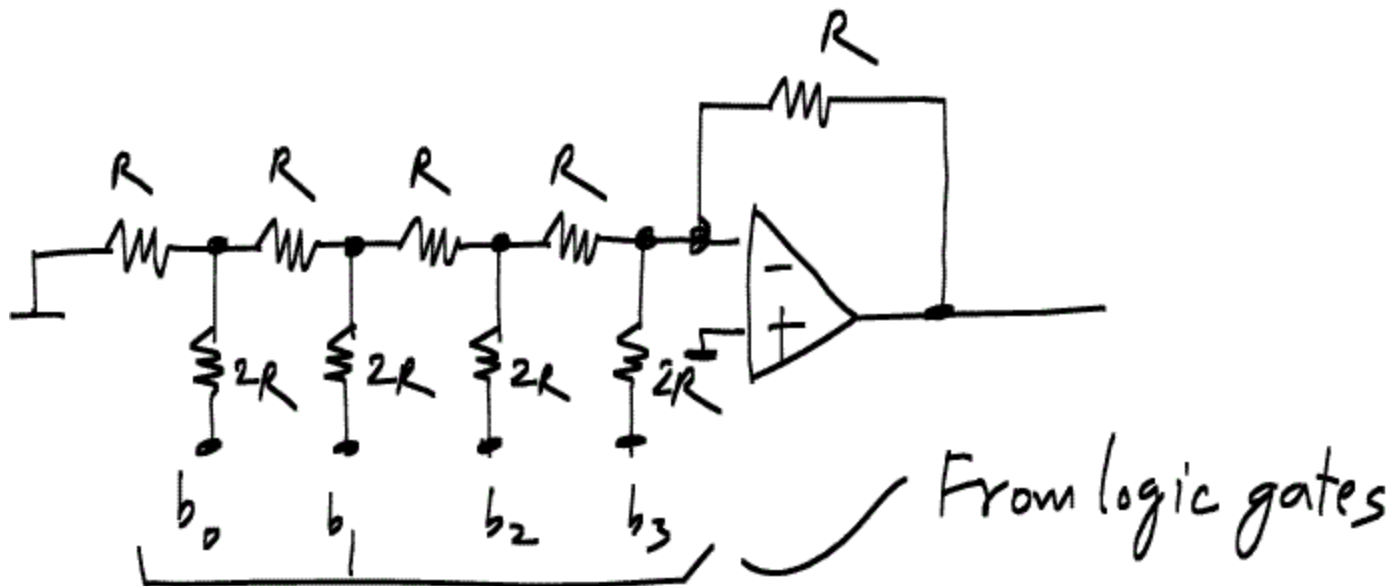

Opamp: Schmitt trigger

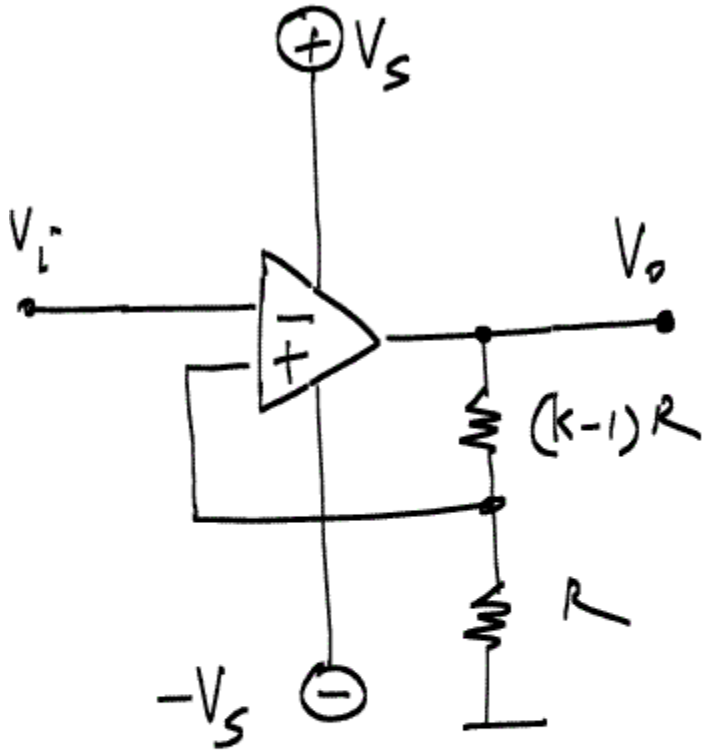





Inverting Schmitt trigger

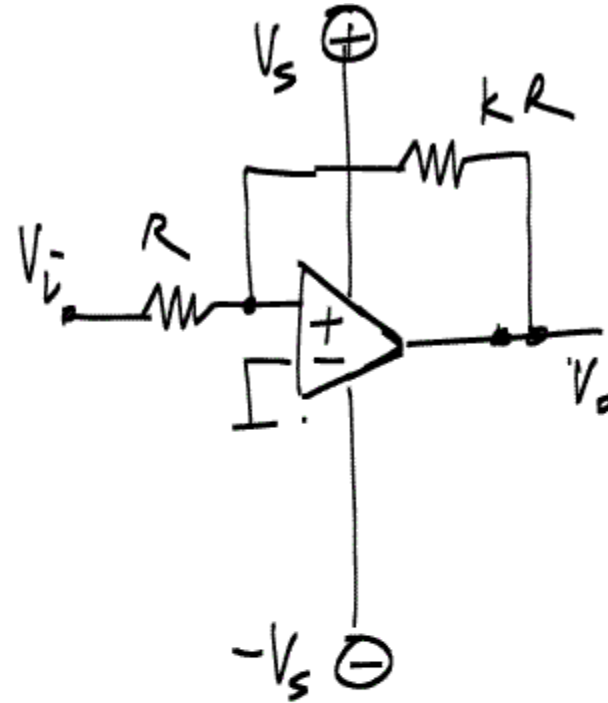

Non inverting schmitt trigger


POSITIVE FEEDBACK: $V_d \neq 0!$

Opamp: Schmitt trigger

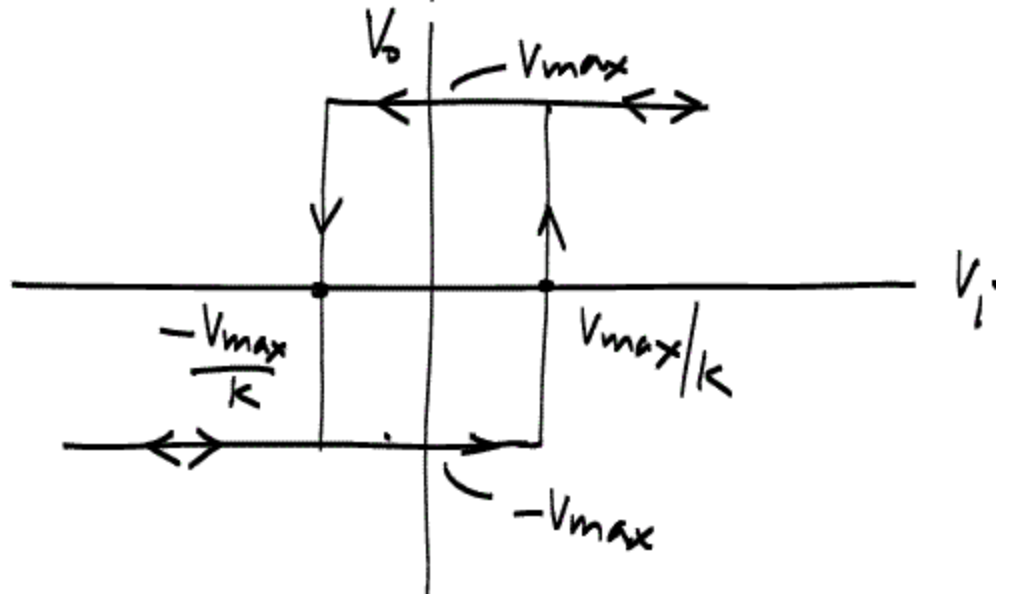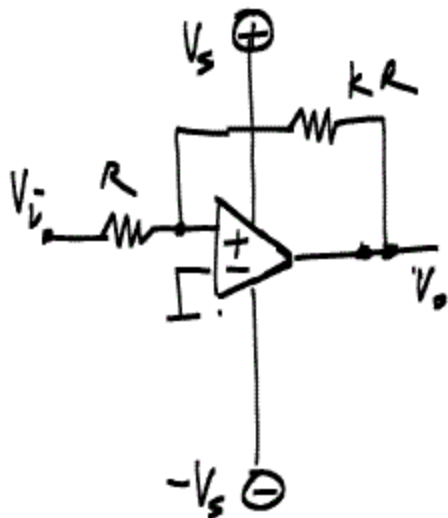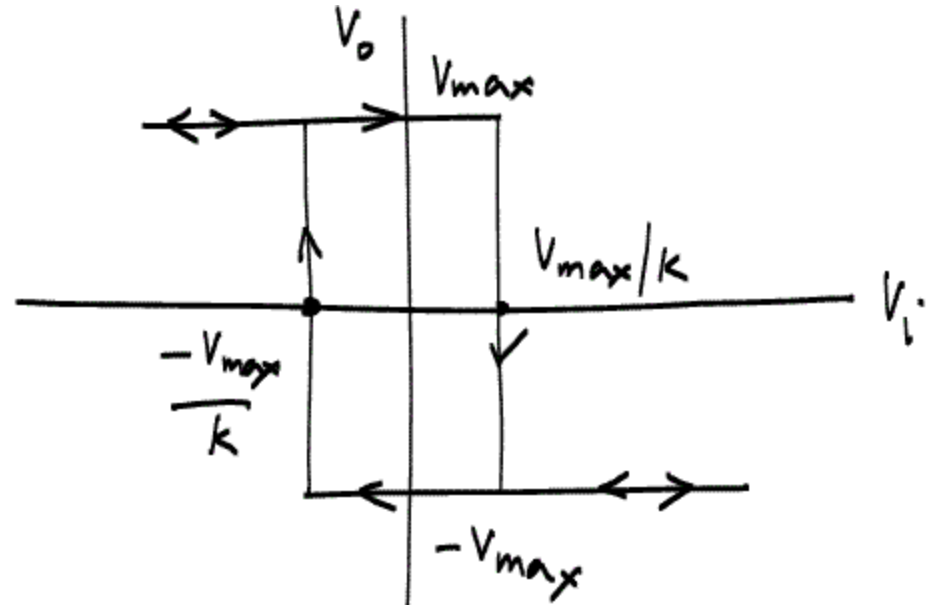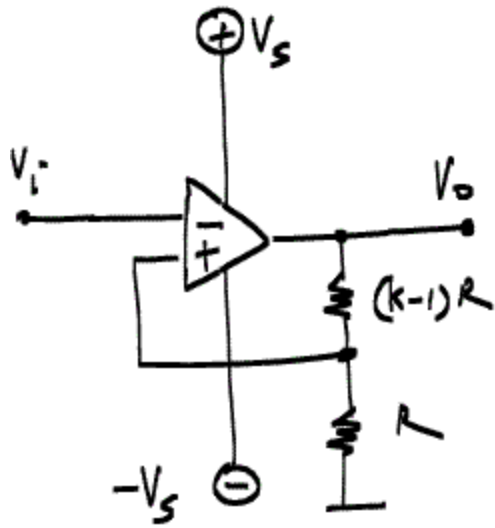

Comparator

Dual-In-Line Package

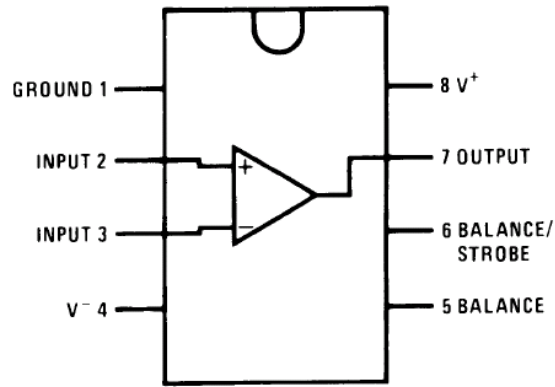

00570434

Top View

Order Number LM111J-8, LM111J-8/883(Note 21),
LM311M, LM311MX or LM311N
See NS Package Number J08A, M08A or N08E

TTL Interface with High Level Logic



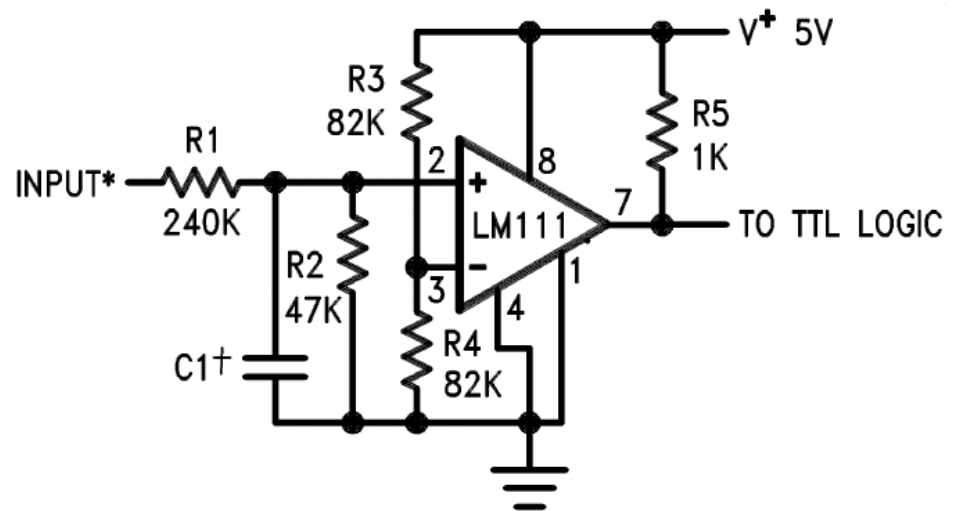
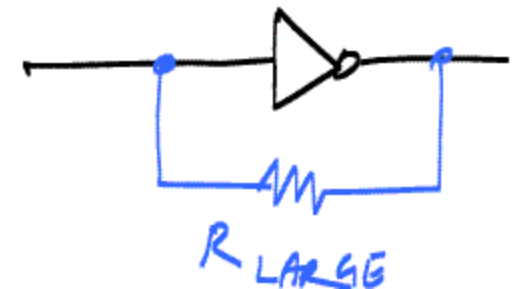
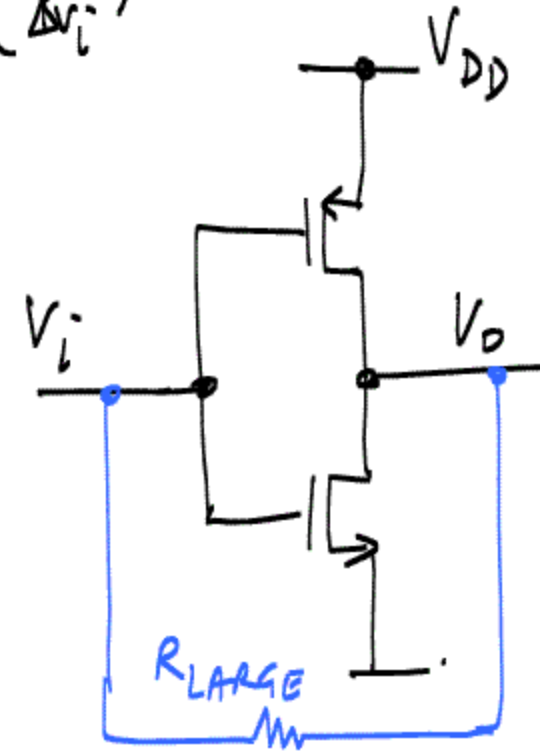
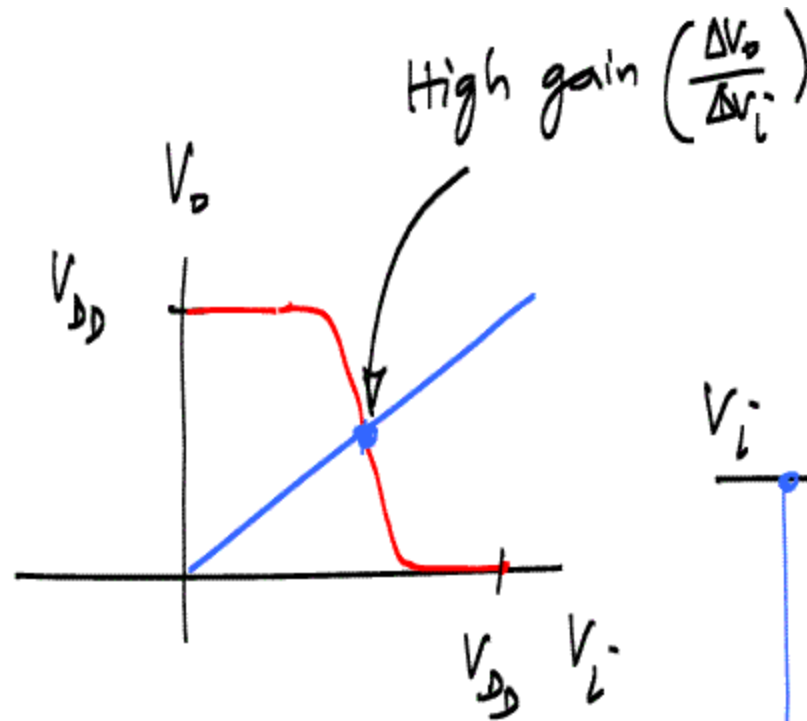


Figure reproduced from manufacturer's datasheet


CMOS inverter for analog

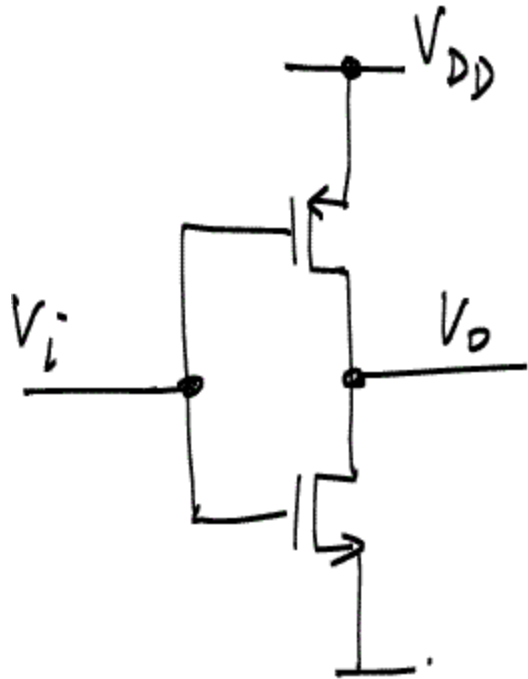

CMOS inverter for analog

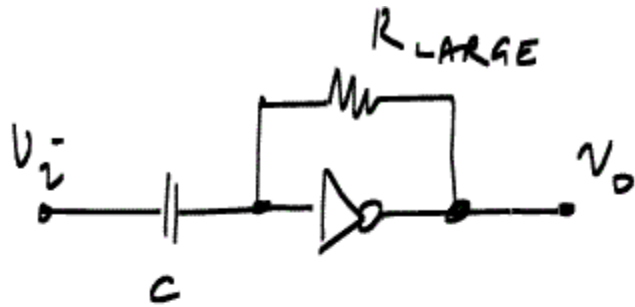
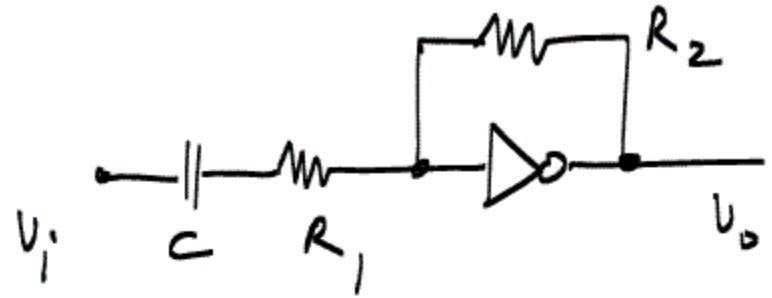
$$\frac{v_o}{v_i} \approx -g_m \cdot r_{ds}$$



$$\frac{v_o}{v_i} \approx -\frac{R_2}{R_1}$$


[Small values of $\frac{R_2}{R_1}$]

Many other circuits at

<http://www.ee.iitm.ac.in/vlsi/courses/ec330-2010/start>


Oscillator circuits

odd # inverters

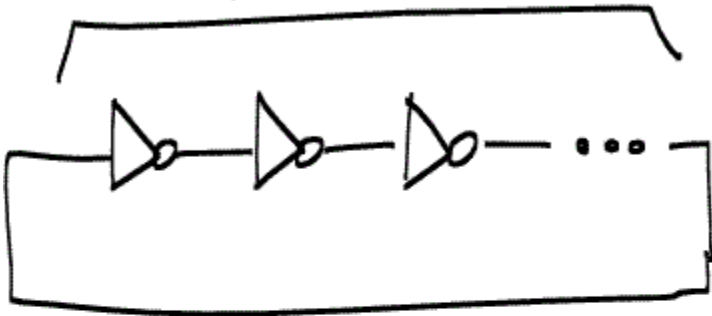



$$f_{osc} = \frac{2N}{t_d}$$

t_d : inverter delay

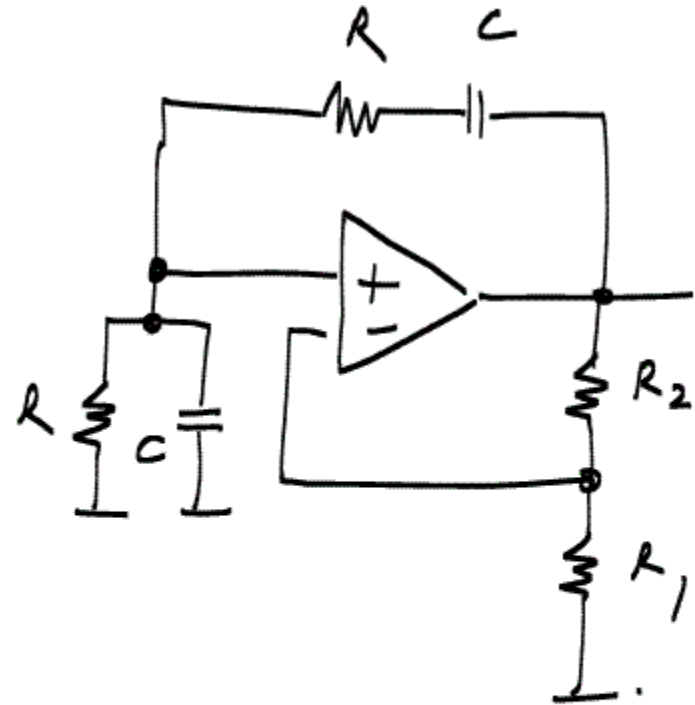

$\frac{R_2}{R_1} = 2$; Try slightly more than 2 if it doesn't oscillate

Oscillator circuits

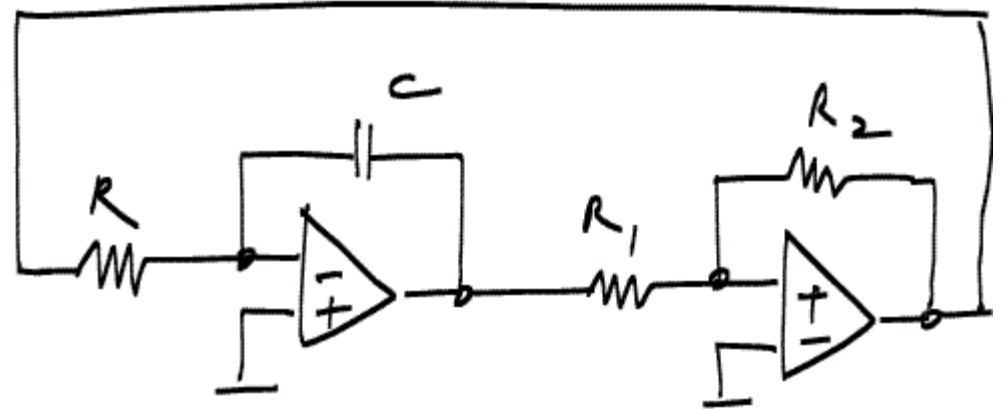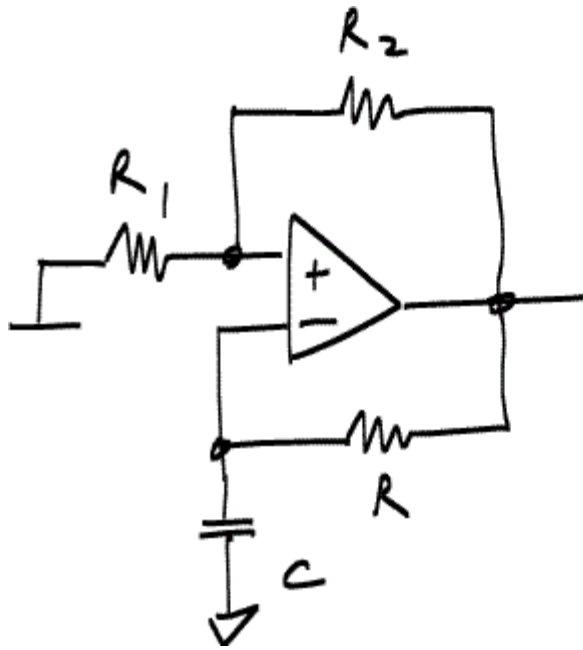


Audio power amplifier-LM386

- LM386 audio amplifier IC ~ Rs. 12/-
- Works without fuss with a minimum number of external components
- Gain of 20 or 200
- Can be used for any of your projects
- Data sheet has several example circuits

Audio power amplifier-LM386


Typical Applications

Amplifier with Gain = 20
Minimum Parts

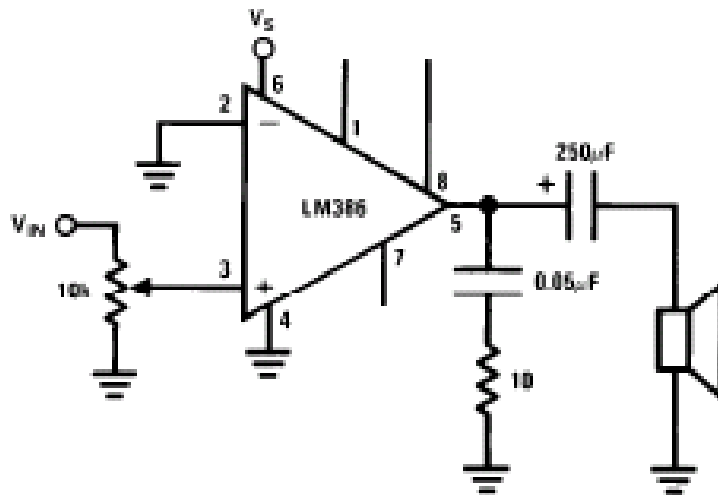

TL/H/6976-3

Amplifier with Gain = 200

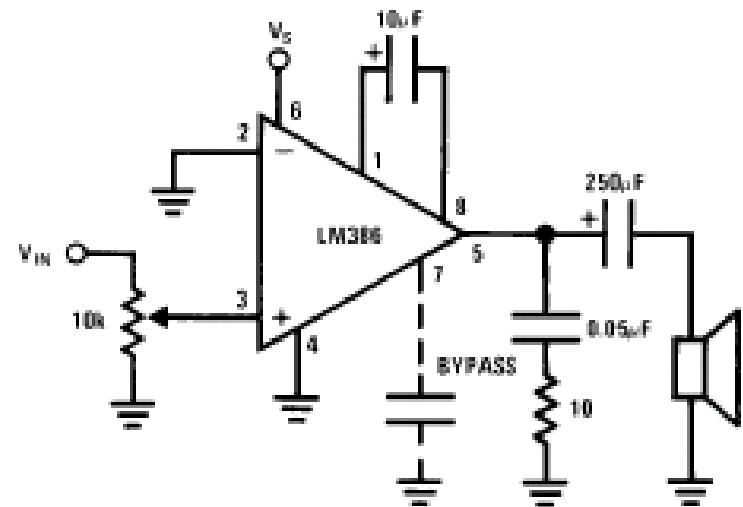

TL/H/6976-4

Figure reproduced from manufacturer's datasheet

Other analog chips

- Analog multiplier
- MC1496 balanced modulator
- CXA1619BM/BS AM/FM radio chip
- LM565 Phase locked loop
- LM566 Voltage controlled oscillator
- ... and many more

More advanced circuit blocks

- Microcontrollers: PIC, 8051
- Microcontrollers with ADC/DAC
- Cypress PSoC
 - Programmable analog and digital blocks


Suggestions for projects

Calculator

- Optimization
 - Minimize the number of chips
 - Combine the adder/subtractor
- Multiplier
 - Shift and add


Analog to digital converter

- ADC using DAC and binary search

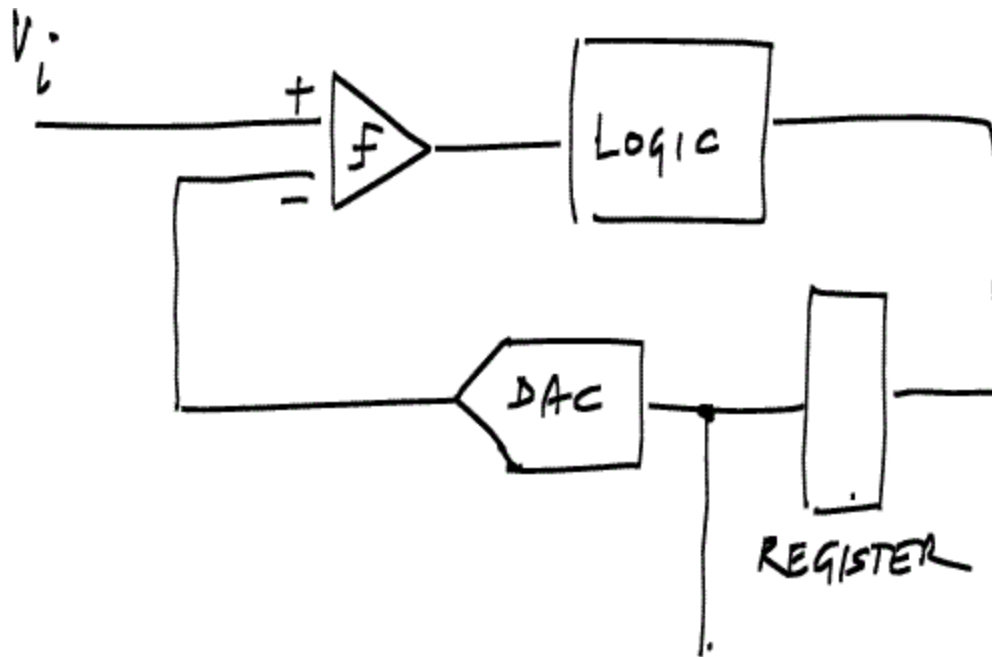


Digital code should result in a DAC output of V_i

Class D audio amplifier

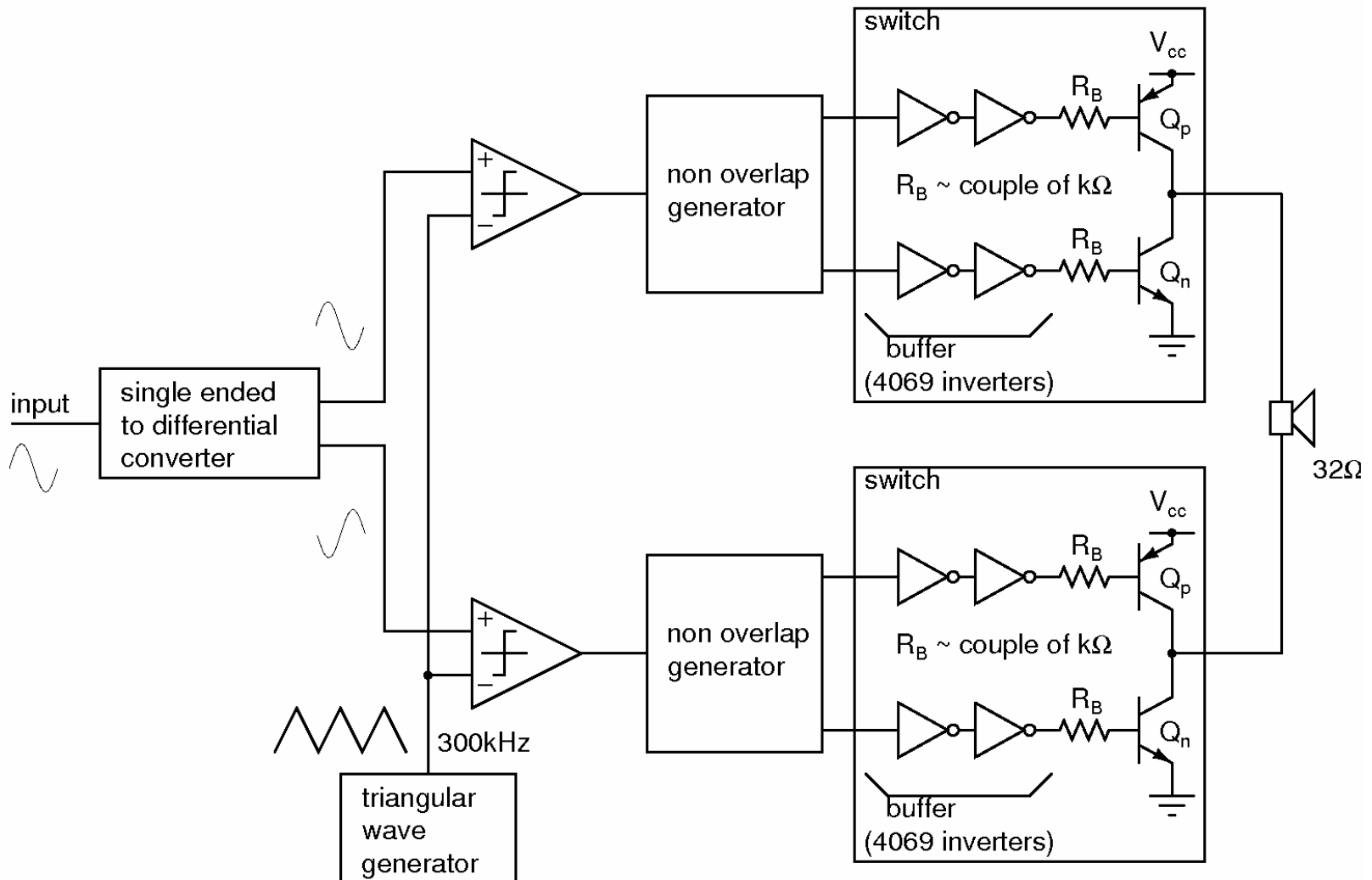

Note: triangular wave and signal inputs to the comparator must be around the same bias point

Spectrum analyzer

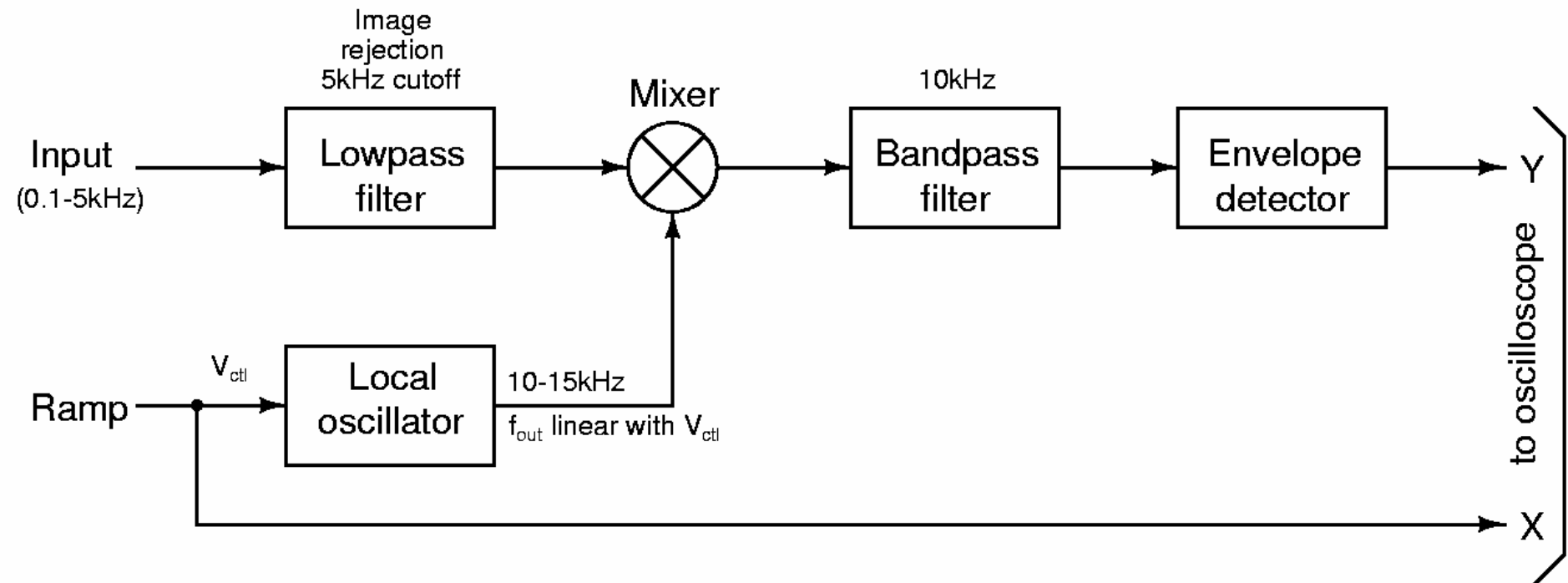

http://www.ee.iitm.ac.in/vlsi/courses/ec330_2010/start

Hobby of the era: Robotics

- Control systems
- Electrical, mechanical engg.
- Digital and analog electronics

- Lots of college level participation
- International level events like Robocon

Radio projects

- See “Radios for the hobbyist” Shaastra 2007 presentation


http://www.ee.iitm.ac.in/~nagendra/misc/20071006iitm_shaastra.pdf

Assembling circuits


Assembling circuits

- Breadboard
 - Quick assembly
 - Low frequency/low precision circuits
 - Not very robust
- PCBs
 - Takes time for assembly
 - High frequency/high precision circuits
 - Very robust


A Neat Board : Guaranteed 😊 ...

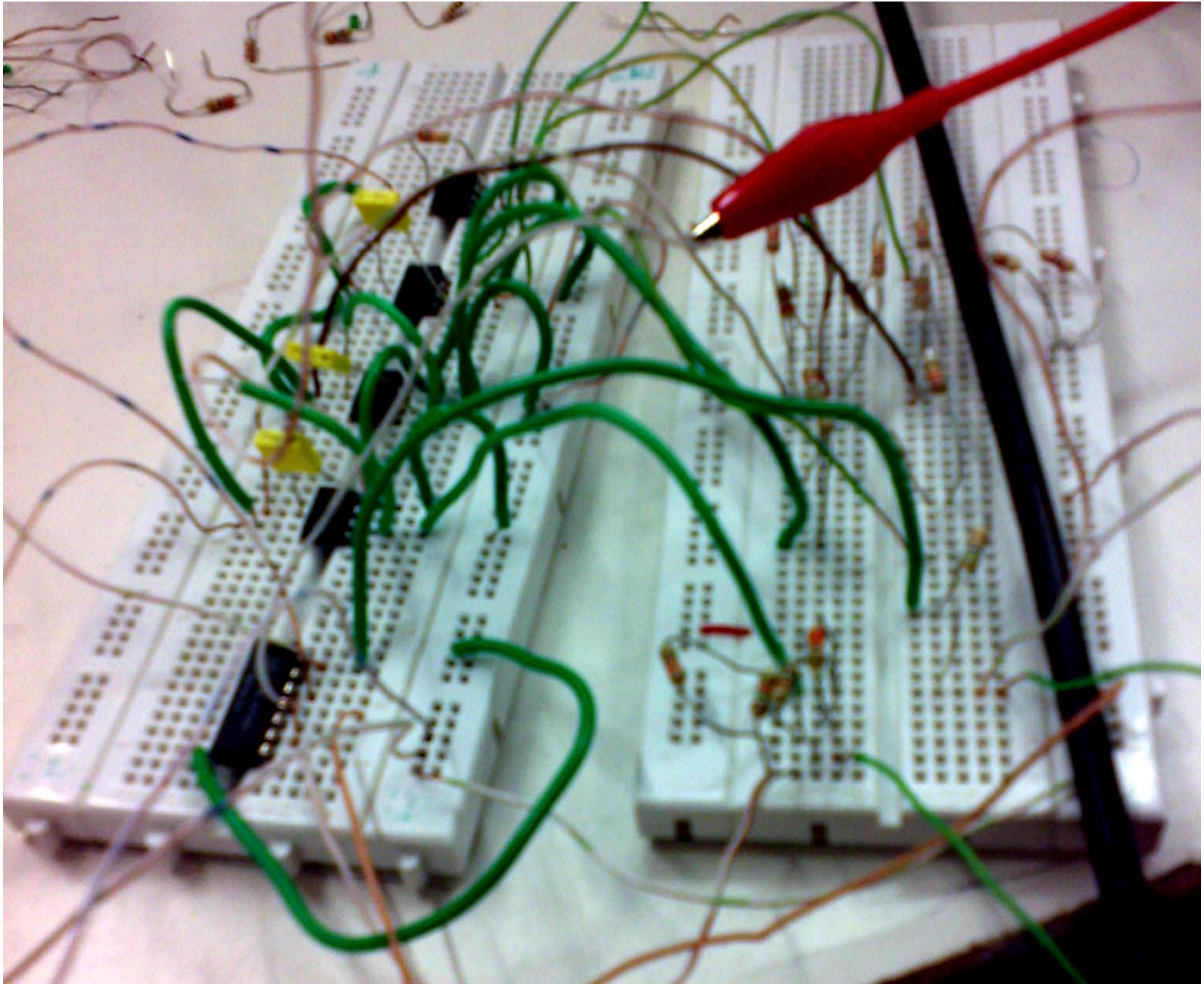


Guaranteed 😊 : Not to work ! ...

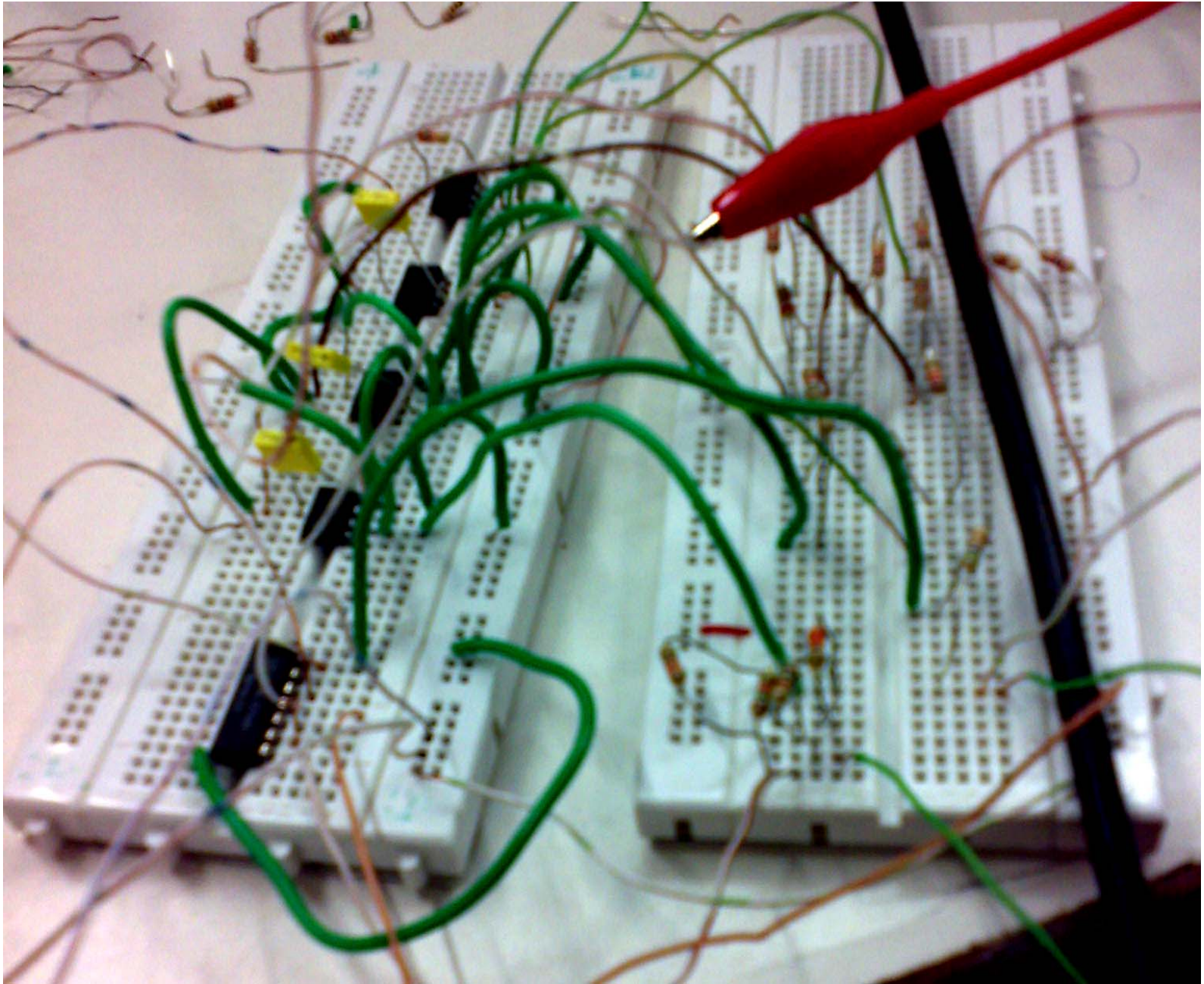

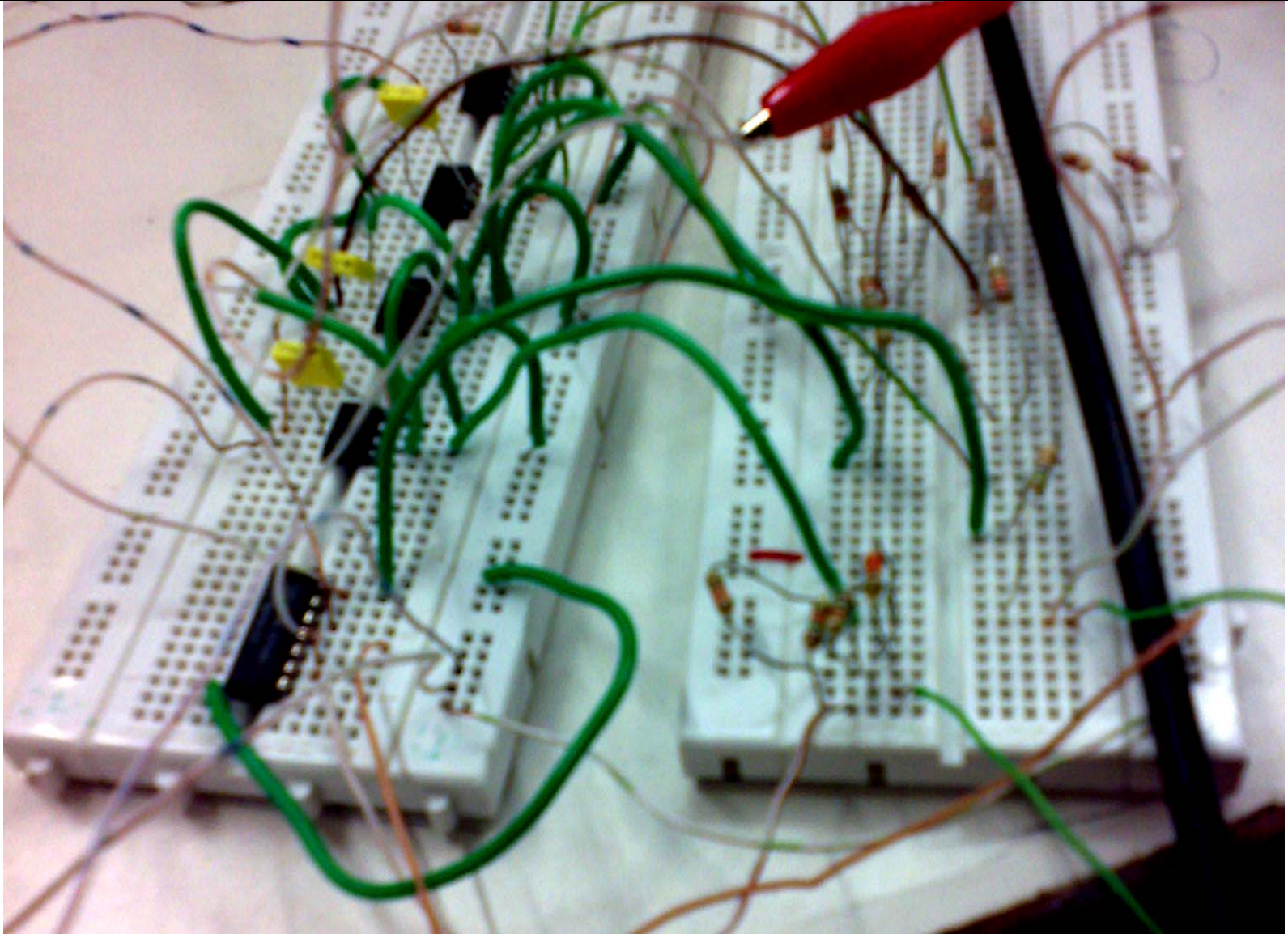
Spaghetti is good stuff, but not on your board





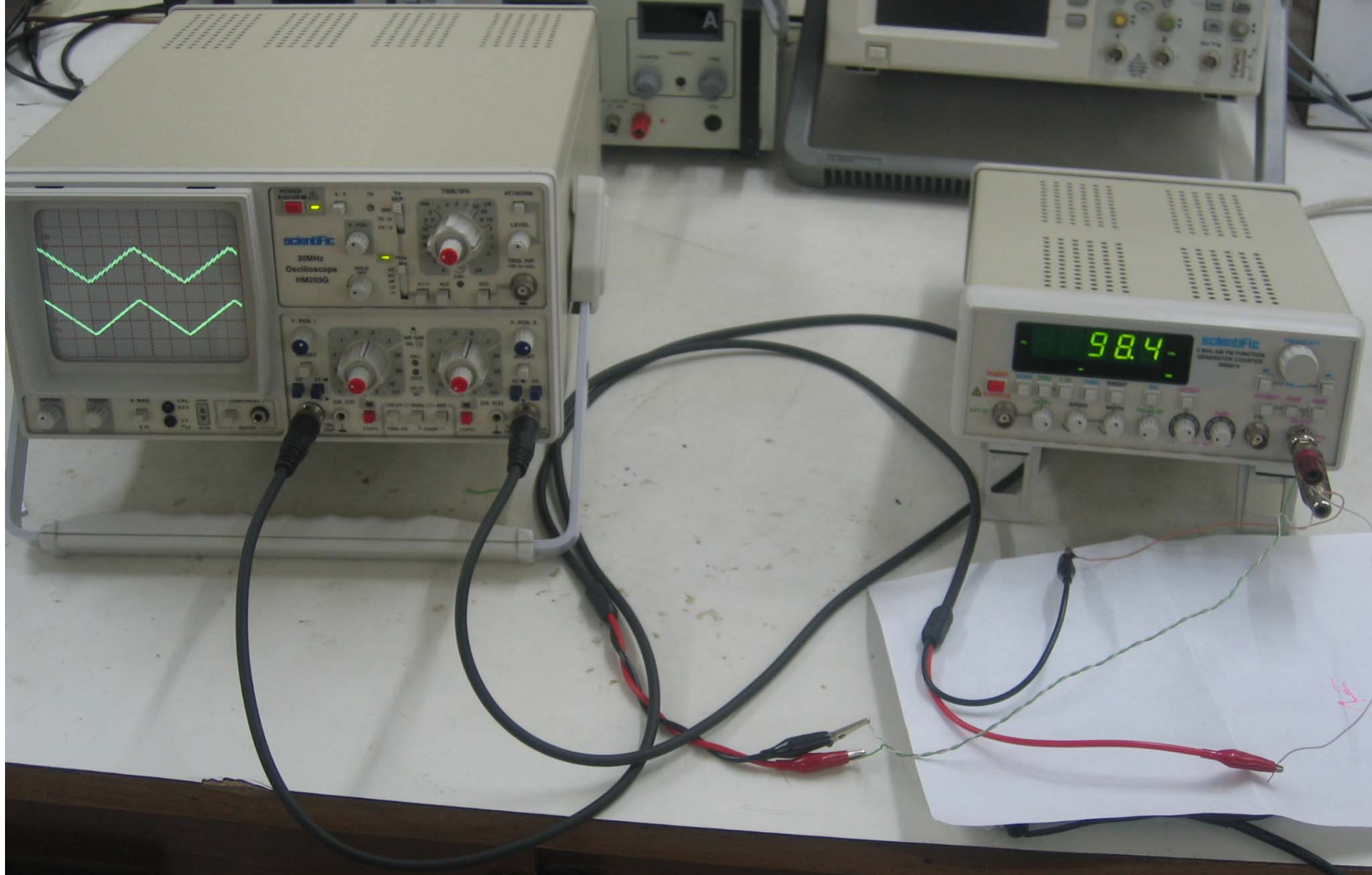


What can happen with messy wiring

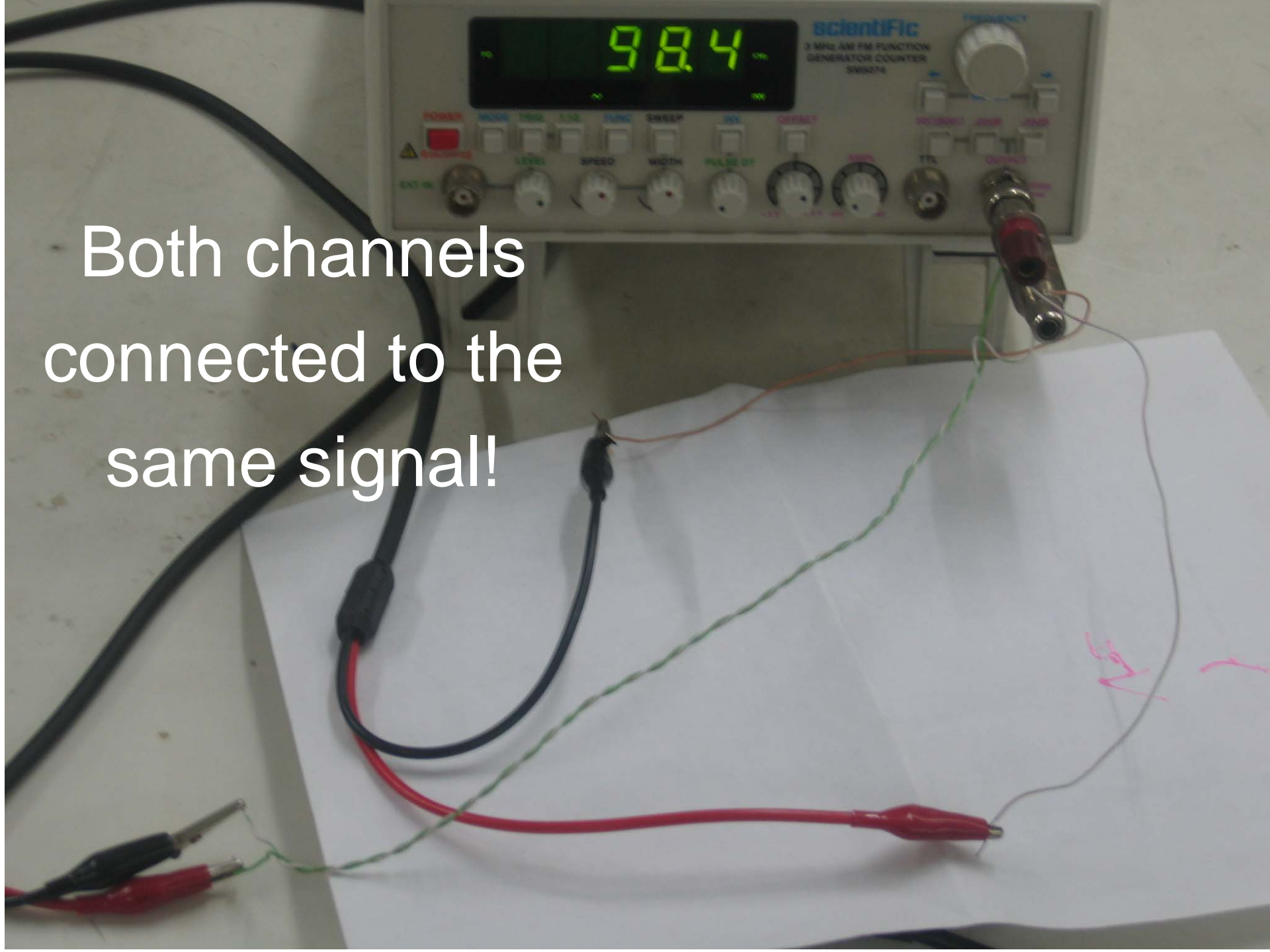Both channels
connected to the
same signal!




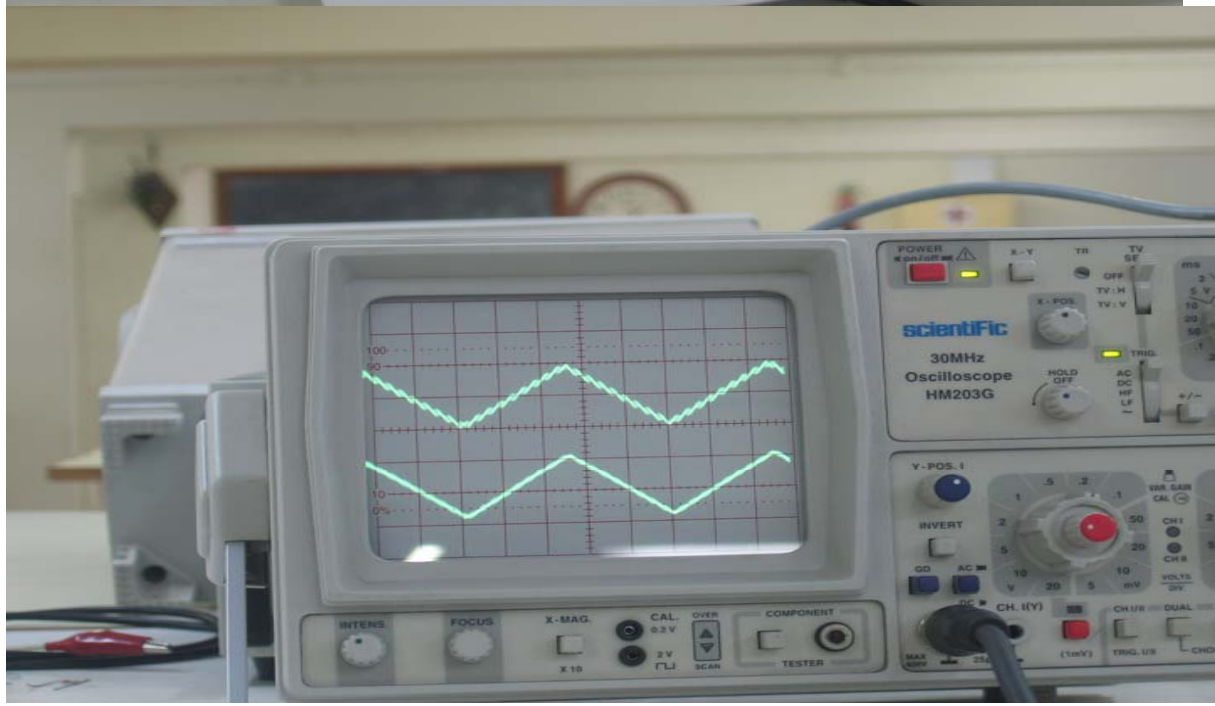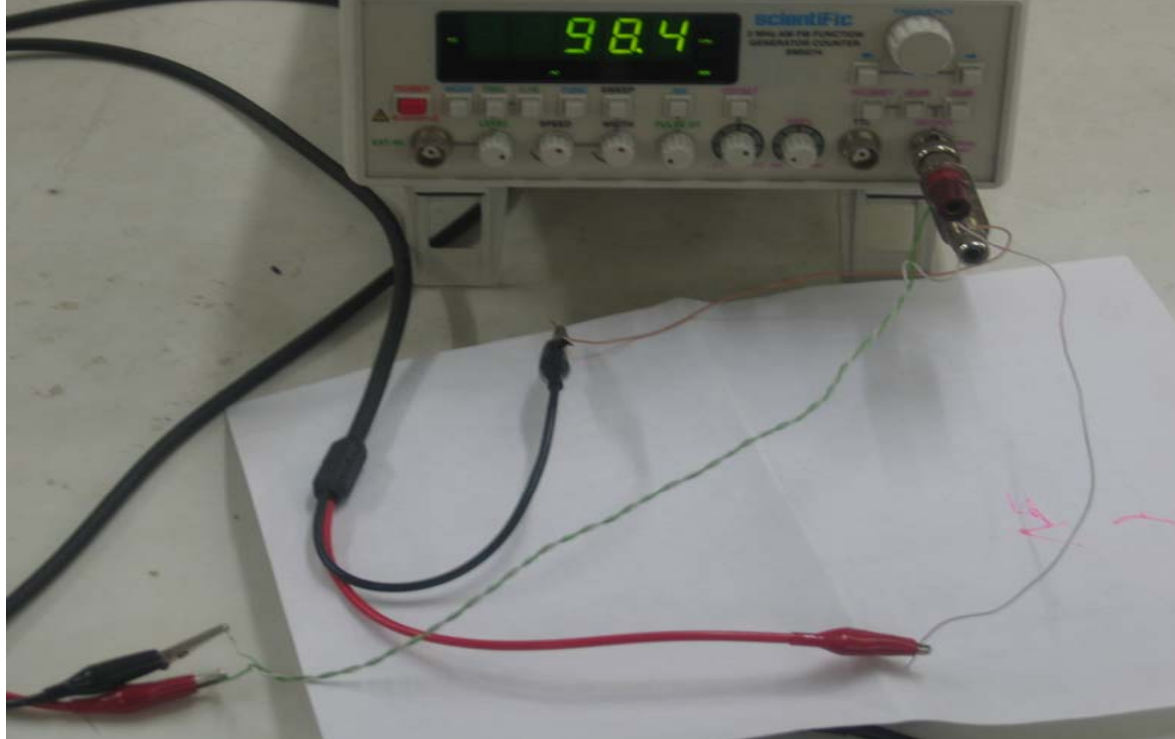


What can happen with messy wiring

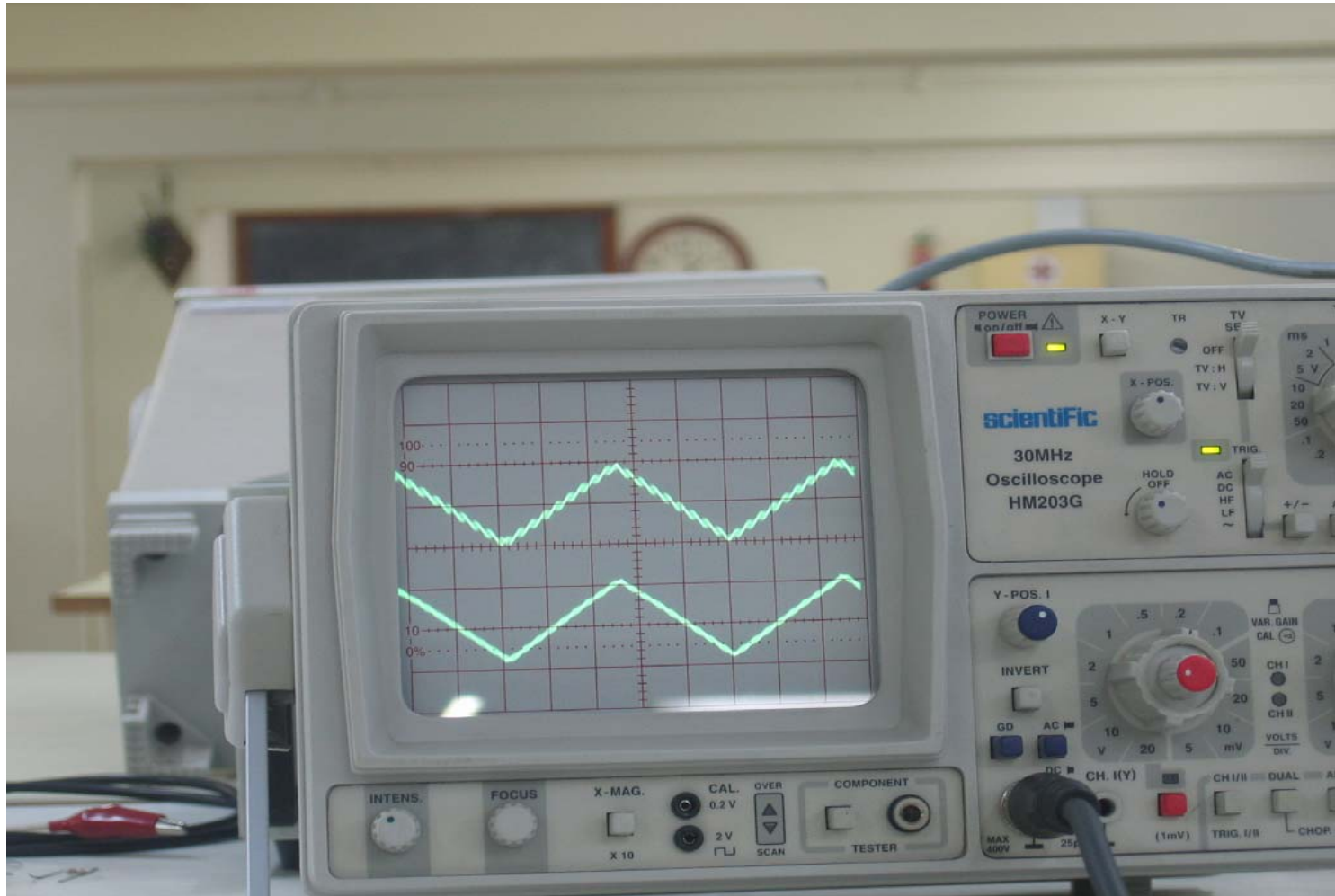


A Neatly Wired Breadboard

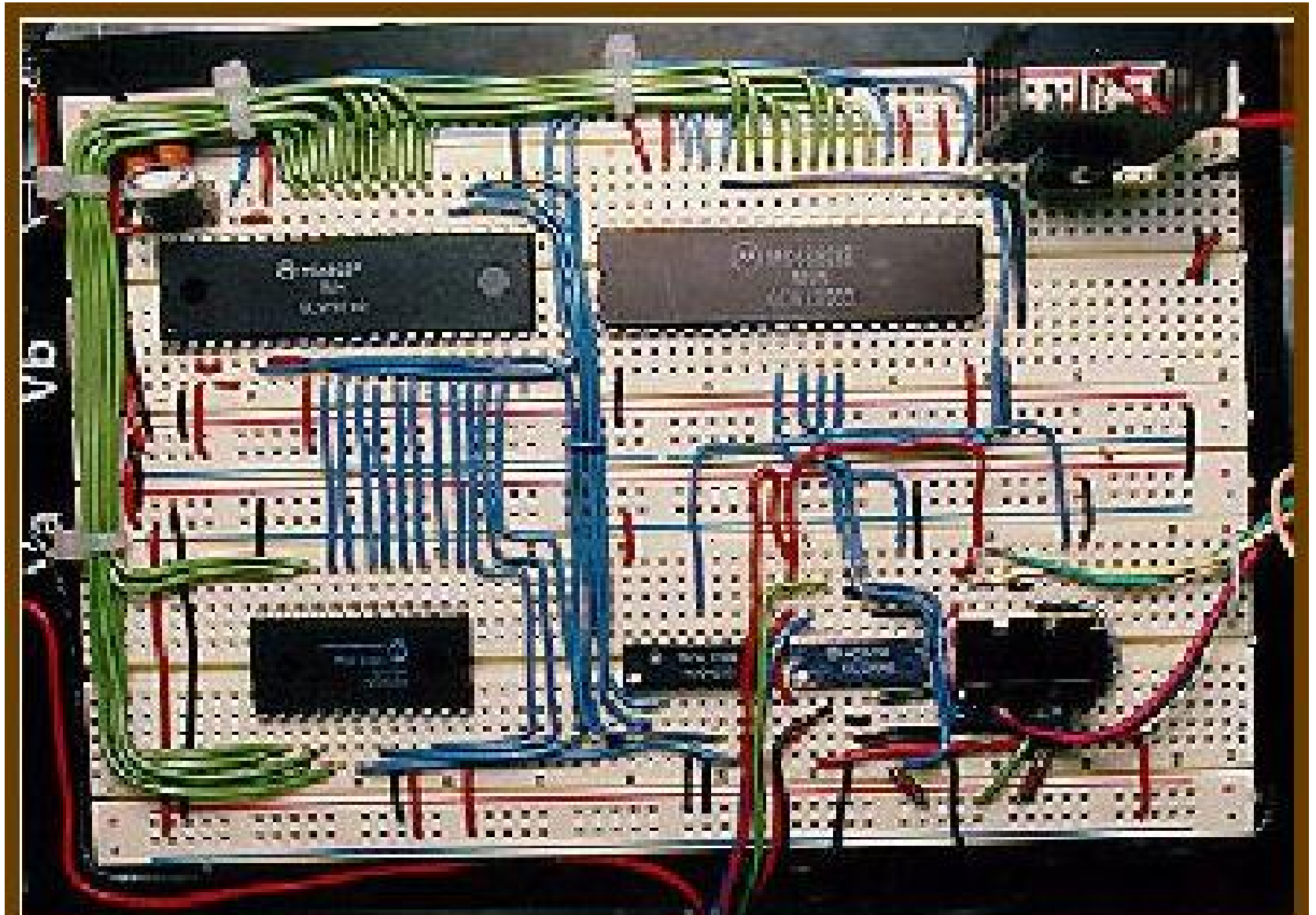

Another one...

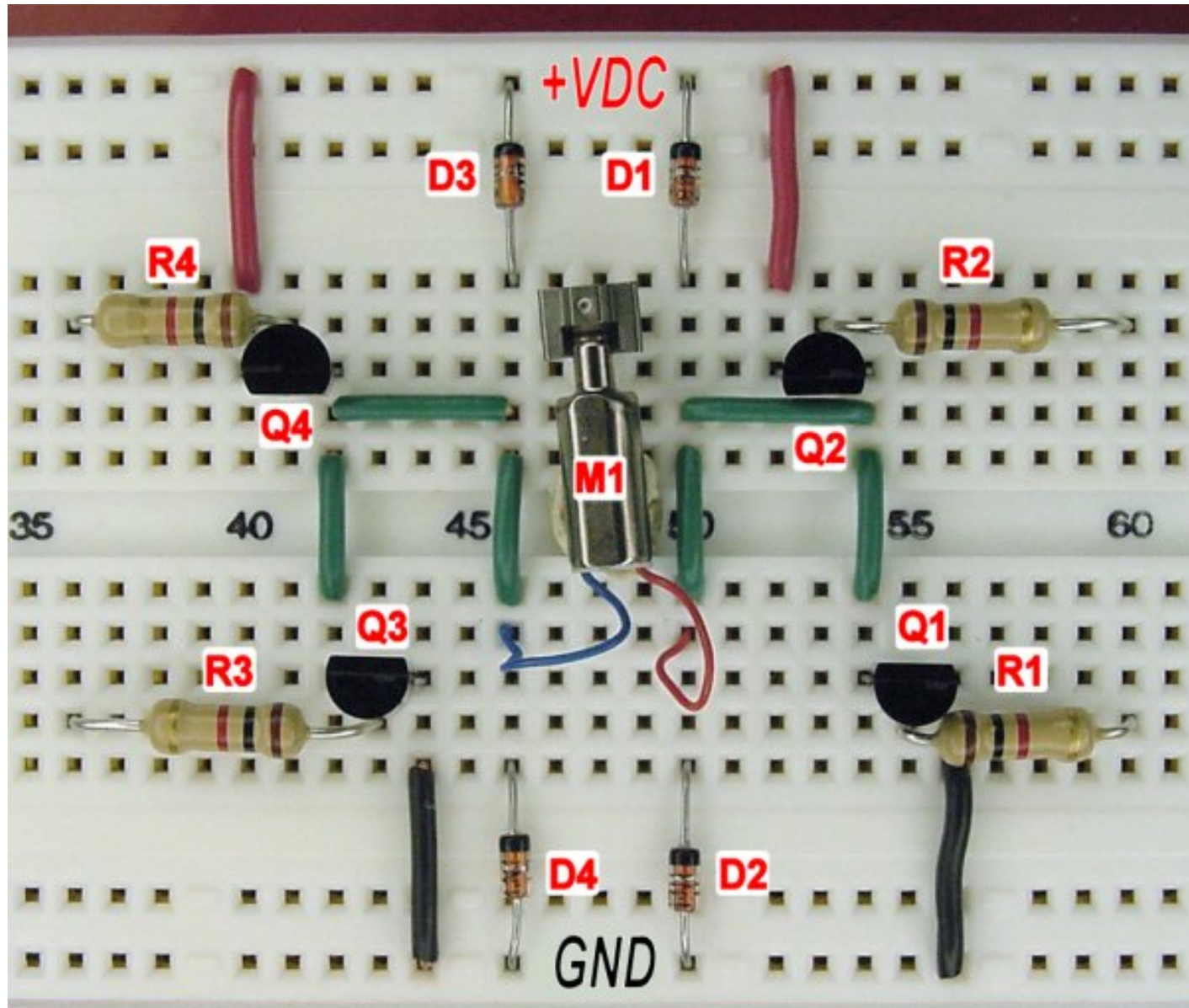


Good practices

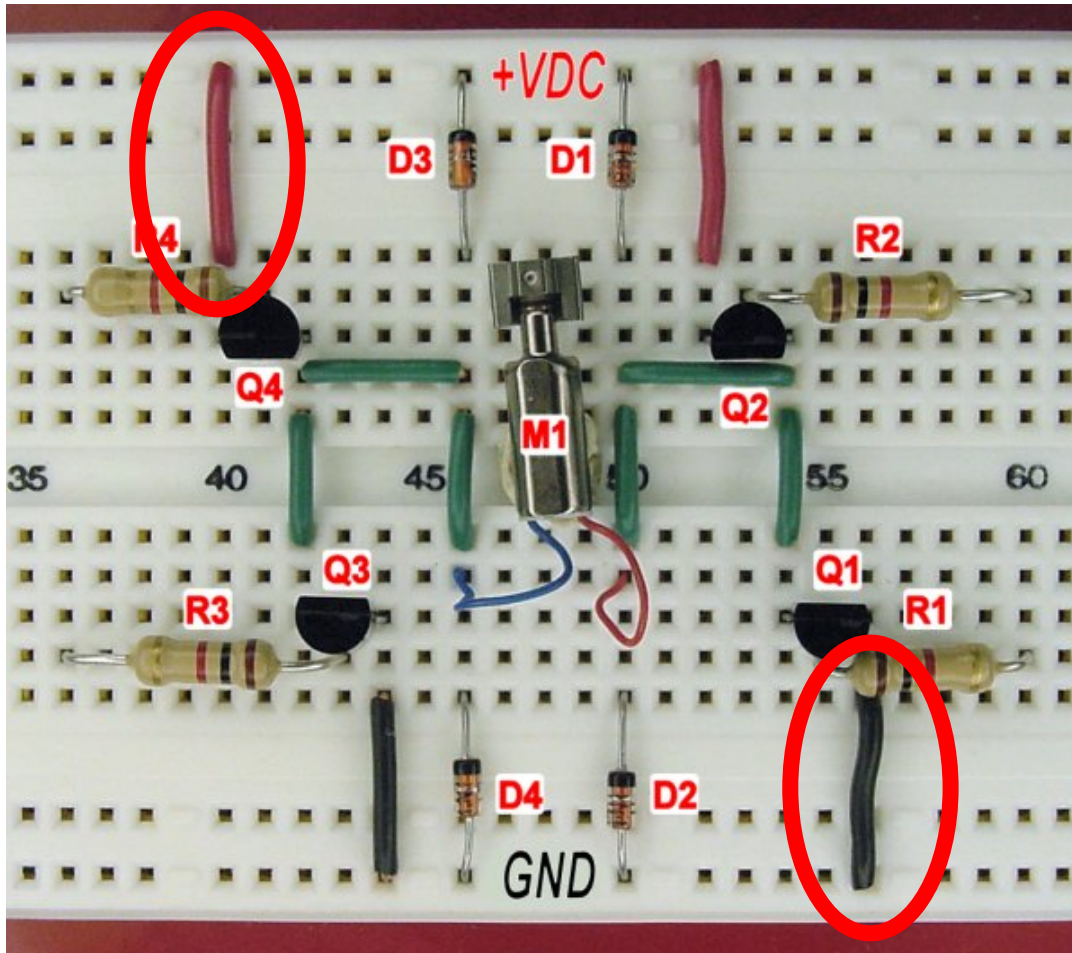

Colour : Red for Vdd, Black for ground

Good practices

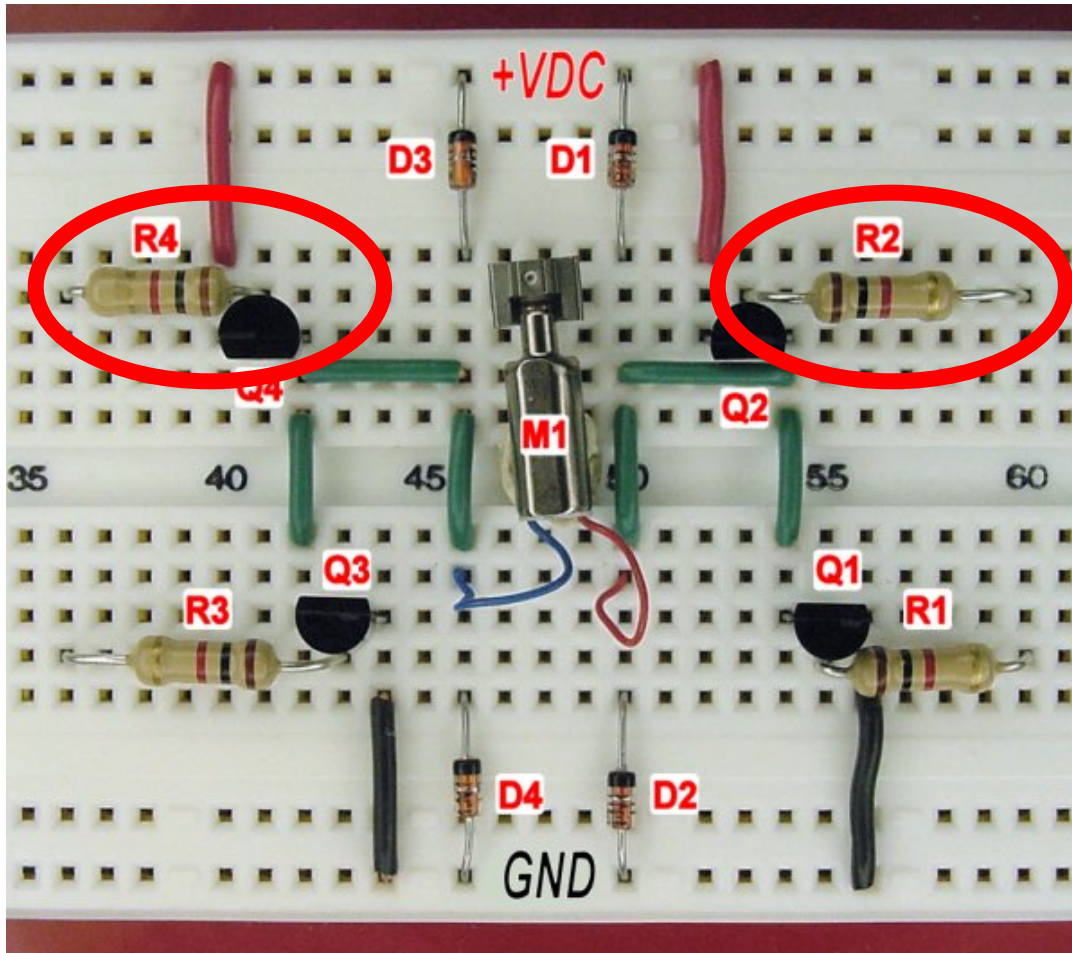

Colour : Neatly placed components

PCBs

- Homebrewing
 - Copper clad board
 - Pattern transfer (from photocopies)
 - Ferric chloride etching
- Commercial (2 layer boards)
 - 3 medium sized boards for Rs. 500/ to 1000/-
 - ~ 1 week for fabrication
 - Many vendors in major cities

From hobby to profession

Theory and practice

- Not separate entities, go hand in hand
- All the stuff from digital and analog circuits classes are used in practical circuits
- Need theory to push circuits' performance
- Need practice to be finally useful
 - Takes a lot more time than solving textbook problems!
- **BE METICULOUS, NOT SLOPPY!**

Links

The internet

- Circuit schematics
- Data sheets
- Troubleshooting information
- Many sites dedicated to hobbyists
 - <http://www.flashwebhost.com/circuit/index.php>
 - <http://www.juliantrubin.com/fairprojects/electronics/radio.html>
 - <http://my.integritynet.com.au/purdic/>
- Many sites dedicated to robotics, many colleges have active robotics groups

My pages

- <http://www.ee.iitm.ac.in/nagendra/E4332/2005/courseinfo.html>
 - E4332: VLSI design laboratory
 - Design of an AM radio and a digital clock on an integrated circuit
- <http://www.ee.iitm.ac.in/nagendra/E4332/2005/handouts/amradio-trf.pdf>
 - AM radio on a chip
 - Theory of Tuned frequency radios
 - Receiver block and schematic diagrams (more suitable for IC designs)
- <http://www.ee.iitm.ac.in/nagendra/E4332/2005/handouts/digital-clock.pdf>
 - Has information on crystal oscillators
- http://www.ee.iitm.ac.in/vlsi/courses/ec330_2010/start
 - Many experiments using CMOS inverters as amplifiers
- http://www.ee.iitm.ac.in/~nagendra/misc/20071006iitm_shaastra.pdf
 - Radios for the hobbyist