

# → Review of transmission line Theory


1. Usual circuit theory assumes physical dimensions of network to be  $\ll$  electrical wavelength ( $\lambda$ ). However, when size become comparable we need to move to a distributed element approach, characterized by transmission line (TL) theory.

There are 2 ways to approach TL theory:

- ① extending circuit theory, or
- ② field approach.

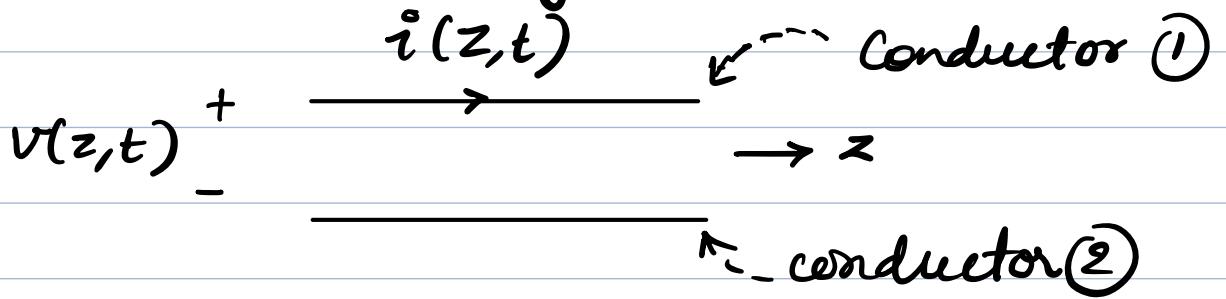2. We will start with approach #1.

Represent a TL by an abstract picture of 2 conductors along the  $z$  direction:



The 4 parameters required to characterize are:

$R \rightarrow$  series resistance  $\Omega/m$


$L \rightarrow$  series inductance  $H/m$

$G \rightarrow$  shunt conductance  $S/m$

$C \rightarrow$  shunt capacitance  $F/m$ .

} all per length.

The equivalent ckt model is:

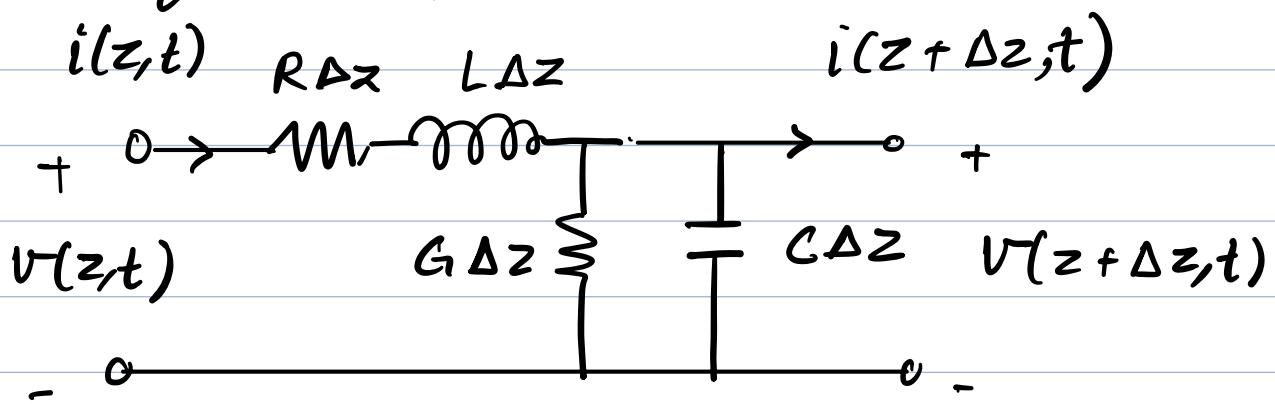

Applying KVL gives us:

$$V(z, t) - V(z + \Delta z, t) = R \Delta z i(z, t) + L \Delta z \frac{d i(z, t)}{dt}$$

Applying KCL gives us:

$$i(z, t) - G \Delta z V(z + \Delta z, t) - C \Delta z \frac{d V(z + \Delta z, t)}{dt} = i(z + \Delta z, t)$$

Standard manipulations follow, div by  $\Delta z$ , take the limit  $\Delta z \rightarrow 0$ , convert to phasors  
 (Recall:  $V(z, t) = \operatorname{Re} [V(z) \exp(j\omega t)]$ ),  
 and use  $\frac{d}{dt} \rightarrow j\omega$ , to get these eqns:

$$\frac{d V(z)}{d z} = - (R + j\omega L) I(z)$$

$$\frac{d I(z)}{d z} = - (G + j\omega C) V(z)$$

Called the Telegrapher eqns.

3. Very easy to solve these coupled eqns:  
(take another  $d/dz$ )

$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z), \quad \frac{d^2 I(z)}{dz^2} = \gamma^2 I(z)$$

$\gamma$  is the complex propagation constant,

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

and this admits two solutions : fwd & bwd waves,  $\exp(\pm \gamma z)$ .

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

[ Aside : why is  $e^{-\gamma z}$  fwd traveling ?

Convert from phasor to time domain :

$$V(z, t) = \text{Re} [ V_0^+ e^{-\gamma z} e^{j\omega t} ]$$

$$= \text{Re} [ V_0^+ e^{-\alpha z} \exp(j(\omega t - \beta z)) ]$$

$$= |V_0^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi_0)$$

To maintain the same phase front in the  $z-t$  coordinate space, i.e.  $\omega t - \beta z + \phi_0 = \text{const}$ , as time  $\uparrow$ ,  $z$  must also  $\uparrow$ .

This implies a right (fwd) travelling wave. ]

Further simplifications from Telegraphers eqns give  $\frac{V_0^+}{I_0^+} = Z_0 = -\frac{V_0^-}{I_0^-}$  where


$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$  is called the characteristic impedance of the IL.

The wavelength on the line is  $\lambda = \frac{2\pi}{\beta}$

and phase velocity  $v_p = \frac{\omega}{\beta} = \lambda f$ .

→ self study: Calculate all parameters for a lossless TL, i.e. when  $R = G = 0$ , including  $V, I$  expressions
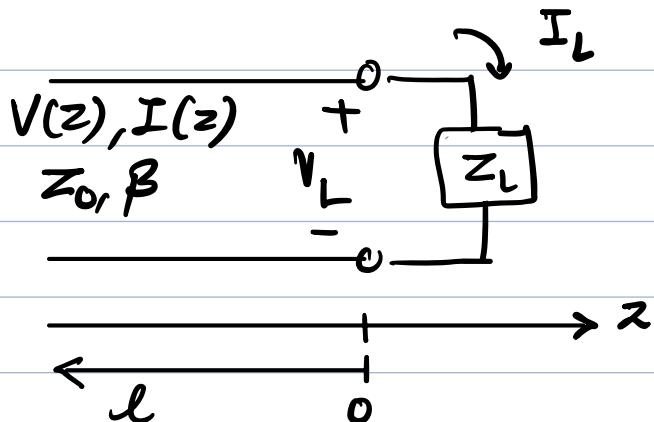
#### 4. Load Terminated TL. (Assume lossless)



$l$  increases in the  $-z$  direction.

To recap:  $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$   
 and  $I(z) = \frac{1}{Z_0} [V_0^+ e^{-j\beta z} - V_0^- e^{j\beta z}]$

∴ At the load end ( $z = 0$ ),  $Z_L = \frac{V(0)}{I(0)}$

and we define  $\Gamma$ , voltage reflection coefficient as  $\Gamma = \frac{V_o^-}{V_o^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$ ,

where  $V_o^-$  was eliminated.

Implications:

- Ⓐ In general when  $\Gamma \neq 0$ , we have both forward & backward waves leading to standing waves due to interference.
- Ⓑ For  $\Gamma = 0$ ,  $Z_L = Z_0$ , called the matched load condition.
- Ⓒ The time avg power in the line is

$$P_{avg} = \frac{1}{2} \operatorname{Re} [V(2)I(2)^*] = \frac{1}{2} \frac{|V_o^+|^2}{Z_0} (1 - |\Gamma|^2)$$

can be seen as power sent by source minus power reflected by load.

Sometimes reported as "Return loss" RL

$$RL = 20 \log |\Gamma| \text{ (dB)}$$

$$\Rightarrow |\Gamma| = 0 \Rightarrow RL \rightarrow \infty$$

$$|\Gamma| = 1 \Rightarrow RL \rightarrow 0 \text{ dB}$$

- Ⓓ In general we will not have  $Z_L = Z_0$

so we will have a voltage wave, i.e.

$$\begin{aligned}|V(z)| &= |V_0^+| \left| e^{-j\beta z} + \Gamma e^{j\beta z} \right| \\&= |V_0^+| \left| 1 + \Gamma e^{2j\beta z} \right| \\&= |V_0^+| \left| 1 + \Gamma e^{-2j\beta l} \right|,\end{aligned}$$

where  $z = -l$  measured from load end.

$$\therefore V_{\max} = |V_0^+| (1 + |\Gamma|)$$

$$V_{\min} = |V_0^+| (1 - |\Gamma|)$$

$$\text{VSWR (voltage standing wave ratio)} = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}, \quad 1 \leq \text{VSWR} \leq \infty.$$

$\text{VSWR} = 1 \Rightarrow \text{matched load.}$

(e) with  $\Gamma = |\Gamma| e^{j\theta}$

$$|V(z)| = |V_0^+| \left| 1 + |\Gamma| e^{j(\theta - 2\beta l)} \right|,$$

$\beta = 2\pi/\lambda$ .  $\Rightarrow l \rightarrow l + \lambda/2$  leads to the same value of  $|V(z)|$  whereas  $l \rightarrow l + \lambda/4$  leads to a max value becoming a min value or vice versa.