

5/9/2023

EES320W Analog IC Design - Lec 1

HW/Projects : 20%.

Quiz 1 : 20%.

Quiz 2 : 20%.

Final Exam : 40%.

ani@ee.iitb.ac.in

100%.

Ref. Textbook



Behzad Razavi:

"Design of Analog
CMOS Integrated
Circuits"




Classes : Every Tue & Thu @ 4-5:15 pm

Alternate Fri @ ?

1) MOSFETs

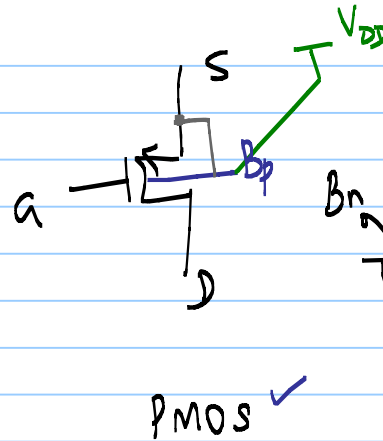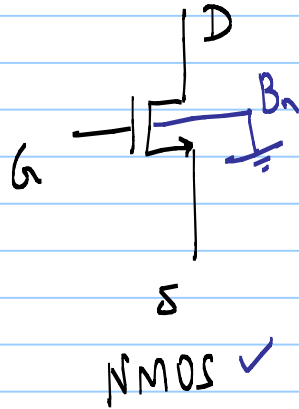




CMOS IC

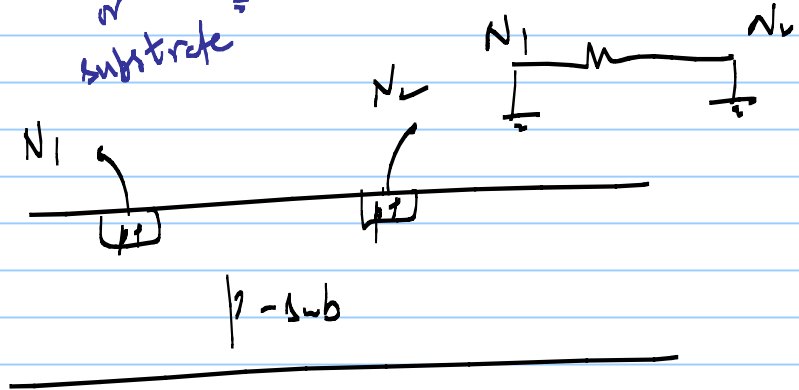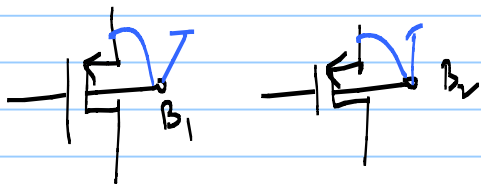
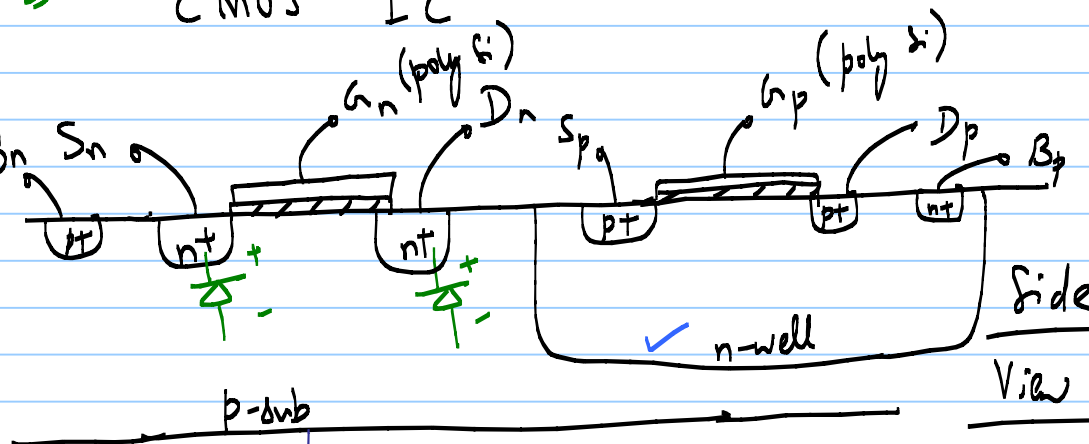


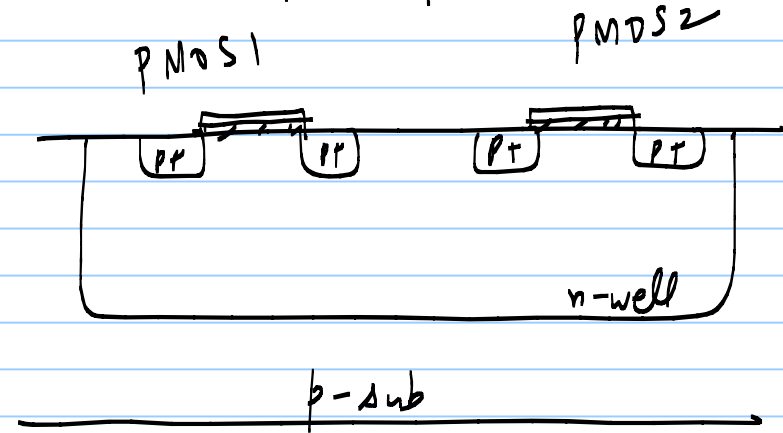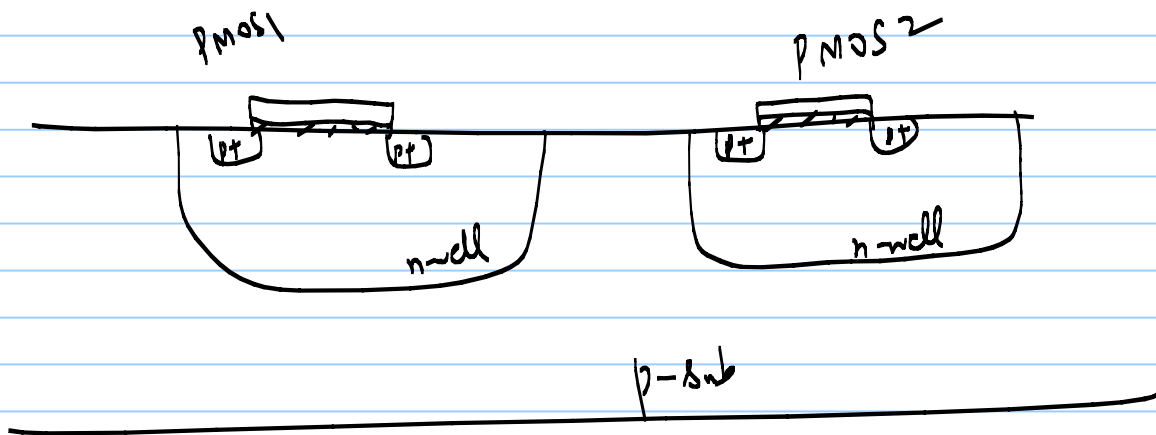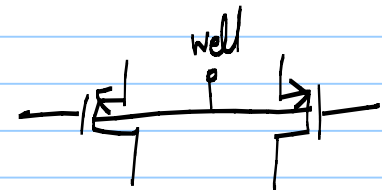2) Resistors

- * poly R - 10's Ω
- * Metal R - m Ω - Ω "silicide"
- * n-well R - 10's Ω "salicide"
- * diffusion R - k Ω

OFF MOSFET (leakage)
 triode MOS (non-linear)




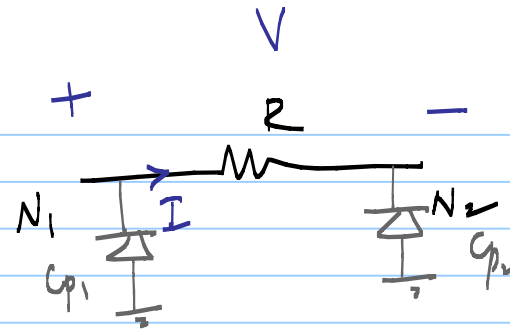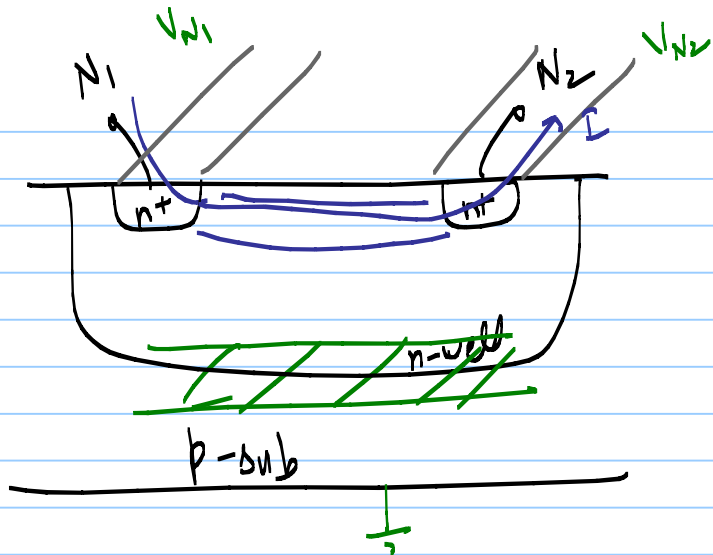



$$I = \frac{1}{R} (V) + \frac{1}{(\quad)} \cdot (V)^2 + \frac{1}{(\quad)} (V)^3 + \dots$$

non-linear R



3) Capacitors

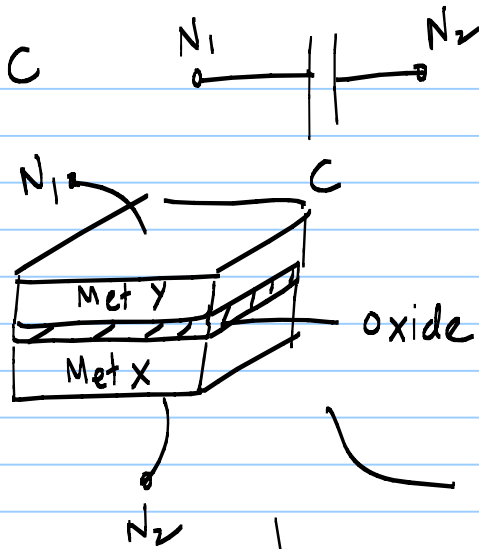


Not dense enough

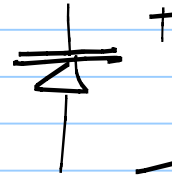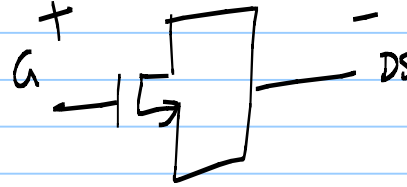

Non linear cap.

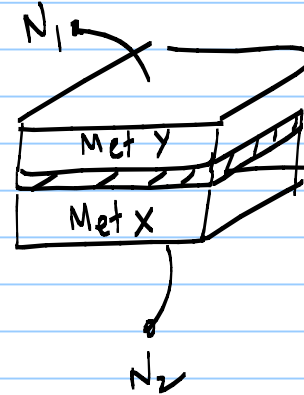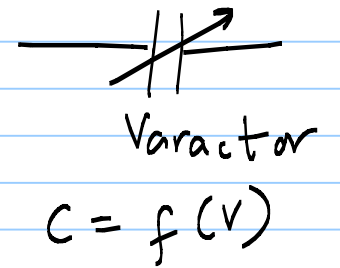


larger C

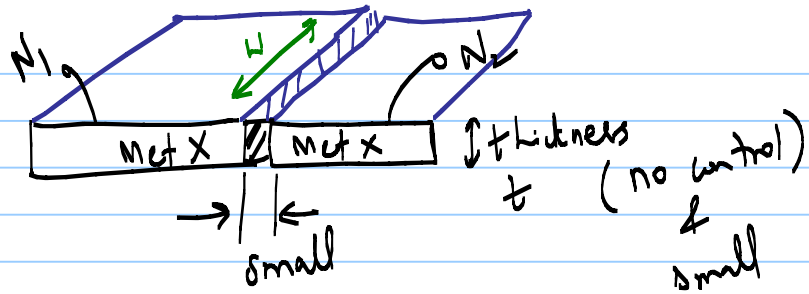


Area of plate = $w \cdot t$

low density cap

top view

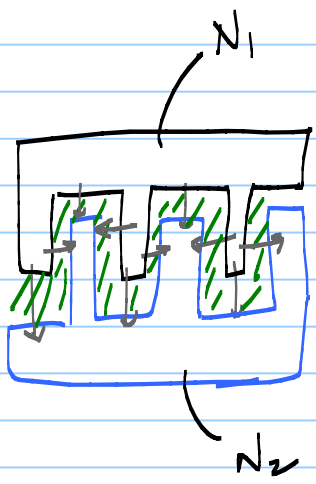

larger cap

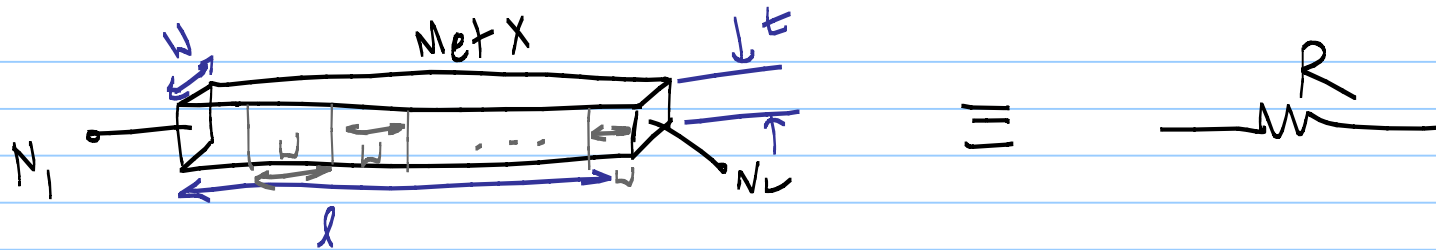

$$R = \frac{\rho \cdot l}{A} = \frac{\rho \cdot l}{w \cdot t} = \left(\frac{\rho}{t} \right) \cdot \left(\frac{l}{w} \right)$$


"sheet" resistance

in Ω / \square

fixed
for a


given metal
layer

number of
squares


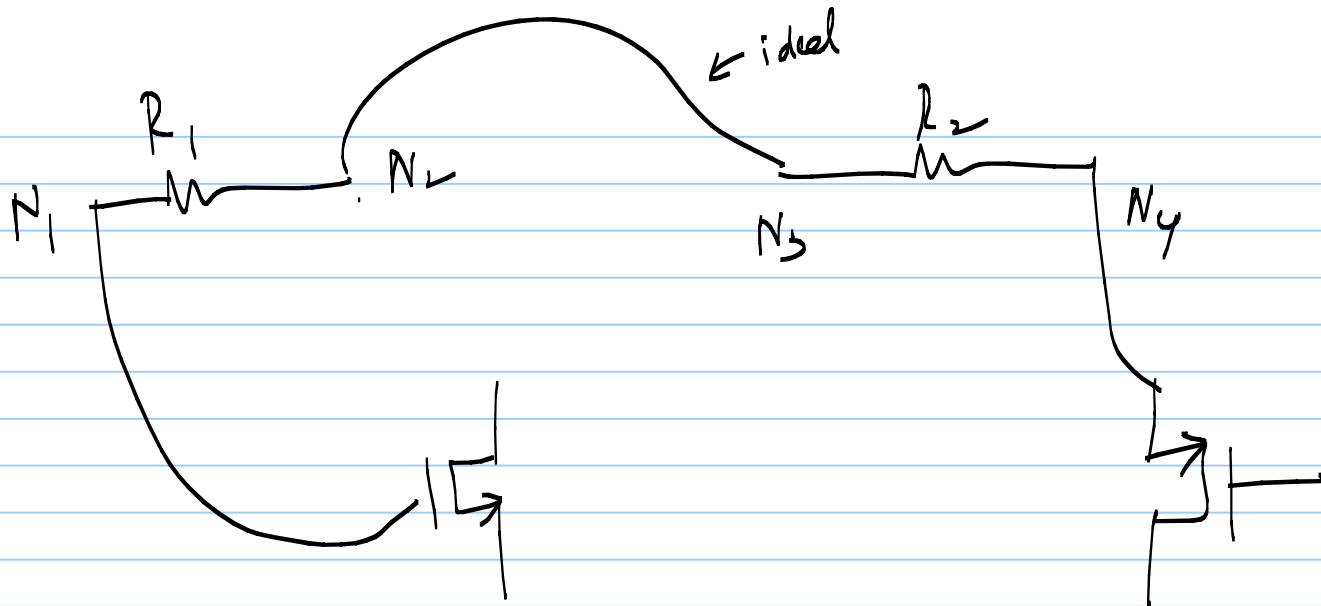


14/9/2023

Lec 2


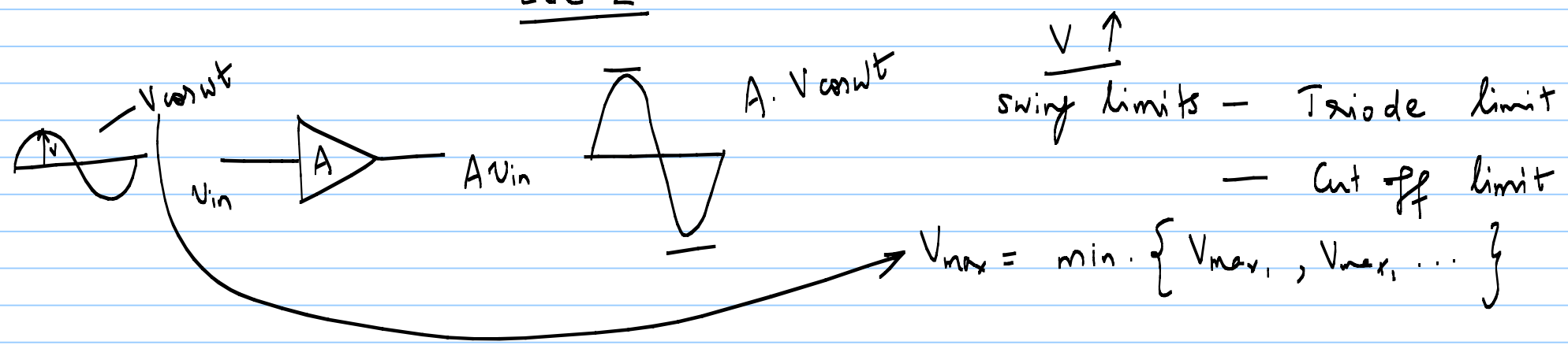


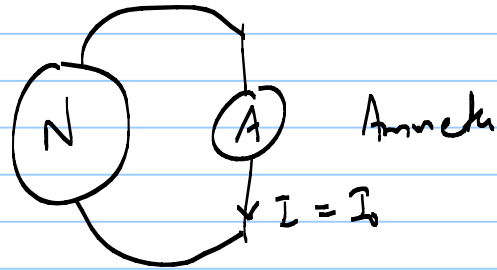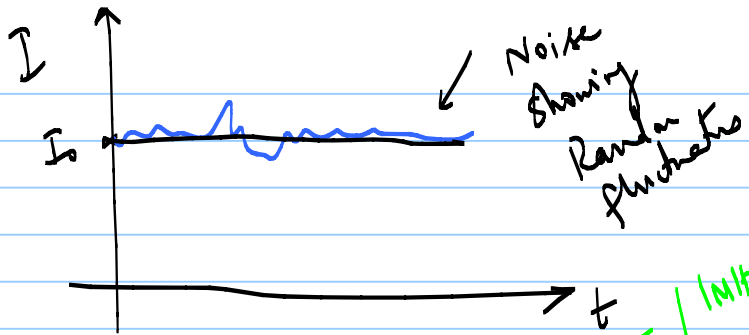$V \downarrow$ → Noise limits the dynamic range on the lower end
→ Random processes → lead to uncertainties
in V_A & I_D inside device



Power Spectral Density

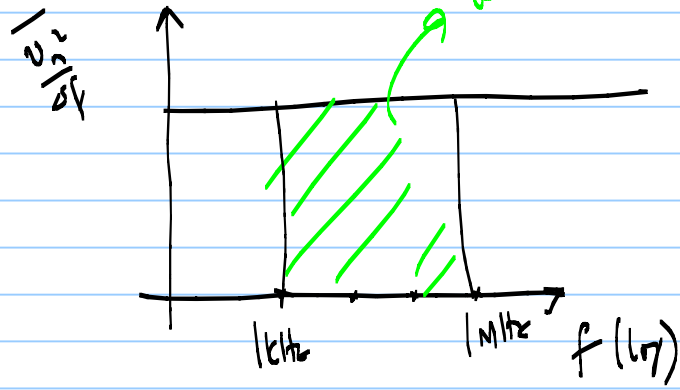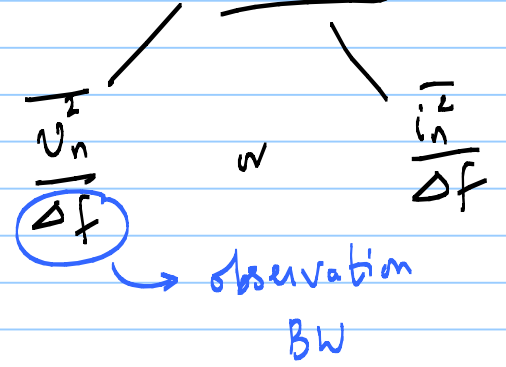area = $\frac{V_n^2}{1\text{kHz}}$ / $\frac{1\text{MHz}}$



$10^{-18} \text{ V}^2/\text{Hz}$

$\frac{V_n^2}{1\text{MHz}} / \frac{1\text{kHz}}{1\text{kHz}} = 10^{-18} \text{ V}^2/\text{Hz}$


Noise in Devices

1) Resistor R N_1 — R — N_2

"thermal" noise

(noise depends on abs. temp. T)

"white" noise — flat PSD

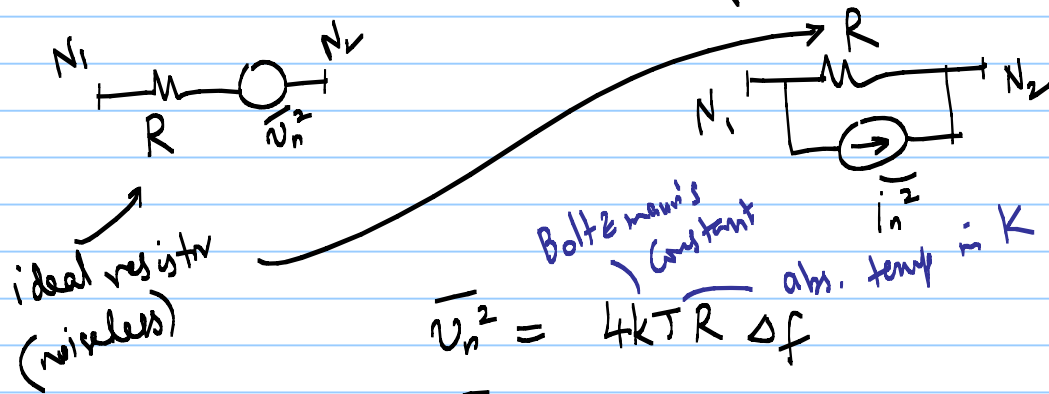

$$\overline{v_n^2} = 4kTR \Delta f$$



$$\frac{\overline{v_n^2}}{\Delta f} = 4kTR$$

$$\overline{i_n^2} = \frac{\overline{v_n^2}}{R^2} = \frac{4kT}{R} \Delta f$$


$$\frac{\overline{i_n^2}}{\Delta f} = \frac{4kT}{R} = 4kTG$$

2) L, C, M - Noiseless

3) MOSFETs

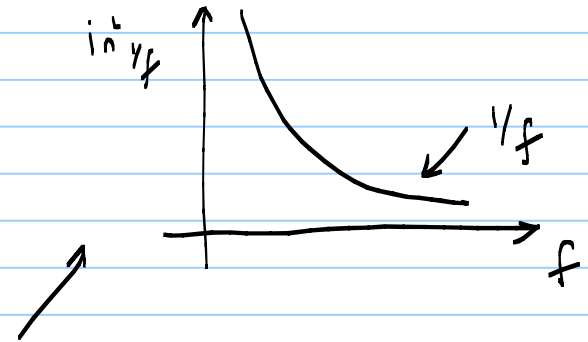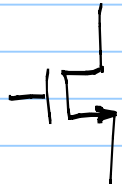


a) Flicker noise
or
 $1/f$ noise

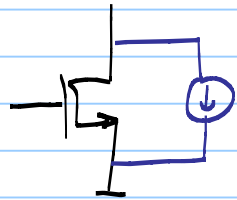


$$\overline{i_{n,1/f}^2} = \frac{K_f \cdot g_m^2}{W \cdot L \cdot C_{ox}} \cdot \frac{1}{f} \cdot \Delta f$$

significant @ low freq.

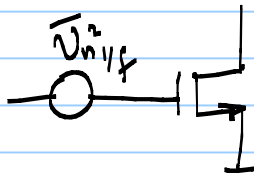

$$\overline{v_{n,1/f}^2} = \frac{K_f}{W L C_{ox}} \cdot \frac{1}{f} \cdot \Delta f$$

b) Drain Thermal Noise

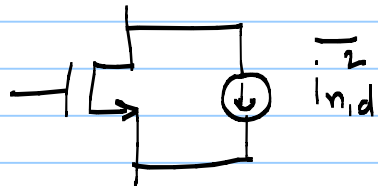

linear region


$$\overline{i_{nd}^2} = 4kT g_{ds} \Delta f$$

$$\left. \frac{\partial I_D}{\partial V_{DS}} \right|_{op. pt.}$$



saturation region

$$\overline{i_{nd}^2} = \frac{8kT}{3} g_m \Delta f$$

flat PSD
"white" noise

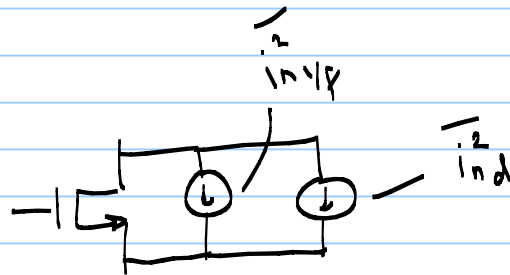


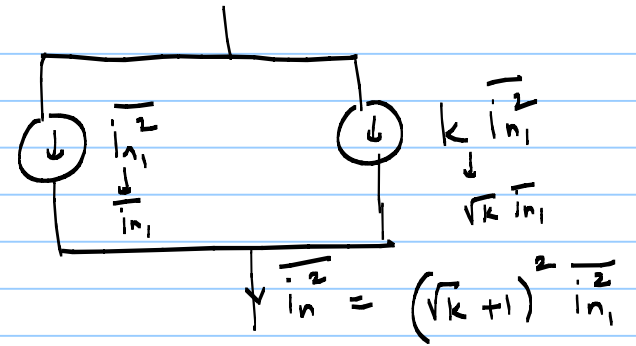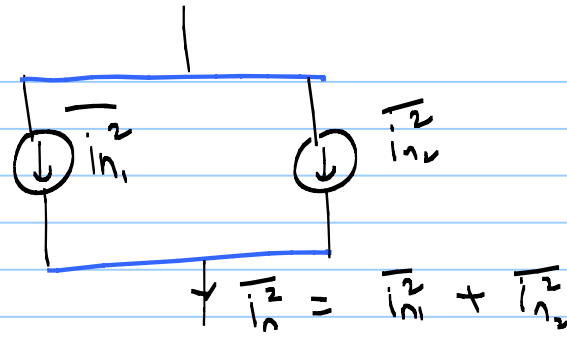
Correlated vs Uncorrelated Noise
 add amplitudes vs add mean squared values



partial correlation


- correlated part
- un correlated part

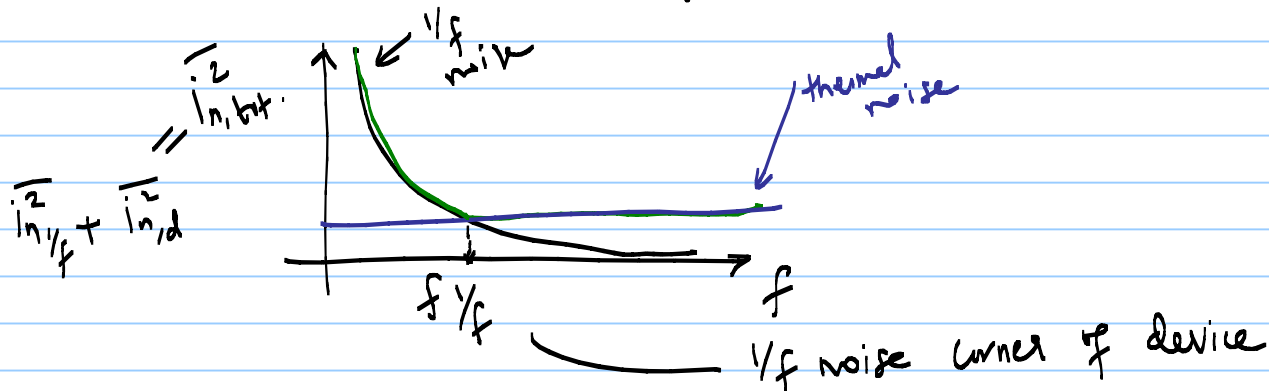

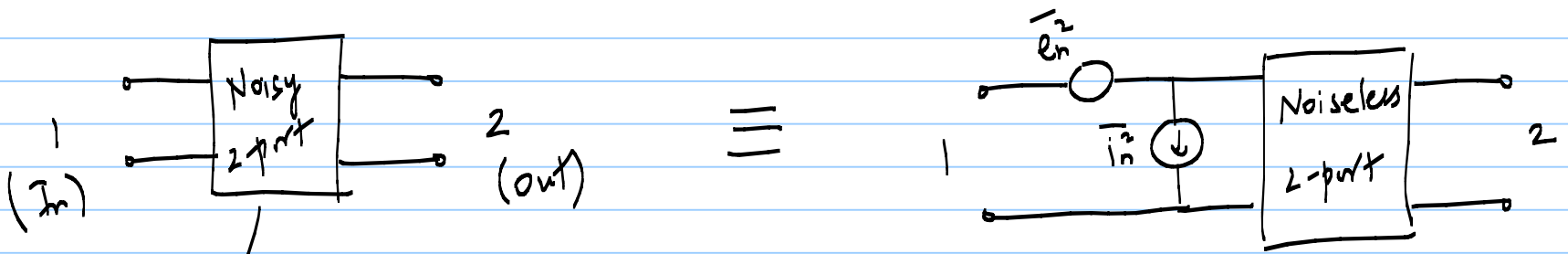



MOSFETs
R's, C, L

fictitious
= abstraction
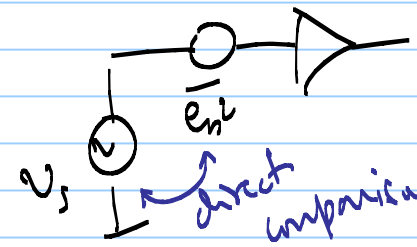
$$\begin{cases} \bar{e}_n = \text{input-referred noise voltage} \\ \bar{i}_n = \text{input-referred noise current} \end{cases}$$

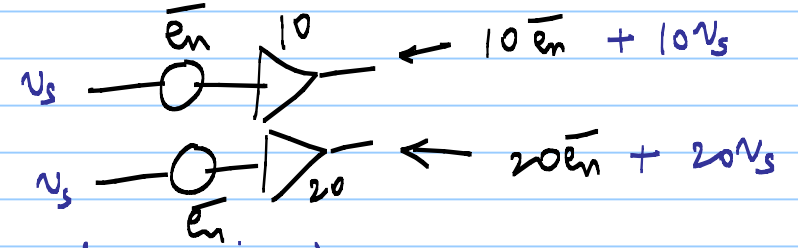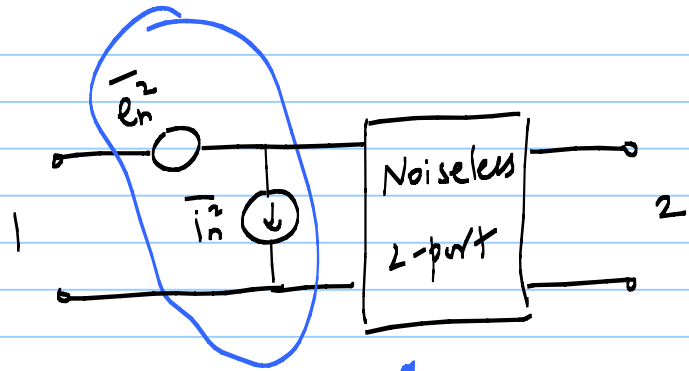
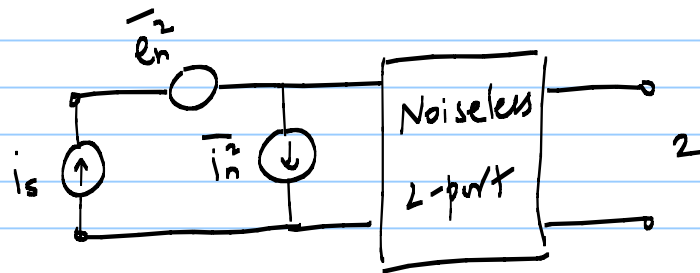
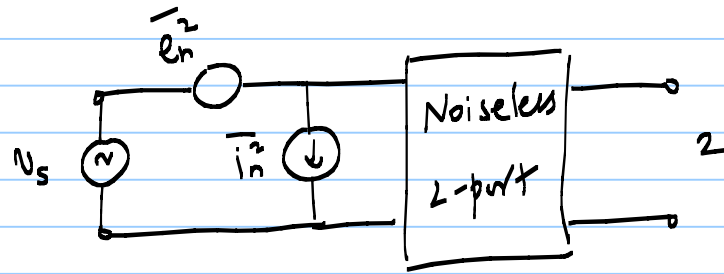
direct comparison \rightarrow SNR degradation is known












characteristic
of a particular
2-port

should not
depend on
 R_s, R_L



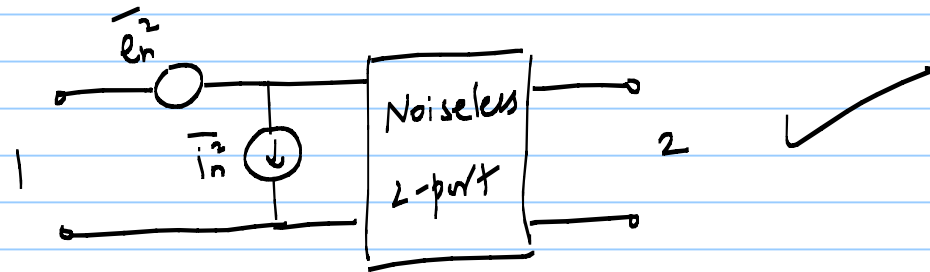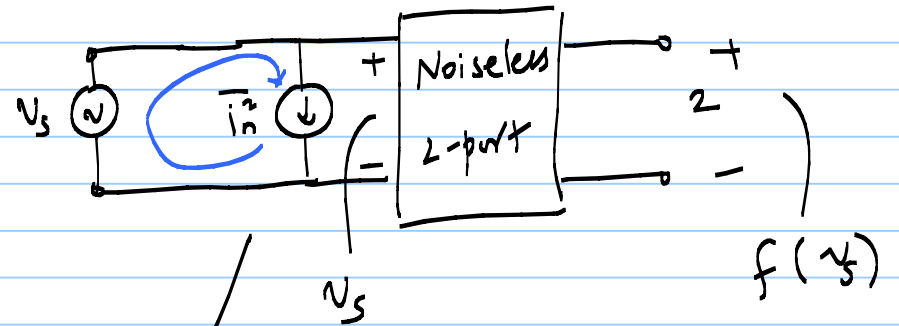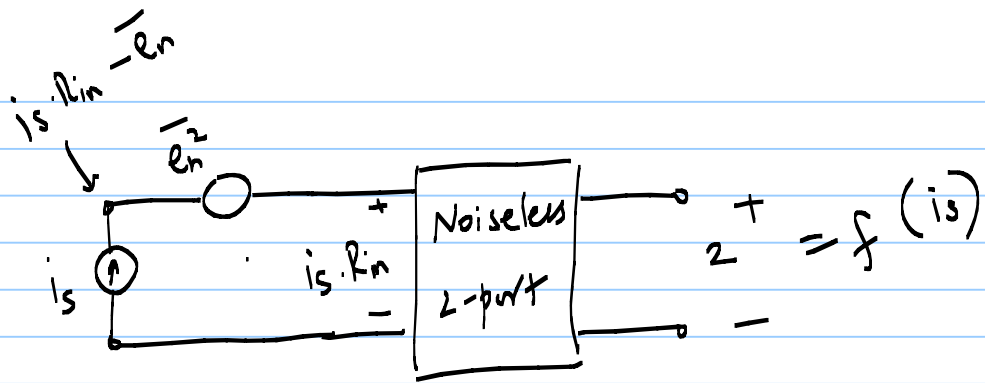

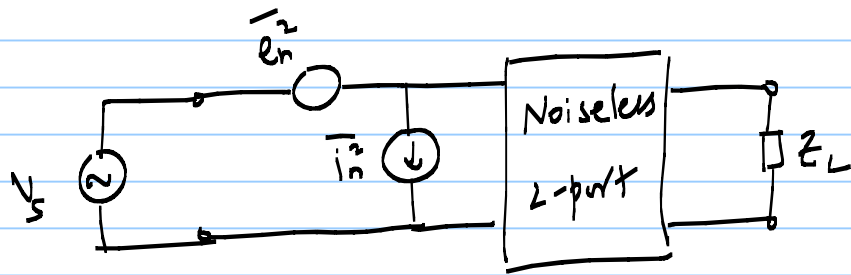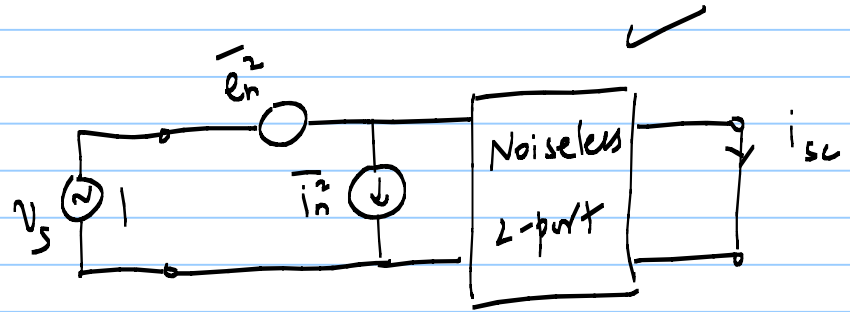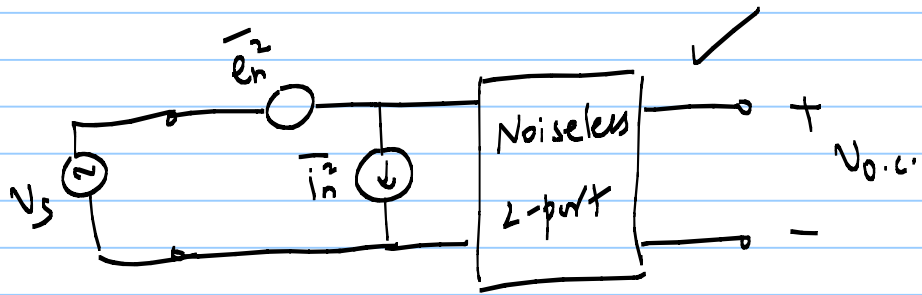


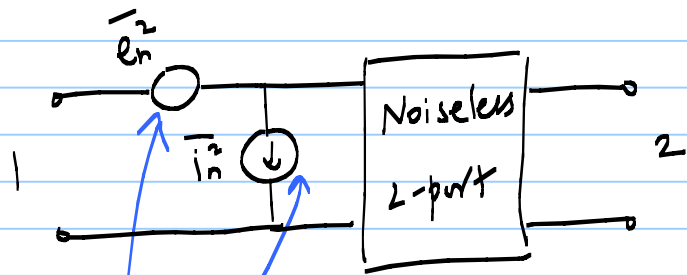


in general,
 e_n & e_{n2} are
partially correlated

19/9/23


Lec 3

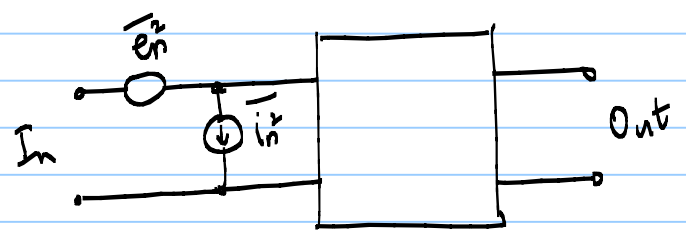


Example #1

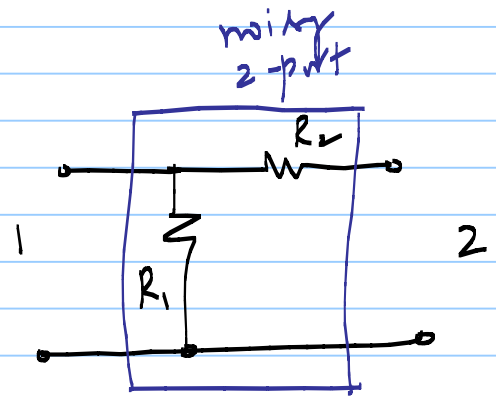


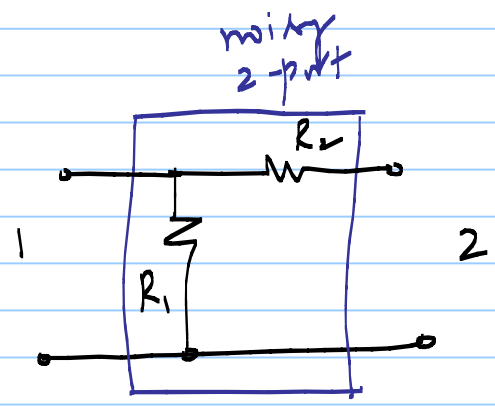
$\overline{e_n^2} = ?$
 $\overline{i_n^2} = ?$



|||

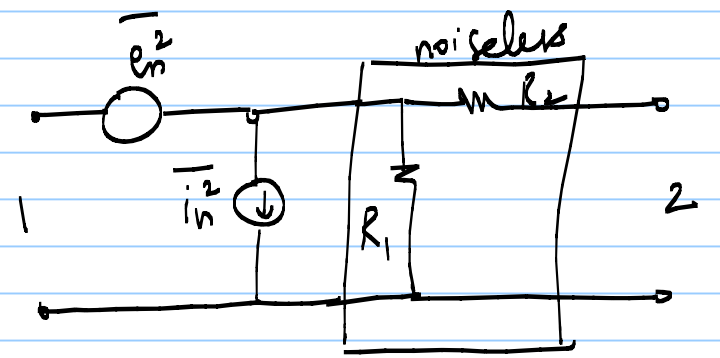

Case 1 $|s_r|$

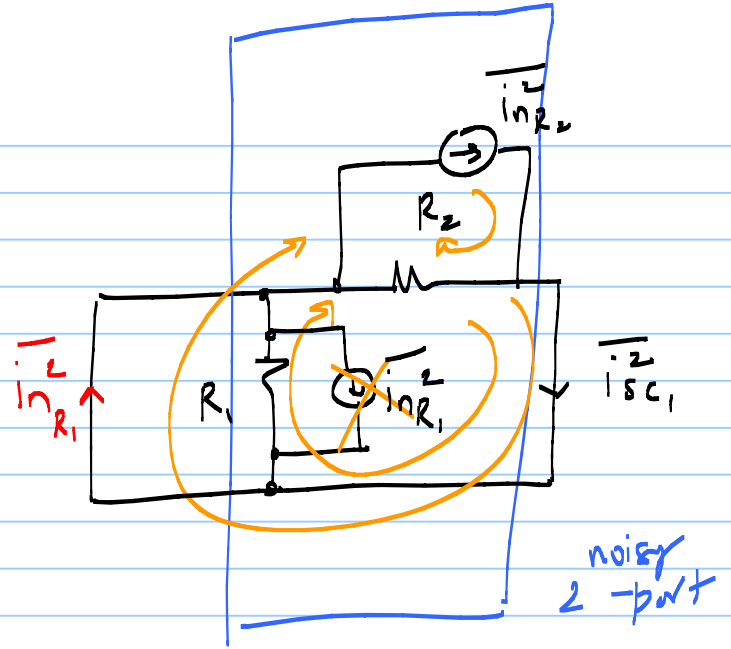
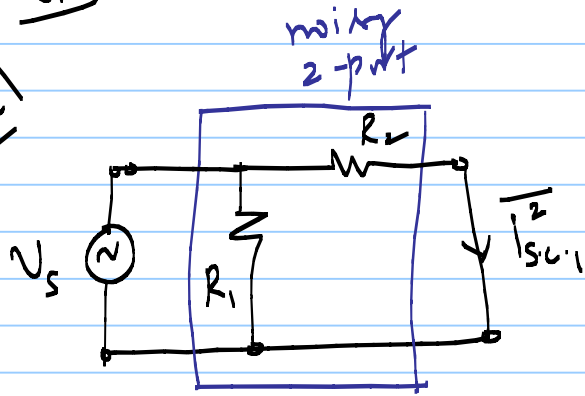


$\frac{i_{sc1}^2}{R_1} \rightarrow i_{sc1}^2(R_1) = 0$

$\frac{i_{sc1}^2}{R_2} \rightarrow i_{sc1}^2(R_2) = i_{nr2}^2 = \frac{4kT}{R_2} \Delta f$

$i_{sc1}^2 = \frac{4kT}{R_2} \Delta f$

Case 2

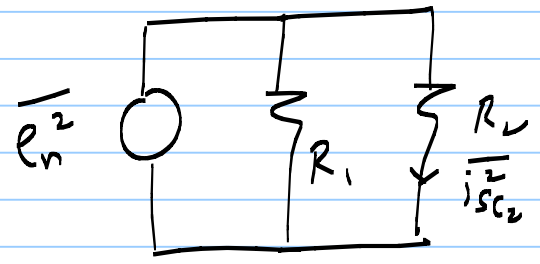
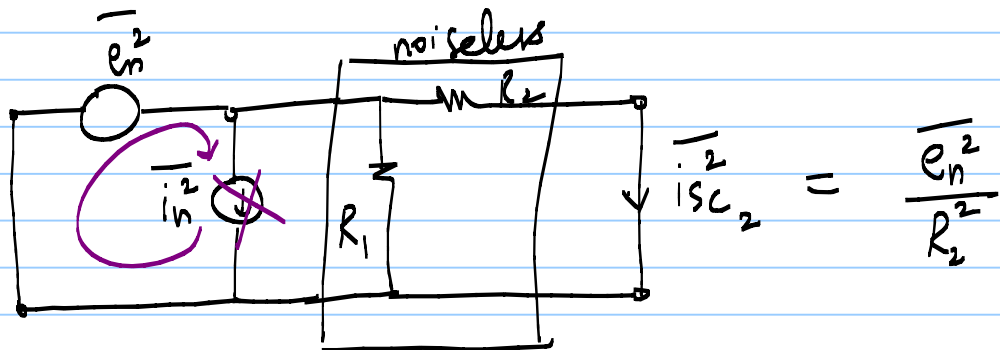


$$\overline{i_{sc1}^2} = \overline{i_{sc2}^2}$$

$$\frac{4kT}{R_L} \cdot \Delta f = \frac{e_{n2}^2}{R_L^2} \Rightarrow \frac{e_{n2}^2}{\Delta f} = 4kTR_L \left(\frac{V^2}{Hz} \right)$$


Case 1

$$\overline{i_n^2}$$

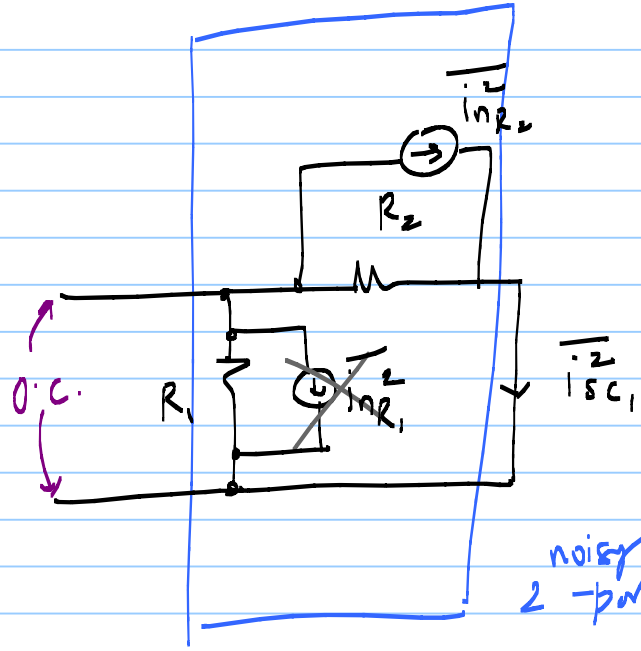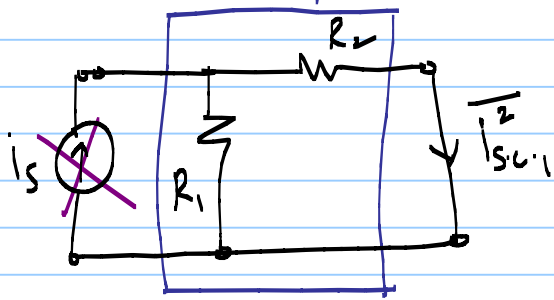

$$\overline{i_{nR_1}^2} : \overline{i_{sc1}^2 (R_1)} = \overline{i_{nR_1}^2} \cdot \left(\frac{R_1}{R_1 + R_2} \right)^2$$
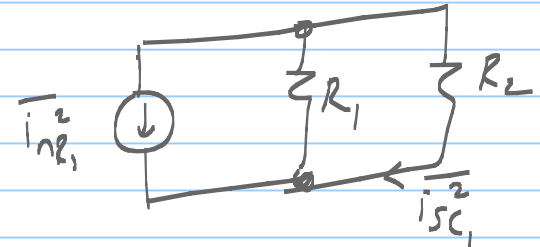
$$\overline{i_{nR_2}^2} : \overline{i_{sc1}^2 (R_2)} = \overline{i_{nR_2}^2} \cdot \left(\frac{R_2}{R_1 + R_2} \right)^2$$




$$\frac{\overline{i_{sc,1}^2}}{\Delta f} = \frac{4kT}{R_1} \times \frac{R_1^2}{(R_1+R_2)^2} + \frac{4kT}{R_2} \times \frac{R_2^2}{(R_1+R_2)^2}$$

$$= \frac{4kT}{(R_1+R_2)^2} \{ R_1 + R_2 \} = \frac{4kT}{R_1+R_2}$$

$$\overline{i_{sc,1}^2} = \frac{4kT}{R_1+R_2} \cdot \Delta f$$

Case 2

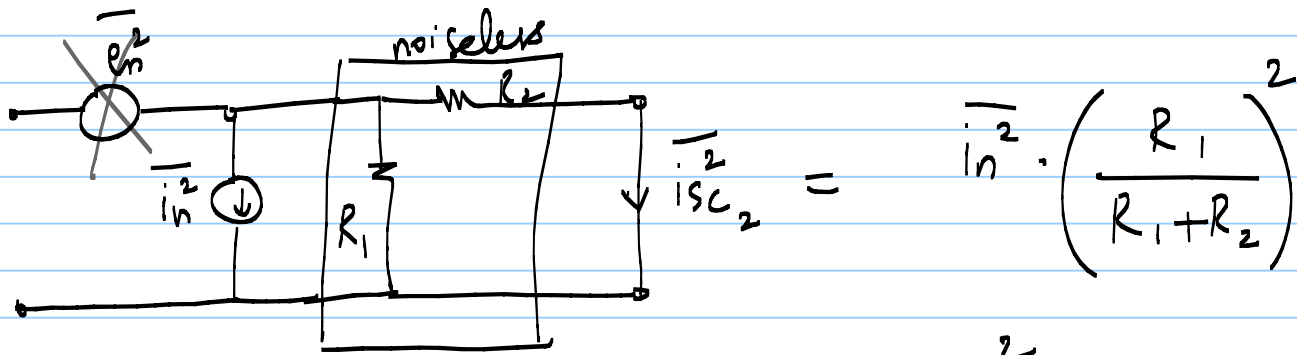

$$\overline{i_{sc1}^2} = \overline{i_{sc2}^2} \Rightarrow \overline{i_n^2} \left(\frac{R_1}{R_1 + R_2} \right)^2 = \frac{4kT}{R_1 + R_2} \cdot \Delta f$$

$$\frac{\overline{i_n^2}}{\Delta f} = \frac{4kT}{R_1} \left(1 + \frac{R_2}{R_1} \right) = \frac{4kT}{R_1} + 4kT \cdot \frac{R_2}{R_1^2} \left(\frac{A^2}{Hz} \right)$$


$$\frac{e}{\Delta f} |S_{n2}| = 4kTR_2 \left(\frac{V^2}{Hz} \right)$$

noise of R_2
why

partially
correlated

$$\frac{e}{\Delta f} |S_{i2}| = \frac{4kT}{R_1} + 4kT \cdot \frac{R_2}{R_1^2} \left(\frac{A^2}{Hz} \right)$$



noise of R_1 & R_2

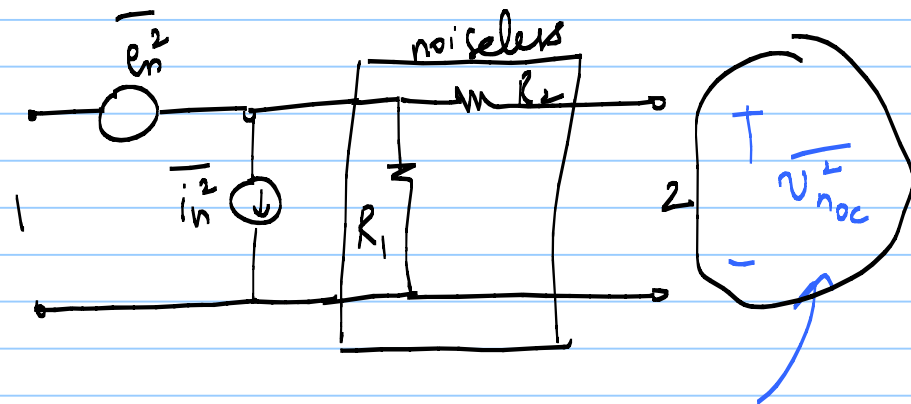


HW

Repeat with open circuit @ port 2
Should get same answer

Example #2

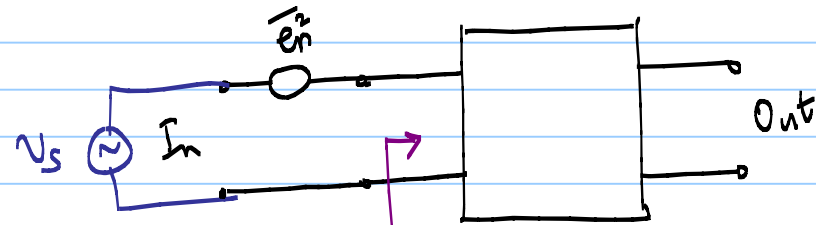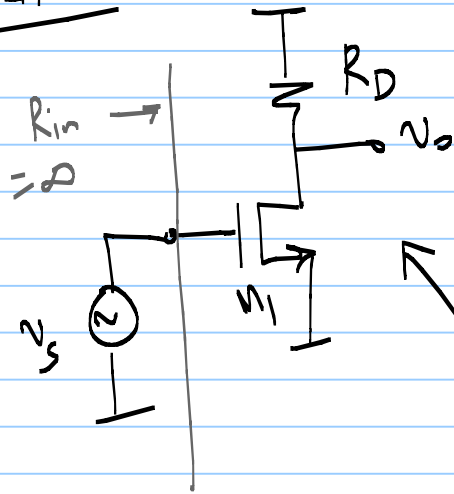


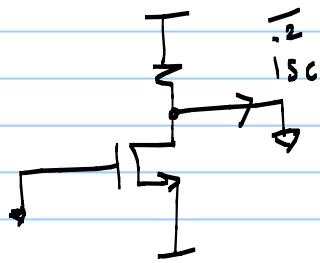$R_{in} = \infty$
→ no i_n input referred noise current



Low-frequency $\overline{e_n} = ?$


Case 1:

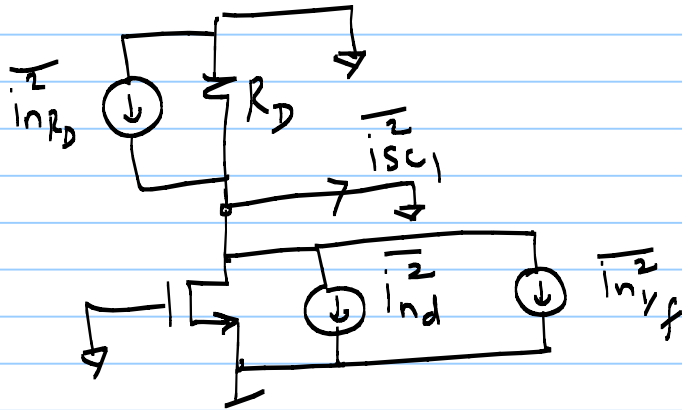

$$\overline{i_{sc1}^2} = \overline{i_{n,R_D}^2} + \overline{i_d^2} + \overline{i_{n,gf}^2}$$



$$e_{n1}^2 = \frac{\overline{i_{n,R_D}^2} + \overline{i_d^2} + \overline{i_{n,gf}^2}}{g_m^2}$$

Case 2:

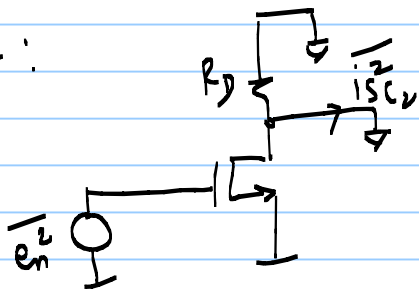

$$\overline{i_{sc2}^2} = g_m^2 \cdot e_{n1}^2$$
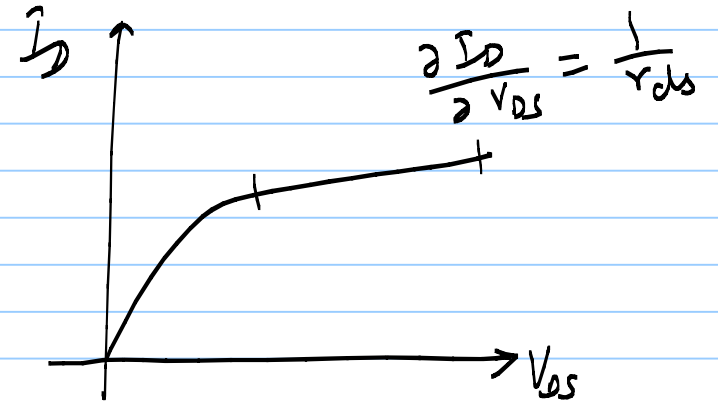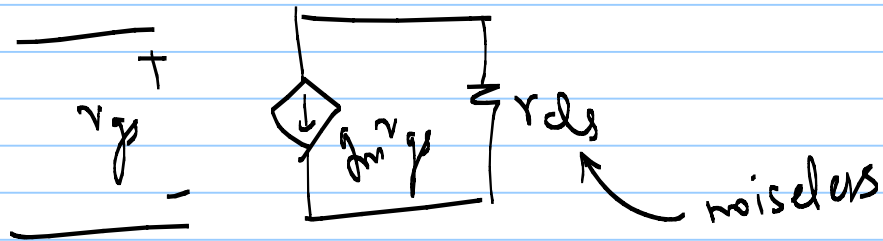
$$\frac{\Delta v_{sc}^2}{\Delta f} = \frac{4kT}{g_m^2 R_D} + \frac{8kT}{3g_m} + \frac{k_f}{W \cdot L \cdot C_{ox}^2} \cdot \frac{1}{f}$$




$\overline{e_n^2}$ & $\overline{i_n^2}$ → measure SNR degradation due to the 2-port

CSA

$$\frac{\overline{e_n^2}}{\Delta f} = \frac{4kT}{g_m^2 R_D} + \frac{8kT}{3g_m} + \frac{k_f}{W.L. C_{ox}} \cdot \frac{1}{f}$$

* Want to reduce $\overline{e_n^2}$

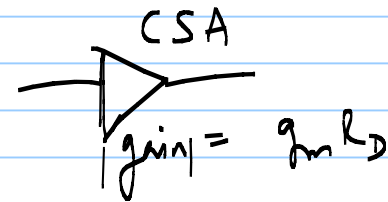

keep $g_m R_D$ constant

$$\frac{\Delta \omega^2}{f} = \frac{4kT}{g_m(g_m R_D)} + \frac{8kT}{3g_m} + \frac{k_f}{W \cdot L \cdot C_{ox}} \cdot \frac{1}{f}$$

reduce
by $\uparrow g_m$


reduce
by $\uparrow g_m$

reduce by
 $\uparrow W \& L$
keeping $\frac{W}{L}$ constant

$\uparrow g_m$ by
 $\uparrow I_{bias}$ or $\uparrow \left(\frac{W}{L}\right)$ or both



21/9/2023

Lec 4



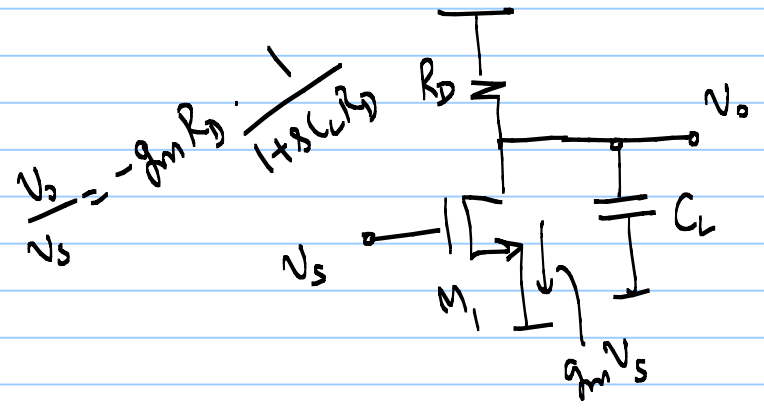


$e_n^2 = ?$

$e_n^2 =$ same as before
(without C_L)

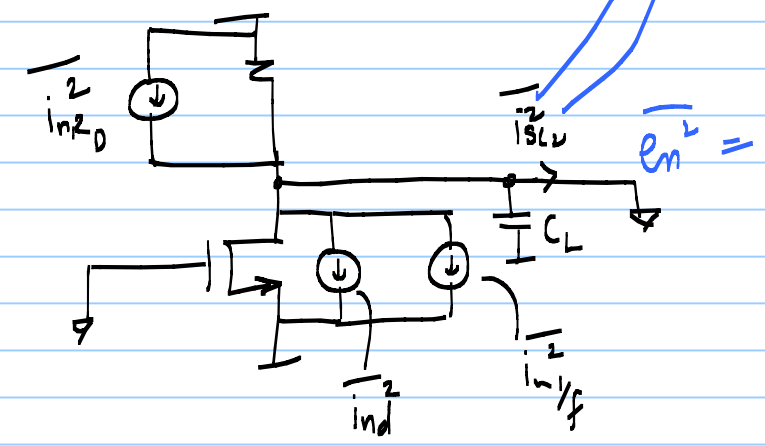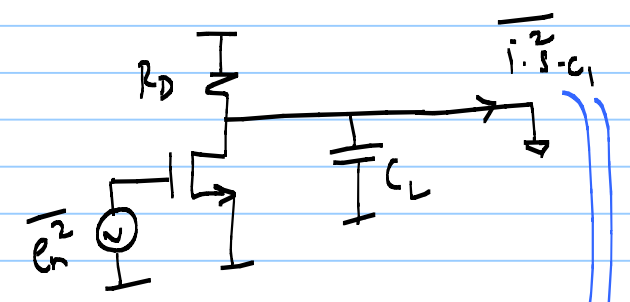

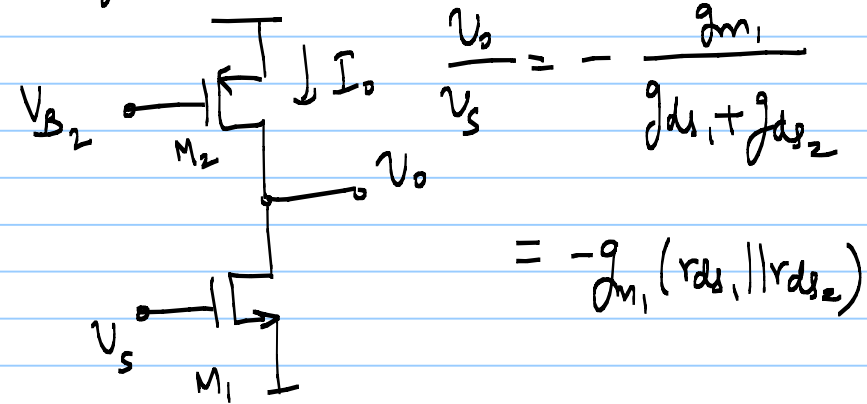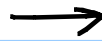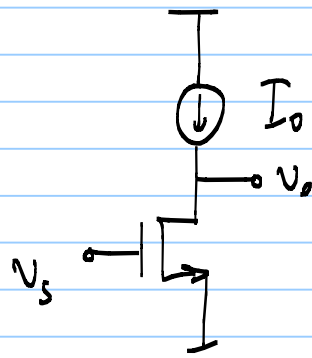Example #3 CSA with active load (only thermal noise)




$$\frac{v_o}{v_s} = - \frac{g_{m1}}{g_{ds1} + g_{ds2}}$$

$$= -g_{m1} (r_{ds1} || r_{ds2})$$


$\overline{i_n}$ doesn't exist
because $R_{in} = \infty$

Case 2:

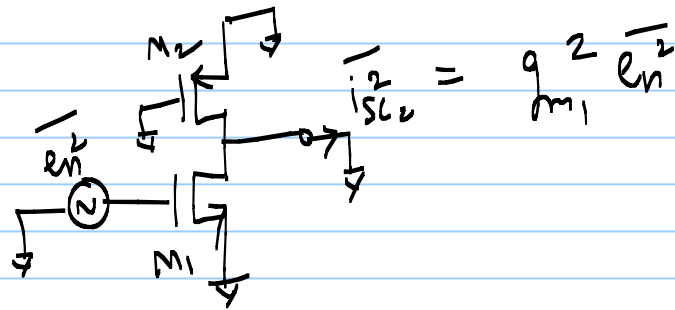

$$\overline{i_{sc2}^2} = g_{m1}^2 \overline{e_n^2}$$

Case 1:

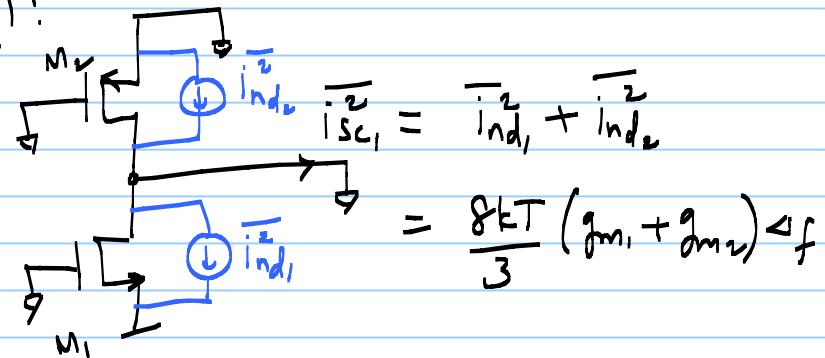

$$\overline{i_{sc1}^2} = \overline{i_{nd1}^2} + \overline{i_{nd2}^2}$$

$$= \frac{8kT}{3} (g_{m1} + g_{m2}) \Delta f$$



$$g_{m1}^2 \overline{e_n^2} = \frac{8kT}{3} (g_{m1} + g_{m2}) \Delta f$$

$$\frac{\overline{e_n^2}}{\Delta f} = \underbrace{\frac{8kT}{3g_{m1}}}_{M_1} + \underbrace{\frac{8kTg_{m2}}{g_{m1}}}_{M_2}$$


Low Noise : $\uparrow g_{m1}$ and $\downarrow g_{m2}$

Example #4



CGA

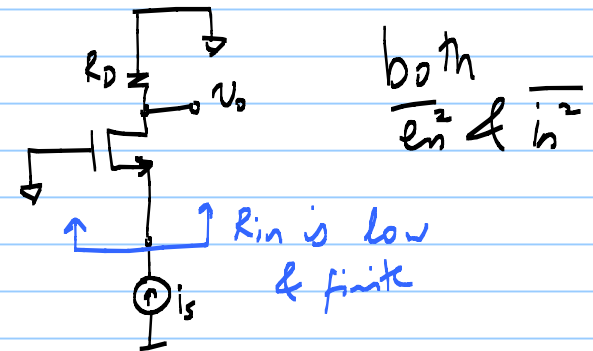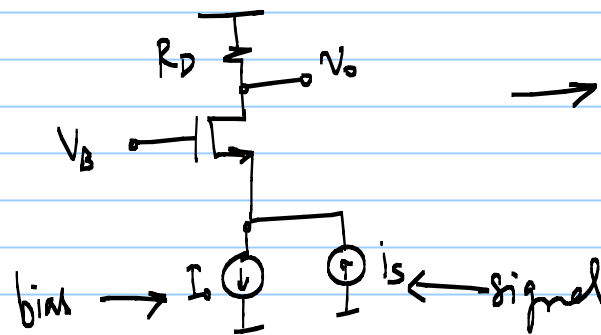


$$\frac{I_{n2}}{I_{n1}}$$

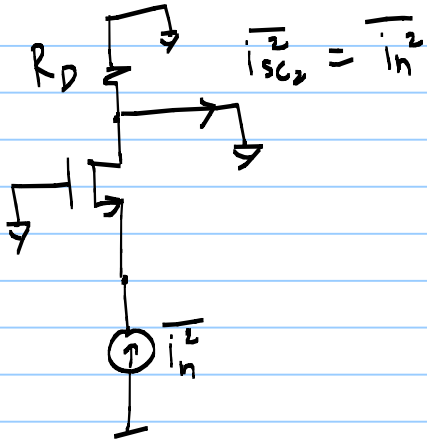


Case 1:

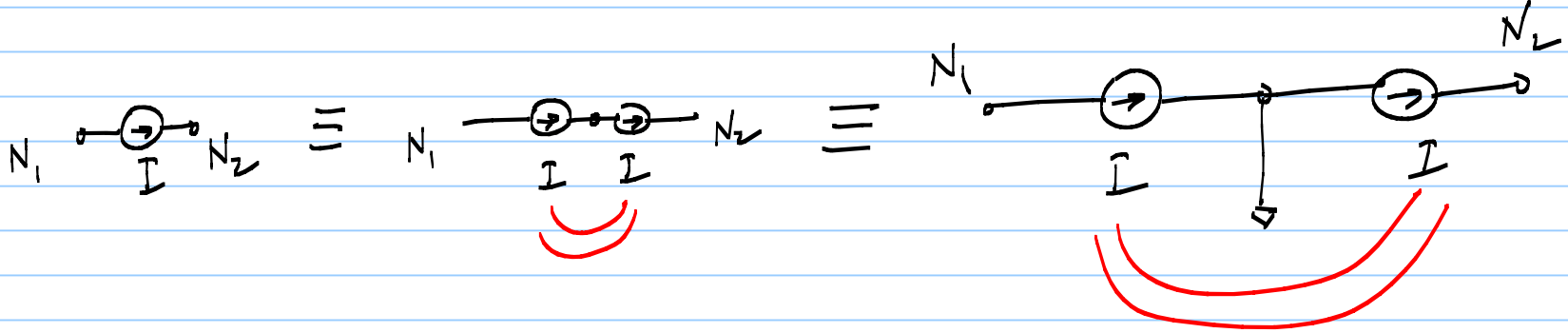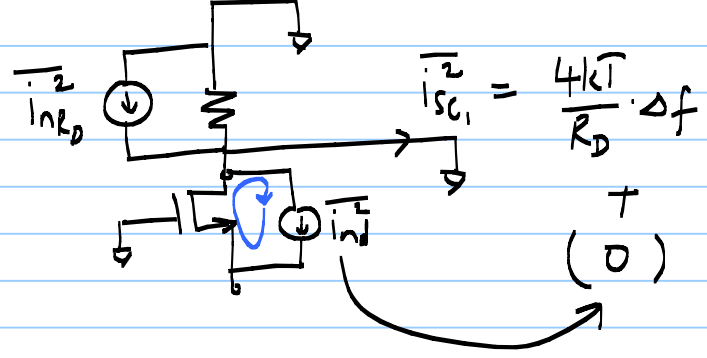


Case 1 : $\overline{i_{n2}}$

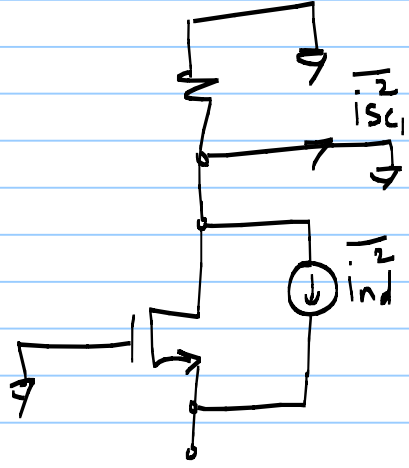

|||

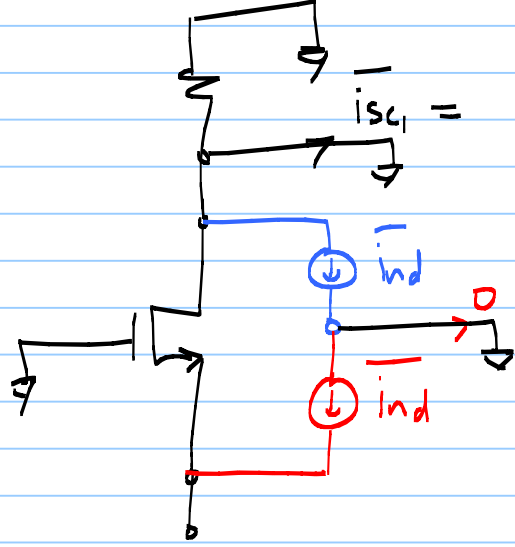

$$i_{sc1} = () + ()$$

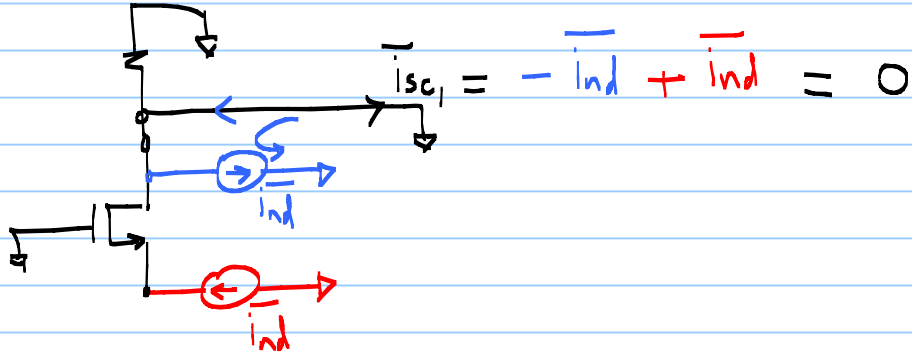


$$i_{sc1} = -\overline{i_{n2}} + \overline{i_{n2}} = 0$$

$$\overline{i_{sc1}} = \overline{i_{sc2}}$$

$$\overline{\Delta i_{n2}} = \frac{4kT}{R}$$

$$\overline{e_n^2}$$

Case 2:

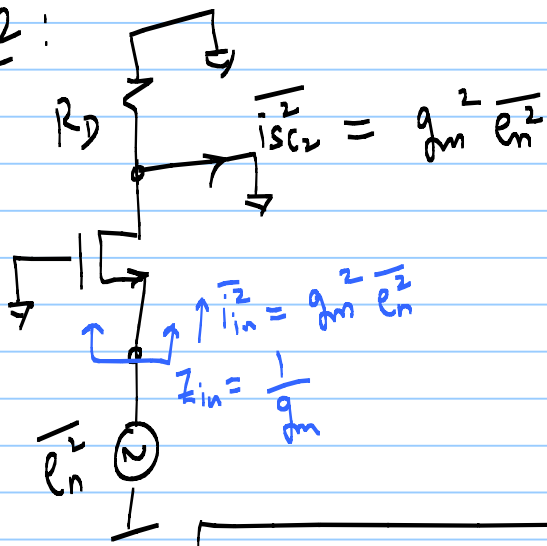


$$\overline{i_{sc1}^2} = \overline{i_{sc2}^2}$$

⇒

$$\frac{\overline{e_n^2}}{\Delta f} = \frac{8kT}{3g_m} + \frac{4kT}{g_m^2 R_D}$$

Case 1:


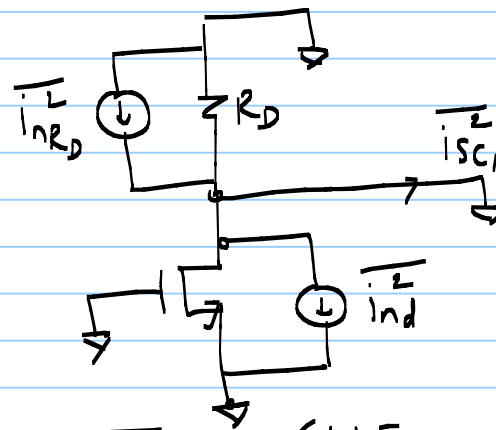


$$\overline{i_{sc1}^2} = \overline{i_{nD}^2} + \overline{i_{nd}^2} = \left(\frac{4kT}{R_D} + \frac{8kT}{3} g_m \right) \Delta f$$

$$\frac{\overline{i_{nD}^2}}{\Delta f} = \frac{4kT}{R_D}$$


partially correlated

Example #5 Cascoded CSA

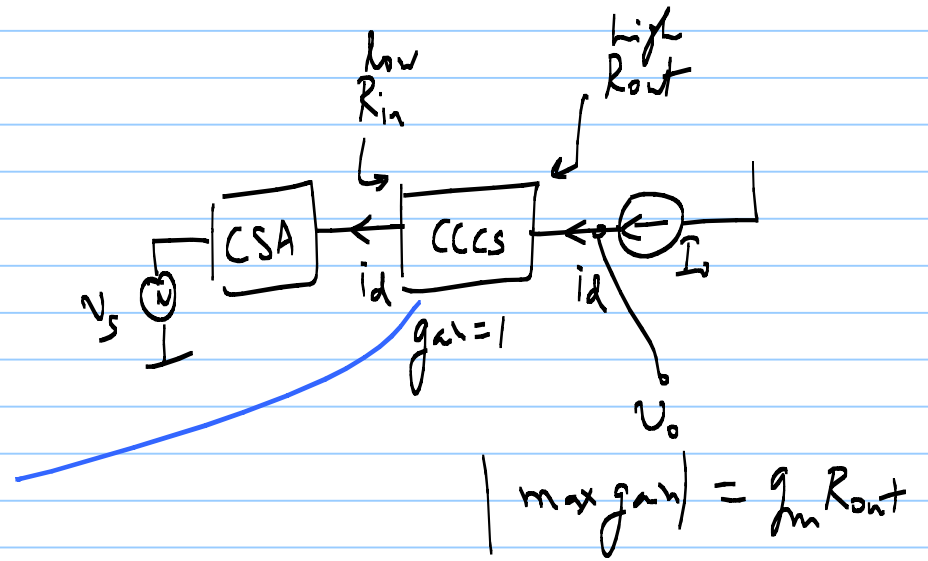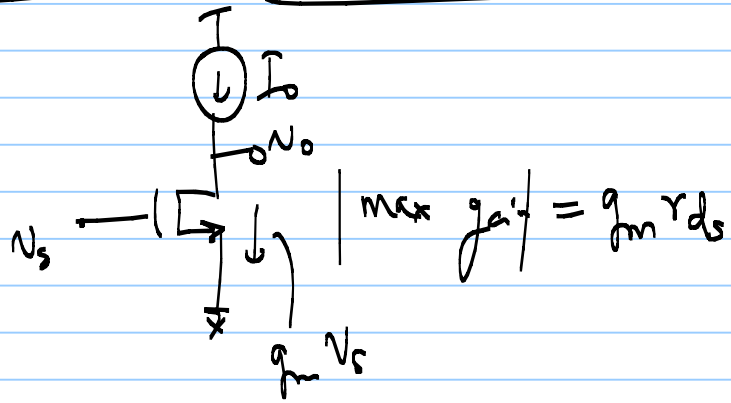

CGA

$R_{out} \gg r_{ds}$

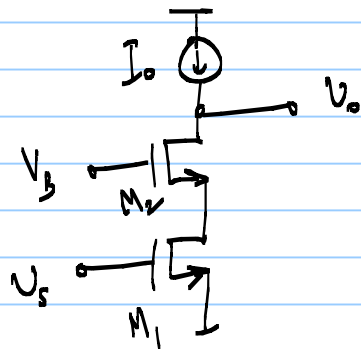


$\frac{v_o}{v_s} = -g_{m1} \cdot g_{m2} \cdot r_{ds1} \cdot r_{ds2}$


$\overline{e_n^2} = ?$

Cascoded CS amplifier


Case 2

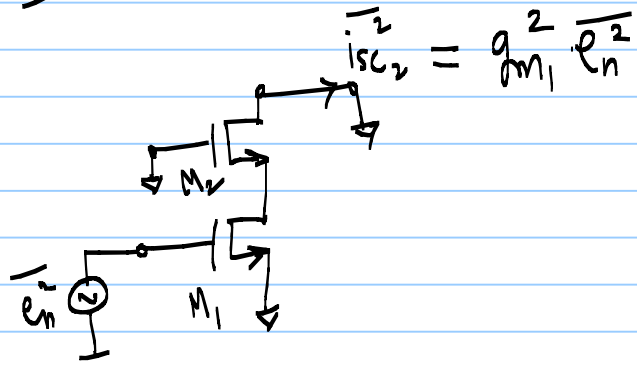


Case 1

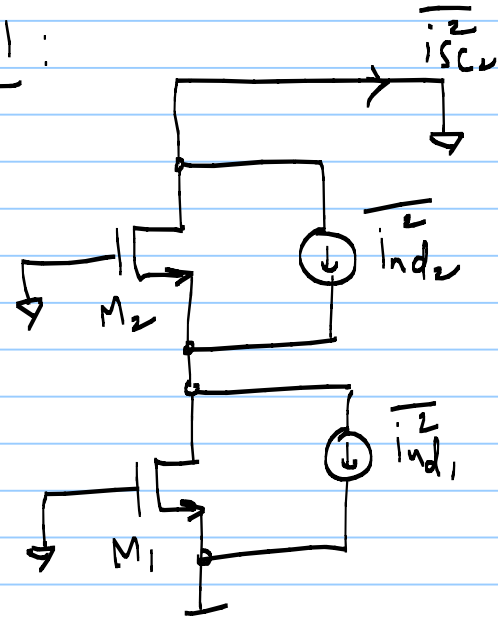

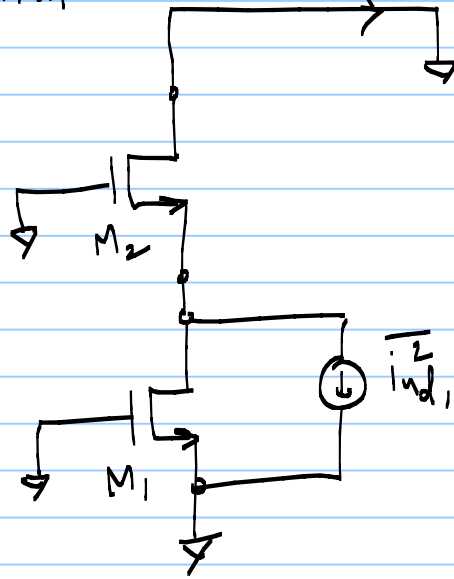(a) $\overline{i_{d1}^2}$ $\overline{i_{sc1}^2} = \overline{i_{d1}^2}$




(b) $\overline{i_{d2}^2}$

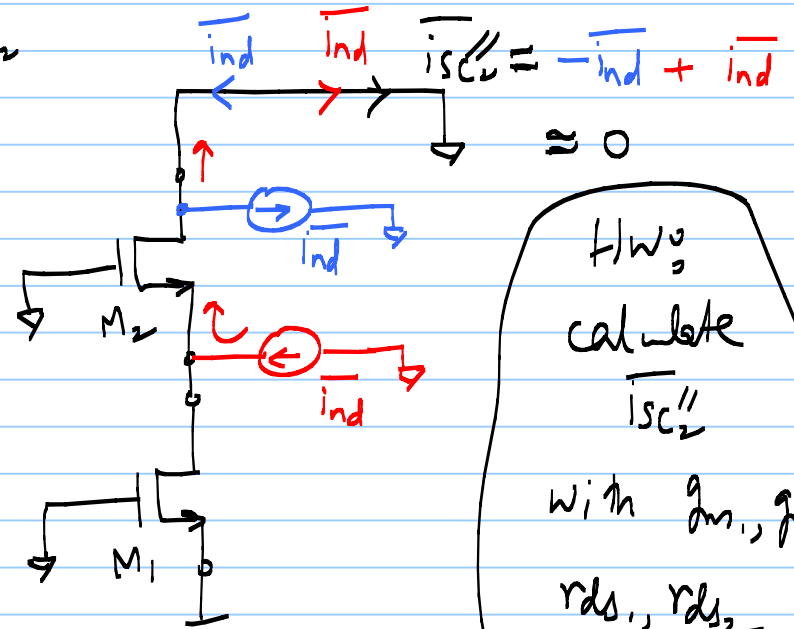

HW:
calculate $\overline{i_{sc2}^2}$
with g_{m1}, g_{m2}
 r_{ds1}, r_{ds2}

22/9/2023

Lec 5

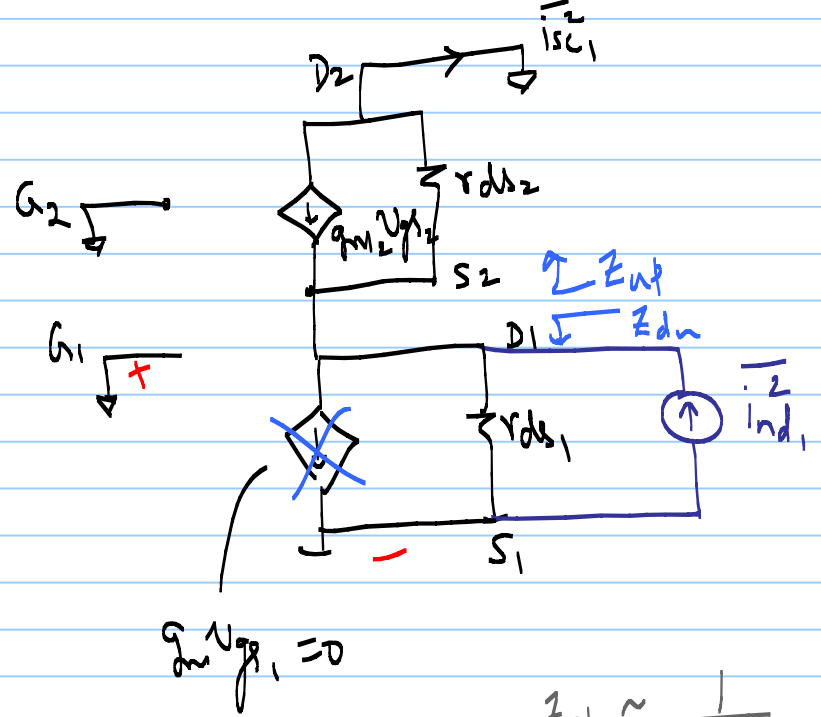

$$\bar{i}_{sc1} = \left[\frac{r_{ds1}}{\frac{1}{g_{m2}} \parallel r_{ds2} + r_{ds1}} \right] \cdot \bar{i}_{nd1}$$

$$Z_{dn} = r_{ds1}$$


$$Z_{up} = \frac{1}{g_{m2} + g_{ds2}} = \frac{r_{ds2}}{1 + g_{m2} r_{ds2}}$$

$$\bar{i}_{up} = \bar{i}_{sc1} = \left[\frac{Z_{dn}}{Z_{dn} + Z_{up}} \right] \cdot \bar{i}_{nd1}$$

$$Z_{up} \approx \frac{1}{g_{m2}} \quad \text{if } g_{m2} r_{ds2} \gg 1$$


$$\bar{i}_{sc1} \approx \bar{i}_{nd1} \quad \text{if } g_{m2} \gg \frac{1}{r_{ds1}}$$

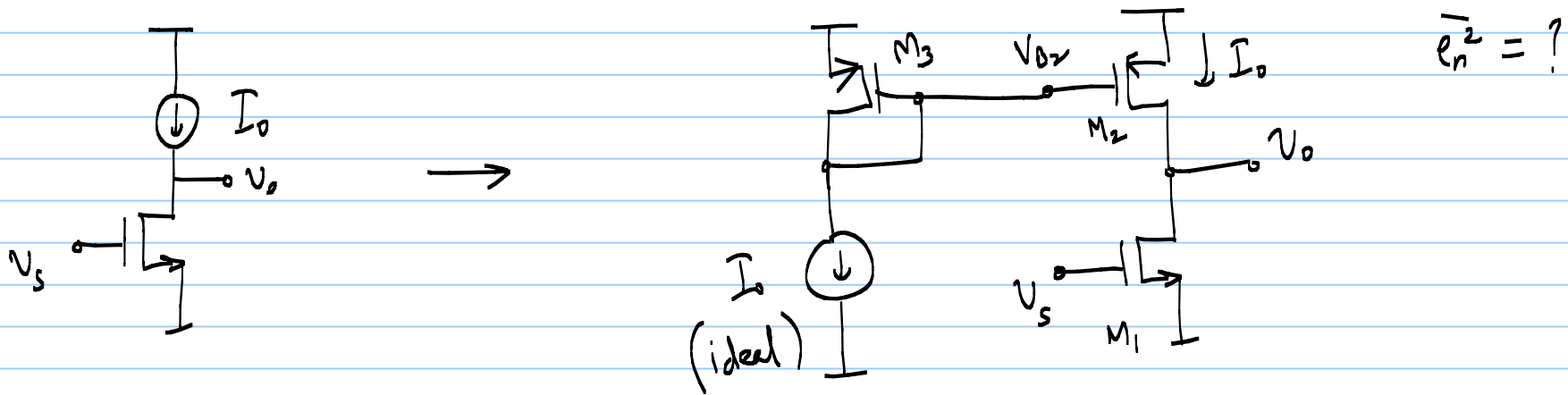Example #6 CSA with active load (only thermal noise)




Without } $\frac{|e_n|^2}{4f} = \frac{8kT}{3g_{m1}} + \frac{8kT g_{m2}}{g_{m1}^2}$

M_3


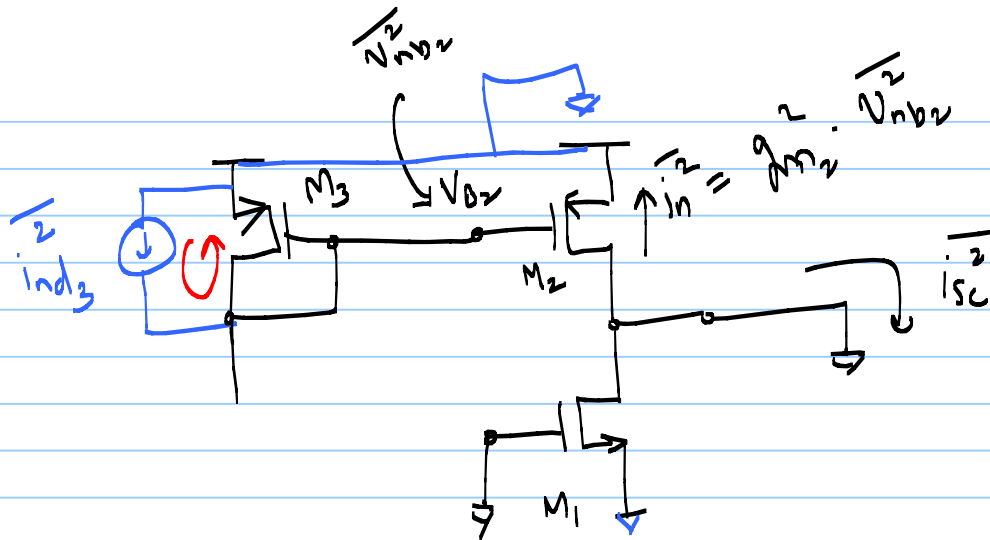


1) ~~no effect?~~ i_{ind3}^2 circulates inside M_3

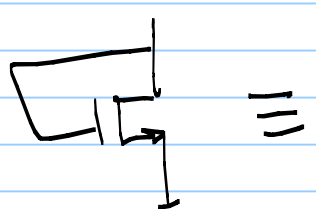2) $v_{nb2}^2 = \frac{i_{ind3}^2}{g_{m3}^2} \rightarrow$ applied to M_2



$$\frac{1}{g_m + g_{ds}}$$

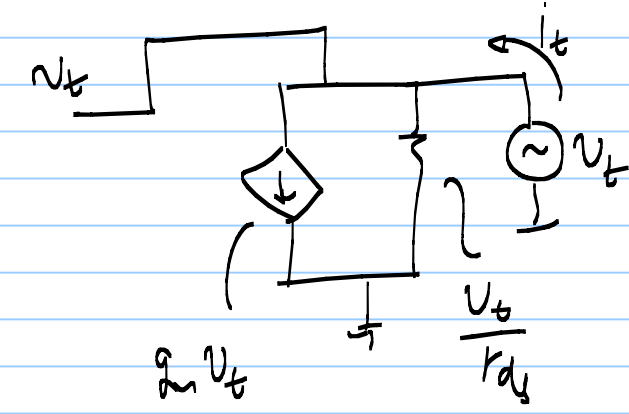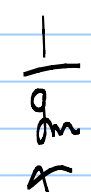



$$\overline{i_{sc1}^2} = \frac{g_{m2}^2}{g_{m3}^2} \cdot \overline{i_{nd3}^2}$$

here 1:1 C. Mirror

$$\overline{i_{sc1}^2} = \overline{i_{nd3}^2}$$
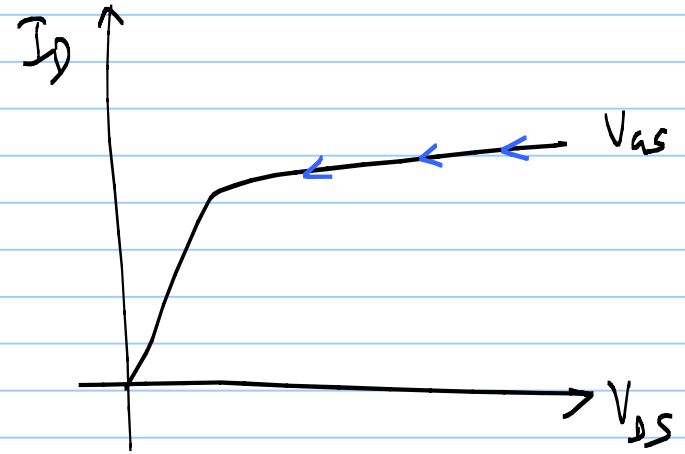
$$\frac{\overline{e_n^2}}{\Delta f} = \underbrace{\frac{8kT}{3g_{m1}}}_{M_1} + \underbrace{\frac{8kT g_{m2}}{g_{m1}^2}}_{M_2} + \underbrace{\frac{8kT g_{m3}}{g_{m1}^2}}_{M_3}$$



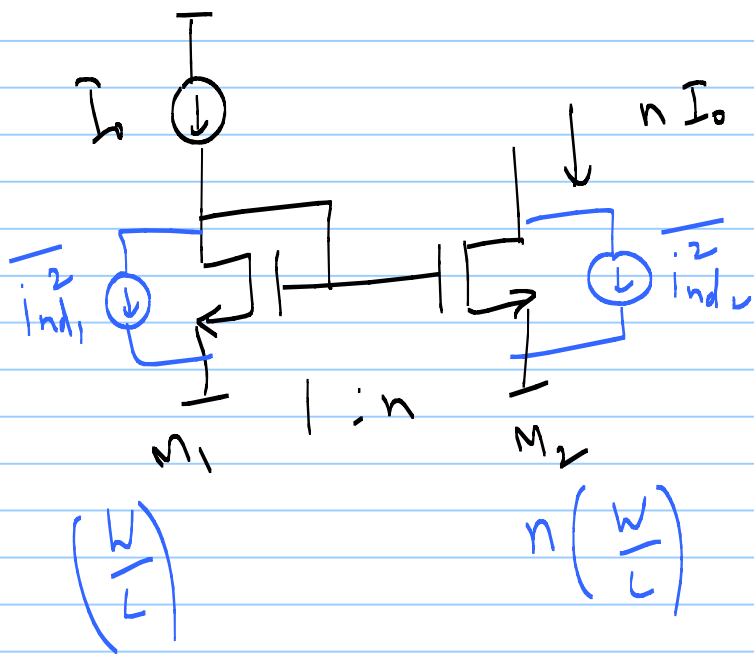

$$\overline{i_{d2}^2} + n^2 \overline{i_{d1}^2} = \frac{8kT}{3} g_{m2} + n^2 \cdot \frac{8kT}{3n} g_{m1}$$


$$= \frac{8kT}{3} g_{m2} (1+n)$$

$$g_{m2} = n g_{m1}$$

$$\overline{i_{d2}^2} = \frac{8kT}{3} \cdot g_{m2}$$


$$\overline{i_{d1}^2} = \frac{8kT}{3} \cdot g_{m1} = \frac{8kT}{3n} \cdot g_{m2}$$


Example #7 Cascode CSA with a cap

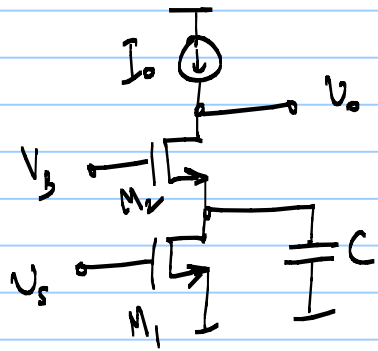

$\overline{e_n^2} = ?$

1)

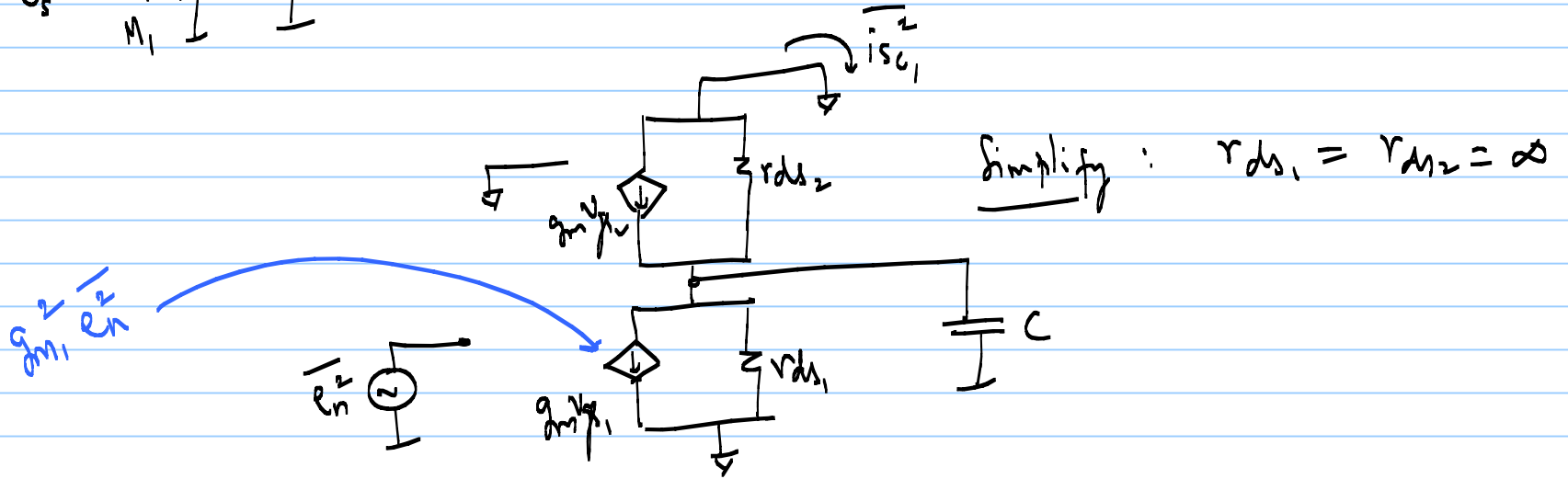

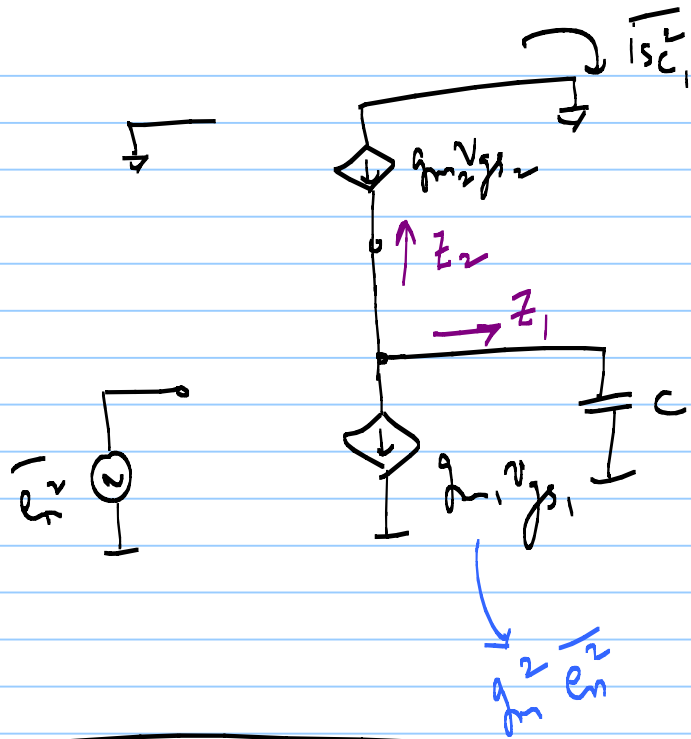

$$\overline{i_{sc1}^2} = \frac{g_{m1}^2 \cdot g_{m2}^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{e_n^2}$$

$$\overline{i_{sc1}^2} = \overline{i_{Z_2}^2}$$

$$\overline{i_{Z_2}^2} = g_{m1}^2 \overline{e_n^2} \left| \frac{Z_1}{Z_1 + Z_2} \right|^2$$

$$\overline{i_{sc1}^2} = g_{m1}^2 \overline{e_n^2} \cdot \frac{\left| \frac{1/j\omega C}{1/j\omega C + 1/g_{m2}} \right|^2}{g_{m2}^2}$$

$$\overline{i_{sc1}^2} = \frac{g_{m1}^2}{g_{m2}^2 + \omega^2 C^2} \overline{e_n^2}$$