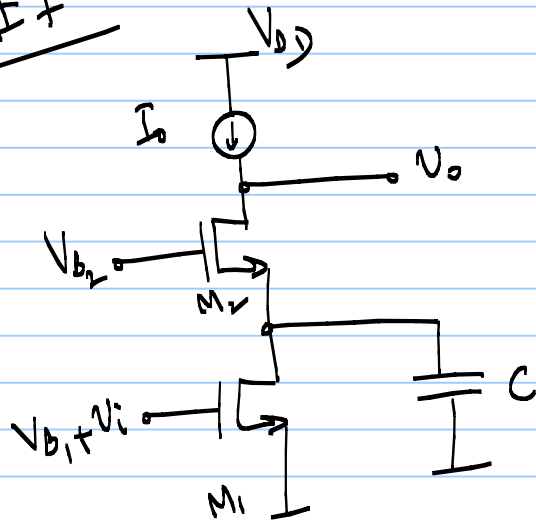


26/9/23

Lec 6


Example #7



1) work with \bar{e}_n^2

$$Z_2 = \frac{1}{g_{m2}}$$


$$Z_c = \frac{1}{j\omega C}$$

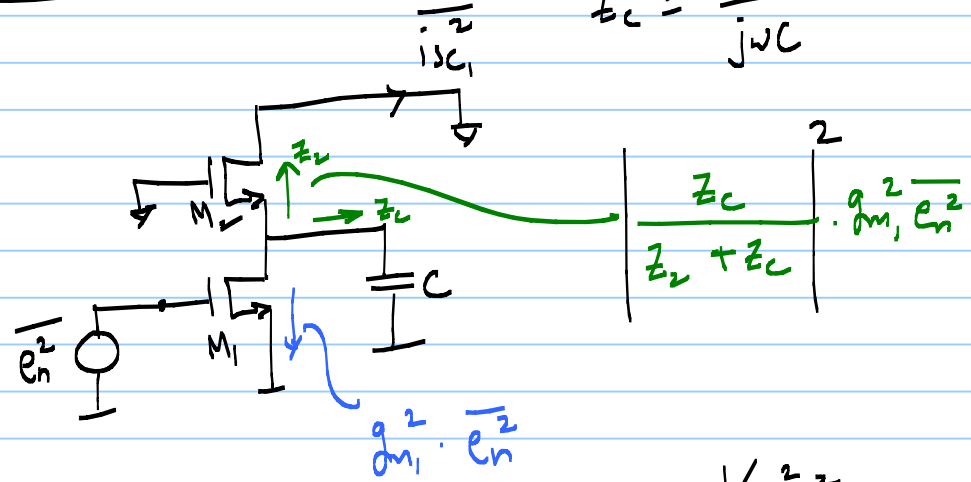


$$\bar{i}_{sc1}^2 = g_{m1}^2 \bar{e}_n^2 \cdot \left| \frac{Z_c}{Z_2 + Z_c} \right|^2 = g_{m1}^2 \bar{e}_n^2 \cdot \frac{1/\omega^2 C^2}{\frac{1}{g_{m2}^2} + \frac{1}{\omega^2 C^2}}$$

$$\overline{i_{sc1}^2} = \frac{g_{m1}^2 \cdot g_{m2}^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{e_n^2}$$


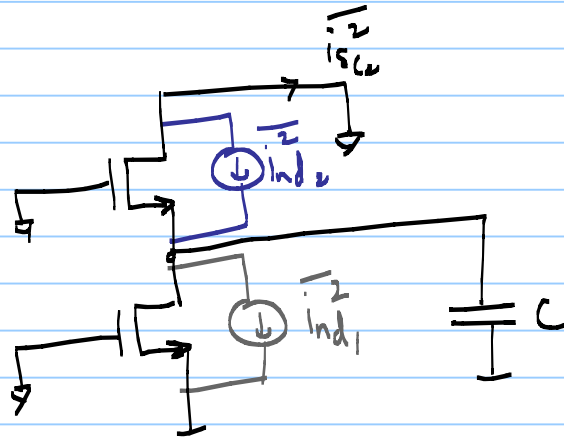
2) case with $\overline{i_{nd1}^2}$ & $\overline{i_{nd2}^2}$



a) $\overline{i_{nd1}^2}$

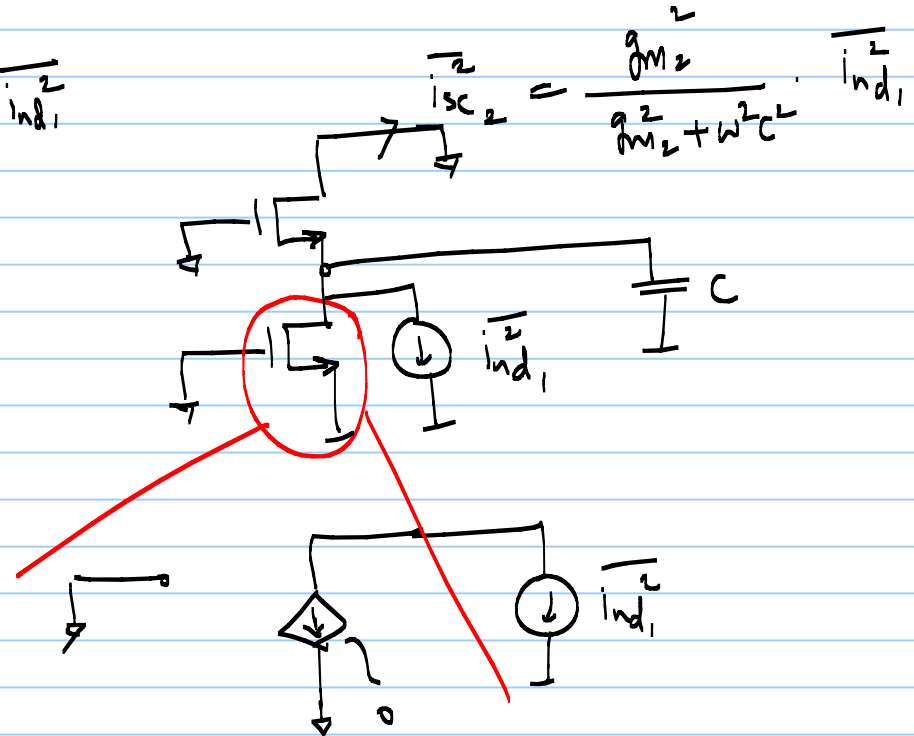

b) noise from M_2

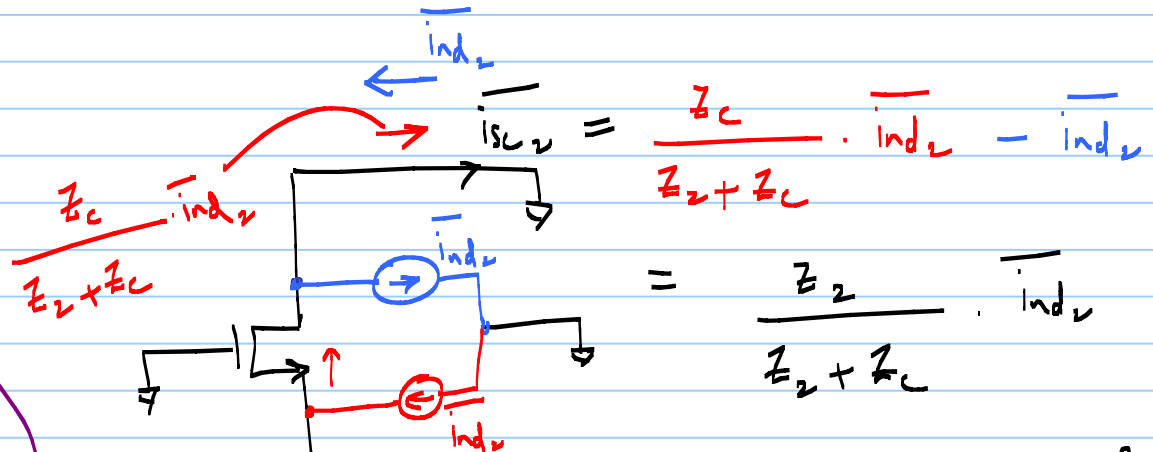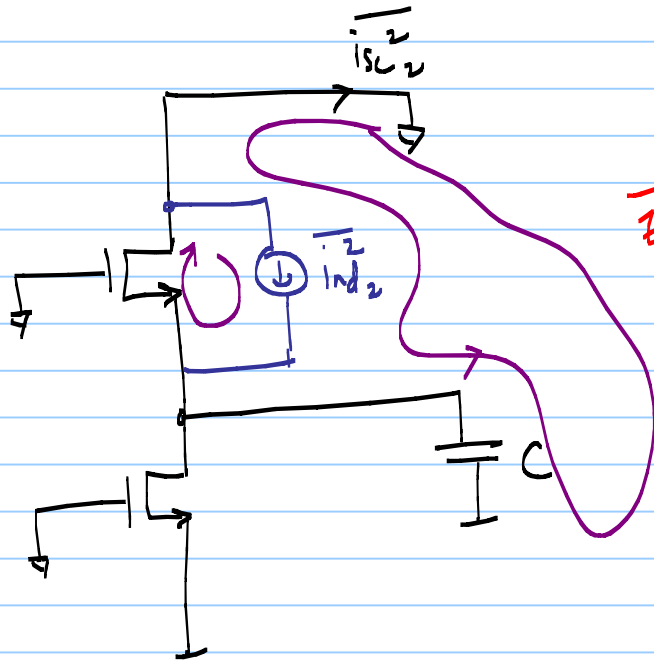

$$\overline{i_{sc_2}} = \frac{Z_c}{Z_2 + Z_c} \cdot \overline{i_{nd_2}} - \overline{i_{nd_2}}$$

$$= \frac{Z_2}{Z_2 + Z_c} \cdot \overline{i_{nd_2}}$$

$$\overline{i_{sc_2}^2} = \left| \frac{Z_2}{Z_2 + Z_c} \right|^2 \cdot \overline{i_{nd_2}^2}$$

$$= \left| \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{j\omega C}} \right|^2 \cdot \overline{i_{nd_2}^2}$$

$$\overline{i_{sc2}} = \frac{\omega^2 C^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{i_{nd2}}$$

Total $\overline{i_{sc2}}$

$$\overline{i_{sc2, \text{tot}}} = \frac{g_{m2}^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{i_{nd1}} + \frac{\omega^2 C^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{i_{nd2}}$$


set $\overline{i_{sc1}} = \overline{i_{sc2}}$

$$\frac{g_{m1}^2 \cdot g_{m2}^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{e_n^2} = \frac{g_{m2}^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{ind_1^2} + \frac{\omega^2 C^2}{g_{m2}^2 + \omega^2 C^2} \cdot \overline{ind_2^2}$$

$$\overline{e_n^2} = \frac{\overline{ind_1^2}}{g_{m1}^2} + \frac{\omega^2 C^2}{g_{m1}^2 g_{m2}^2} \cdot \overline{ind_2^2}$$

$$\frac{\overline{e_n^2}}{\Delta f} = \frac{8kT}{3g_{m1}} + \frac{8kT \cdot \omega^2 C^2}{3g_{m1}^2 g_{m2}^2}$$

with gain factor

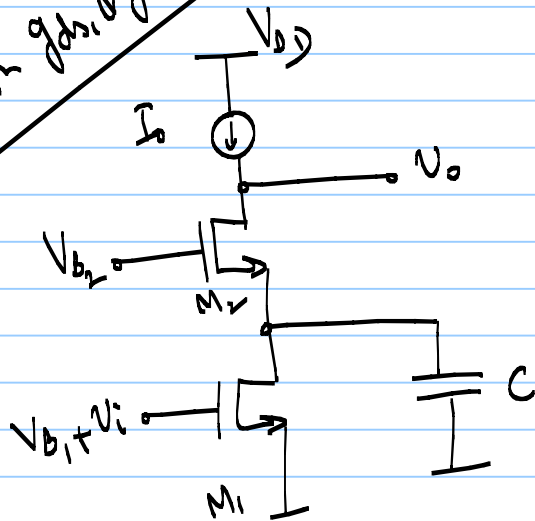

$$\frac{e_{n2}^2}{\Delta f} =$$

$$\frac{\delta kT}{3 g_{m1}} +$$

$$\frac{\delta kT}{3 g_{m1}^2} \cdot g_{m2}$$

$$\left[\frac{r_{ds2}^2 + \omega^2 c^2 r_{ds1}^2}{r_{ds2}^2} \right]$$

$$\frac{r_{ds1}^2 + g_{m2}^2 r_{ds1}^2 r_{ds2}^2}{r_{ds1}^2 + g_{m2}^2 r_{ds1}^2 r_{ds2}^2}$$


$$\frac{\omega^2 c^2 + g_{ds1}^2}{g_{m2}^2 + g_{m2}^2}$$

?


Next class

Noise of Differential circuits

Op amp

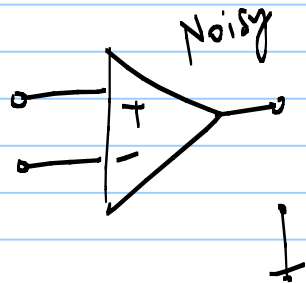


≡

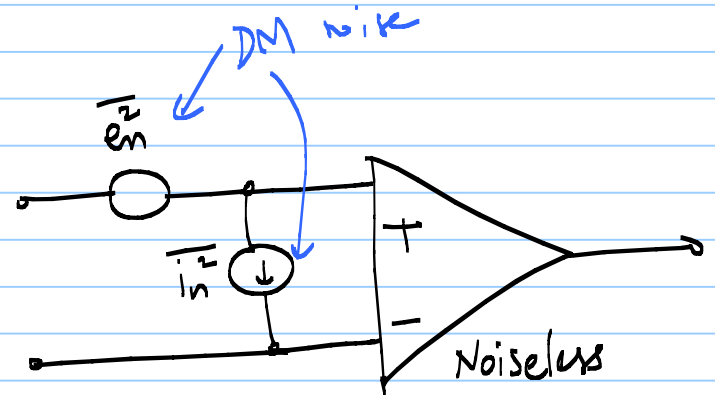

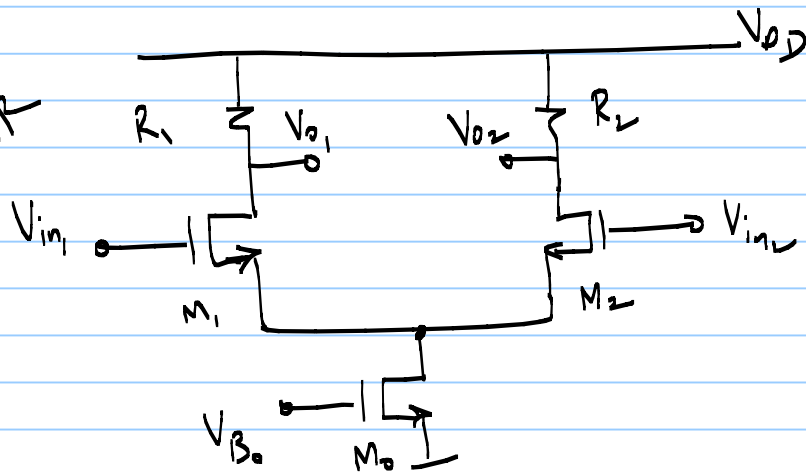Example #8

$M_1 \equiv M_2$
 $R_1 \equiv R_2 \equiv R$



DM :

$$V_{in1} = +v_i/2$$

$$V_{in2} = -v_i/2$$

$$V_{o1} = +v_o/2$$


$$V_{o2} = -v_o/2$$

CM :


$$V_{in1} = V_{in2} = v_i$$

$$V_{o1} = V_{o2} = v_o$$


1) case with e_{n2}

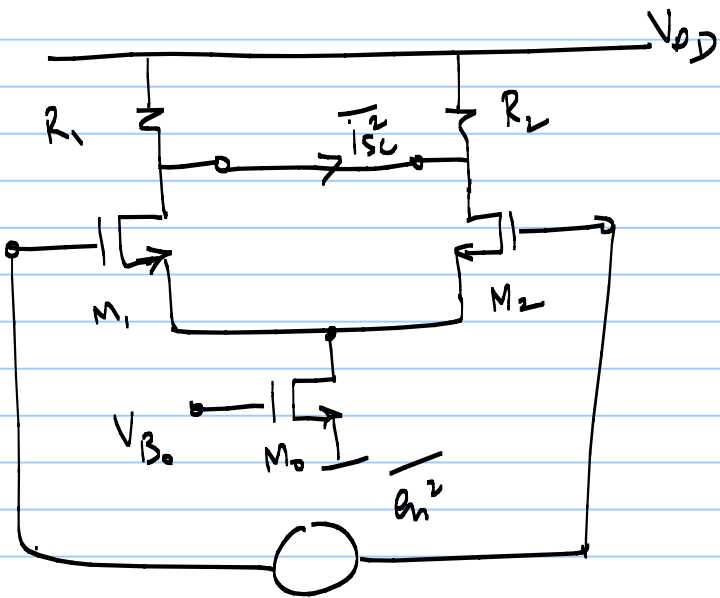

2

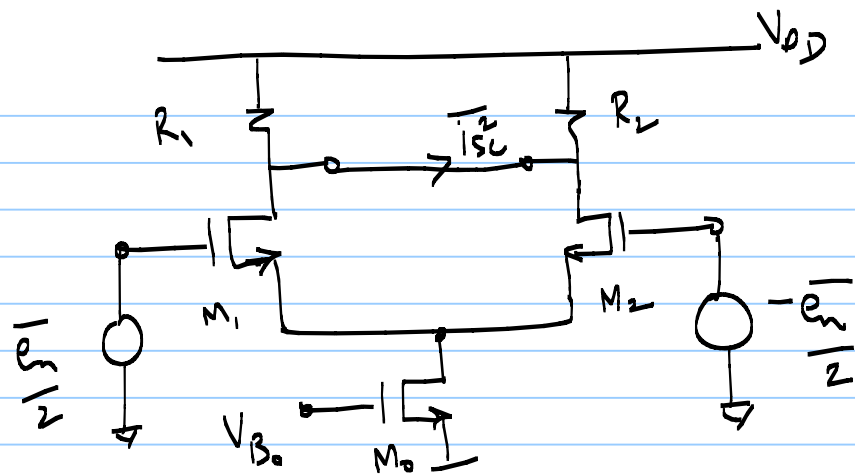


1/3/1

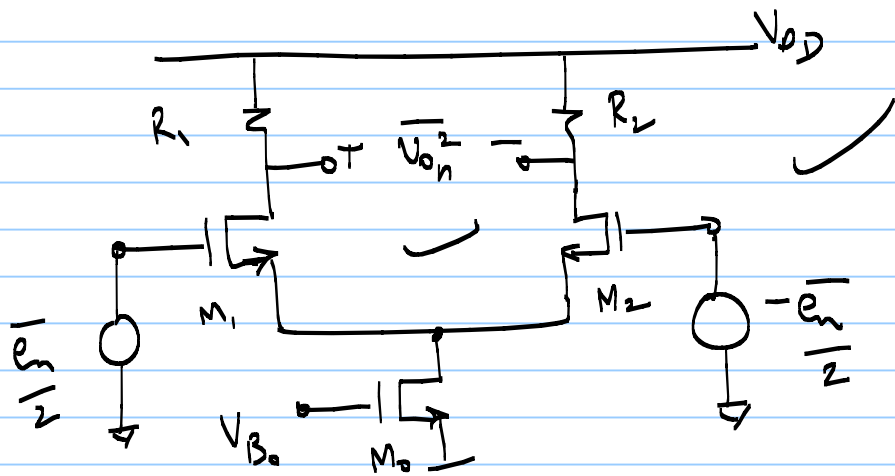

$$v_{o_n} = v_{o_+} - v_{o_-} = g_{m1} R_1 \cdot \frac{e_{n2}}{2} - (g_{m2} R_2 \cdot \frac{e_{n2}}{2})$$


$$v_{o_n} = g_{m1} R_1 \cdot e_{n2} \Rightarrow v_{o_n^2} = g_{m1}^2 R_1^2 e_{n2}^2$$

2) Case with noise sources

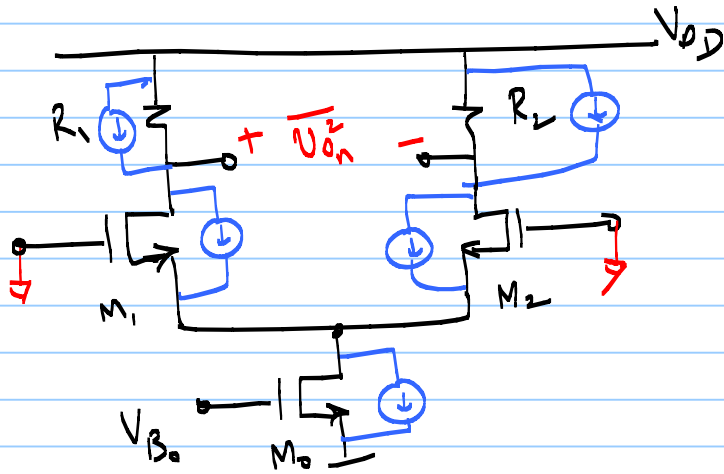

assume $r_{ds} = \infty$, $g_{ds} = 0$

a) $\overline{i_{nR_1}^2}$

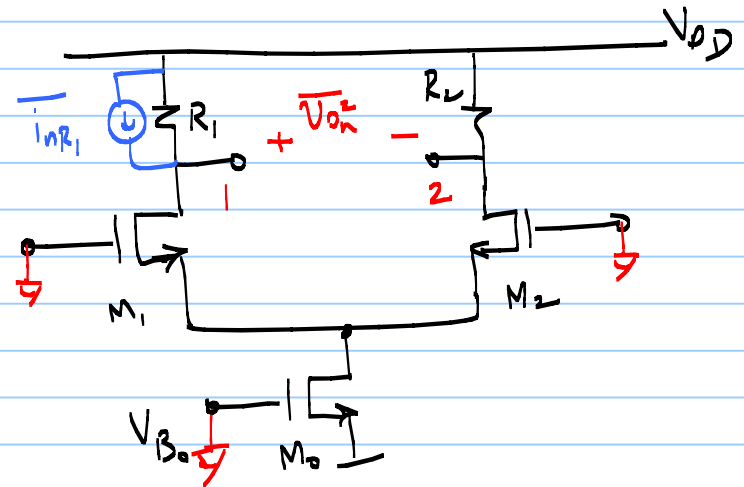

* For noise Analysis:

DO NOT USE ANY SYMMETRY


ARGUMENTS

$$\overline{v_{on1}} = \overline{i_{nR_1}} \cdot R_1 ; \overline{v_{on2}} = 0$$

$$\overline{v_{on}} = \overline{v_{on1}} - \overline{v_{on2}} = \overline{i_{nR_1}} \cdot R_1$$

$$\overline{v_{on}^2} = \overline{i_{nR_1}^2} \cdot R_1^2 = 4kTR_1 \Delta f$$

b) R_2

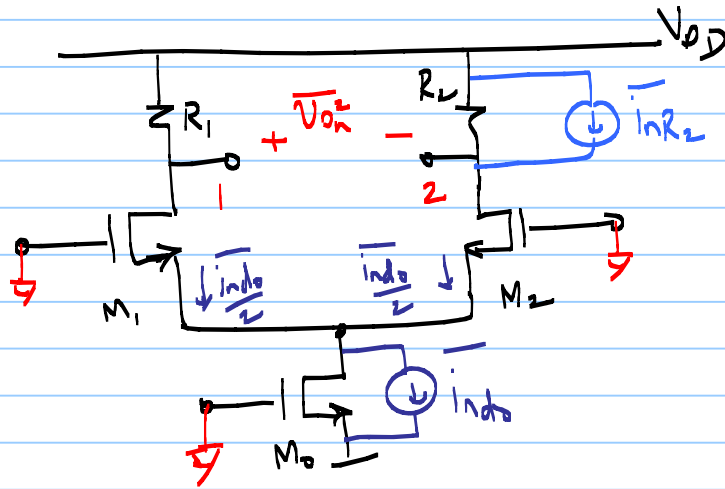

$$\begin{aligned} \overline{V_{on}} &= \overline{V_{on1}} - \overline{V_{on2}} \\ &= 0 - \overline{i_{n2}} R_2 \end{aligned}$$



$$\overline{V_{on}^2} = \overline{i_{n2}^2} \cdot R_2^2 = 4kTR_2 \cdot \Delta f$$

c) $M_0 - \frac{i_{idc}}{2}$

$$\overline{V_{on1}} = -\frac{i_{idc}}{2} \cdot R_1 \quad ; \quad \overline{V_{on2}} = -\frac{i_{idc}}{2} \cdot R_2 \quad \left. \begin{array}{l} \text{CM} \\ \text{mode} \end{array} \right\}$$



$$\overline{V_{on}} = \overline{V_{on1}} - \overline{V_{on2}} = 0$$

d) Noise of M_1

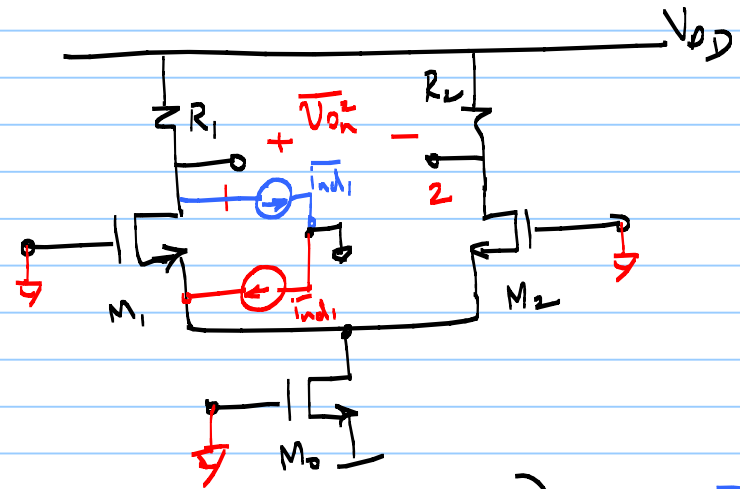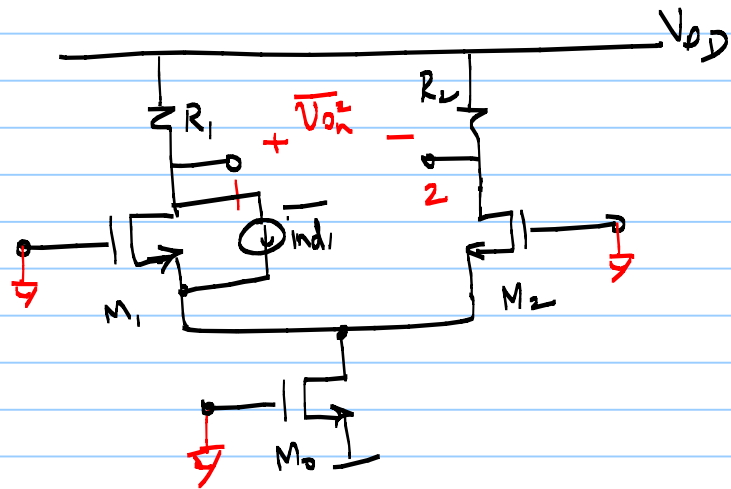

$$\begin{aligned}
 \text{(i) } \overline{ind_1} &: \overline{V_{out1}} = -\overline{ind_1} R_1 ; \overline{V_{out2}} = 0 \Rightarrow \overline{V_{out}} = -\overline{ind_1} R_1 \\
 \text{(ii) } \overline{ind_1} &: \overline{V_{out1}} = \frac{\overline{ind_1}}{2} \cdot R_1 ; \overline{V_{out2}} = \frac{\overline{ind_1}}{2} \cdot R_2 \Rightarrow \overline{V_{out}} = 0
 \end{aligned}
 \left. \vphantom{\begin{aligned} \text{(i)} \\ \text{(ii)} \end{aligned}} \right) \begin{aligned}
 \overline{V_{out}} &= \overline{V_{out1}} + \overline{V_{out2}} \\
 &= -\overline{ind_1} R_1 \\
 \overline{V_{out}^2} &= \overline{ind_1^2} \cdot R_1^2
 \end{aligned}$$

e) Noise of M_2

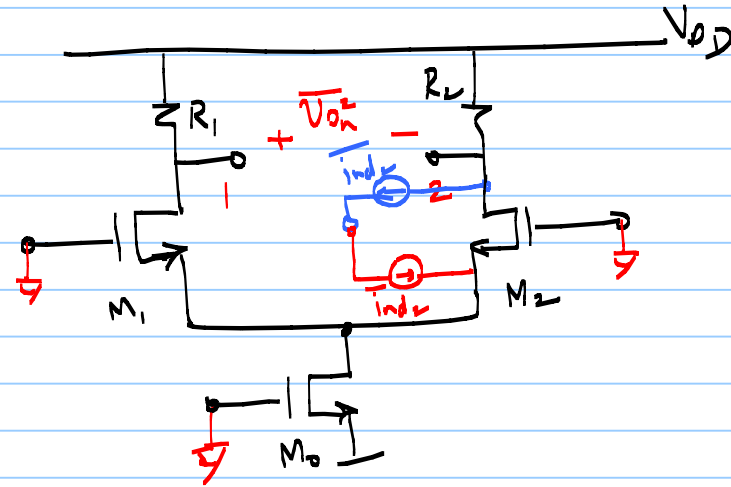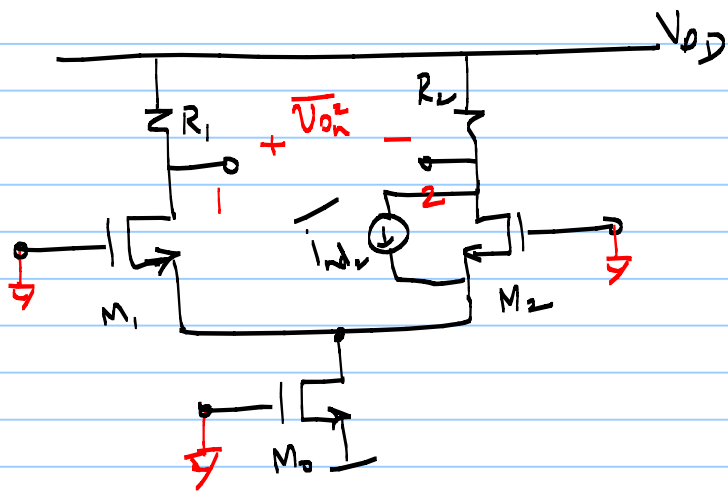

$\overline{ind_2}$
 $\overline{ind_2}$
 $\overline{V_{on1}} = 0$; $\overline{V_{on2}} = -\overline{ind_2} \cdot R_2$
 $\overline{V_{on1}} = \frac{\overline{ind_1}}{2} \cdot R_1$; $\overline{V_{on2}} = \frac{\overline{ind_2}}{2} \cdot R_2$

$\overline{V_{on}} = \overline{ind_2} \cdot R_2$
 $\overline{V_{on}^2} = \overline{ind_2}^2 \cdot R_2^2$

$\overline{V_{oD}^2} = \overline{ind_{R_1}}^2 \cdot R_1^2 + \overline{ind_{R_2}}^2 \cdot R_2^2 + \overline{ind_1}^2 \cdot R_1^2 + \overline{ind_2}^2 \cdot R_2^2$

28/9/23

Lec 7

$$\overline{V_{on}^2} = \overline{i_{nR_1}^2} \cdot R_1^2 + \overline{i_{nR_2}^2} \cdot R_2^2 + \overline{i_{nd_1}^2} \cdot R_1^2 + \overline{i_{nd_2}^2} \cdot R_2^2$$

$$\overline{V_{on}^2} = g_{m1}^2 R^2 \overline{e_n^2}$$


$$g_{m1}^2 R^2 \overline{e_n^2} = \overline{i_{nR_1}^2} \cdot R^2 + \overline{i_{nR_2}^2} \cdot R^2 + \overline{i_{nd_1}^2} \cdot R^2 + \overline{i_{nd_2}^2} \cdot R^2$$

$$\overline{e_n^2} = \frac{1}{g_{m1}^2} \left\{ \frac{4kT}{R} \Delta f + \frac{4kT}{R} \Delta f + \frac{8kT}{3} g_{m1} + \frac{8kT}{3} g_{m1} \right\}$$

$$\boxed{\frac{\overline{e_n^2}}{\Delta f} = \frac{8kT}{g_{m1}^2 R} + \frac{16kT}{3g_{m1}}}$$

← Input Referred noise voltage squared density of Diff. Amp.


Mismatch

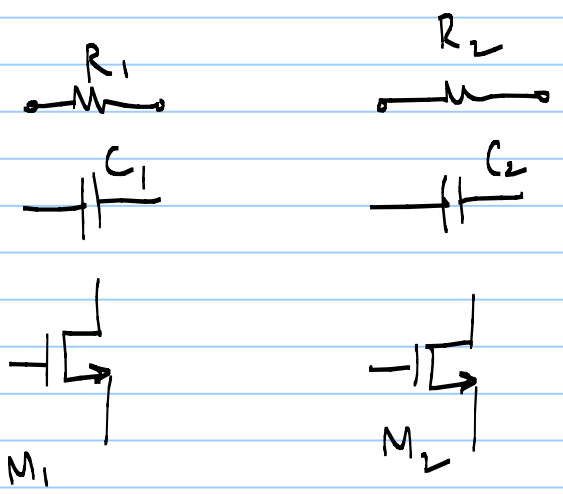

expect $R_1 = R_2 = R$
 " $C_1 = C_2 = C$
 " $M_1 = M_2$

Nominally identical but may not be exactly the same

Mismatch

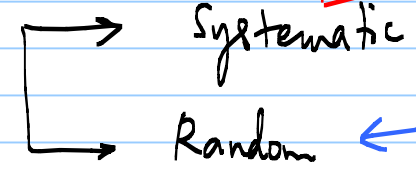


design ✓
 layout ✓
 processing ✓
 * mostly non-zero mean distributions


* statistical phenomena (beyond your control)
 * expect zero-mean distribution

Systematic Mismatch

R_1

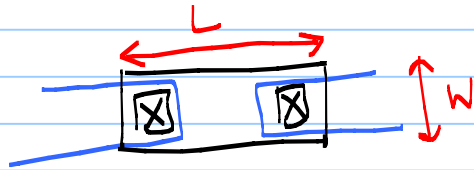

R_2

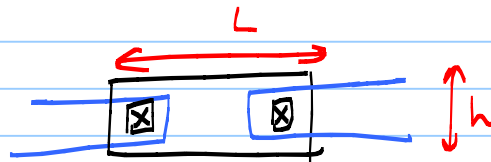

$$\text{Sheet resistance} = \frac{\rho}{t}$$

$$R = \left(\# \text{ of squares} \right) \times \left(\text{Sheet res.} \right)$$

||
 L/W

We want $R_1 = R_2 = R$

* Choose same type of Res.

* Choose same L & same W


second order effects

e.g. (1) current density effects (crowding)

(2) parasitic resistance, capacitance etc.


* Choose same environment

e.g. proximity effects

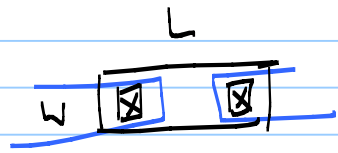


$$R_1 = R$$

actual $R' = R + 2R_{via}$

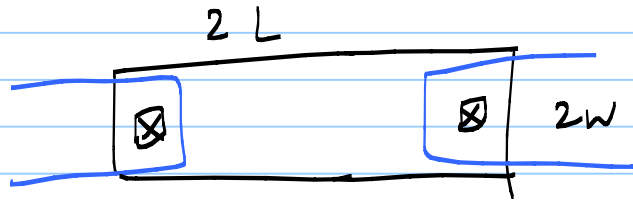


$$R_2 \quad \times$$

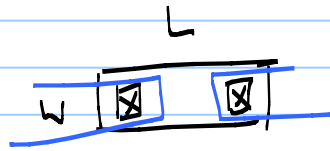


$$R'_2 = R + 2R_{via}$$

$$R + 2R_{via}$$

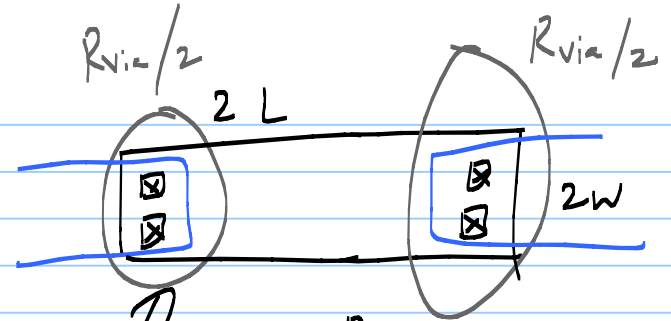


$$R_2 \quad \times$$


 \leftarrow for a via or contact, a & b are fixed.

$R_{es/via}$ is known

$$R + R_{via}$$

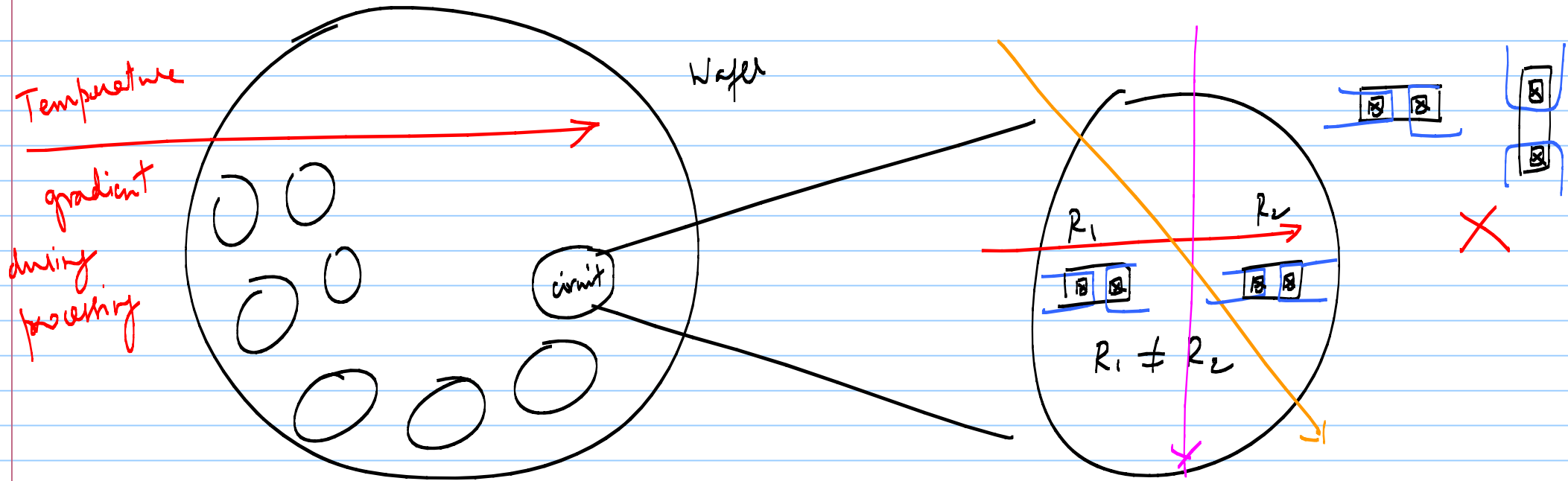

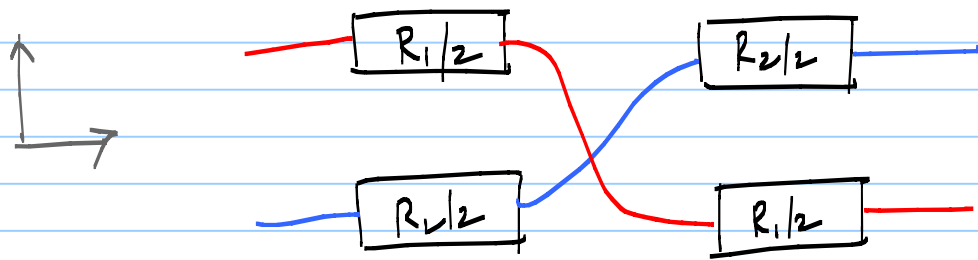* Keep R_1 & R_2 as close to each other as possible in layout





"Common Centroid" Layout

Capacitors

$$C_1 = C$$

$$C_2 = C$$

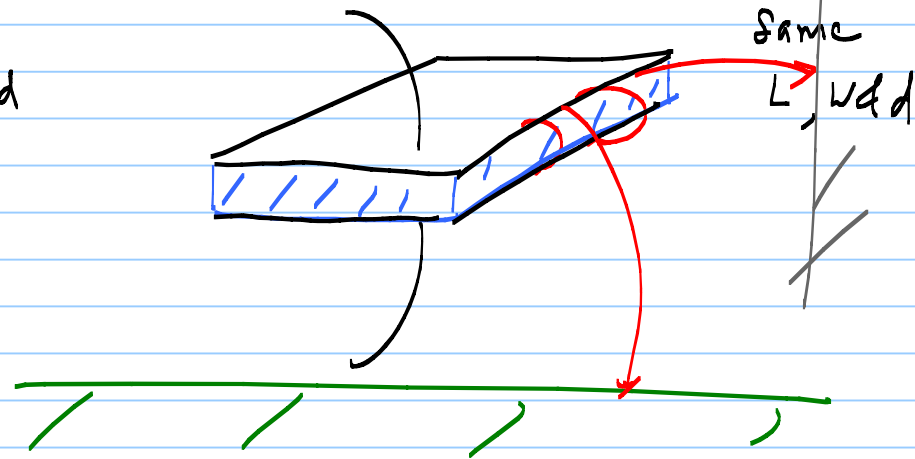
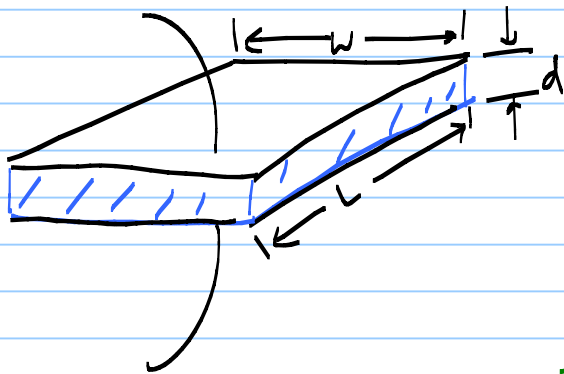
$$C = \frac{\epsilon_0 \epsilon_r (W \cdot L)}{d}$$



$$R_2 = nR_1$$


$$C_2 = nC_1$$

$$M_2 = nM_1$$

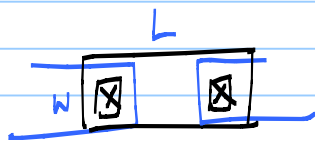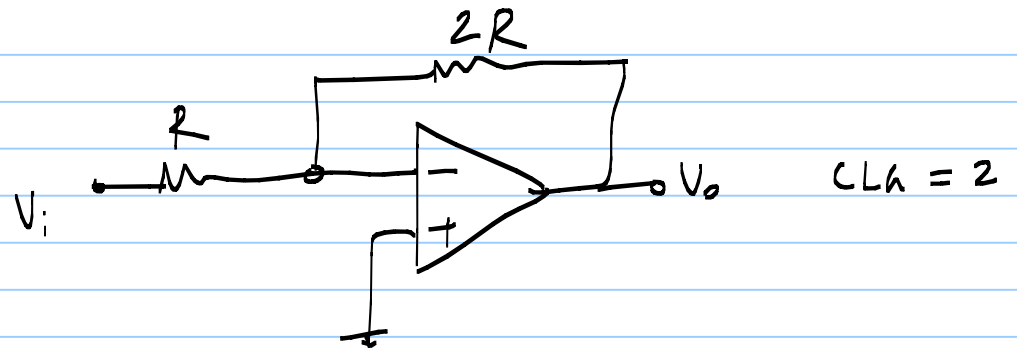


$$R_1 = R + 2R_{via}$$

$$R_2 \neq 2R_1$$

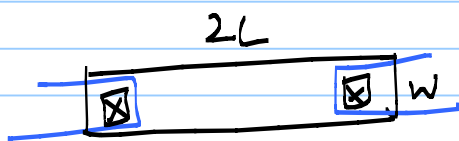



$$R_2 = 2R + 2R_{via}$$

X

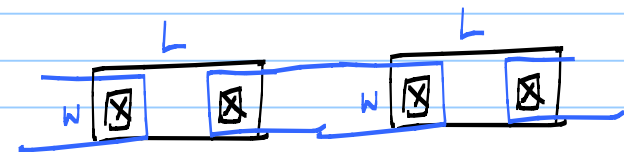

$$R_2' = R + 2R_{via} + R + 2R_{via}$$


$$= 2R + 4R_{via} = 2R_1' \checkmark$$

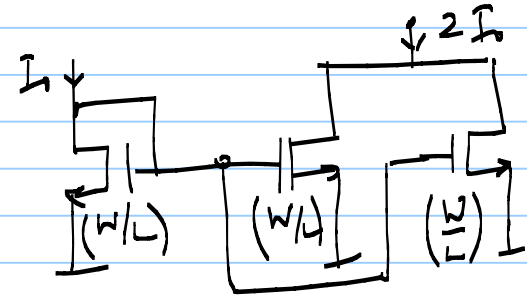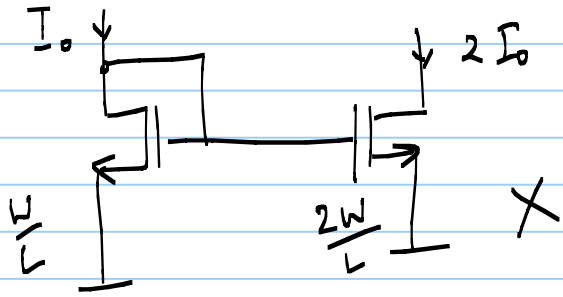

You might have $V_T = f(\omega)$
 $\lambda = f(\omega)$ etc.


3/10/23

Lec 8

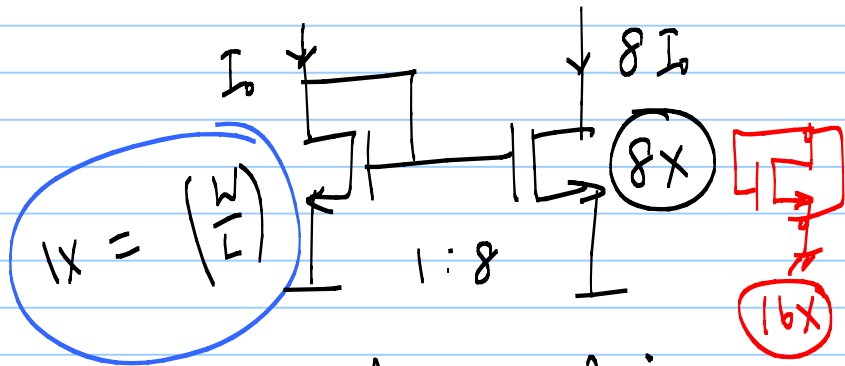


Array of devices

Same environment for every CM device

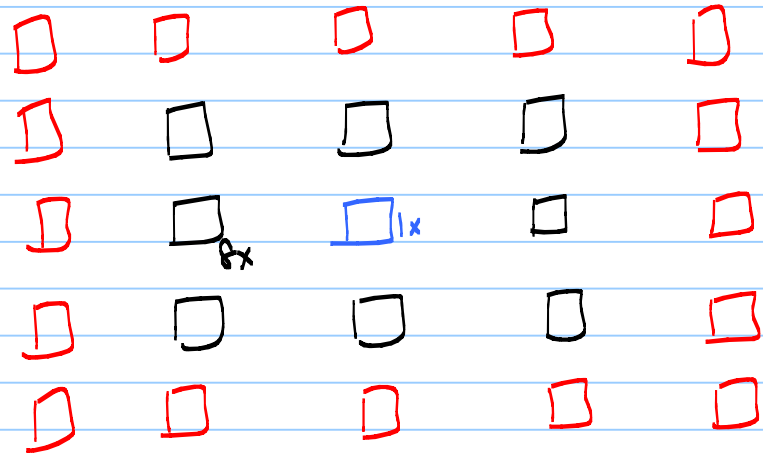


Dummy devices

Random mismatch

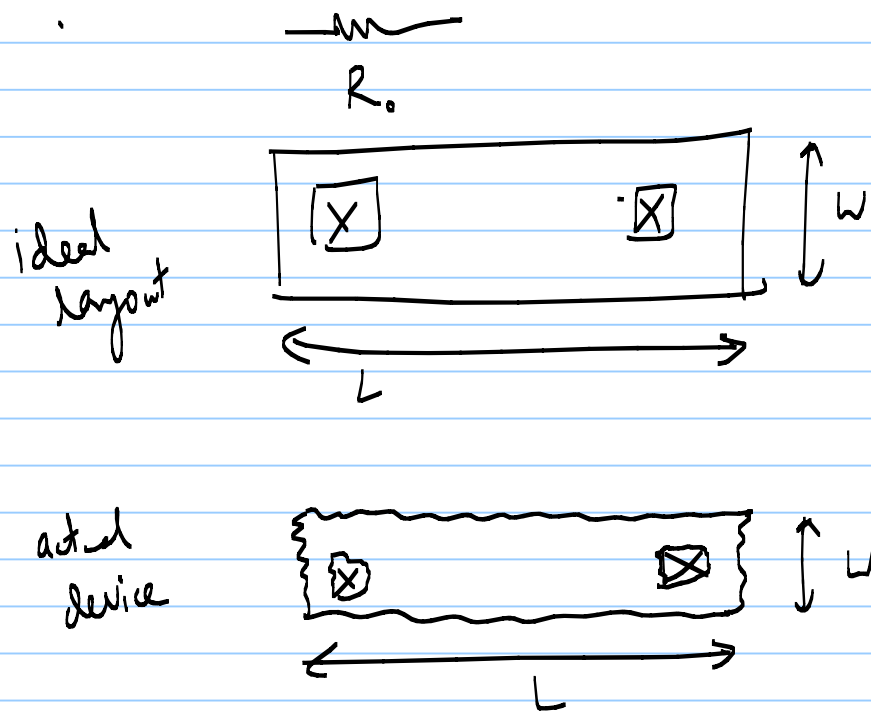


Random imperfections in device

R, C, MOSFET etc.






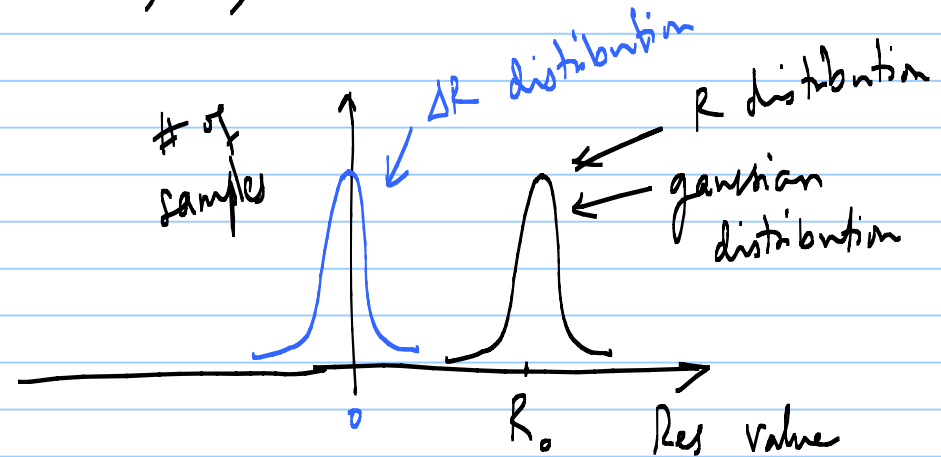


$$R = R_0 + \Delta R$$

↳ described by σ^2

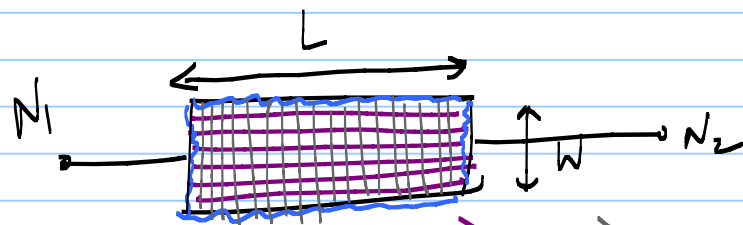

$$\# \text{ of squares} = \frac{L}{W}$$

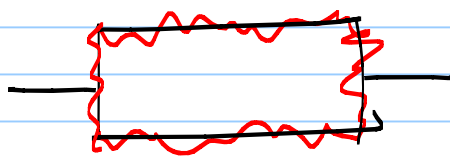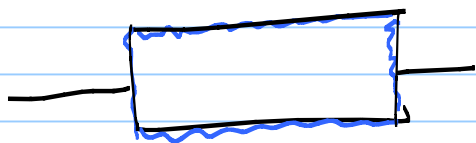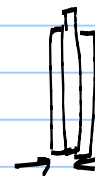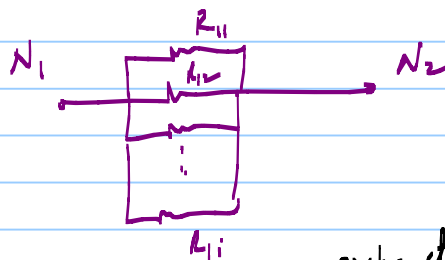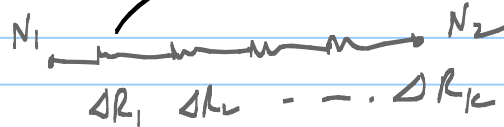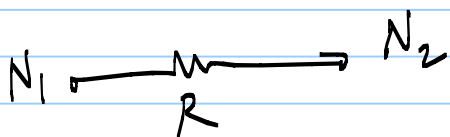

expect

$$\sqrt{R} < \sqrt{R}$$

empirical factor

$$\sigma_R \propto \frac{1}{\sqrt{W_R \cdot L_R}}$$

$$\sigma_R = \frac{A_R}{\sqrt{W_R \cdot L_R}}$$

Low mismatch \leftrightarrow High area

$$\left(\beta = \mu C_{ox} \right)$$


In general: $\sigma \propto \frac{1}{\sqrt{\text{Area}}}$


Extend to other components

$$\sigma_C = \frac{A_C}{\sqrt{W_C \cdot L_C}}$$

cap
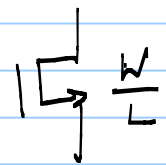
$$\sigma_{V_T} = \frac{A_{V_T}}{\sqrt{W \cdot L}}$$
$$\sigma_{\beta} = \frac{A_{\beta}}{\sqrt{W \cdot L}}$$



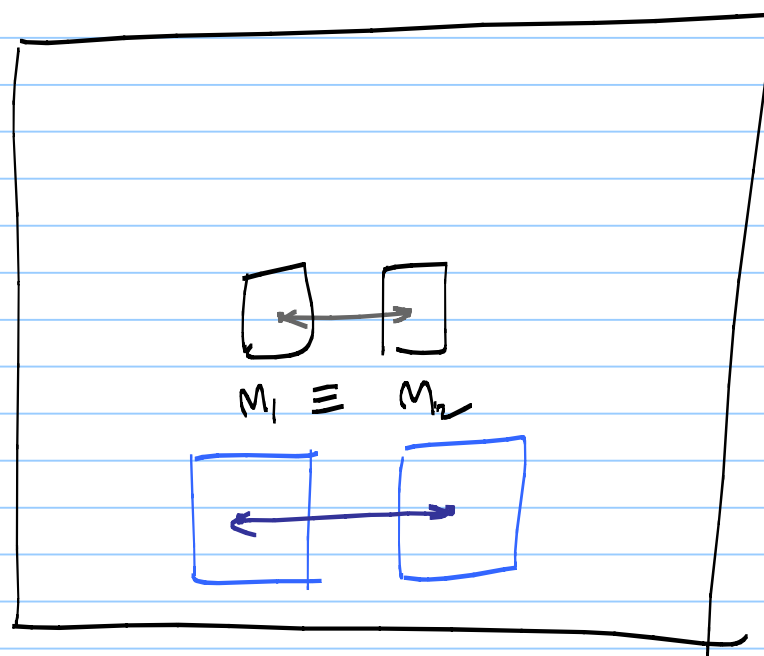


$$I_D = \mu \omega \times \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$W \rightarrow nW$
 $L \rightarrow nL$

I_D stays the same
 choose n so that σ is acceptable

Example #1

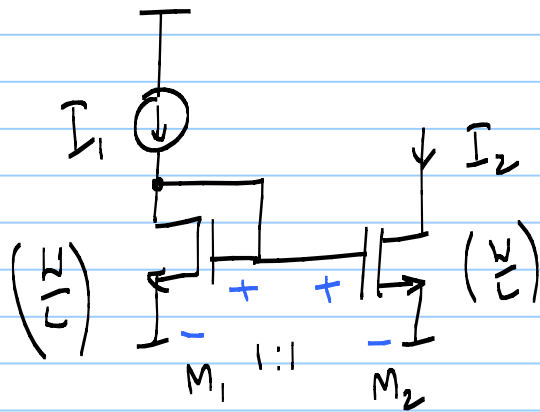

* No systematic mismatch

* $V_{T1} \neq V_{T2}$ only V_T mismatch

$$V_{T2} = V_{T1} + \Delta V_T$$

small

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$\frac{\partial I_D}{\partial V_T} = -\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T) = -g_m$$

$$\Delta I_D = \frac{\partial I_D}{\partial V_T} \cdot \Delta V_T = -g_m \Delta V_T$$

$$\left. \begin{array}{l} \text{relative} \\ \text{change} \end{array} \right\} = \frac{\Delta I_D}{I_D} = \frac{-g_m \Delta V_T}{I_D}$$


$$\sqrt{\frac{\Delta I}{I}}^2 = \frac{g_m^2}{I_D^2} \cdot \sqrt{V_T}^2$$

$$g_m^2 = \left(\frac{2 I_D}{V_{DS} - V_T} \right)^2$$



$$\sqrt{\frac{\Delta I}{I}}^2 = \frac{4}{V_{DSat}^2} \sqrt{V_T}^2$$

larger $V_{DSat} \leftrightarrow$ smaller $\frac{\Delta I}{I}$

Mismatch in Differential Amplifiers

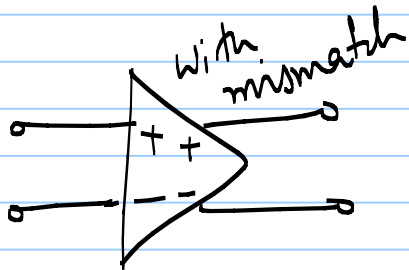

≡

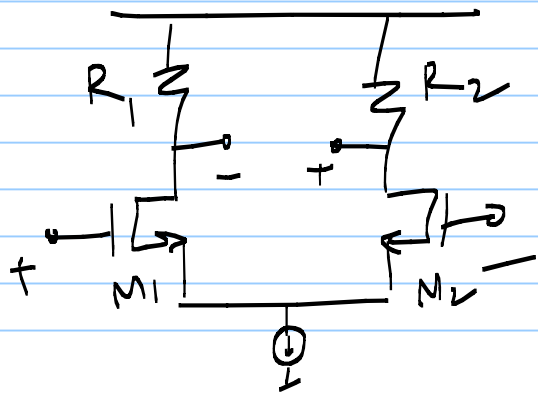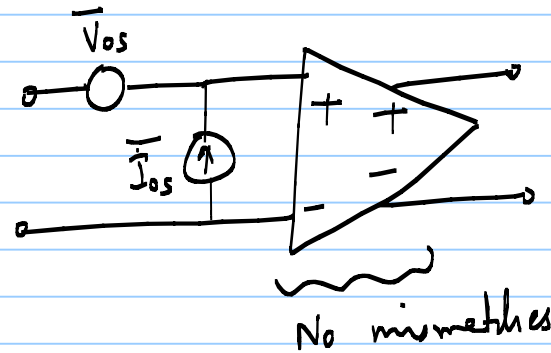


$$R_1 \equiv R_2$$


$$M_1 \equiv M_2$$

* No systematic mismatch
 $\hookrightarrow \bar{V}_{0s}$ & \bar{I}_{0s} have zero mean

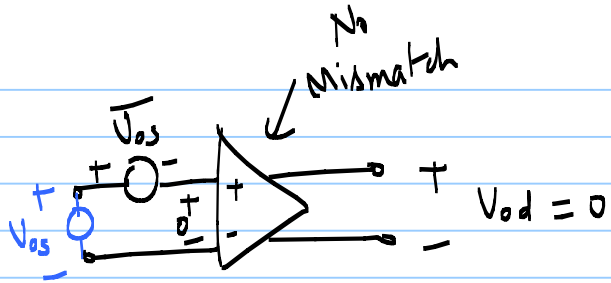* $\bar{I}_{0s} = 0$ for MOS σ amps when input is applied @ gate



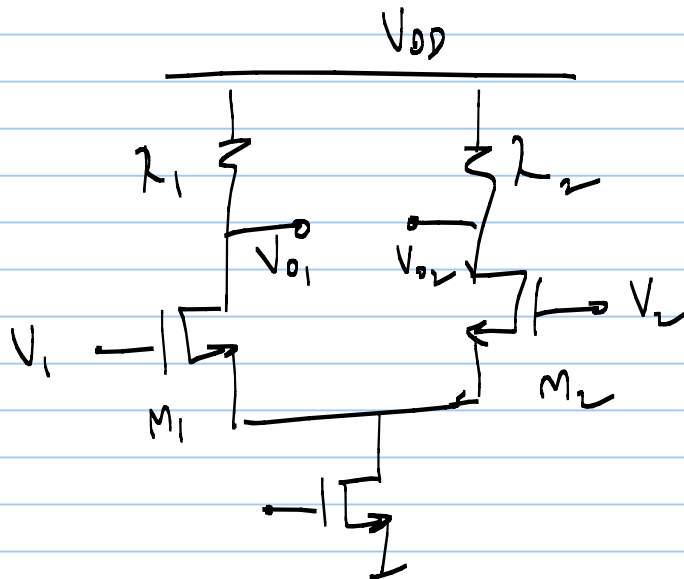V_{os} = voltage to be applied @ input so that $V_{od} = 0$




$V_{os} = V_1 - V_2$ that makes $V_{o1} - V_{o2} = 0$

5/10/2023

Lec 9

Mismatch in differential amplifier

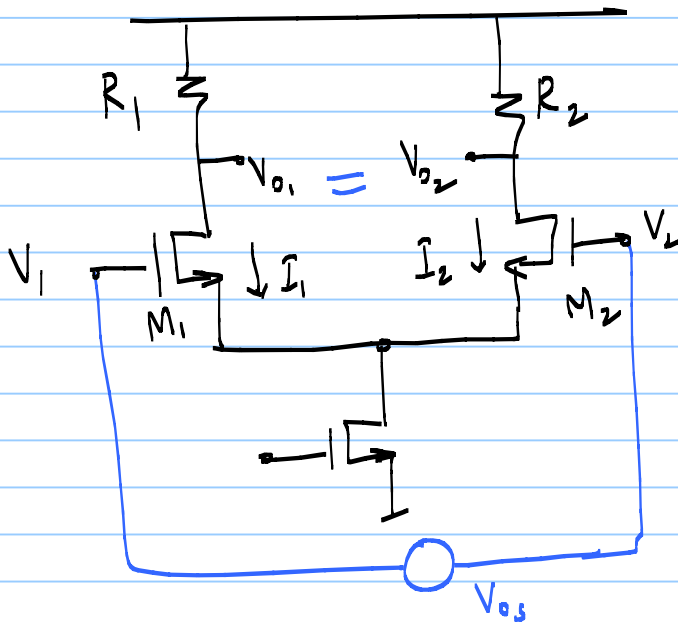

$$R_1 \neq R_2$$

$$V_{T1} \neq V_{T2}$$

$$\left(\frac{W}{L}\right)_1 \neq \left(\frac{W}{L}\right)_2$$

Small mismatches

$$R = \frac{R_1 + R_2}{2}$$

$$\Delta R = \frac{R_1 - R_2}{2}$$

$$V_T = \frac{V_{T1} + V_{T2}}{2}$$

$$\Delta V_T = V_{T1} - V_{T2}$$

$$\left(\frac{W}{L}\right) = \frac{(W/L)_1 + (W/L)_2}{2}$$

$$\Delta\left(\frac{W}{L}\right) = \frac{(W/L)_1 - (W/L)_2}{2}$$

$$\left. \begin{aligned} V_{o1} &= V_{o2} \\ V_{DD} - I_1 R_1 &= V_{DD} - I_2 R_2 \end{aligned} \right\} I_1 R_1 = I_2 R_2$$

$$I = \frac{I_1 + I_2}{2} ; \Delta I = \frac{I_1 - I_2}{2}$$

$$I_1 = I + \Delta I$$

$$I_2 = I - \Delta I$$

$$R_1 = R + \Delta R ; R_2 = R - \Delta R$$

$$V_{T1} = V_T + \frac{\Delta V_T}{2} ; V_{T2} = V_T - \frac{\Delta V_T}{2}$$


$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \Delta\left(\frac{W}{L}\right) ; \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \Delta\left(\frac{W}{L}\right)$$

$$I_1 R_1 = I_2 R_2 \Rightarrow (I + \Delta I)(R + \Delta R) = (I - \Delta I)(R - \Delta R)$$

$$\cancel{IR} + I\Delta R + \Delta IR + \cancel{\Delta I\Delta R} = \cancel{IR} - \Delta IR - I\Delta R + \cancel{\Delta I\Delta R}$$

$$\cancel{2\Delta IR} = -\cancel{2I\Delta R}$$
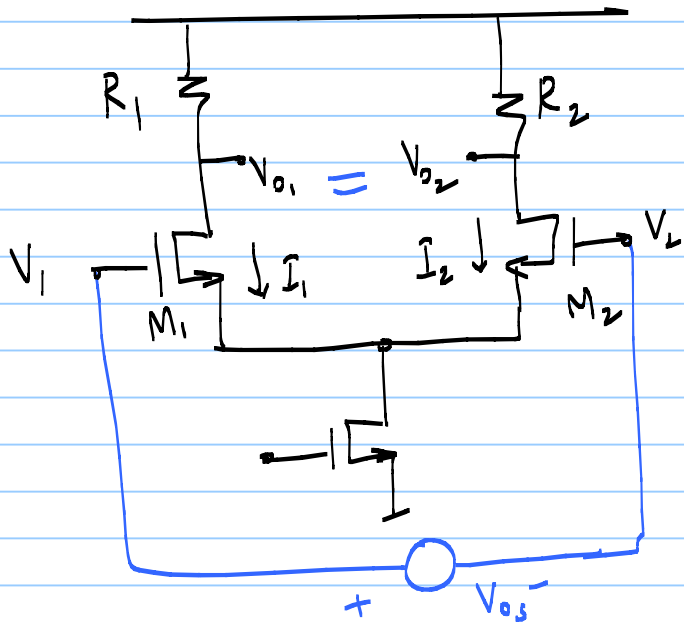
$$\frac{\Delta I}{I} = -\frac{\Delta R}{R}$$



$$V_{os} = V_1 - V_2 = V_{as1} - V_{as2}$$

$$= \left[V_{T1} + \sqrt{\frac{2I_1}{\mu C_{ox} \left(\frac{W}{L}\right)_1}} \right] - \left[V_{T2} + \sqrt{\frac{2I_2}{\mu C_{ox} \left(\frac{W}{L}\right)_2}} \right]$$

$$= \Delta V_T + \sqrt{\frac{2}{\mu C_{ox}}} \left[\sqrt{\frac{I_1}{\left(\frac{W}{L}\right)_1}} - \sqrt{\frac{I_2}{\left(\frac{W}{L}\right)_2}} \right]$$

$$V_{os} = \Delta V_T + \sqrt{\frac{2}{\mu C_{ox}}} \left[\sqrt{\frac{I + \Delta I}{\left(\frac{W}{L}\right) + \frac{\Delta W}{L}}} - \sqrt{\frac{I - \Delta I}{\left(\frac{W}{L}\right) - \frac{\Delta W}{L}}} \right]$$

$$= \Delta V_T + \underbrace{\sqrt{\frac{2I}{\mu C_{ox} \left(\frac{W}{L}\right)}}}_{\text{nom. } V_{DSat}} \left[\sqrt{\frac{1 + \Delta I/I}{1 + \frac{\Delta(W/L)}{(W/L)}}} - \sqrt{\frac{1 - \Delta I/I}{1 - \frac{\Delta(W/L)}{(W/L)}}} \right]$$

$$= \Delta V_T + V_{DSat} \left[\left(1 + \frac{\Delta I}{2I}\right) \left(1 - \frac{\Delta(W/L)}{2(W/L)}\right) - \left(1 - \frac{\Delta I}{2I}\right) \left(1 + \frac{\Delta(W/L)}{2(W/L)}\right) \right]$$


$$V_{os} = \Delta V_T + V_{Dsat} \left[\cancel{1} + \frac{\Delta I}{2I} - \frac{\Delta(W/L)}{2(W/L)} - \frac{\cancel{\Delta I \cdot \Delta(W/L)}}{4I(W/L)} \right]$$

$$\left[\cancel{-1} + \frac{\Delta I}{2I} - \frac{\Delta(W/L)}{2(W/L)} + \frac{\cancel{\Delta I \cdot \Delta(W/L)}}{4I(W/L)} \right]$$

$$= \Delta V_T + V_{Dsat} \left(\frac{\Delta I}{I} - \frac{\Delta(W/L)}{(W/L)} \right)$$

$$V_{os} = \Delta V_T + V_{Dsat} \left(-\frac{\Delta R}{R} - \frac{\Delta(W/L)}{(W/L)} \right)$$



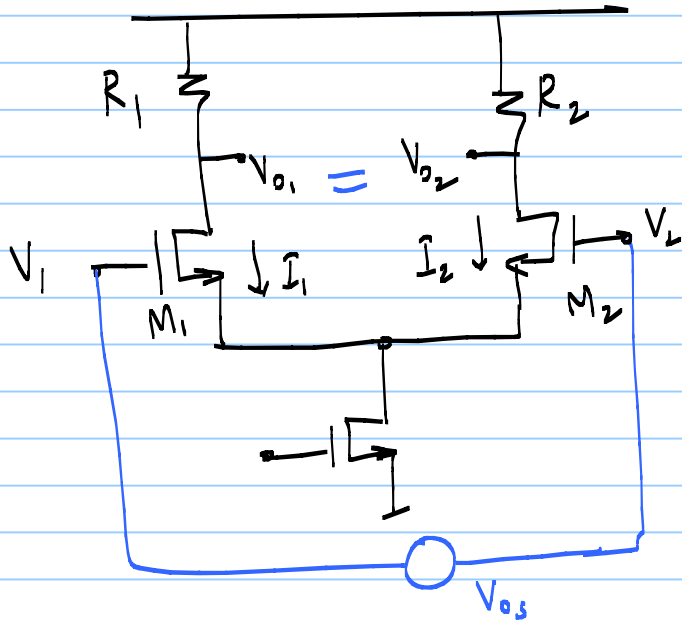
$$\sqrt{v_{os}^2} = \sqrt{v_T^2} + V_{Dsat}^2 \left[\sqrt{\frac{2}{\Delta R/R}} + \sqrt{\frac{\Delta W/L}{W/L}} \right] \checkmark$$



only $V_{T,1,2}$ mismatch

$$V_{os} = \Delta V_T$$

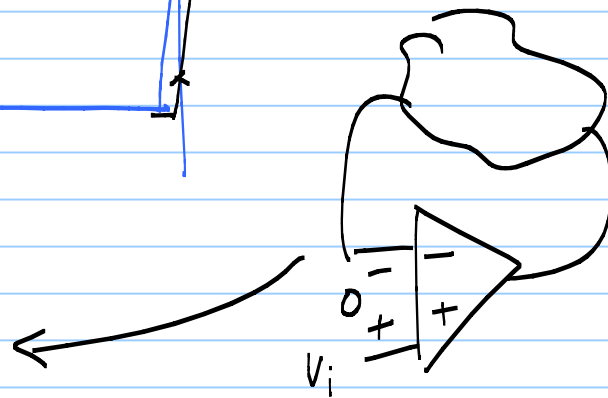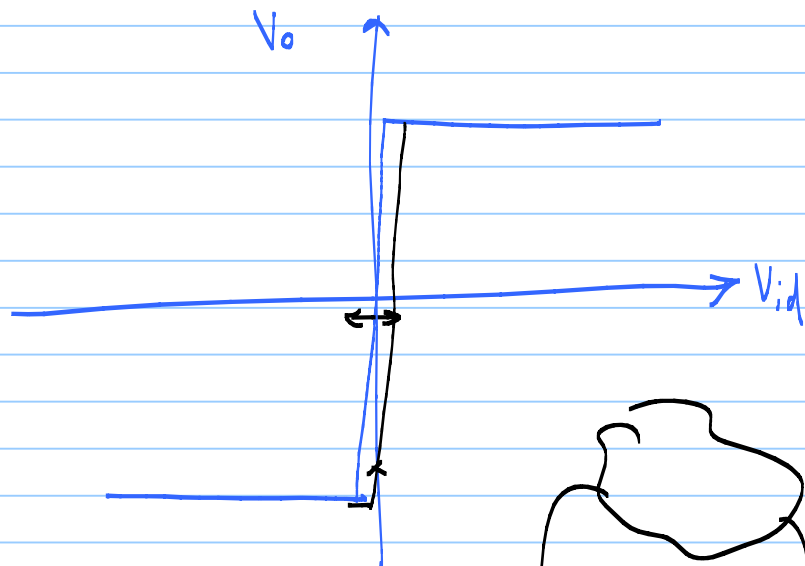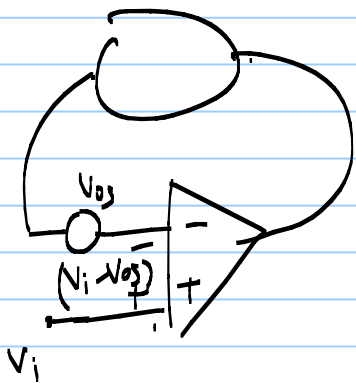
$$\begin{aligned} V_{os} &= V_{as1} - V_{as2} \\ &= \Delta V_T + \underbrace{\Delta V_{Dsat}}_0 \end{aligned}$$



10/10/23

Lec 10


One stage of amp

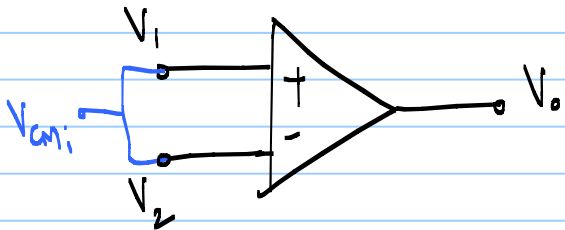


$$\left. \begin{array}{l} I_p \\ M_1 \equiv M_2 \\ \& \\ M_3 \equiv M_4 \end{array} \right\} \begin{array}{l} V_0 = V_{DD} - V_{S_{G3}} \\ = V_{ref} \end{array}$$

$$\left. \begin{array}{l} I_p \\ M_1 \not\equiv M_2 \\ \text{or} \\ M_3 \not\equiv M_4 \end{array} \right\} V_0 \neq V_{DD} - V_{S_{G3}}$$

$$\begin{array}{l} V_{hS_1} = V_{hS_2} \\ I_1 + I_2 = 2I_0 \end{array} \left| \begin{array}{l} V_{S_{G3}} = V_{S_{G4}} \\ I_1 = I_3 ; I_2 = I_4 \end{array} \right.$$

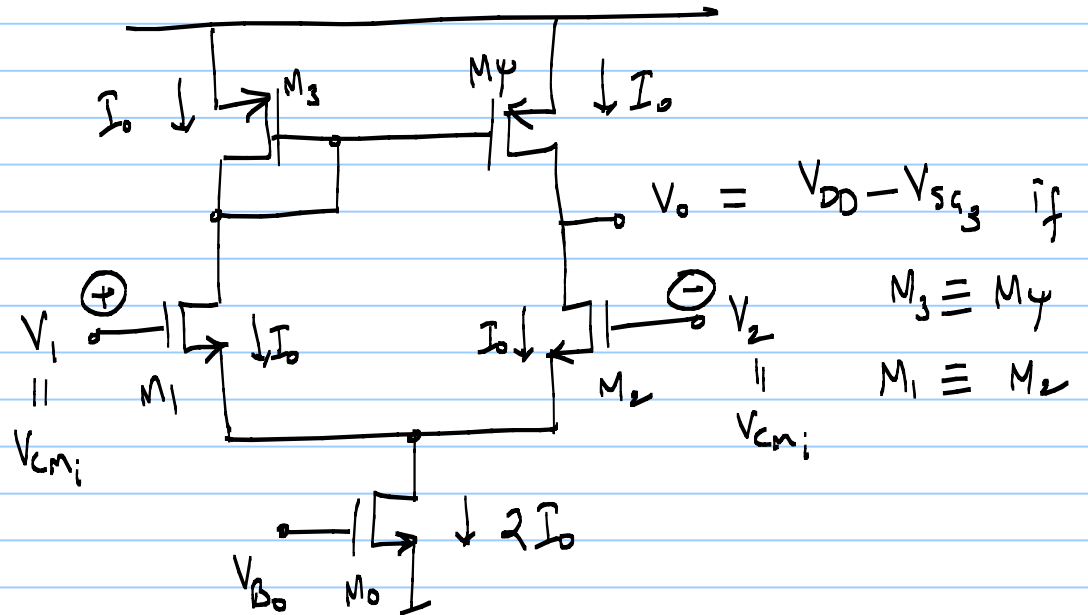

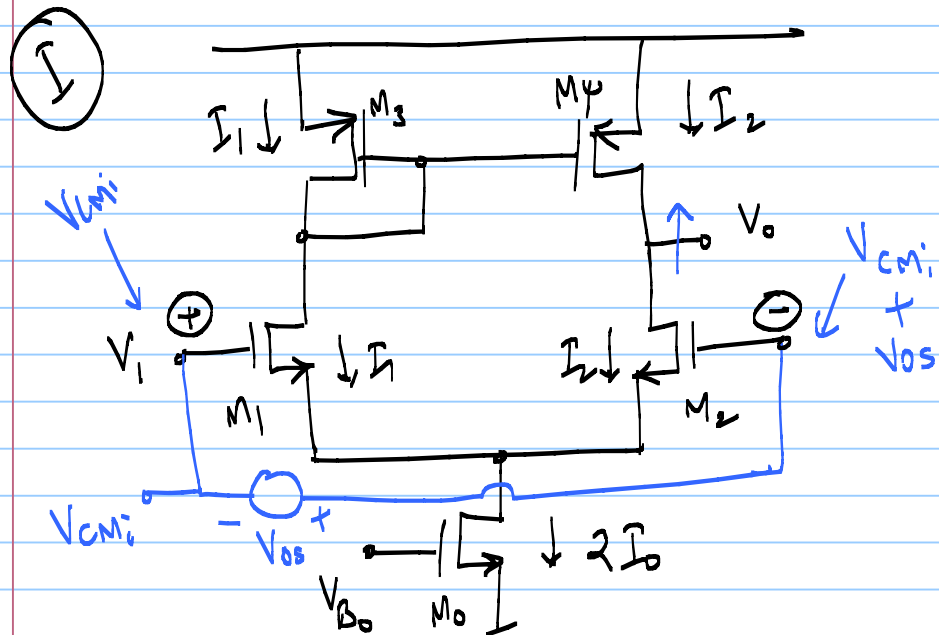

Assume mismatch only in V_{T1} & V_{T2}

$$V_{T1} = V_T ; \quad V_{T2} = V_T + \Delta V_{T1}$$





Apply $V_1 - V_2 = V_{os}$ so that $V_o = V_{DD} - V_{s_{q3}} = V_{o_{ref}}$

$$\left. \begin{aligned} I_1 &= I_0 + g_{m1} \Delta V_{T1} / 2 \\ I_2 &= I_0 - g_{m1} \Delta V_{T1} / 2 \end{aligned} \right\} I_1 > I_2$$


$$V_o > V_{o_{ref}}$$

$$I_f \quad V_{os} = \Delta V_{T1} \Rightarrow I_1 = I_2 = I_0$$
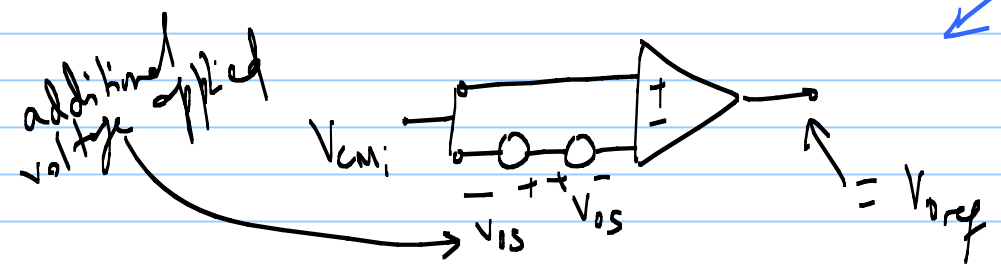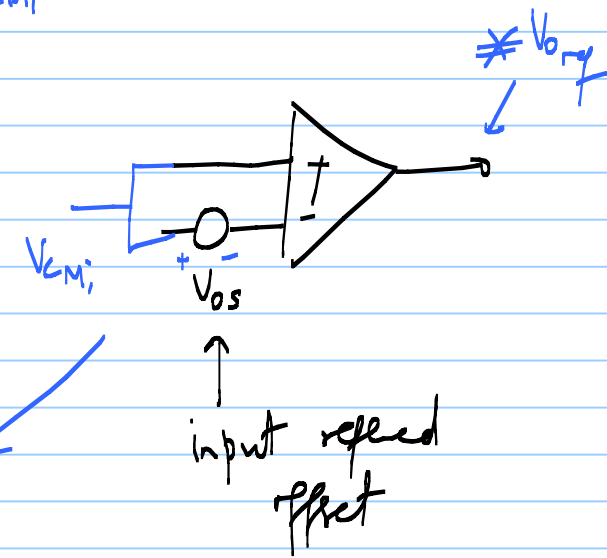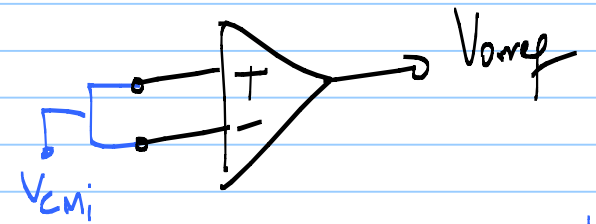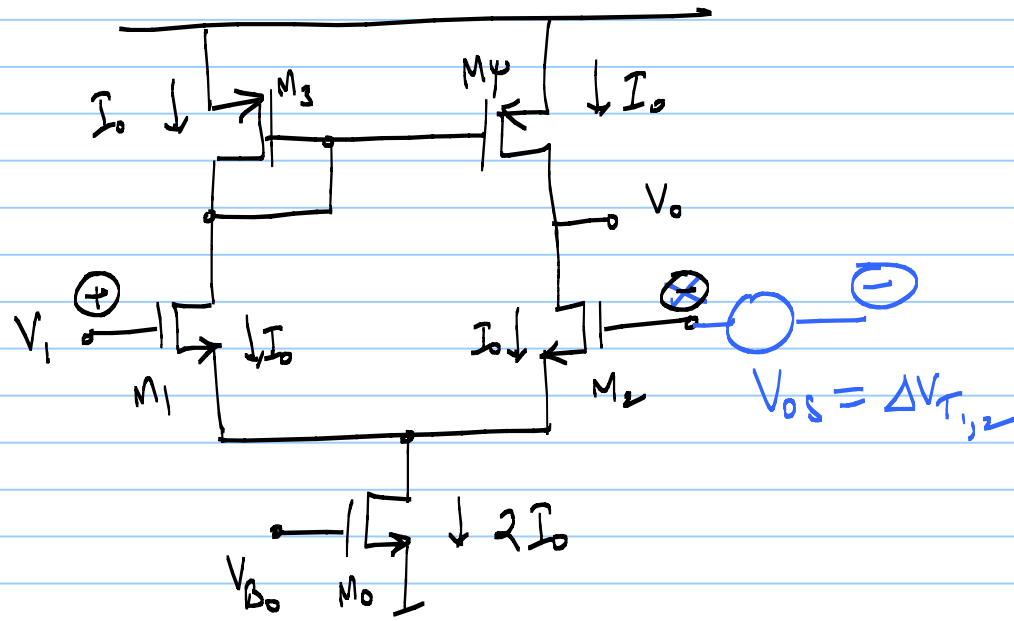
$$\rightarrow \sigma_{os}^2 = \sigma_{V_{T1}}^2$$



①

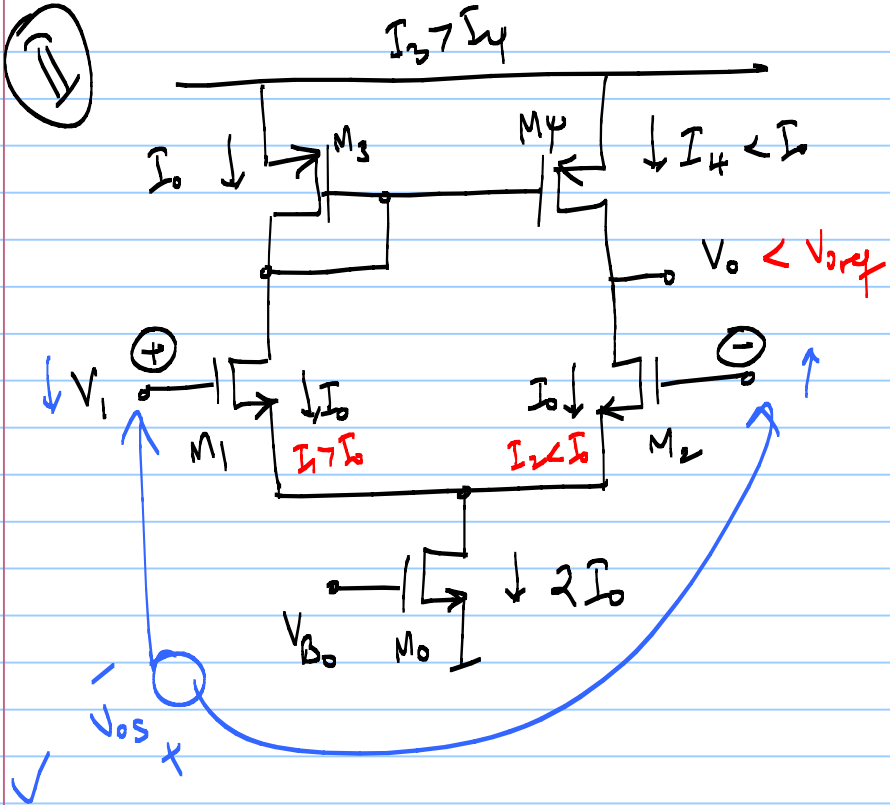

Assume $V_{T3} = V_{Tp}$; $V_{T4} = V_{Tp} + \Delta V_{T3}$

$M_1 \equiv M_2$

$V_o < V_{ref}$

$I_1 = I_3$

$I_2 = I_4$

$I_1 + I_2 = 2I_0$



$I_1 = I_3 > I_0$

$I_2 = I_4 < I_0$

$I_2 = I_4 = I_0 - g_{m3} \Delta V_{T3} / 2$


$I_1 = I_3 = I_0 + g_{m3} \Delta V_{T3} / 2$

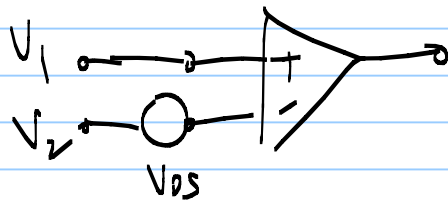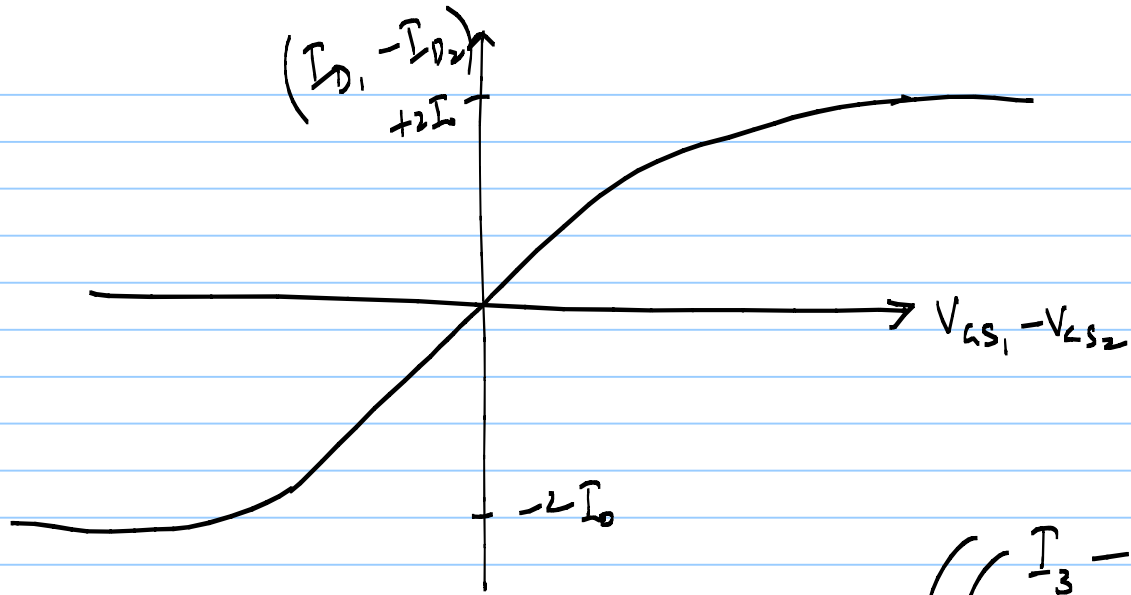$I_1 - I_2 = I_3 - I_4 = g_{m3} \Delta V_{T3}$



$$\left(\begin{array}{l} I_3 - I_4 = g_{m3} \Delta V_{T3} \\ I_1 - I_2 = g_{m1} V_{OS} \end{array} \right.$$
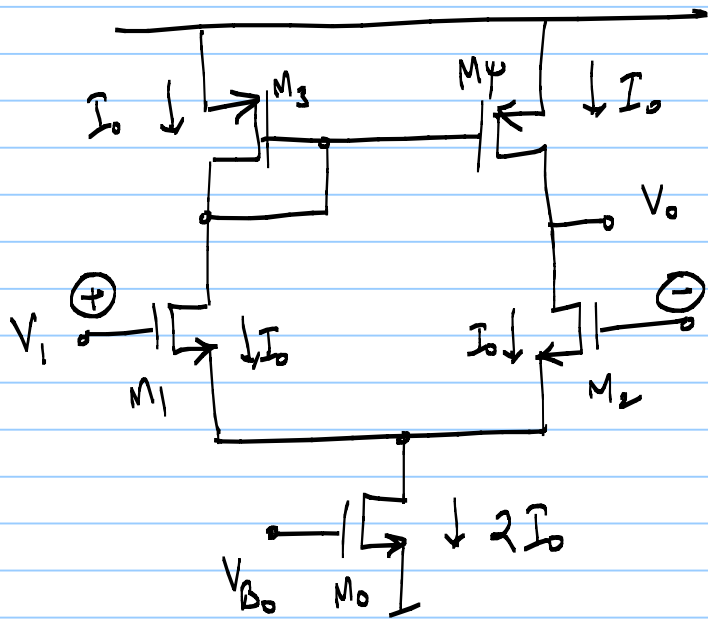
$$V_{OS} = \frac{g_{m3}}{g_{m1}} \Delta V_{T3} \rightarrow \sigma_{OS}^2 = \left(\frac{g_{m3}}{g_{m1}} \right)^2 \sigma_{V_{T3}}^2$$



BoK

$$\begin{cases} V_{T1} = V_{Tn} & ; & V_{T2} = V_{Tn} + \Delta V_{T1} \\ V_{T3} = V_{Tp} & ; & V_{T4} = V_{Tp} + \Delta V_{T3} \end{cases}$$

$$r_{os}^2 = \sqrt{V_{T1}}^2 + \underbrace{\left(\frac{g_{m3}}{g_{m1}} \right)^2}_{\text{wavy line}} \sqrt{V_{T3}}^2$$






low offset from $M_3, M_4 \rightarrow \downarrow g_{m3}$
 $\uparrow g_{m1}$

(similar for noise) ←

12/10/2023

Lec 11

One-stage opamp datasheet

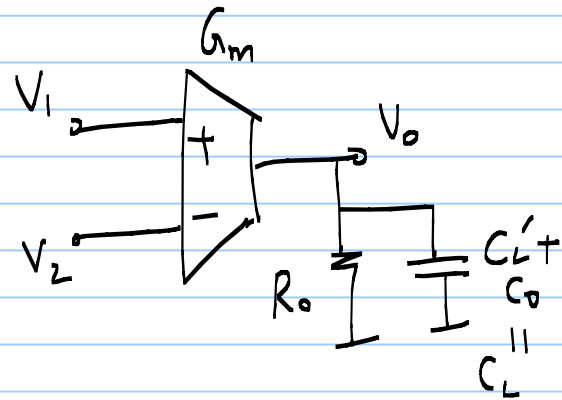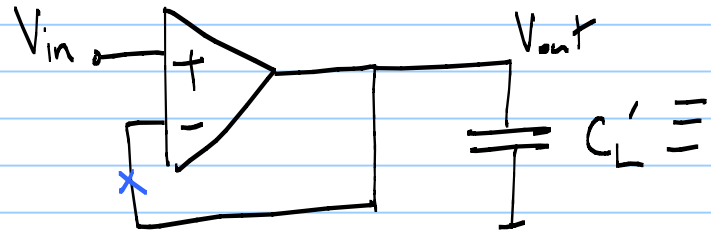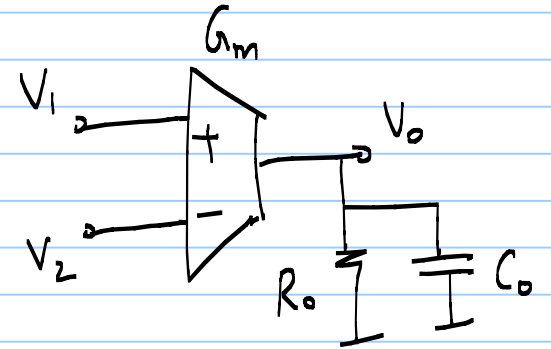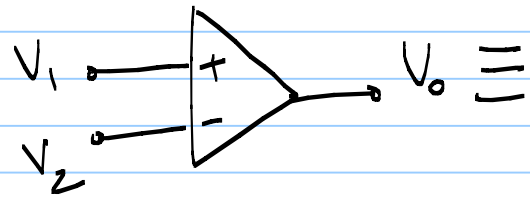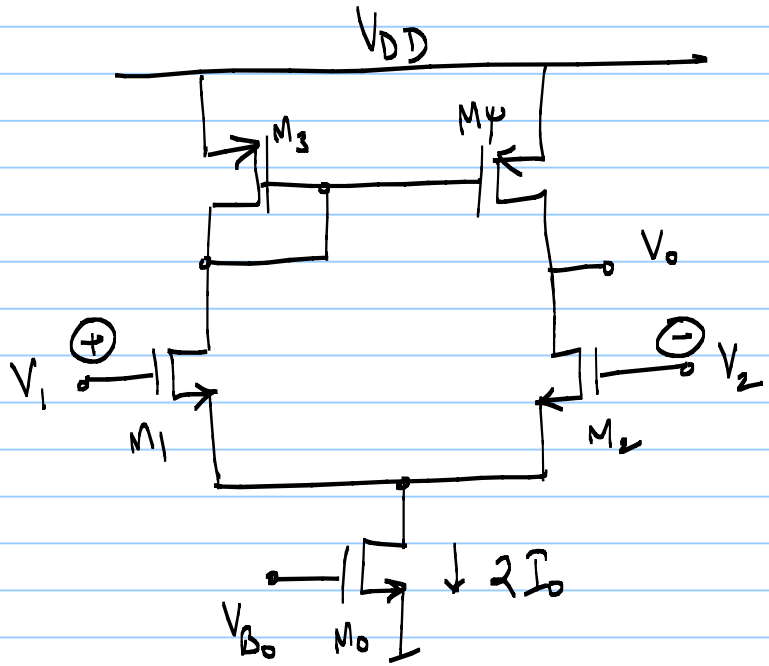

$$1) \text{ DC gain} = A_0 = G_m R_o = g_{m1} (r_{ds4} \parallel r_{ds2}) = \frac{g_{m1}}{g_{ds2} + g_{ds4}}$$



$$2) G_m = g_{m1}$$

$$3) \underset{\text{(UGF)}}{\omega_u} = \frac{G_m}{C_L} = \frac{g_{m1}}{C_L} \iff \underset{\substack{\text{(dominant} \\ \text{pole)}}}{\omega_d} = \frac{1}{R_o C_L} = \frac{G_o}{C_L} \quad (\text{LHP})$$

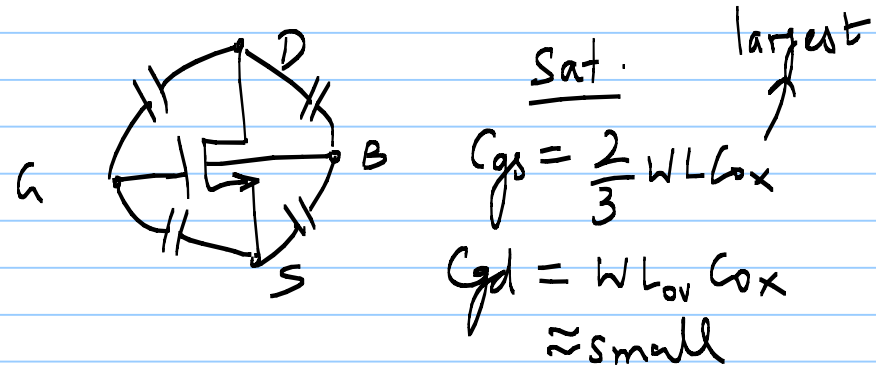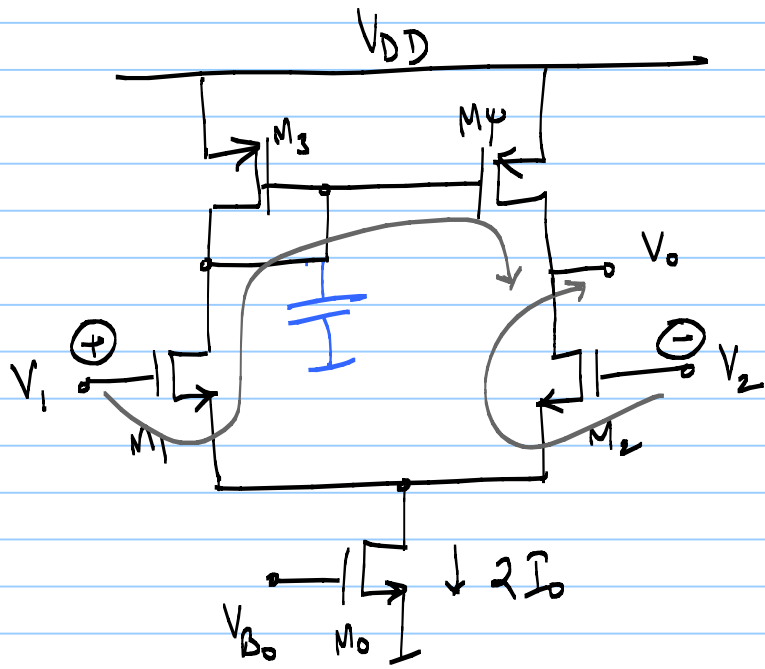
4) Non-dominant poles & zeroes:




$$\text{LHP } \omega_{nd} = \frac{g_{m3}}{C_p}$$


$$\text{LHP } z_{ND} = \frac{2g_{m3}}{C_p}$$



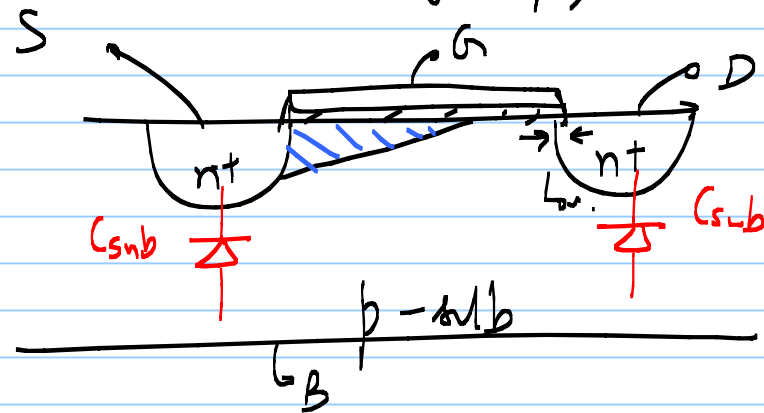$C_{db} = \text{jn. cap}$, $C_{sb} = \text{jn cap}$




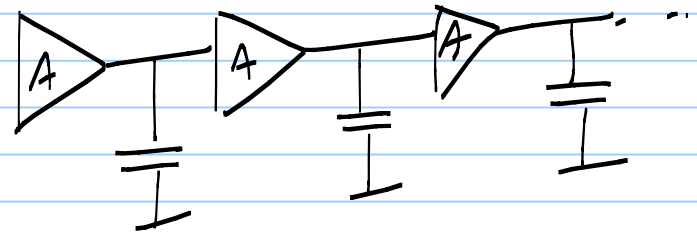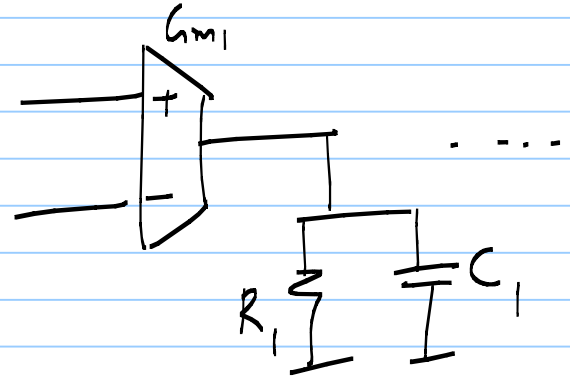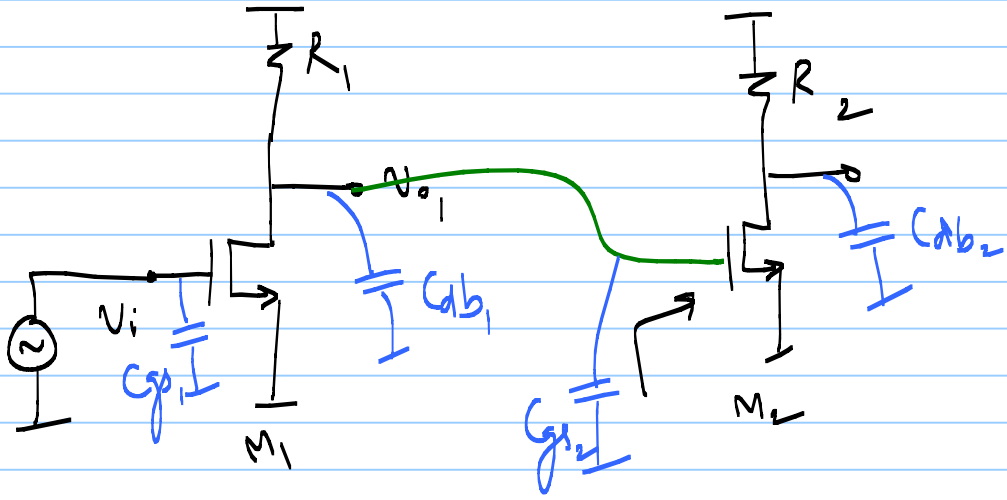

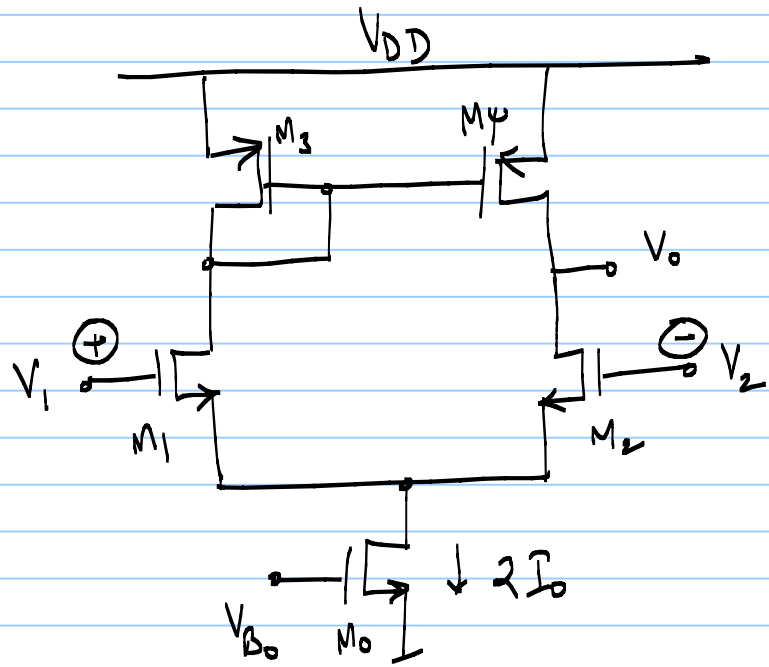

$$M_1 \equiv M_2$$


$$M_3 \equiv M_4$$

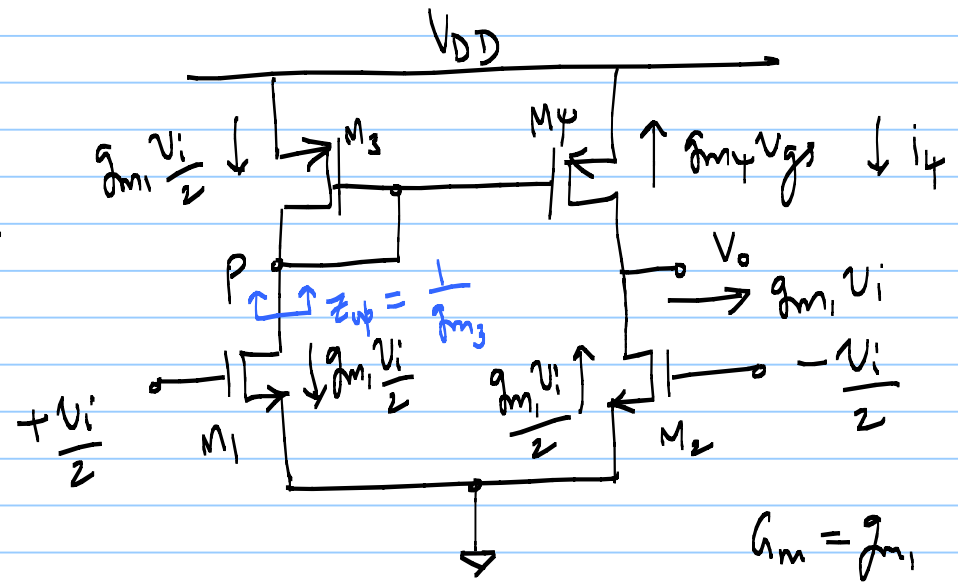

$$G_m = g_{m1}$$

$$v_p = - \frac{g_{m1} v_i / 2}{g_{m3}}$$
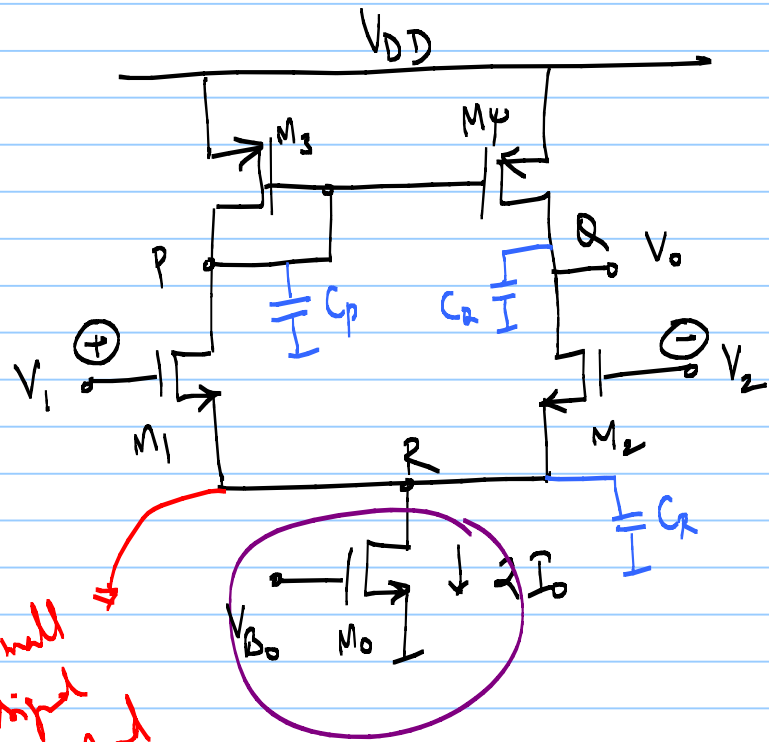
$$i_4 = \frac{g_{m1}}{g_{m3}} \times g_{m4} \cdot \frac{v_i}{2} = g_{m1} v_i / 2$$




Small
signal
DM gain

$$C_p = C_{db3} + C_{gs3} + C_{db1} + C_{gs4}$$

$$C_Q = C_{db4} + C_{db2} + C_L' = C_L$$


$$C_R = C_{db0} + C_{sb1} + C_{sb2} \leftarrow \text{does not matter for DM analysis}$$

matters for CM gain
& CMRR

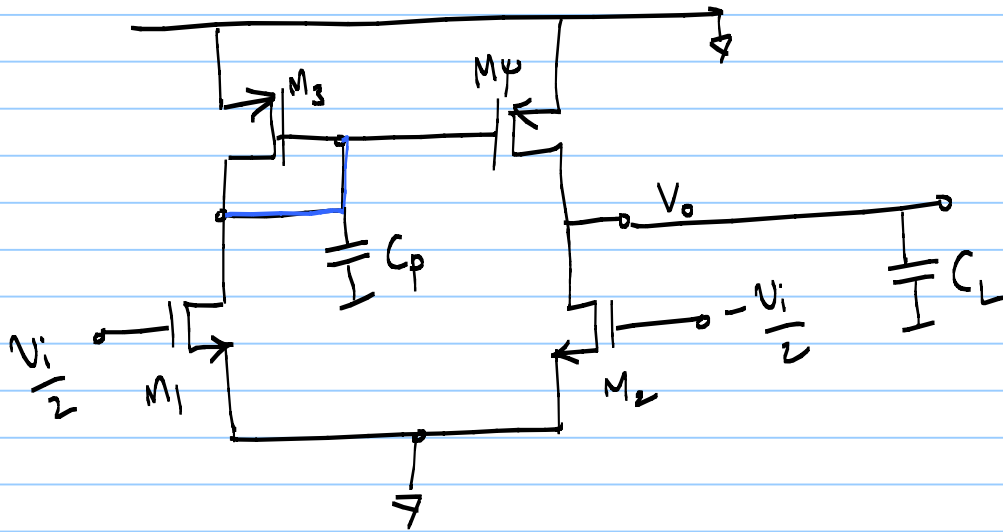

$$\frac{v_o}{v_i}(s) = ?$$
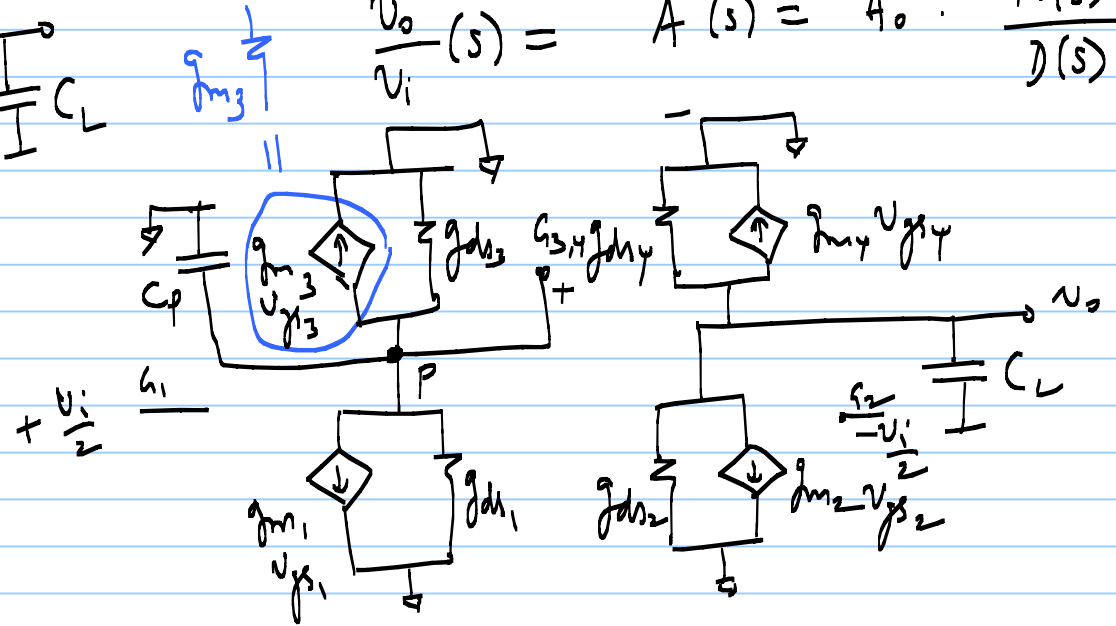
$$\frac{v_o}{v_i}(s) = A(s) = A_0 \cdot \frac{N(s)}{D(s)}$$



current
pulled
out
of output
node

$$i_o(s) = i_2(s) + i_4(s)$$

$$= g_{m2} v_{gs2} + g_{m4} v_{gs4}$$

$$= -g_{m2} \frac{v_i}{2} + g_{m4} v_{gs4}$$

$$i_1(s) = g_{m1} v_{gs1} = g_{m1} \frac{v_i}{2}$$


$$v_p = -i_1(s) \cdot Z_p(s)$$

$$= -g_{m1} \frac{v_i}{2} \cdot \frac{1}{g_{m3} + g_{ds3} + g_{ds1} + sC_p}$$

$$g_{m3} \Rightarrow g_{ds1}, g_{ds3}$$

$$G = g_{m3} + g_{ds3} + g_{ds1}$$

$$C = C_p$$

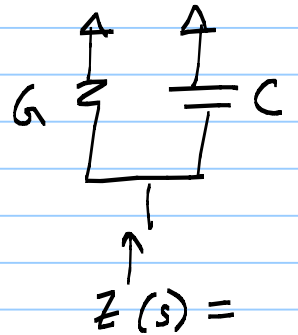

$$Y(s) = G + sC$$

$$Z(s) = \frac{1}{G + sC}$$

$$= \frac{1}{g_{m3} + g_{ds3} + g_{ds1} + sC_p}$$

$$v_p(s) \approx \frac{-g_{m1}}{g_{m3} + sC_p} \cdot (v_i/2) = v_{gs4}$$

$$i_4(s) = g_{m4} \cdot v_p(s) = \frac{-g_{m1} g_{m4}}{g_{m3} + sC_p} \cdot \frac{v_i}{2} = \frac{-g_{m1}}{1 + sC_p/g_{m3}} \cdot \frac{v_i}{2}$$

$$i_o(s) = -g_{m2} \frac{v_i}{2} - \frac{g_{m1}}{1 + \frac{sC_p}{g_{m3}}} \cdot \frac{v_i}{2} = -v_i(s) \cdot \frac{g_{m1}}{2} \left[1 + \frac{1}{1 + \frac{sC_p}{g_{m3}}} \right]$$

$$= -g_{m1} \frac{v_i}{2} \left[\frac{2 + sC_p/g_{m3}}{1 + sC_p/g_{m3}} \right] = -g_{m1} v_i \left[\frac{1 + sC_p/2g_{m3}}{1 + sC_p/g_{m3}} \right]$$

$$V_o(s) = -i_o(s) \times Z_o(s)$$

$$= g_{m1} v_i \cdot \left[\frac{1 + \frac{sC_p}{2g_{m3}}}{1 + \frac{sC_p}{g_{m3}}} \right] \times \left[\frac{1}{g_{d2} + g_{d4} + sC_L} \right]$$

$$A(s) = \frac{V_o(s)}{v_i} = \underbrace{\left[\frac{g_{m1}}{g_{d2} + g_{d4}} \right]}_{A_o} \cdot \left[\frac{\left(1 + \frac{sC_p}{2g_{m3}}\right)}{\left(1 + \frac{sC_p}{g_{m3}}\right) \left(1 + \frac{sC_L}{g_{d2} + g_{d4}}\right)} \right]$$


$\leftarrow N(s)$
 $\leftarrow D(s)$


$$A(s) = \frac{V_o}{V_i}(s) = \underbrace{\left[\frac{g_{m1}}{g_{ds2} + g_{ds4}} \right]}_{A_o} \left[\frac{\left(1 + \frac{s C_p}{2 g_{m3}} \right)}{\left(1 + \frac{s C_p}{g_{m3}} \right) \left(1 + \frac{s C_L}{g_{ds2} + g_{ds4}} \right)} \right]$$

$\rightarrow z_{ND} = \frac{2 g_{m3}}{C_p}$
LHP zero


$\omega_{ND} = \frac{g_{m3}}{C_p}$
LHP pole

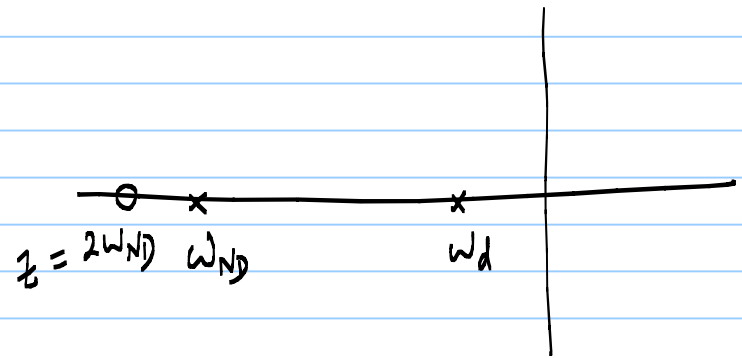$\omega_d = \frac{g_{ds2} + g_{ds4}}{C_L} = \frac{\omega_o}{C_L}$ LHP pole





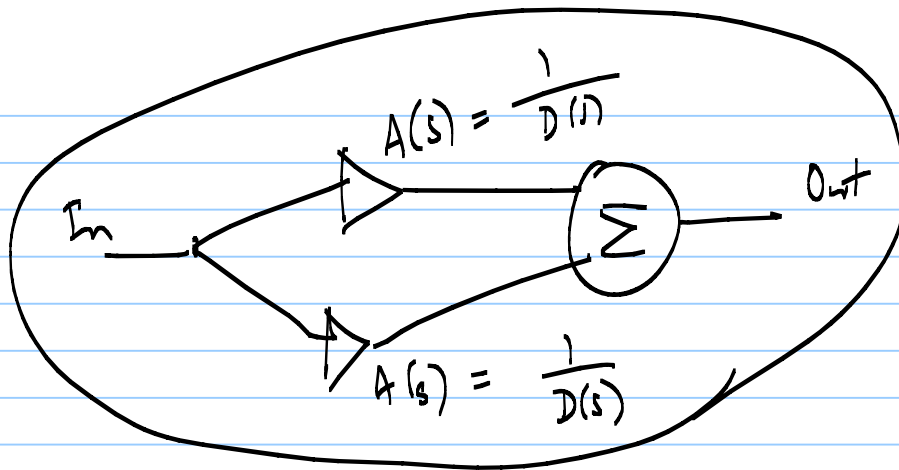

$$2A(s) = \frac{2}{D(s)}$$

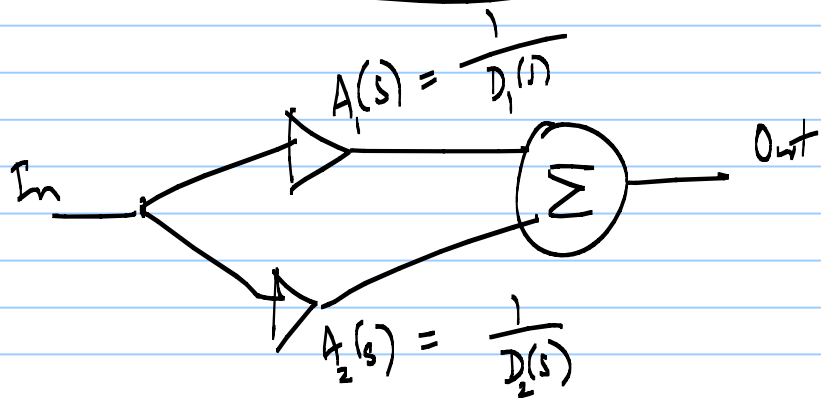

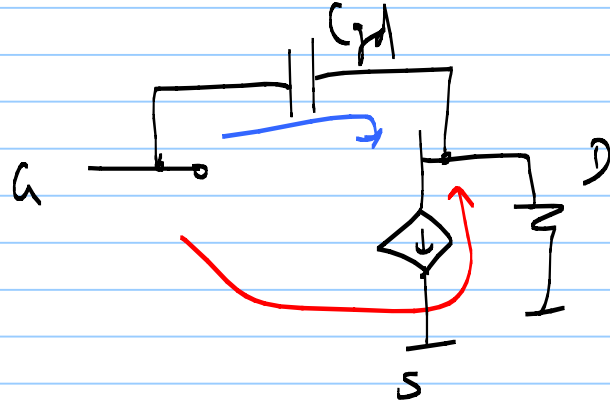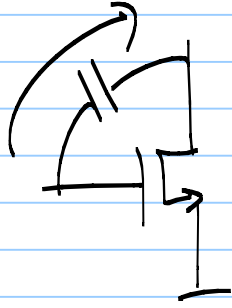
$$\begin{aligned}
 & A_1(s) + A_2(s) \\
 &= \frac{1}{D_1(s)} + \frac{1}{D_2(s)} = \frac{\overset{\text{Zero}}{\downarrow} N(s)}{D(s)}
 \end{aligned}$$




13/10/23

Lec 12

One-stage opamp datasheet

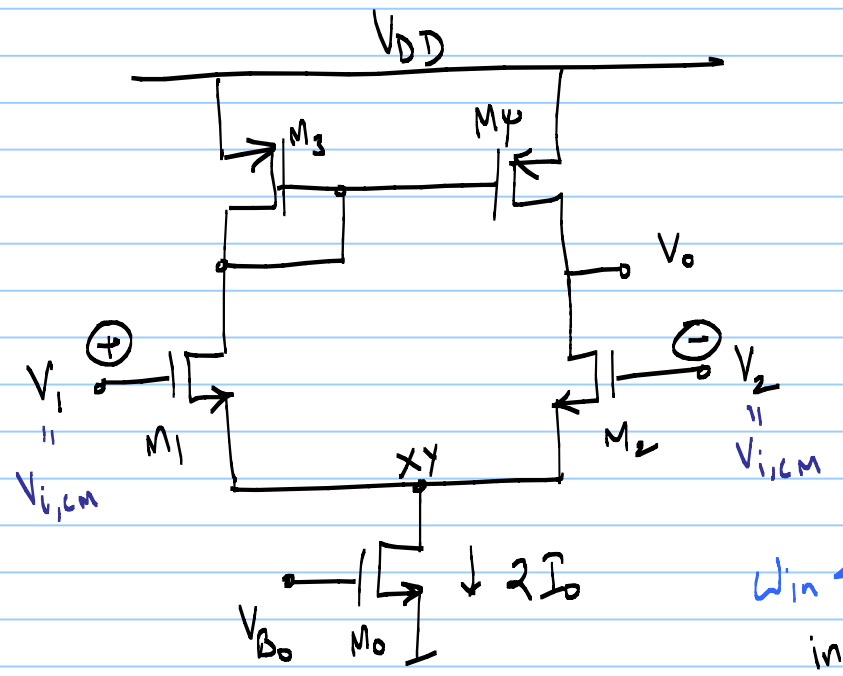

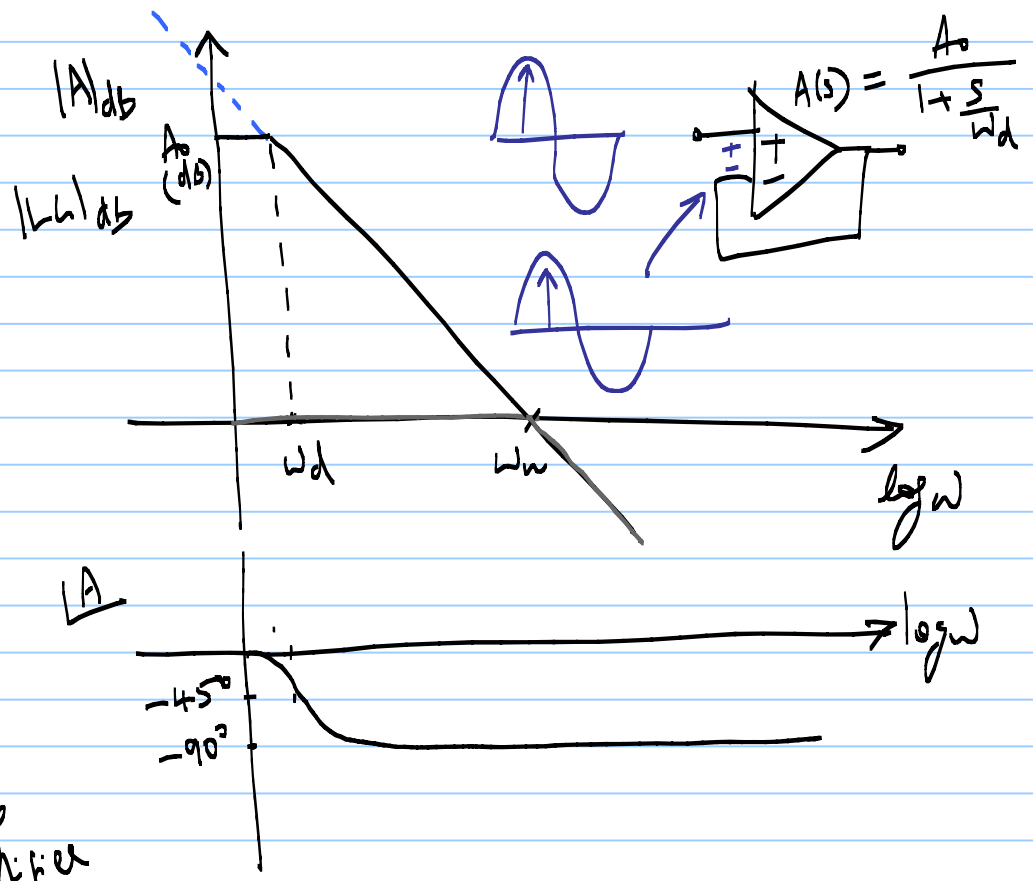$\omega_{in} \ll \omega_u$
in closed loop amplifier




5) Input CM range :


$$ICMR = \left\{ \underbrace{V_{GS1} \Big|_{I_0} + V_{DSat_0}}_{ICMR_{min}} \cdot 2I_0, \quad \underbrace{V_{DD} - V_{SG_3} \Big|_{I_0} + V_{T1}}_{ICMR_{max}} \right\}$$

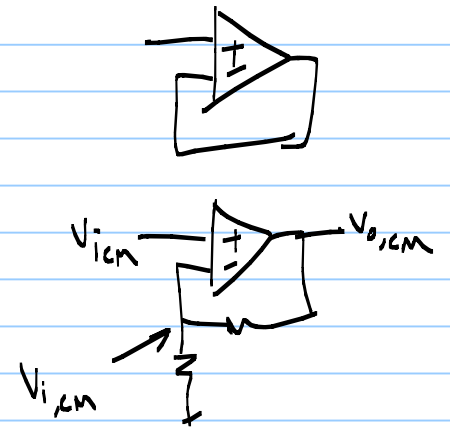6) Output CM range

$$OCMR = \left\{ \underbrace{V_{i,CM} - V_{T2}}_{(min)}, \quad \underbrace{V_{DD} - V_{SG4} + V_{T4}}_{(max)} \right\}$$



7) Noise \bar{e}_n

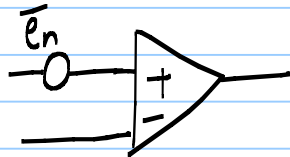

$\bar{i}_n = 0$ @ low freq.

$$\frac{\bar{e}_n^2}{\Delta f} = ?$$

HW


$$\frac{8kT}{3} \cdot g_{m1} \cdot \frac{1}{g_{m2}}$$

$$\frac{\bar{e}_n^2}{\Delta f} = \frac{16kT}{3g_{m1}} + \frac{16kT}{3g_{m1}^2} g_{m3}$$

noise from M_1 & M_2

Noise from M_3 & M_4

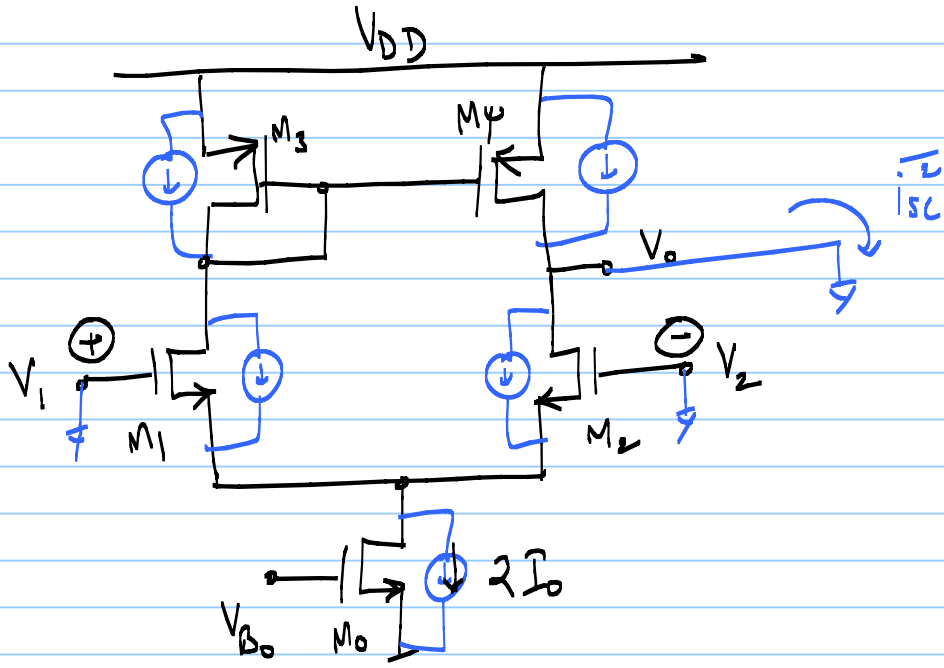
low noise : $\uparrow g_{m1}$
 $\downarrow g_{m3}$



$$\overline{e_n^2} = \frac{i_{sc}^2}{g_m^2}$$

HW

8) Offset $\overline{V_{os}}$

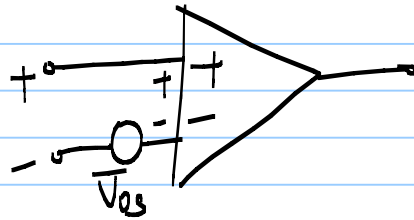


$$\overline{V_{os}} = 0$$

Assume mismatch is $V_{T1} - V_{T2}$
& $V_{T3} - V_{T4}$


$$\overline{V_{os}}^2 = \overline{V_{T1,2}}^2 + \left(\frac{g_{m3}}{g_{m1}} \right)^2 \overline{V_{T3,4}}^2$$

low offset: $\uparrow g_{m1}$
 $\downarrow g_{m3}$

9) "Slew Rate" = $\frac{\pm 2 I_0}{C_L}$


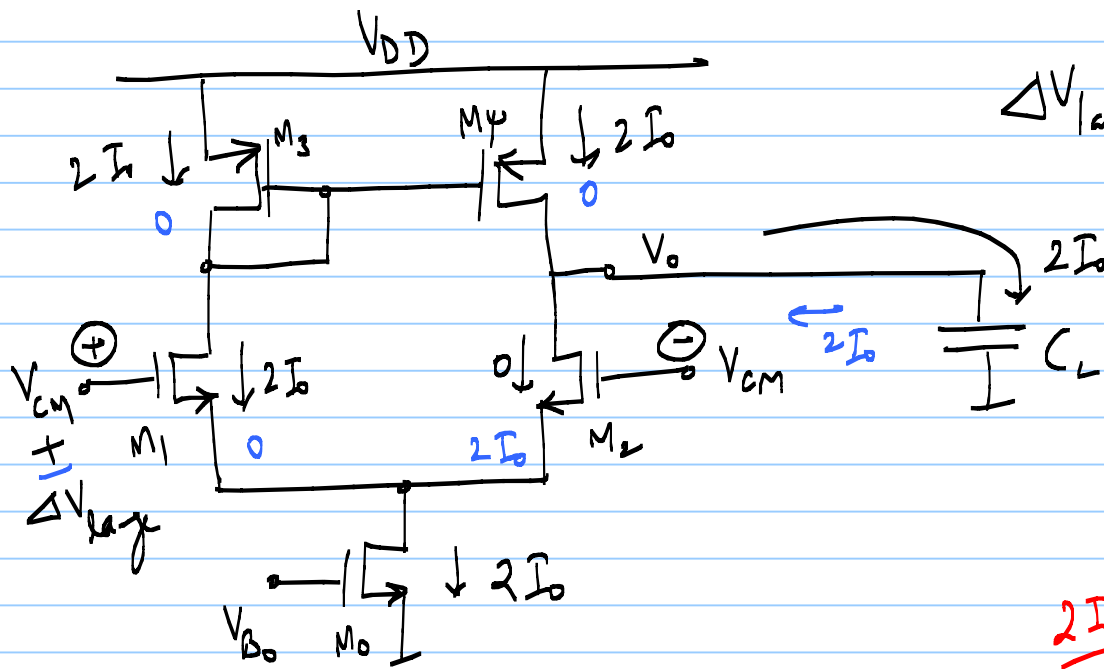


$$\Delta V_{large} = V_{AS1} - V_{AS2}$$

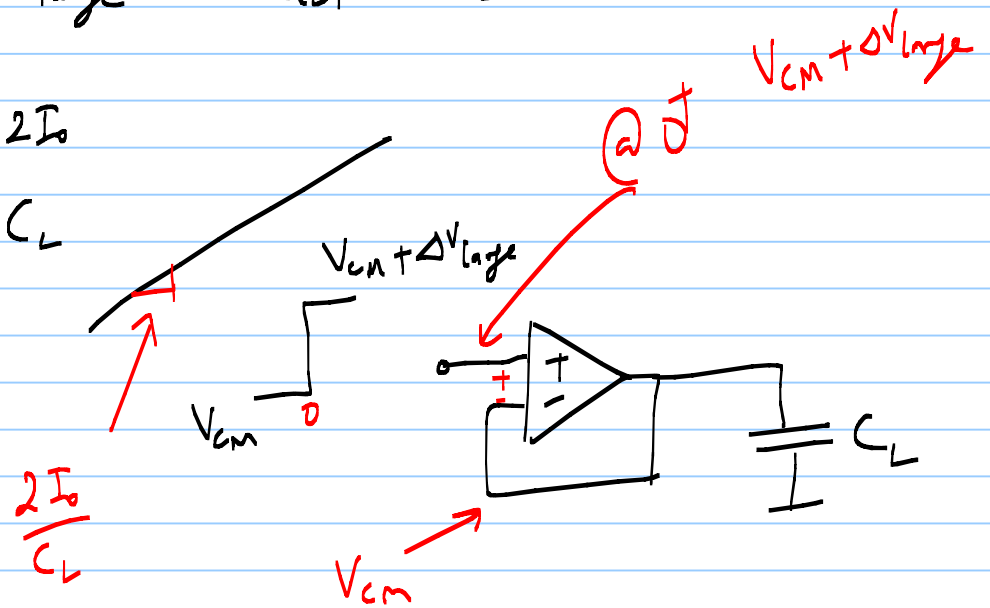




17/10/23


Lec 13

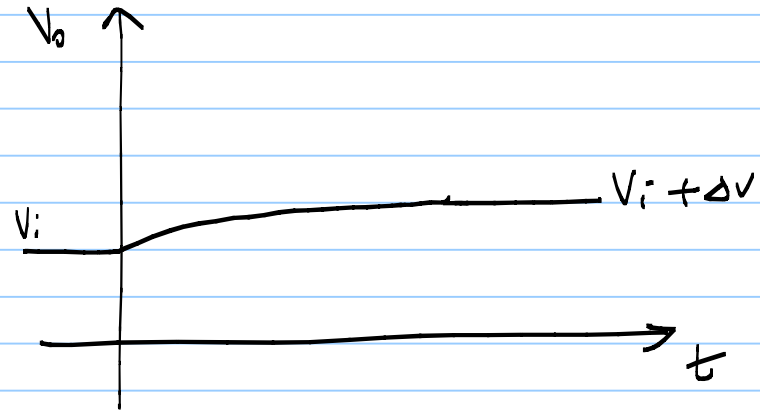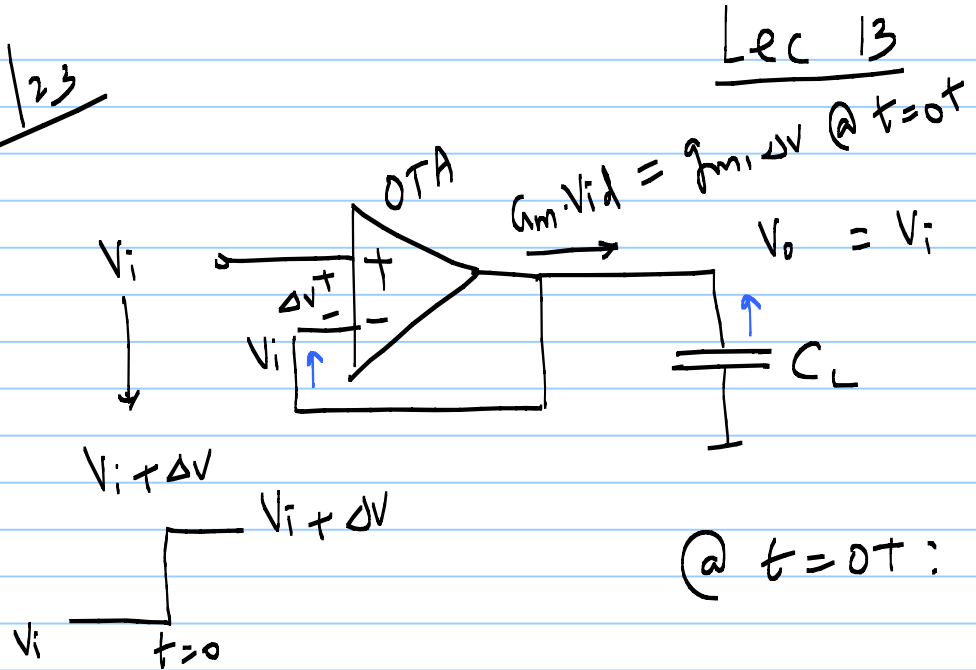




@ $t=0^+$: $\left. \begin{array}{l} V_+ = V_i + \Delta V \\ V_- = V_i \end{array} \right) V_{id}(t=0^+) = \Delta V$

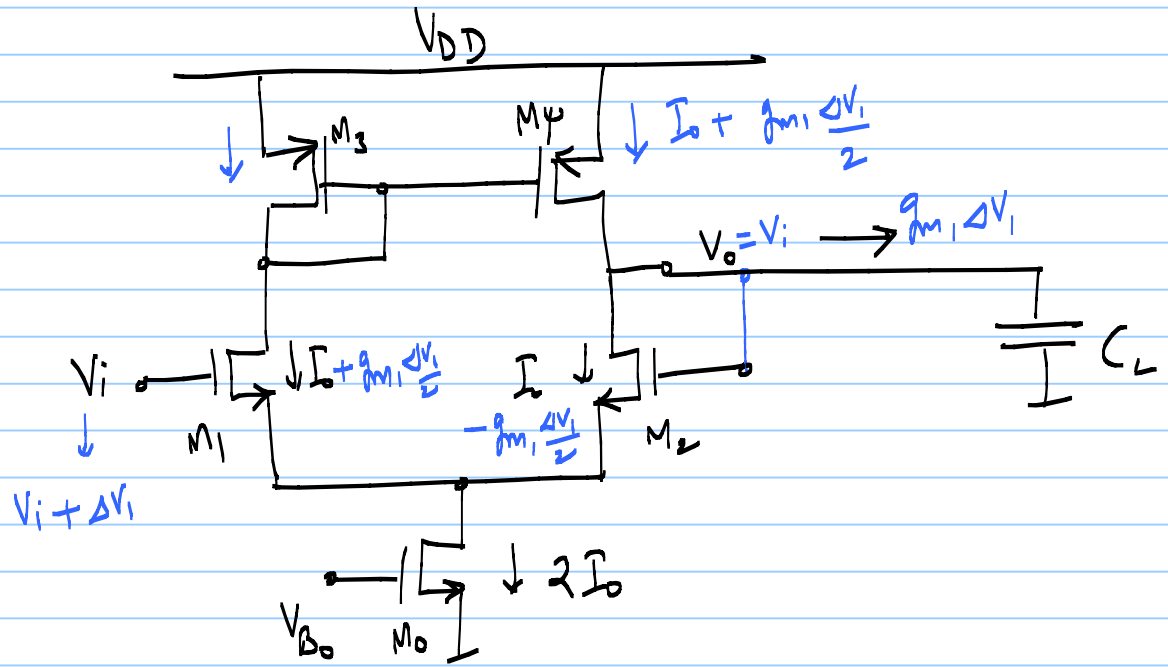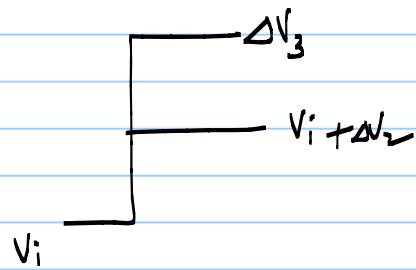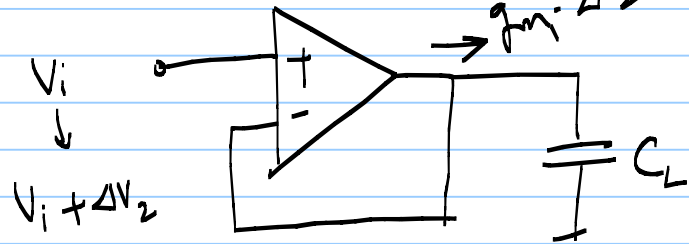
@ $t=0^+$
 $\rightarrow g_m \cdot \Delta V_2 \approx g_{m1} \cdot \Delta V_3$ etc.




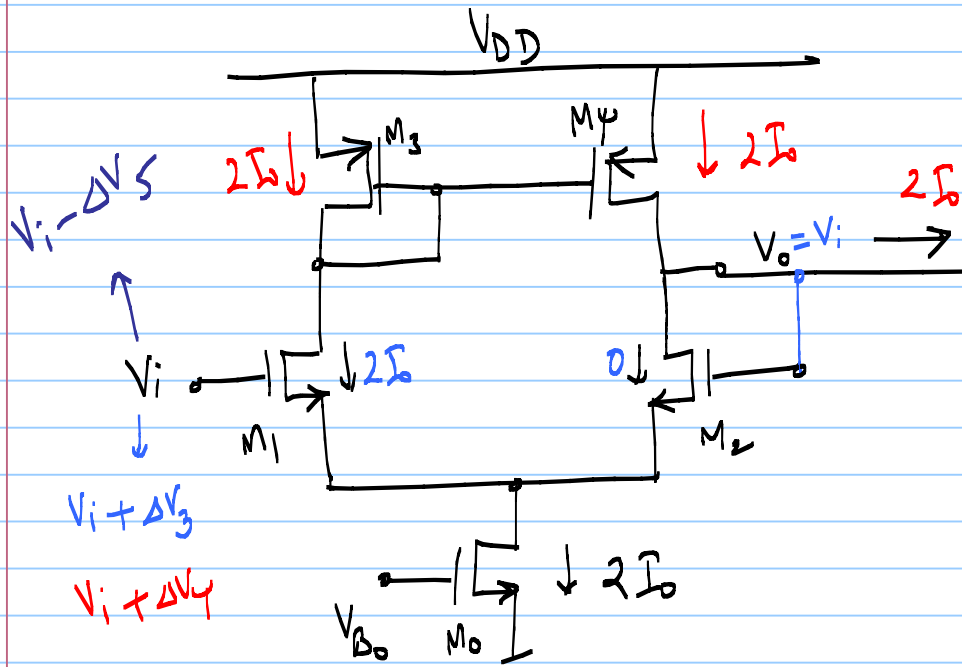

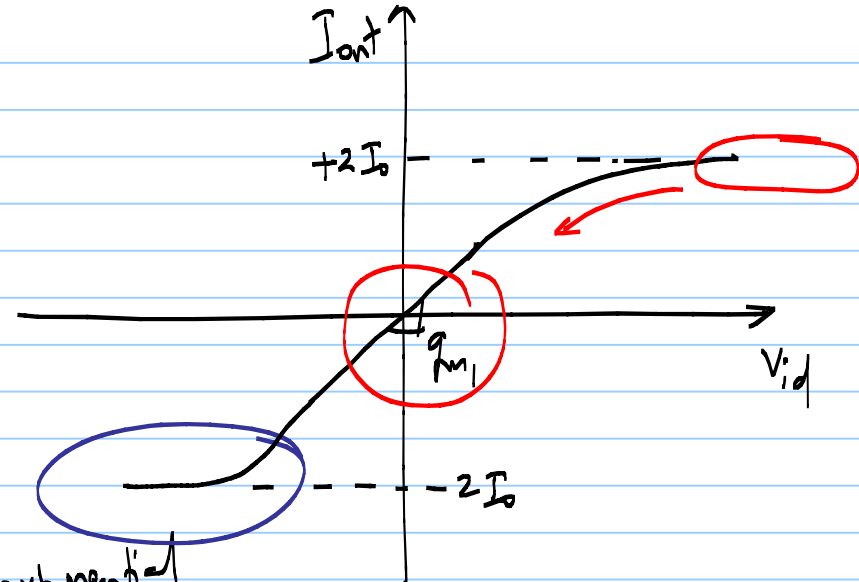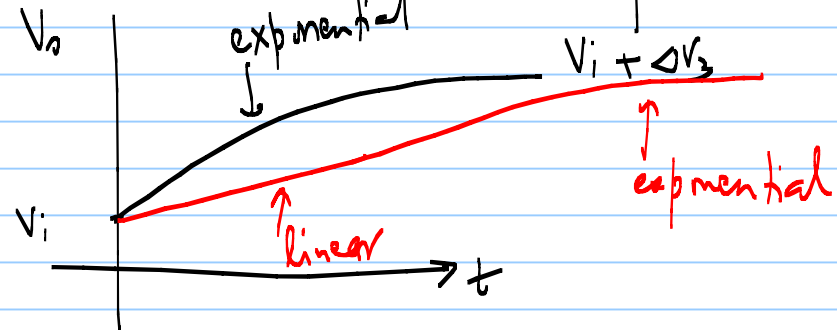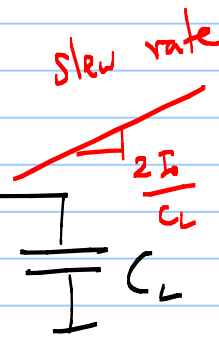
$\Delta V_4 > \Delta V_3$
 $\Delta V_5 > \Delta V_4$







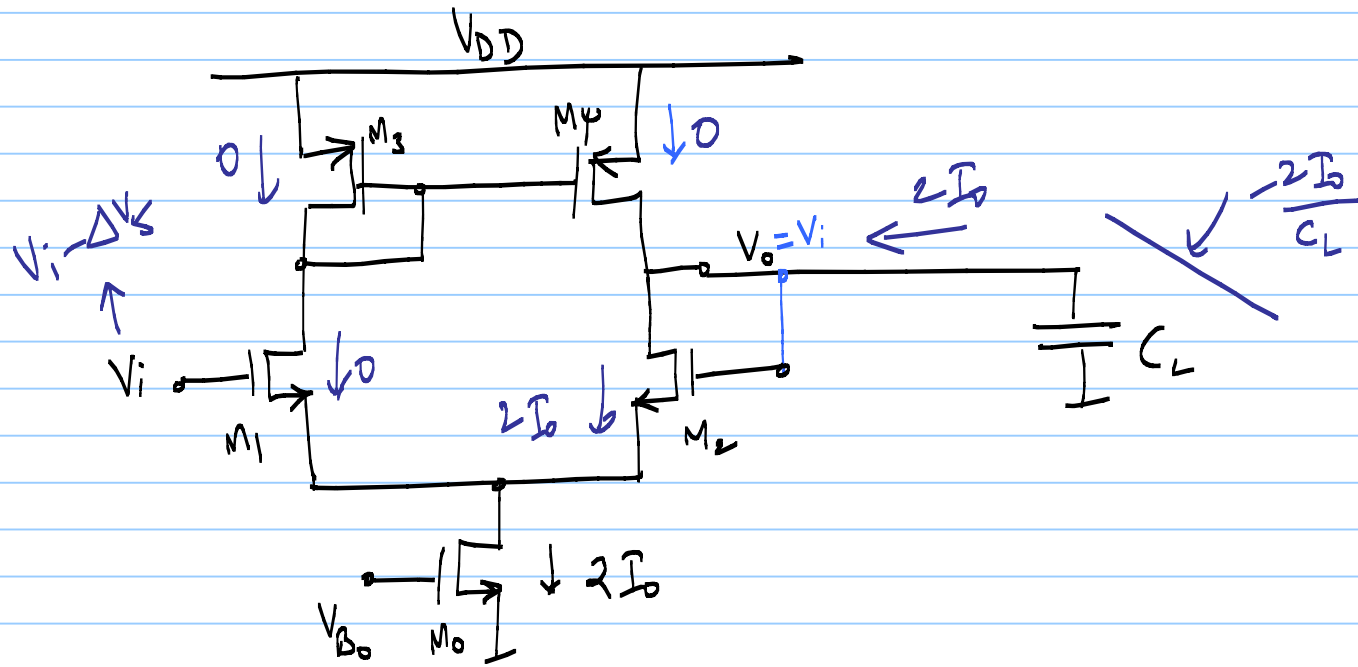

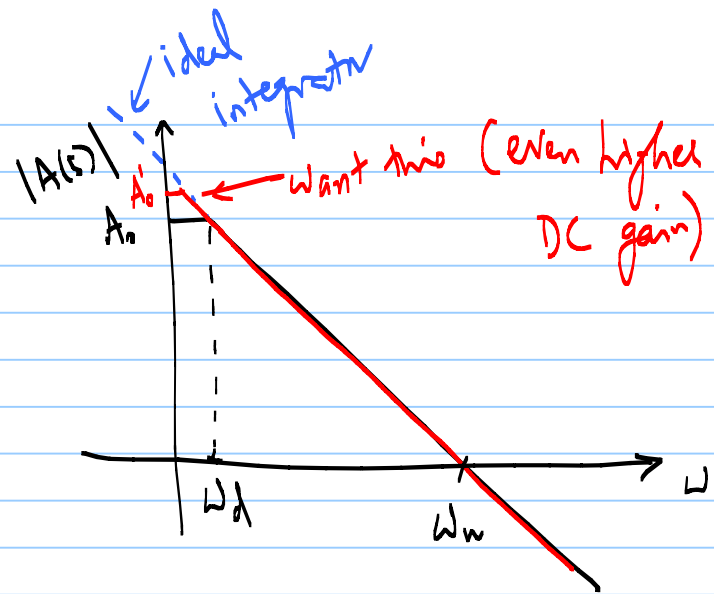


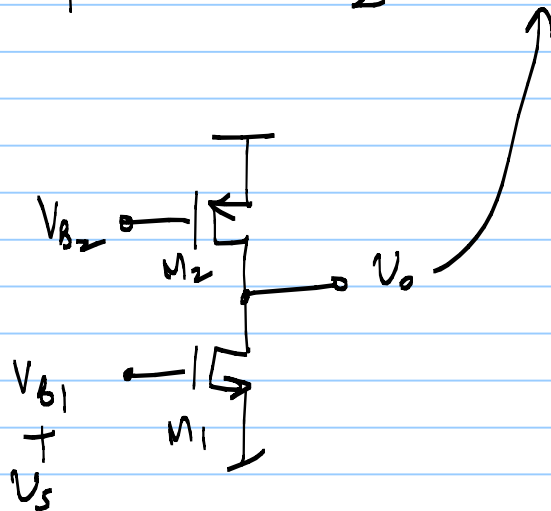DC gain of one-stage opamp = $g_{m1} (r_{ds2} \parallel r_{ds4})$
 $\approx \frac{1}{2} (g_{m1} r_{ds})$



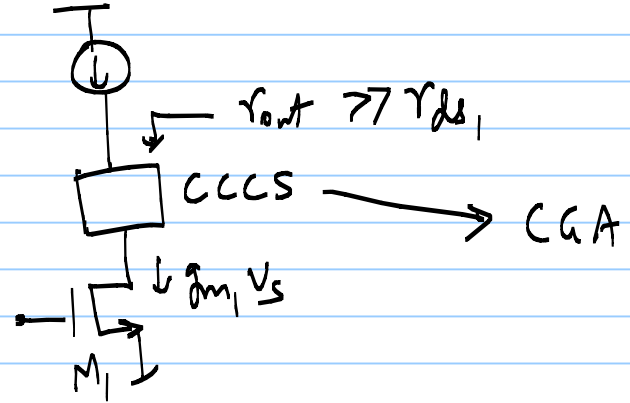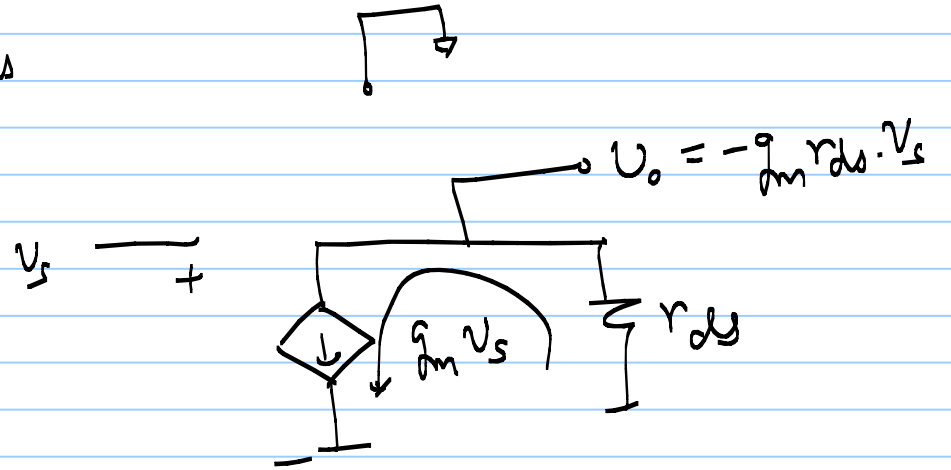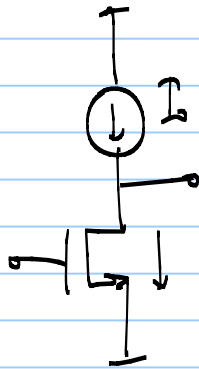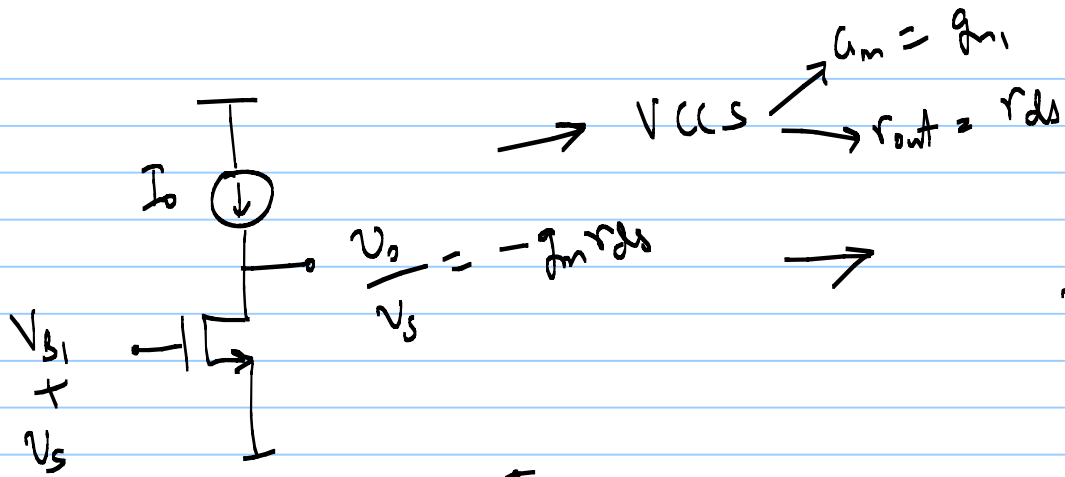

Cascode Amplifier

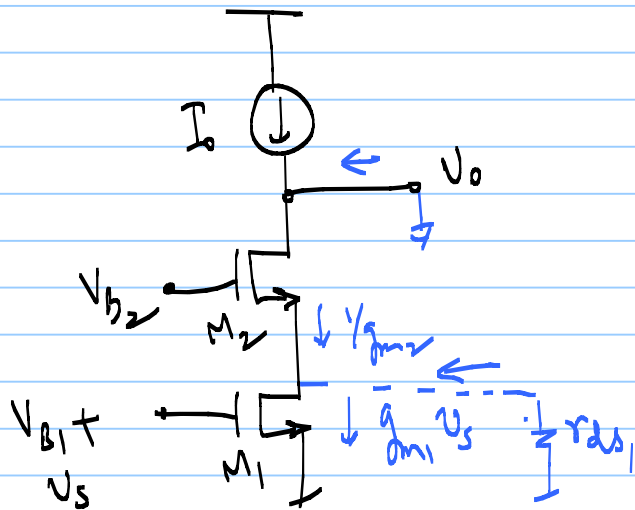

≡

better VCLS



$$G_m = -g_{m1}$$

$$r_{out} \approx (g_{m2} r_{ds2}) \cdot r_{ds1}$$


$$\text{voltage gain} = G_m \cdot r_{out}$$


$$= -g_{m1} g_{m2} r_{ds1} r_{ds2}$$

same gain as 2-stage amplifier

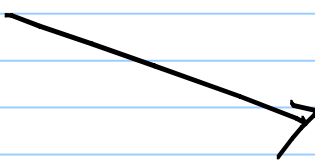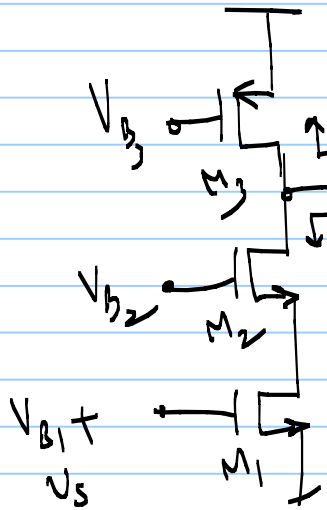


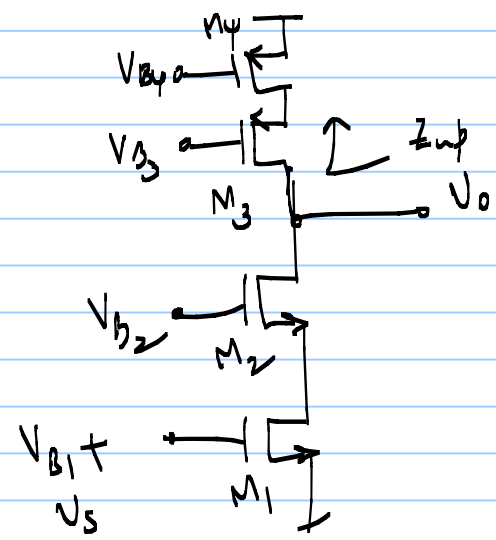
$$\frac{v_o}{v_s} = -g_{m1} \left[\underbrace{(g_{m2} r_{d2}) r_{d1}}_{(Z_{dn})} \parallel \underbrace{r_{d3}}_{(Z_{up})} \right] \approx -g_{m1} r_{d3}$$



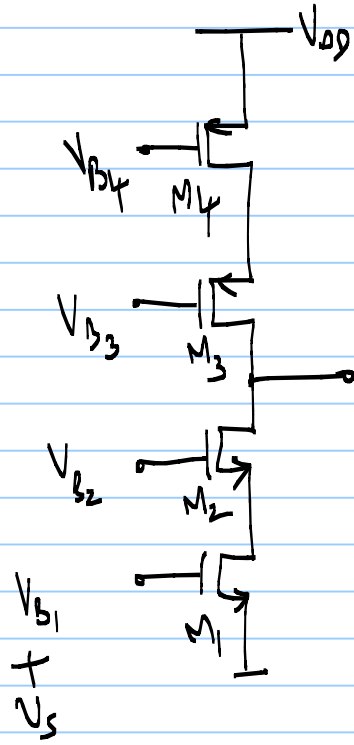


$$r_{ds} \parallel \frac{V_{gs}}{I_D} = -g_{m1} \left[(g_{m3} r_{ds3}) r_{ds4} \parallel (g_{m2} r_{ds2}) \cdot r_{ds1} \right]$$

$$\approx \frac{1}{2} (g_m r_{ds})^2$$

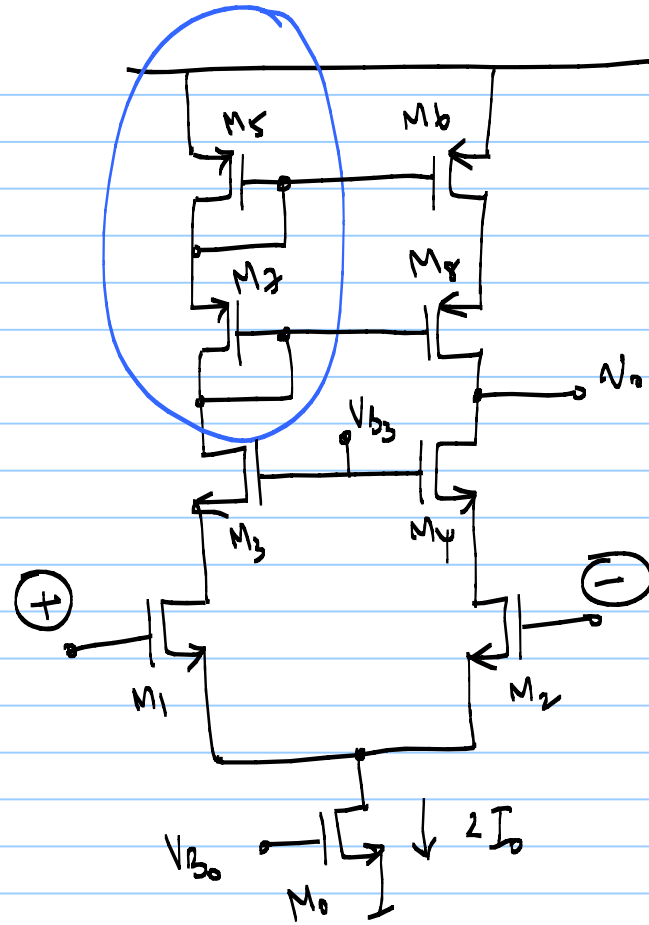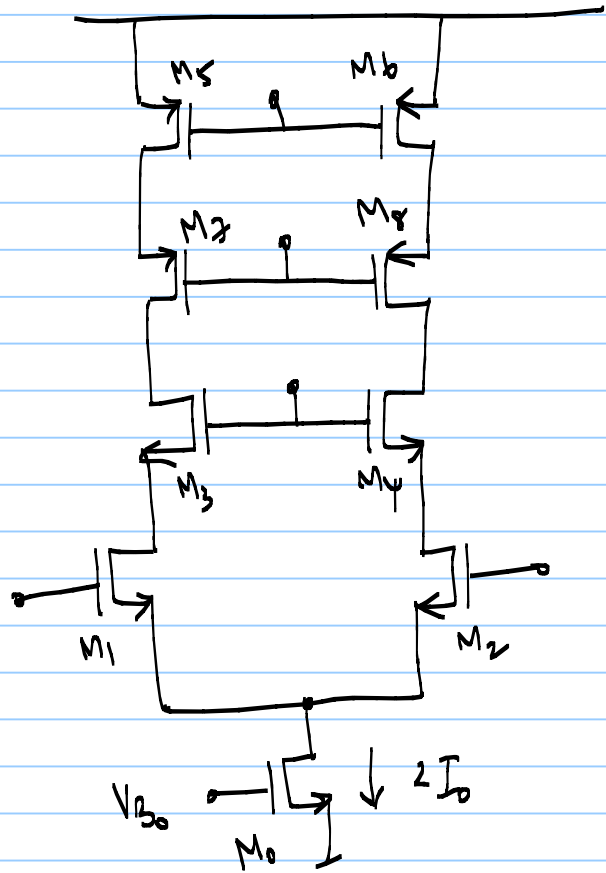


"Telescopic"
Opamp



Also a
"one-stage"
Opamp
(technically)

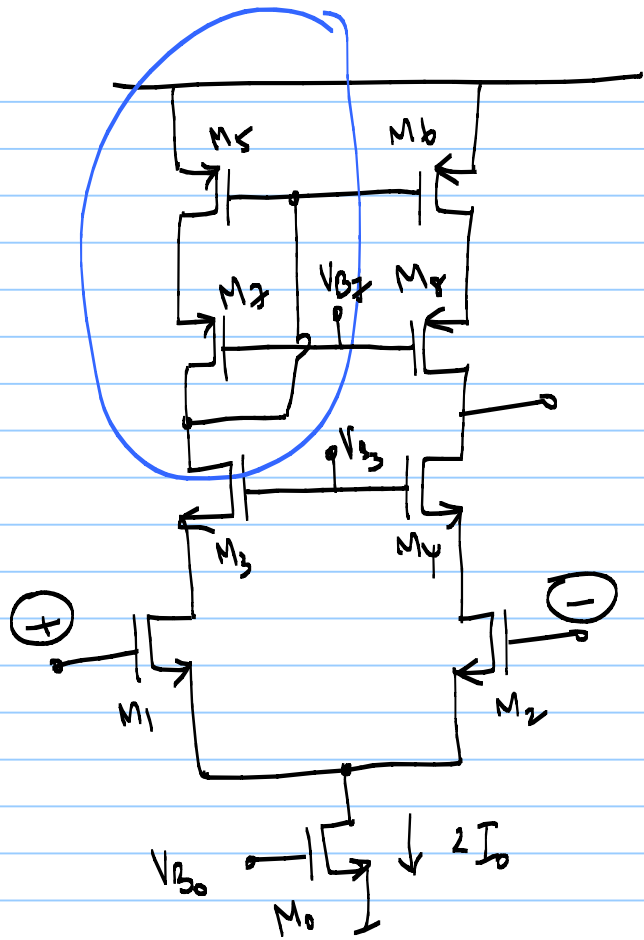

Telescopic opamp

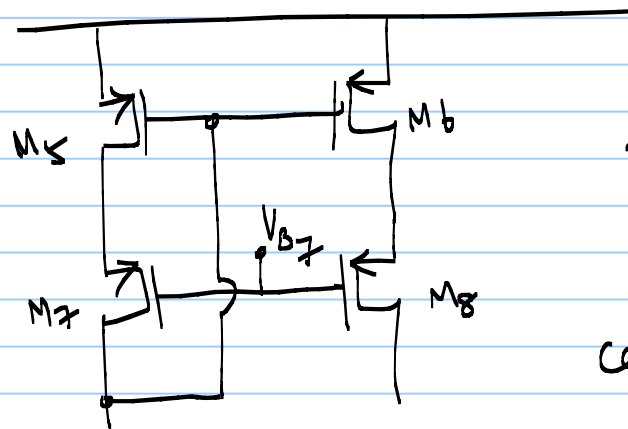

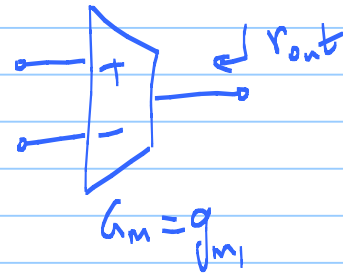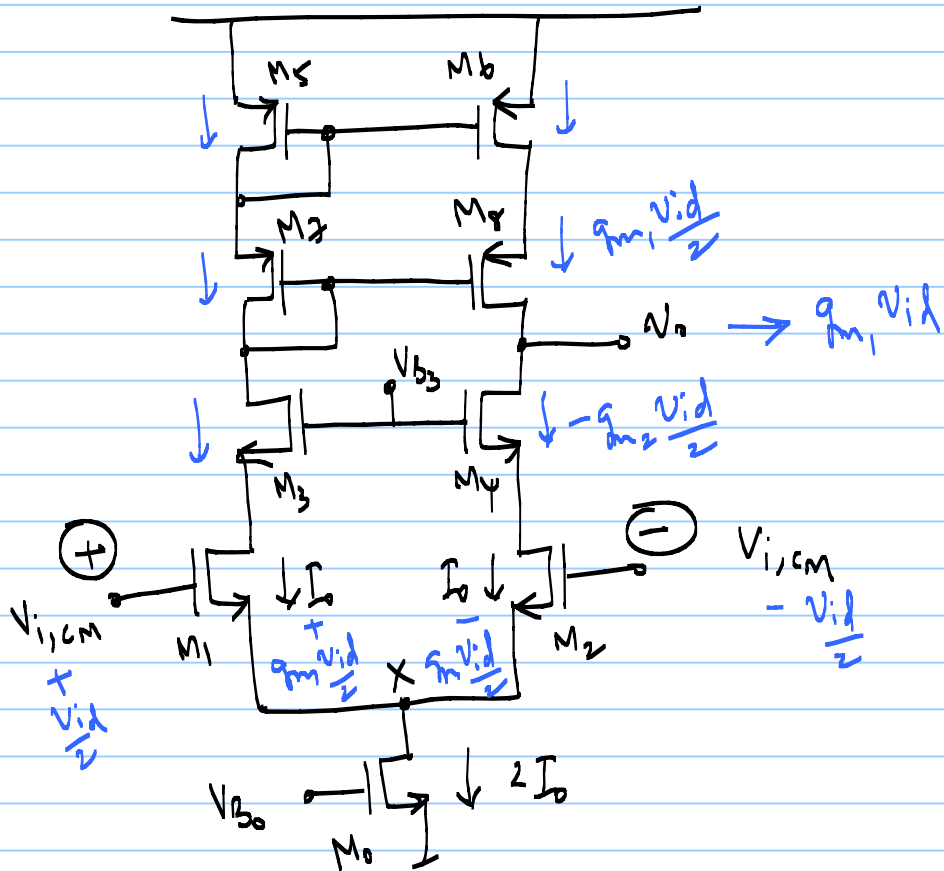High-Swing or
low-voltage
cascode current
mirror





$$r_{out} = \left[(g_{m4} r_{ds4}) r_{ds2} \parallel (g_{m3} r_{ds3}) r_{ds1} \right]$$

$$A'_o = G_m \cdot r_{out} \Rightarrow A_o \text{ for 5-T}$$

one-stage of amp

One-stage ramp?

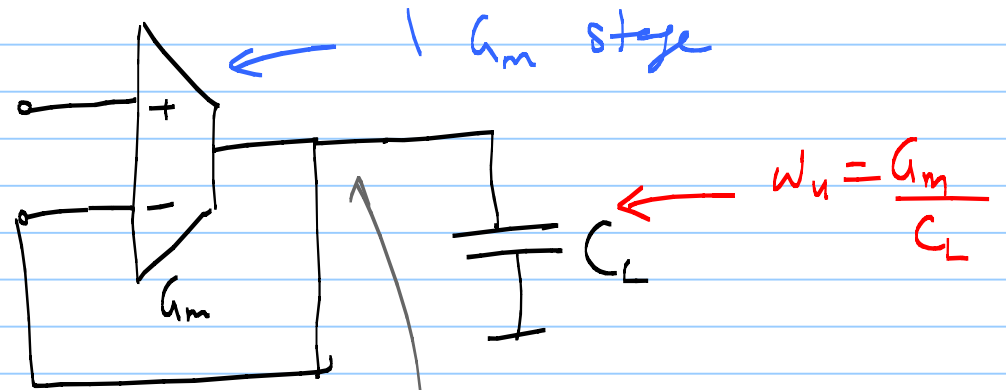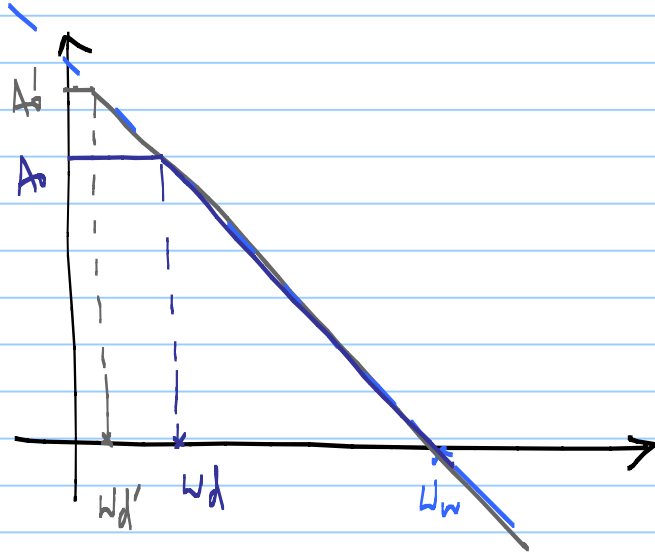

$\omega_{d'}$ @ output node

$\omega_{d'} = \frac{1}{r_{out} C_L}$ has decreased

increased


Telescopic Opamp Data sheet

1) DC gain = $g_{m1} r_{out}$

$$r_{out} = \left[(g_{m4} r_{d14}) \cdot r_{d12} \parallel (g_{m3} r_{d13}) \cdot r_{d11} \right]$$

2) $G_m = g_{m1}$

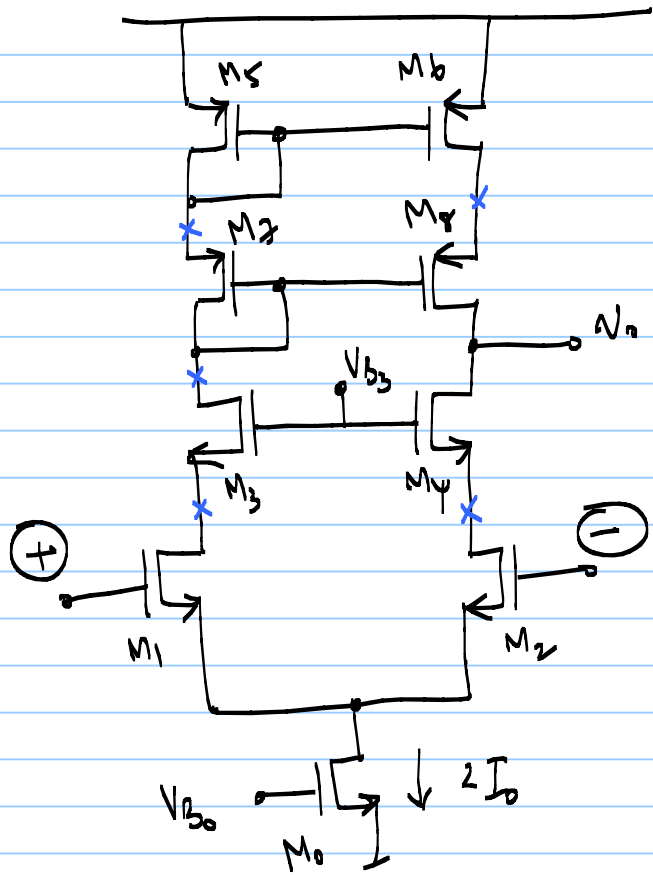3) $\omega_u = \frac{G_m}{C_L} = \frac{g_{m1}}{C_L} \iff \omega_d = \frac{1}{R_o C_L} = \frac{G_o}{C_L} \quad (\text{LHP})$
(UGF) (dominant pole) \parallel r_{out}




guess: 5 ND poles

how many zeroes?

19/10/2023


Lec 14

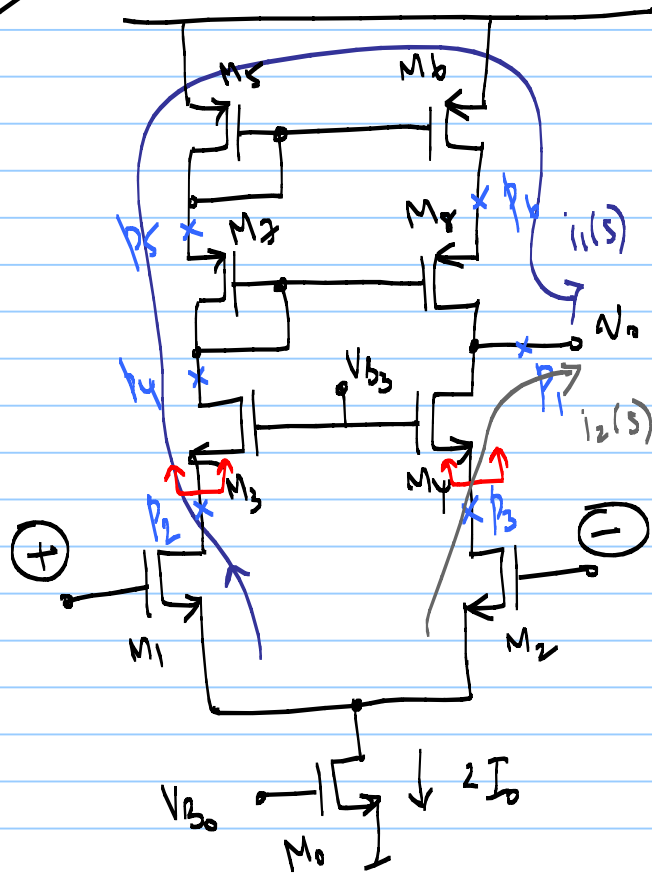

$$\frac{V_o(s)}{V_i(s)} = \frac{N(s)}{D(s)}$$

Is $p_2 = p_3$?


$p_2 \neq p_3$ most likely

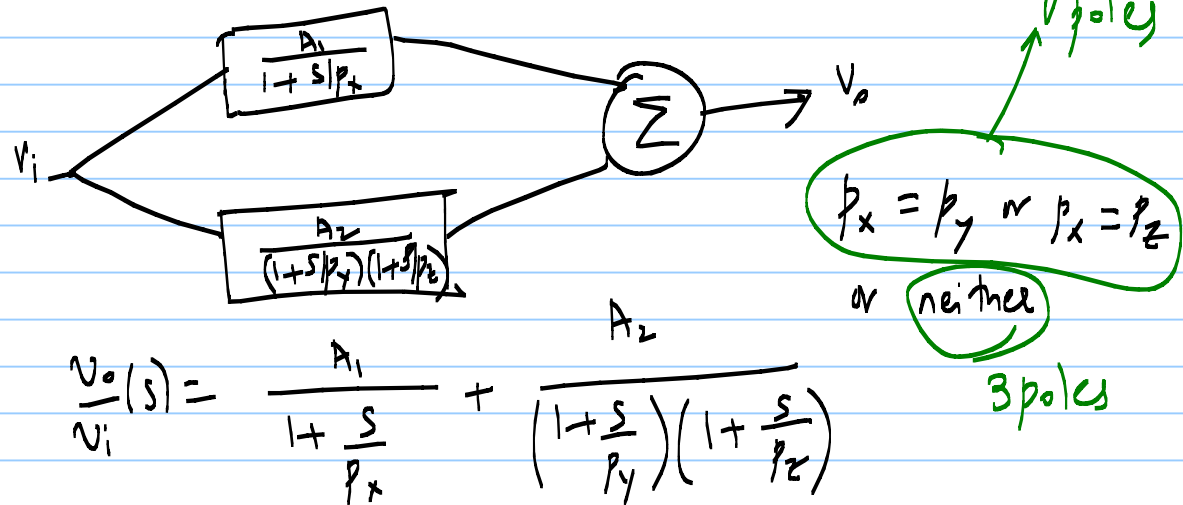

$$\frac{V_o(s)}{V_i(s)} = \frac{A_1}{1 + \frac{s}{p_1}} + \frac{A_2}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)}$$

$p_x = p_y$ or $p_x = p_z$
or neither

3 poles

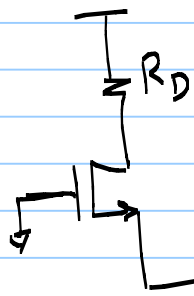


$$Z_{in} = f(g_m, r_{ds}, R_D)$$

HW

$$Z_{in} \approx \frac{1}{g_m} \text{ if } R_D \ll r_{ds}$$




$$V_{out}(s) = i_{out}(s) \cdot Z_{out}(s)$$
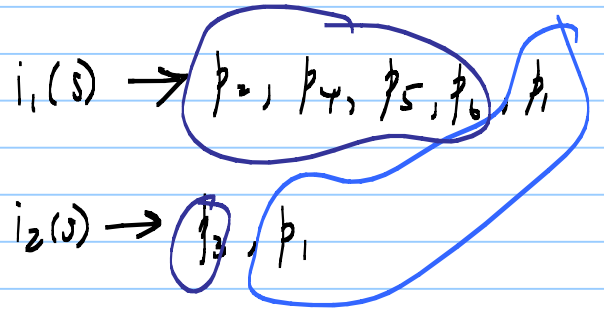
$$= \underbrace{[i_1(s) + i_2(s)]}_{i_{out}(s)} \cdot Z_{out}(s)$$



$$\frac{V_o(s)}{V_{id}} = \frac{N(s)}{D(s)} \quad \text{--- 4 zeroes}$$

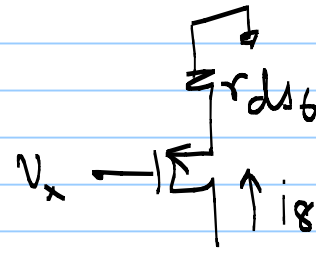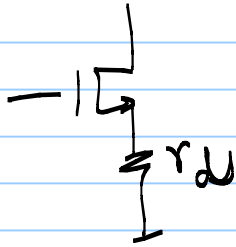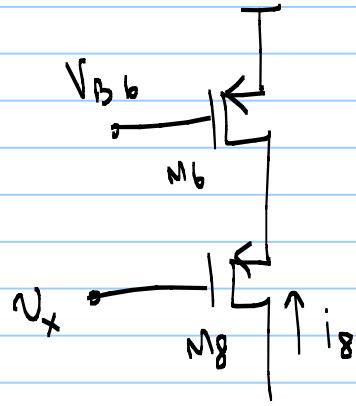6 poles
 p_1 - Dominant pole
 $p_2 - p_6$ - 5 ND poles



$$\frac{i_8}{V_x} = \frac{g_m}{1 + g_m r_{ds6}} \approx \frac{1}{\frac{1}{g_m} + r_{ds6}}$$

— very small

4) ND poles & zeroes


5 ND poles


4 ND zeroes

$$5) \text{ICMR} = \left(V_{GS1} \Big|_{I_0} + V_{DSat2} \Big|_{2I_0} \right)$$

$$\left. V_{T1} + V_{B3} - V_{GS3} \Big|_{I_0} \right\}$$

$$6) \text{DCMR} = \left\{ V_{B3} - V_{T4}, V_{DD} - V_{GS5} \Big|_{I_0} - V_{GS7} \Big|_{I_0} + V_{T8} \right\}$$

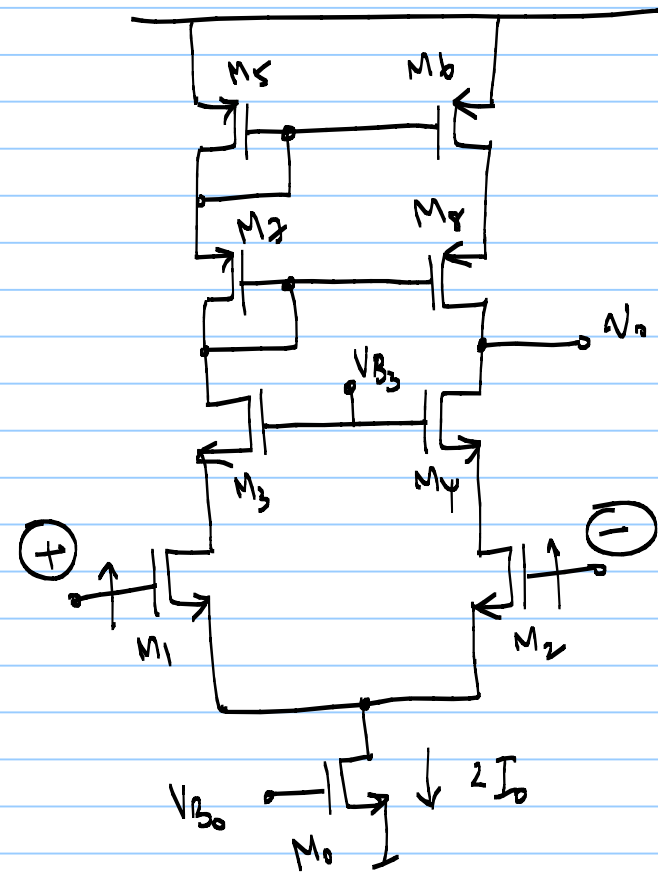

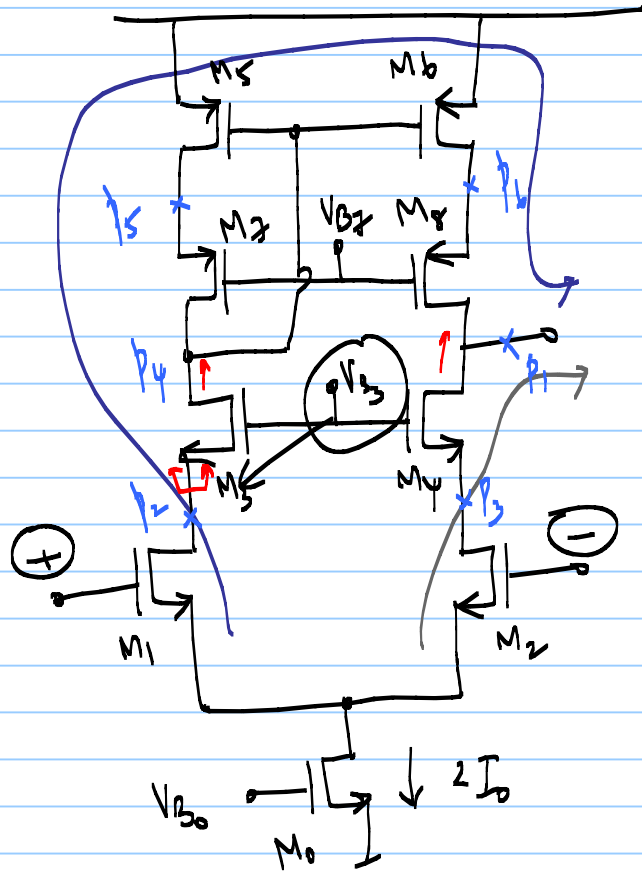


High Swing Telescopic opamp

- 1) DC gain = same
- 2) $G_m = \text{same}$
- 3) $\omega_n = \text{same}$, $\omega_d = \text{same}$
- 4) ND poles = 5 LHP poles
ND zeros = 4
- 5) ICMR = same
- 6) OCMR = $\{V_{B3} - V_{T4}, V_{B7} + V_{T8}\}$

$$V_{B7} > V_{DD} - V_{S_{h5}} - V_{S_{h7}}$$

(H.S.) (L.S.)

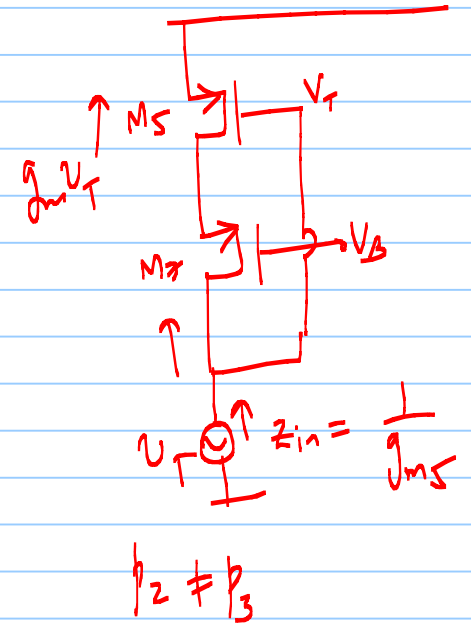


7) Noise $\frac{\overline{e_n^2}}{\Delta f} = \frac{16kT}{3g_{m1}} + \frac{16kT}{3g_{m1}^2} \cdot g_{m5}$

same as 1-stage opamp


* No noise from cascode devices M_3, M_4, M_7, M_8 @ low frequencies

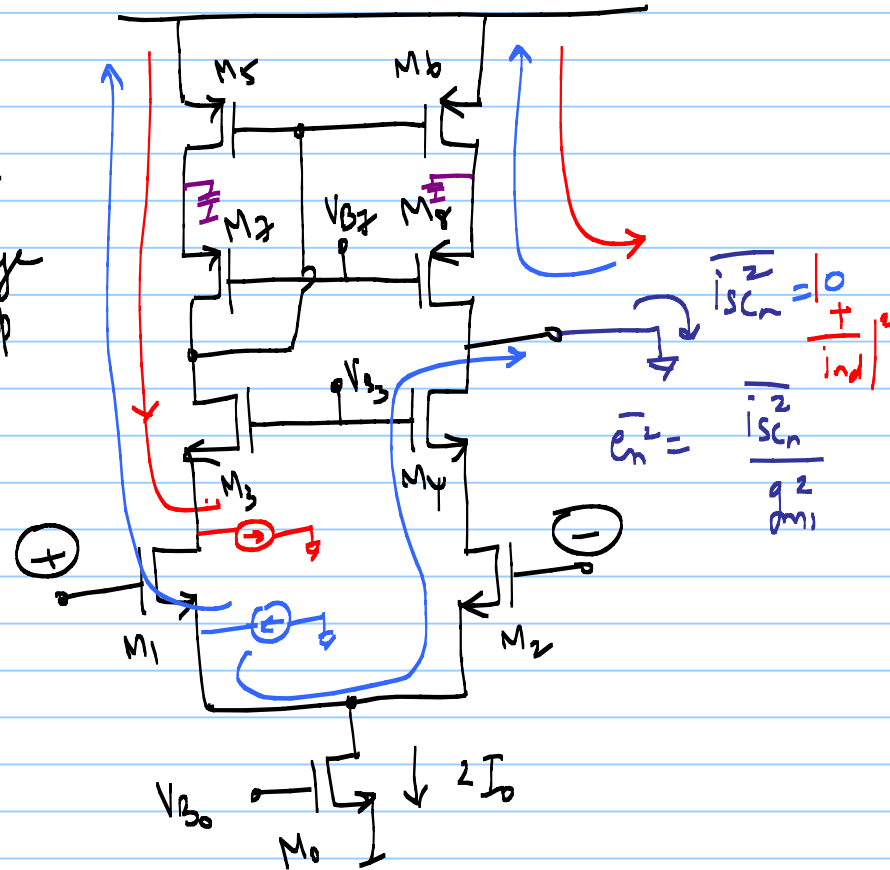* Noise of Telescopic opamp is worse than one-stage opamp @ high frequencies



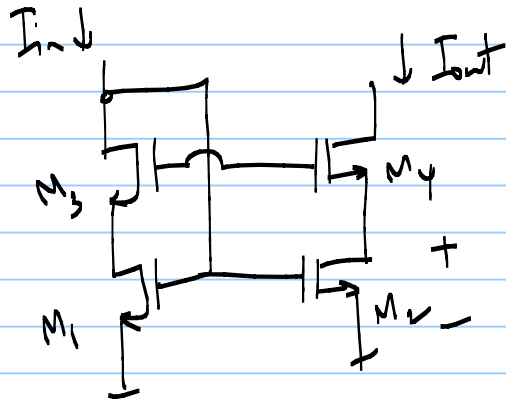8) Mismatch:
$$r_{os}^2 = r_{V_{T1,2}}^2 + \left(\frac{g_{m5}}{g_{m1}} \right)^2 r_{V_{T5-6}}^2$$


$M_{3,4}$ & M_{7-8} V_T - mismatches will not contribute to r_{os}^2




$$V_{T3} = V_T, \quad V_{T4} = V_T + \Delta V_T$$



$$\Delta I_{out} = ?$$

$$V_{T1} = V_{T2} = V_T$$

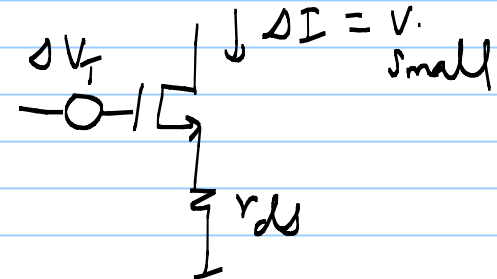

9) Slew Rate = $\pm \frac{2I_0}{C_L}$

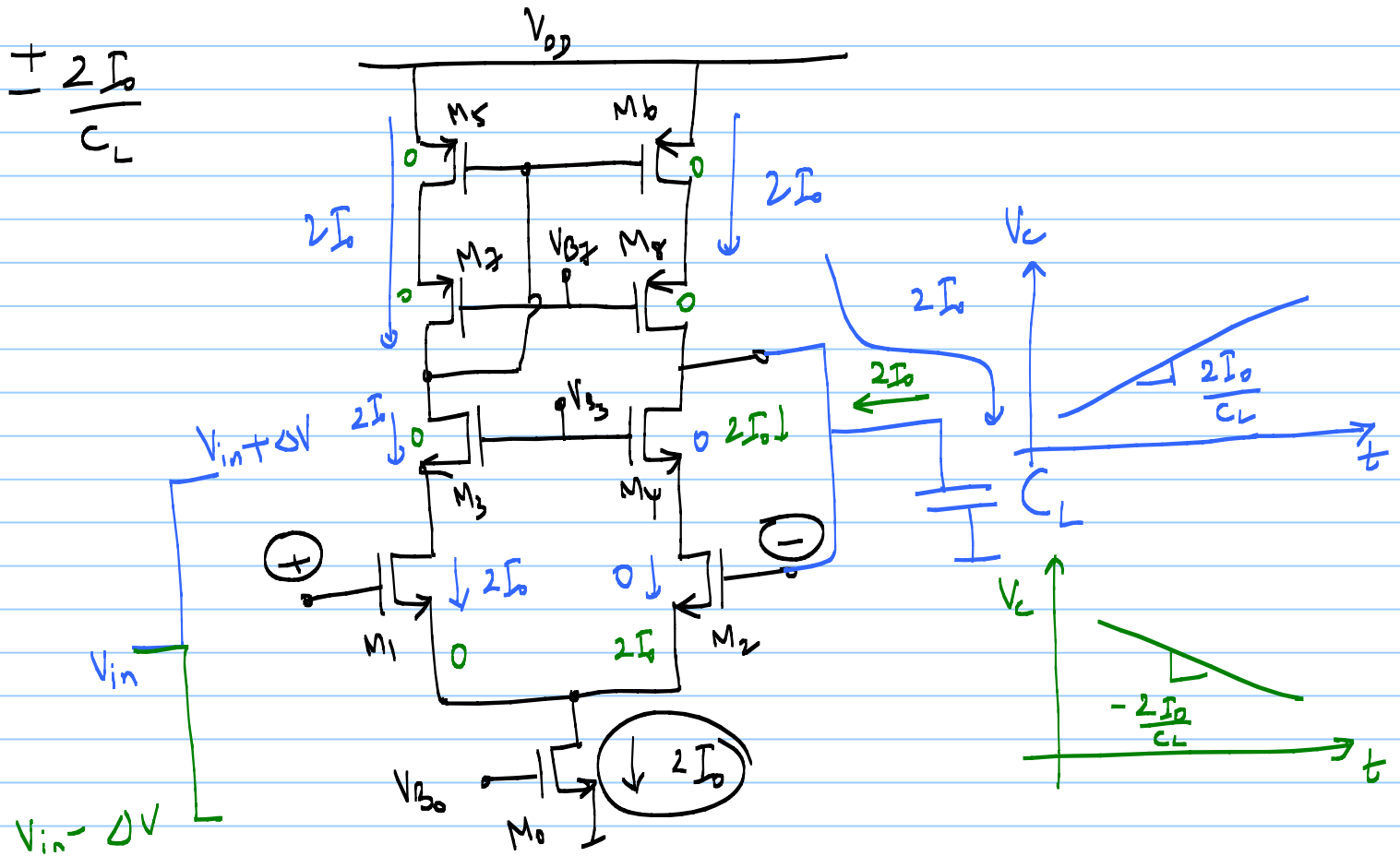

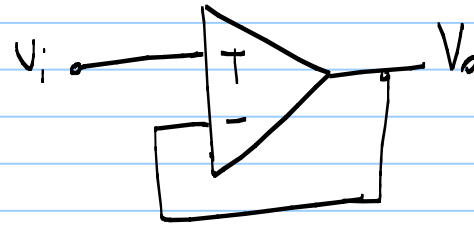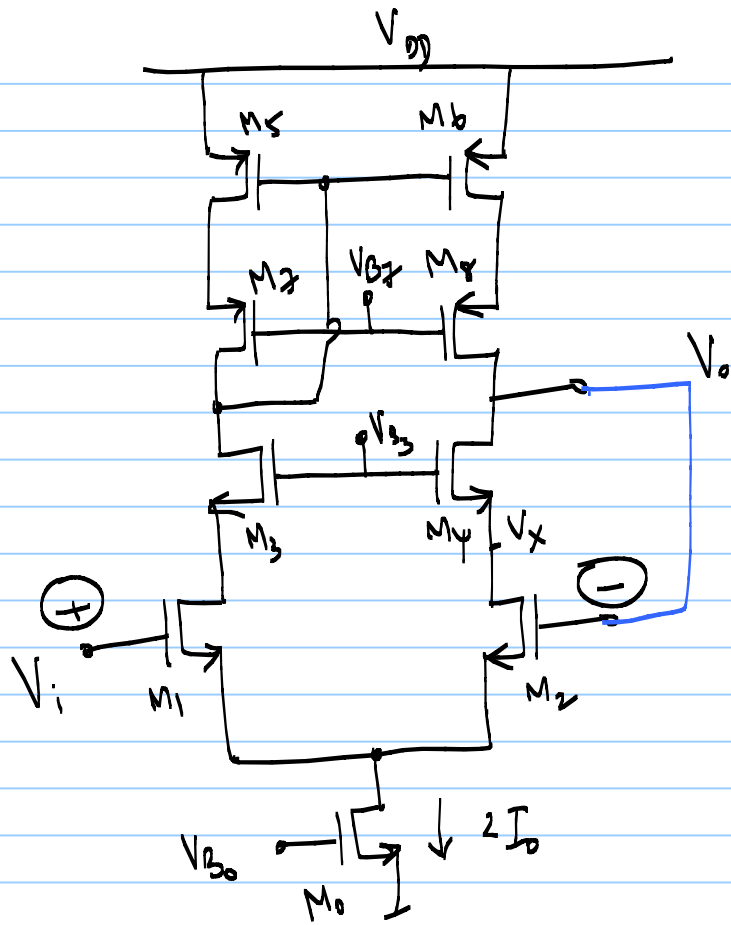

$$V_{o\min} = \text{larger of } \rightarrow \left\{ V_{DS2} + V_{osato} \right\}$$

and

$$\left\{ V_{B3} - V_{T4} \right\} \checkmark$$

$$V_{o\max} = \text{smaller of } \rightarrow \left\{ V_{B3} - V_{DS4} + V_{T2} \right\} \checkmark$$

and

$$\left\{ V_{B7} + V_{T8} \right\}$$

$$V_{o, \min} = V_{B3} - V_{T4}$$




$$V_{o, \max} = V_{B3} - V_{A54} + V_{T2} = V_{B3} - V_{T4} - V_{D54} + V_{T2}$$

$$V_{o, \max} - V_{o, \min} = V_{T4} - V_{D54} \quad \text{very small!}$$

26/10/23




Lec 15

NMOS

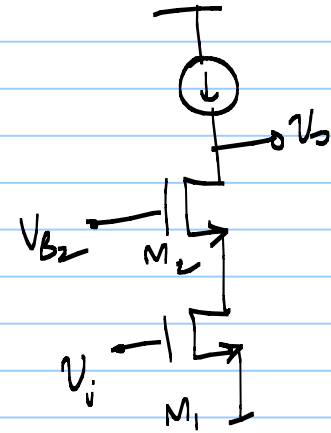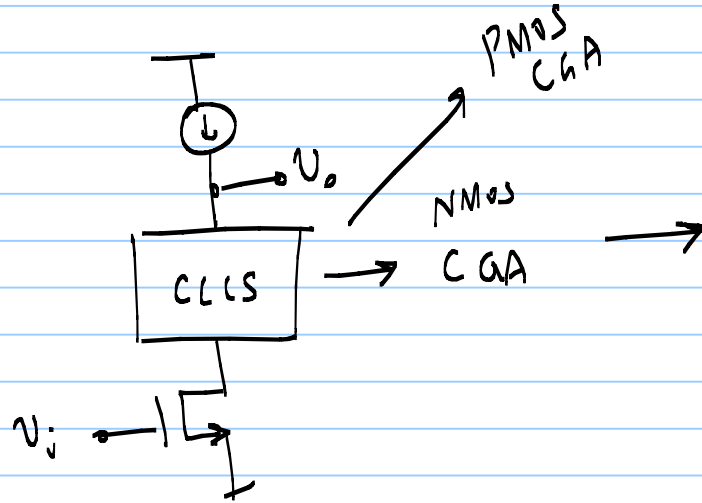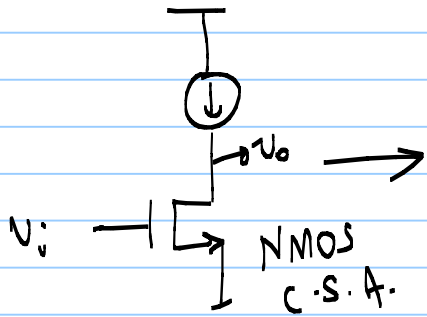



Telescopic
opamp
(NMOS)

PMOS

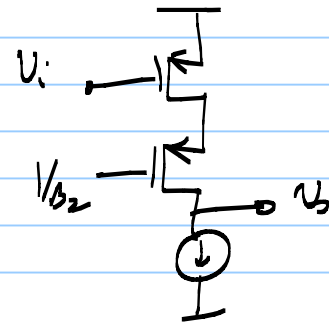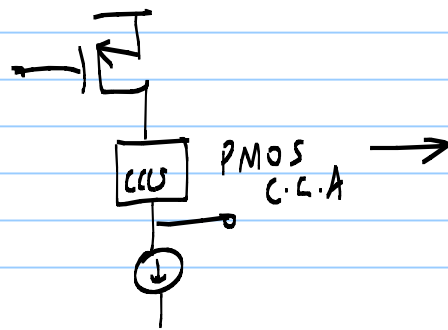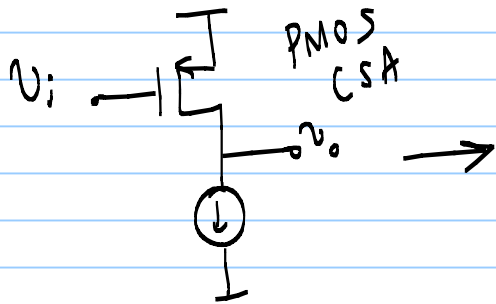


Telescopic
opamp
with PMOS
input pair

NMOS CSA + PMOS CCA ?

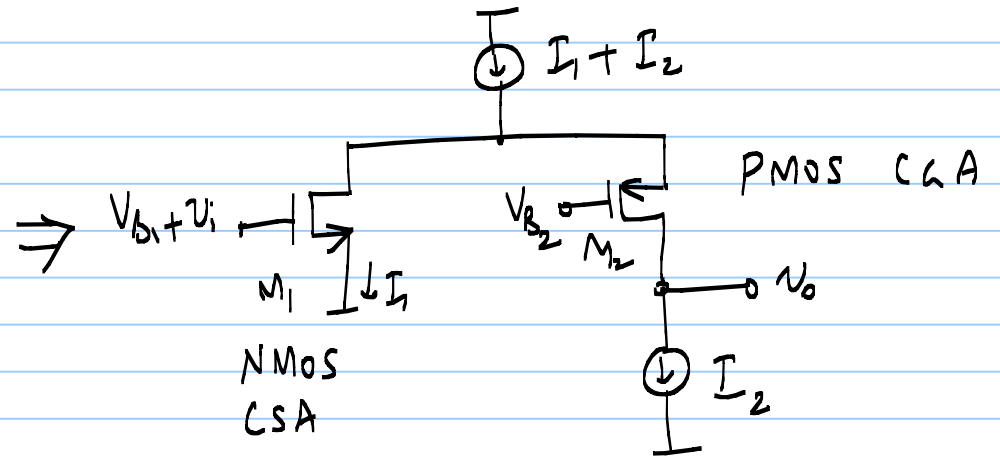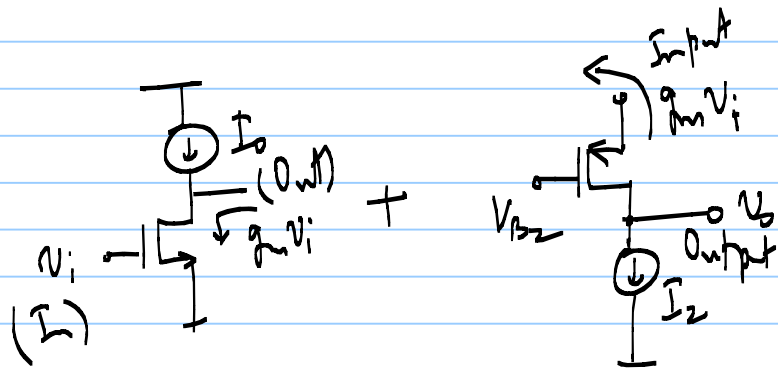

"Folded Cascode" Amplifier

"
Folded
Cascode
opamp"

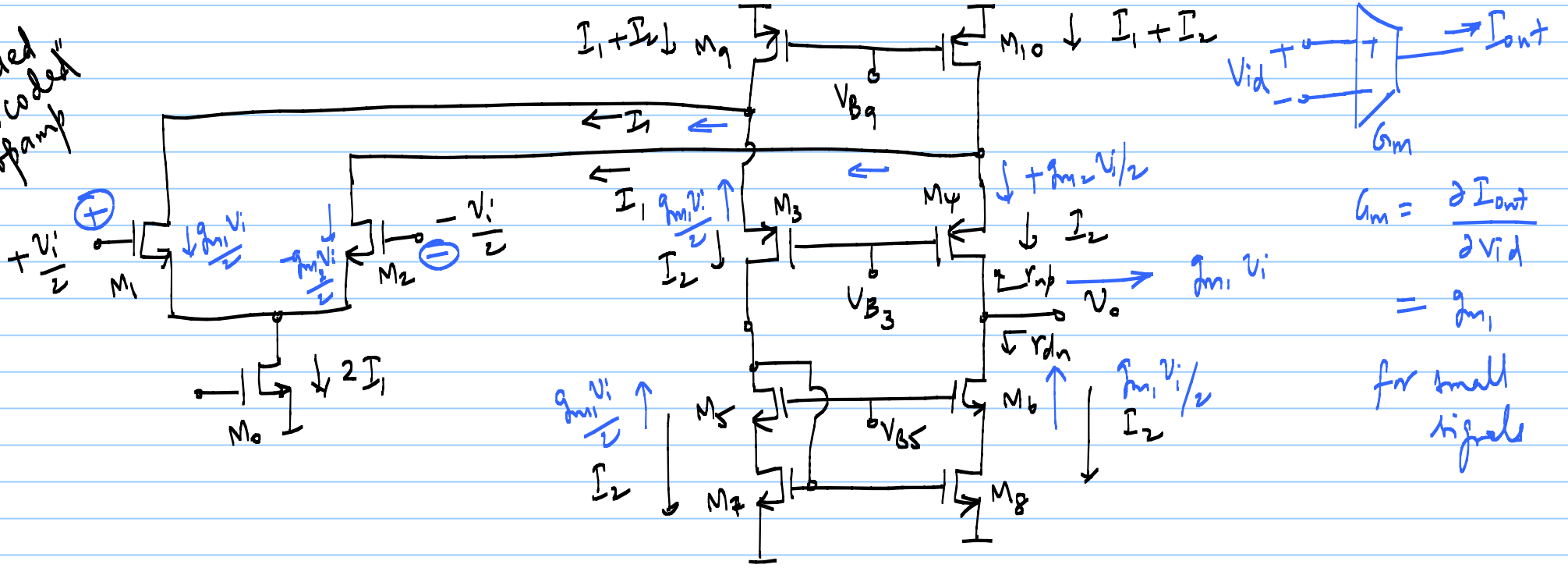

$$G_m = \frac{\partial I_{out}}{\partial v_{id}} = g_{m1}$$

for small signals

$$1) \quad \underline{\text{DC gain}} = g_{m1} r_{out} \quad r_{out} = (r_{dn} \parallel r_{up}) = \text{slightly smaller than that of Telescopic of amp}$$

$$r_{dn} = g_{m6} r_{ds6} \cdot r_{ds8}$$


$$r_{up} = g_{m4} r_{ds4} \cdot (r_{ds2} \parallel r_{ds10})$$

$$2) \quad G_m = g_{m1}$$

$$3) \quad \omega_n = \frac{G_m}{C_L} = \frac{g_{m1}}{C_L}; \quad \omega_d = \frac{g_{out}}{C_L} = \frac{1}{r_{out} C_L} = p_b$$

dominant pole

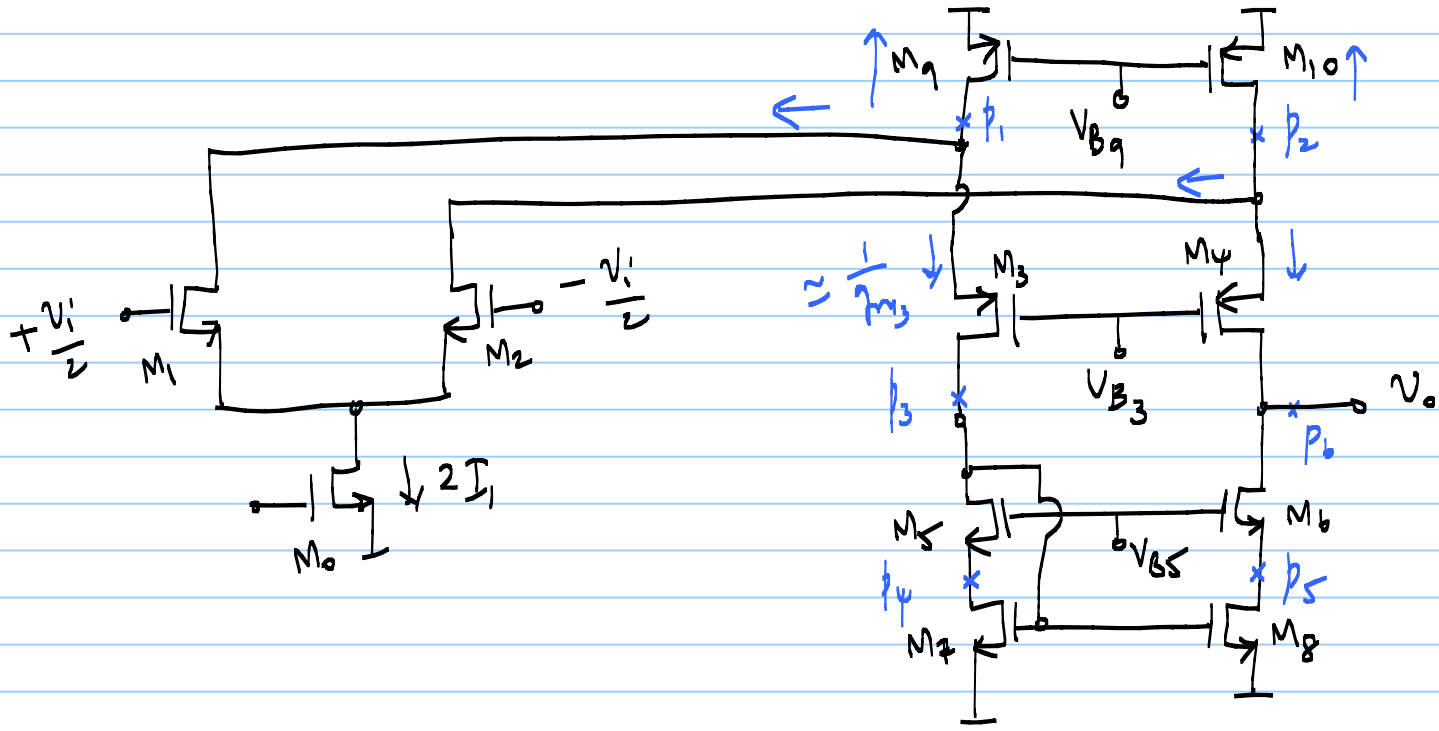4) ND poles & zeroes: 5 ND poles & 4 zeroes
 $p_1 - p_5$




$$5) \quad I_{CMR} = \left\{ V_{Dsat_0} \mid 2I_1 + V_{Ks_1} \mid I_1, \quad V_{B_3} + V_{Sg_3} \mid I_2 + V_{T_1} \right\}$$


$$6) \quad O_{CMR} = \left\{ V_{B_5} - V_{T_6}, \quad V_{B_3} + V_{T_4} \right\}$$


$$7) \quad \text{Noise } \frac{\overline{e_n^2}}{\Delta f} = \frac{1}{g_{m1}^2} \left[\overline{i_{nd_1}^2} + \overline{i_{nd_2}^2} + \overline{i_{nd_7}^2} + \overline{i_{nd_8}^2} + \overline{i_{nd_9}^2} + \overline{i_{nd_{10}}^2} \right]$$
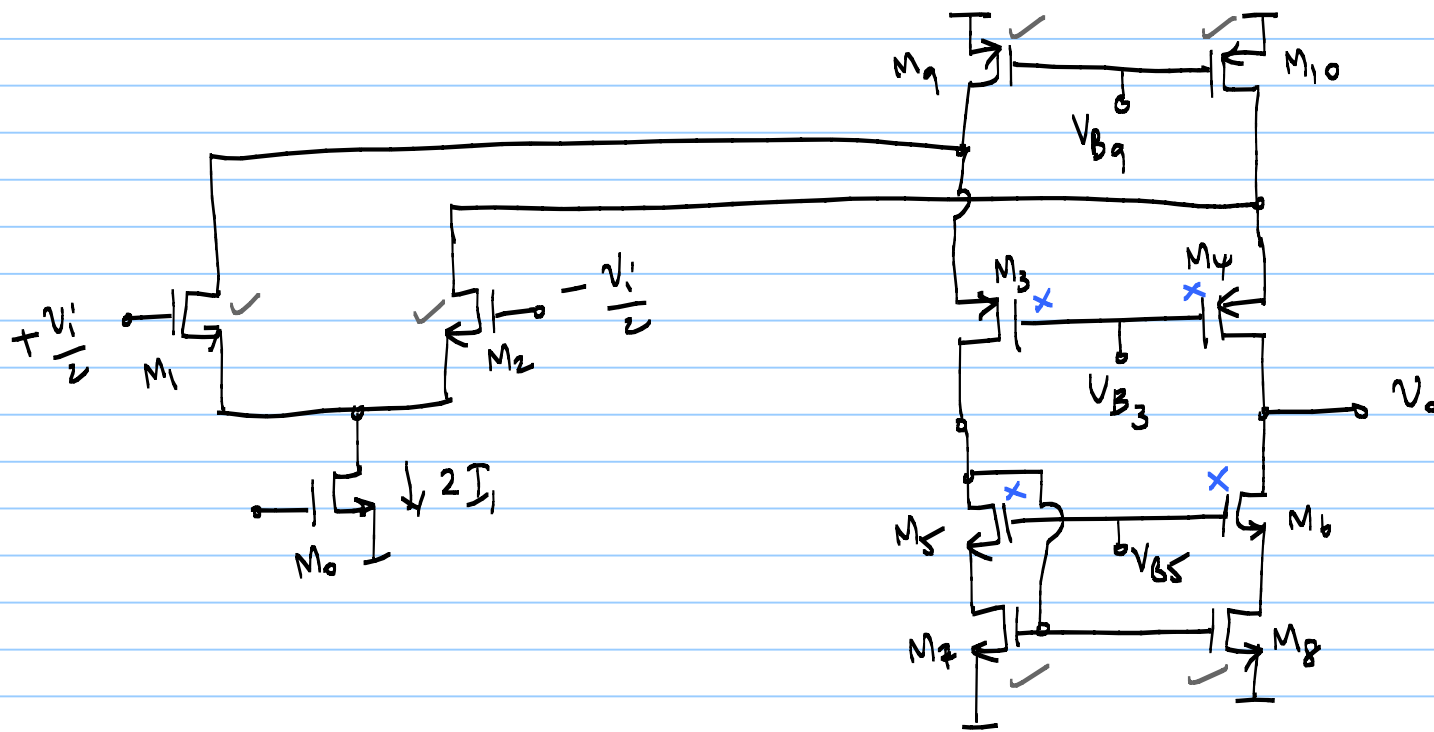
$$= \frac{16kT}{3g_{m1}} + \frac{16kT g_{m7}}{3g_{m1}^2} + \frac{16kT g_{m9}}{3g_{m1}^2} \left. \vphantom{\frac{16kT}{3g_{m1}}} \right\} \text{slightly worse than that of telescopic or one-stage opamp}$$



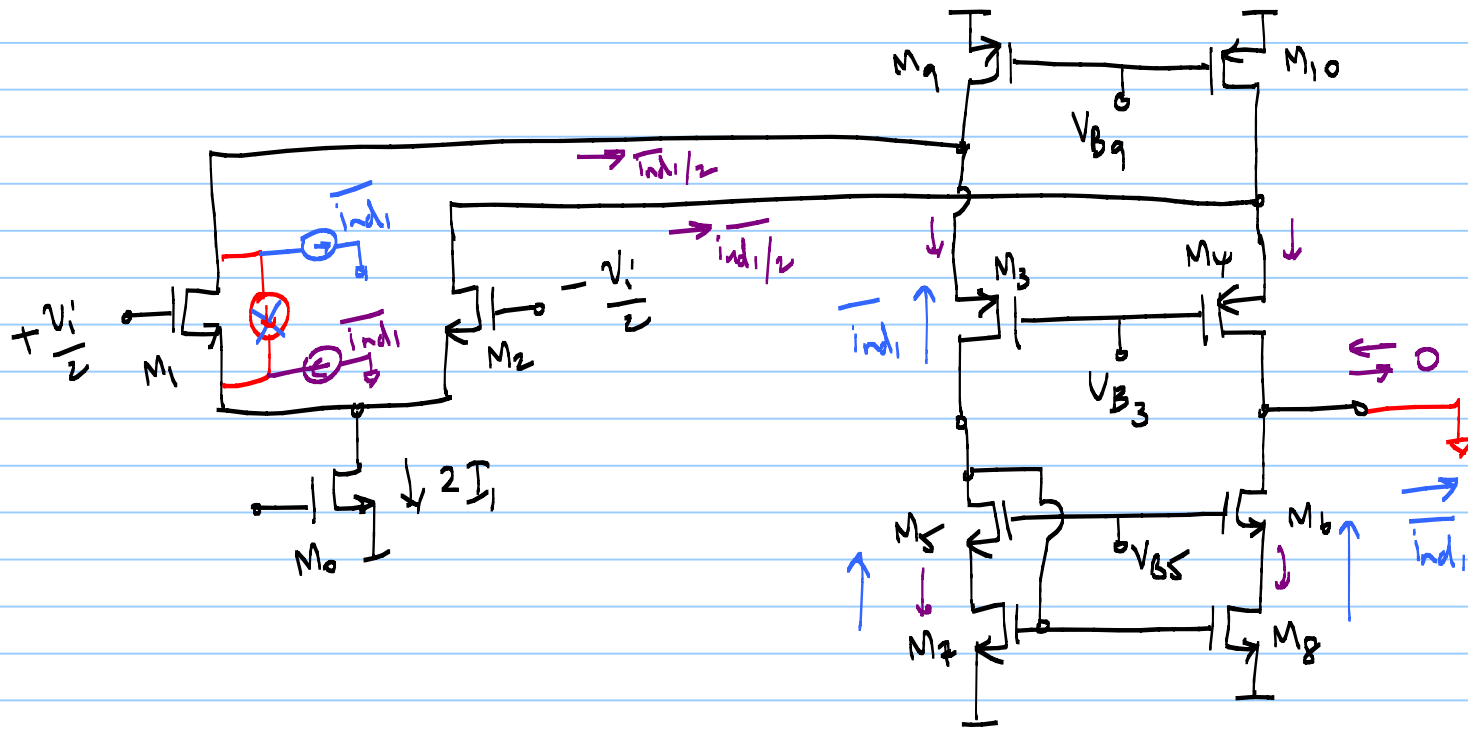x noise of cascode
 devices do not
 contribute to \bar{E}_n at
 low freq.



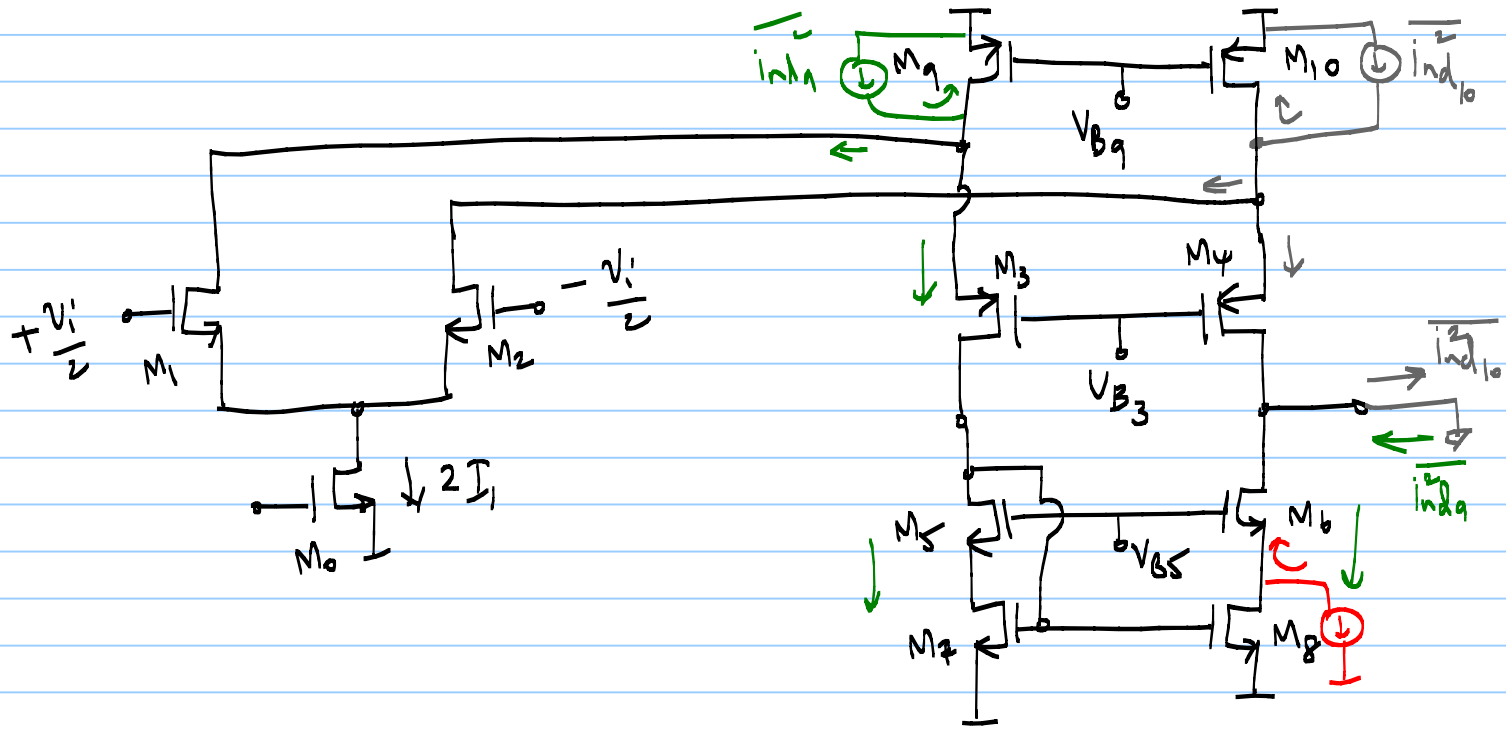


8) Mismatch
$$v_{os}^2 = v_{T_{1,2}}^2 + \left(\frac{g_{m9}}{g_{m1}}\right)^2 \cdot v_{T_{9,10}}^2 + \left(\frac{g_{m7}}{g_{m1}}\right)^2 \cdot v_{T_{7,8}}^2$$


9) Slew Rate - 2 cases

$$\frac{I_1 + I_2}{C_L} \approx \frac{2I_2}{C_L}$$

HW

- ΔV
(-ve SR)

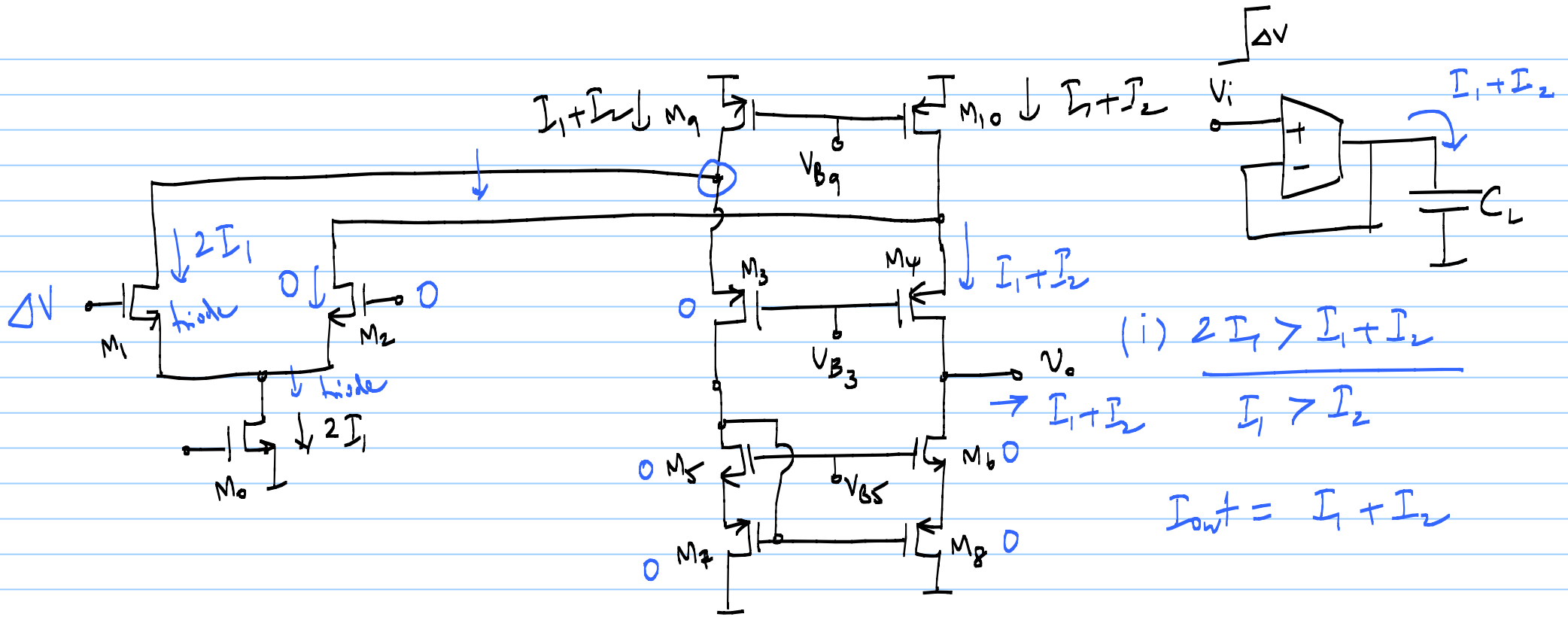

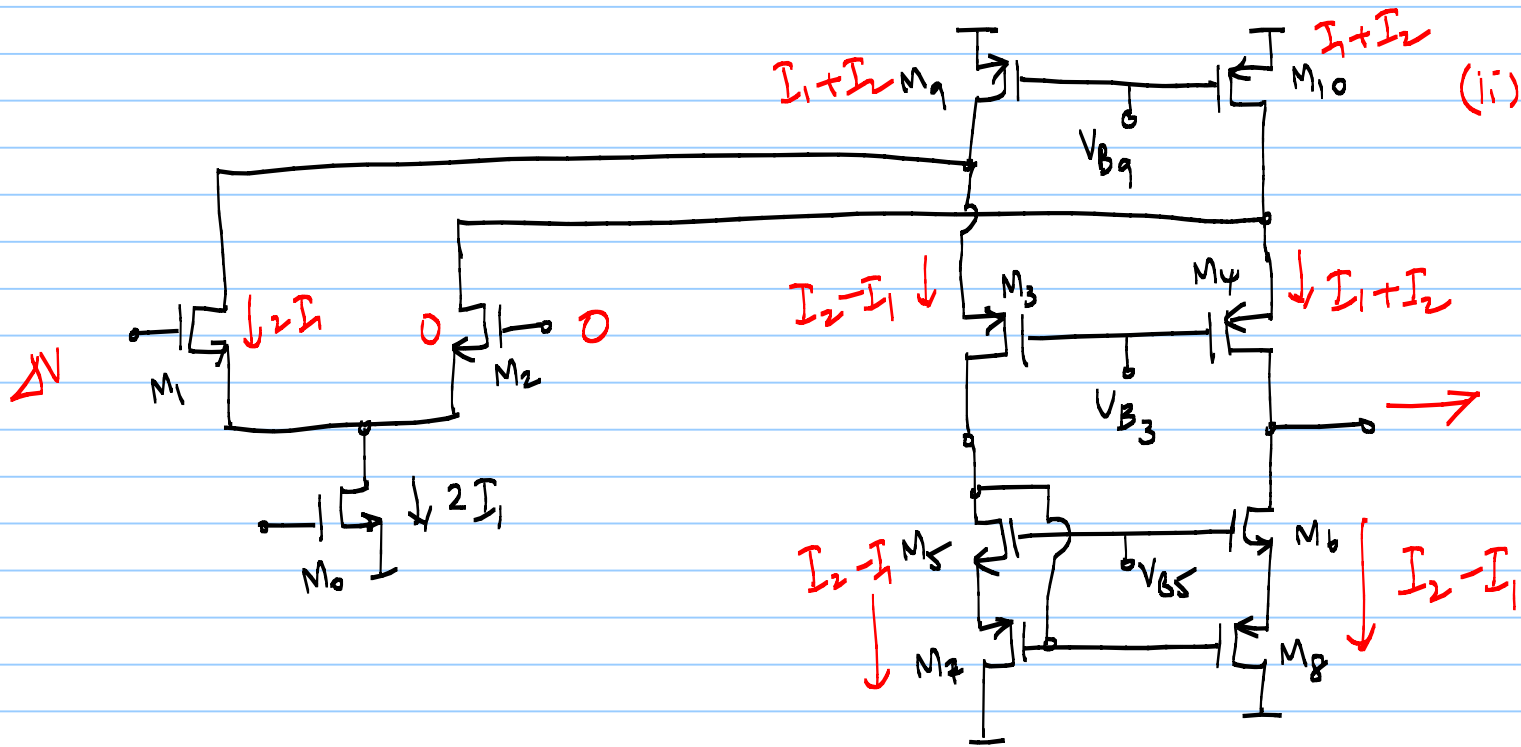


(ii) $2I_1 < I_1 + I_2$

$I_1 < I_2$

$$I_b = I_1 + I_2 - 2I_1 = I_2 - I_1$$

$$\rightarrow I_{out+} = (I_1 + I_2) - (I_2 - I_1) = 2I_1$$

HW

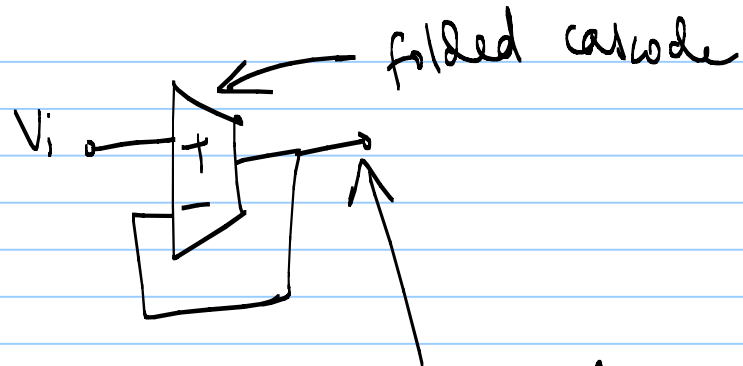

swing limits in unity gain fb.
⇒ confirm that the problem in Telescopic opamp does not exist here

HW

PMOS input pair versions of all opamps


↳ Only difference is in ICMR & OCMR

Quiz 1 → Saturday Nov 4th, 2023

9-10am


27/10/23


Lec 16

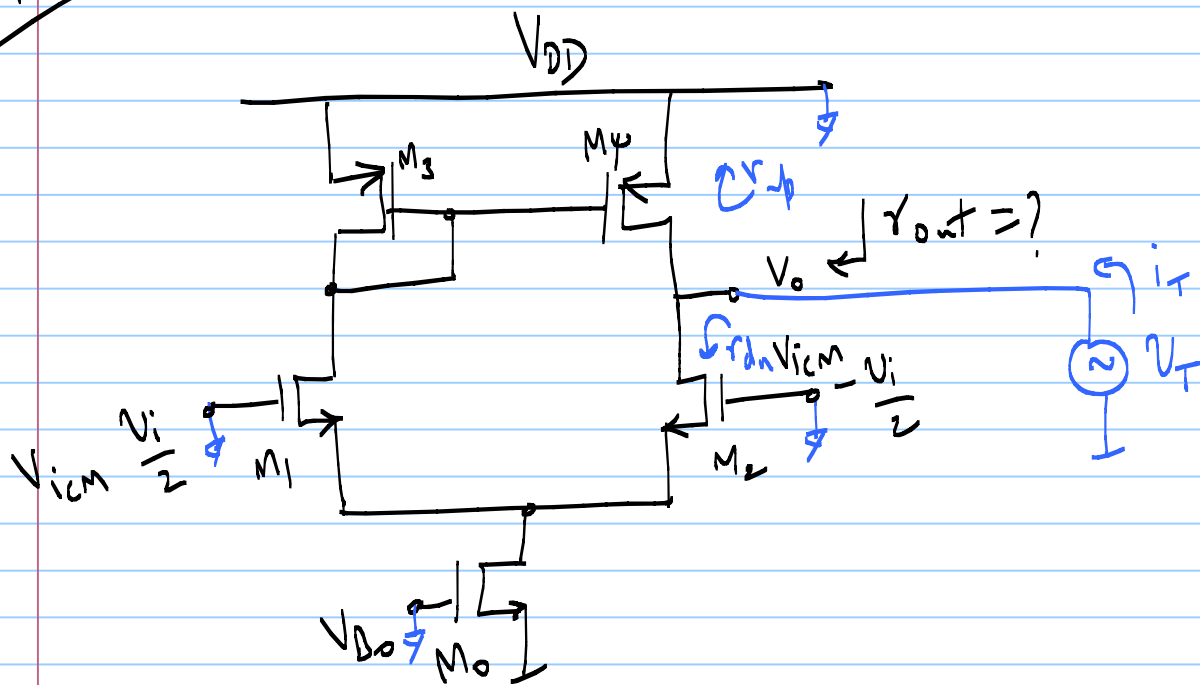

$$r_{out} = r_{up} \parallel r_{dn}$$

$$\approx r_{ds1} \parallel r_{ds2}$$

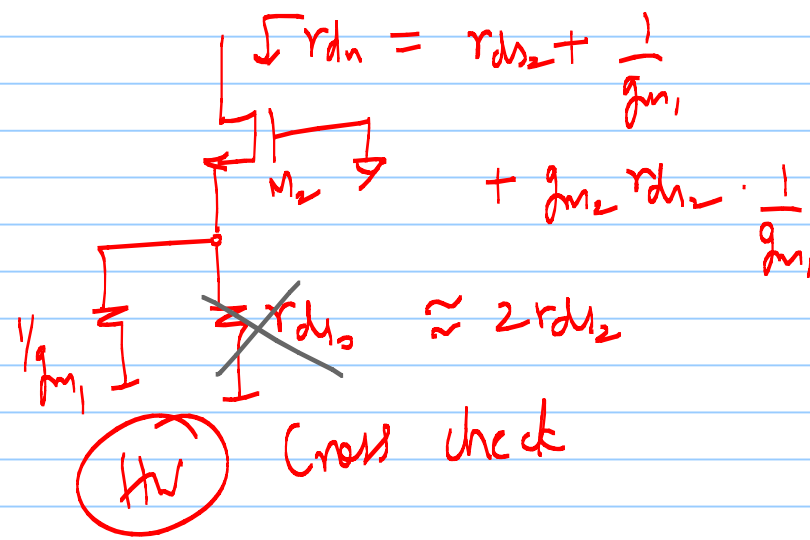

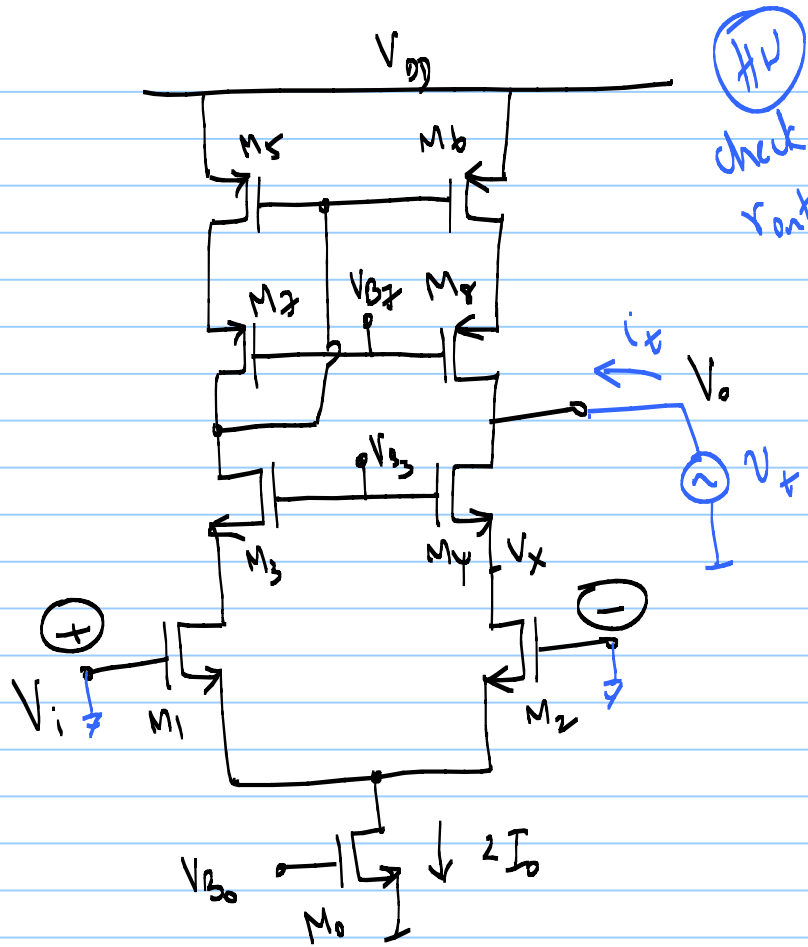

HW


check r_{out}

for telescopic & folded cascode as well.

$$r_{out} = \frac{V_o}{i_0}$$

One Stage of pump


- 5T OTA
- Telescopic
- Folded Cascode

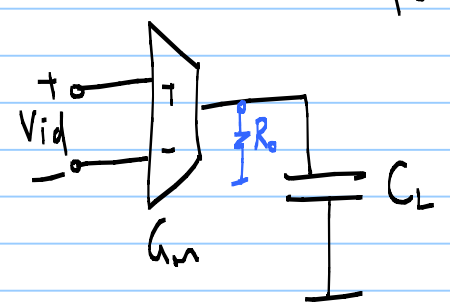

$$w_u = \frac{G_m}{C_L}$$




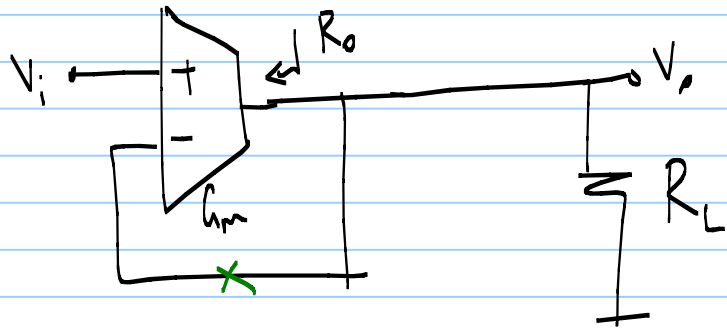
1) We need higher gain? Not necessarily the issue
 ↳ one-stage opamp have gain
 5-T OTA $\approx g_m r_{ds}$
 Telescopic / Folded Cascode $\approx (g_m r_{ds})^2$ ✓





$$|LG| = g_m (R_o \parallel R_L)$$




high \nearrow \nwarrow low
 $\approx g_m R_L$ (too low)

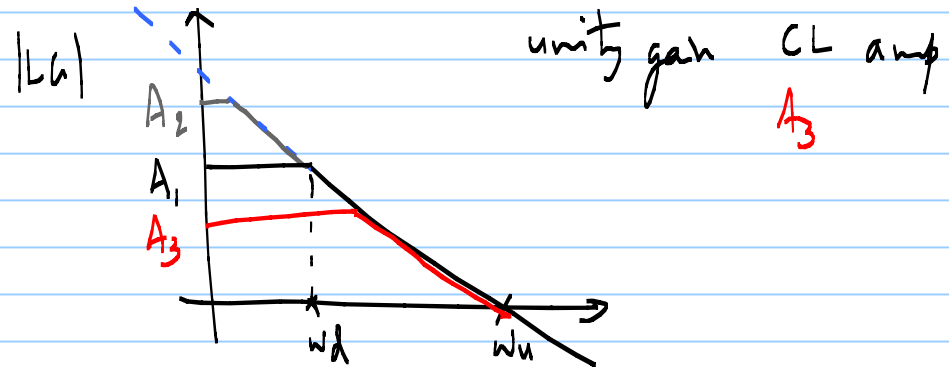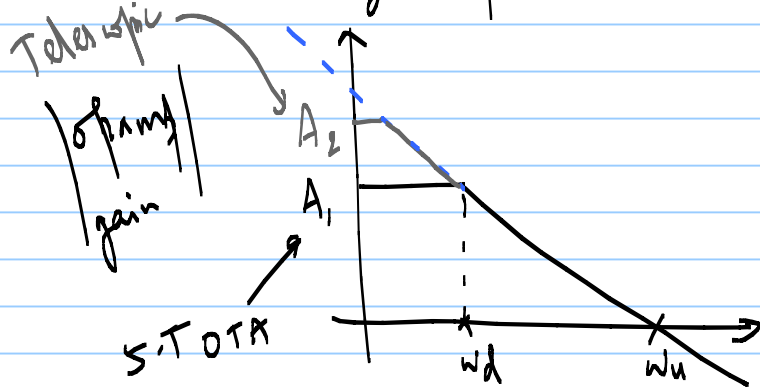* One stage opamp cannot drive resistive loads



Two Stage Opamp

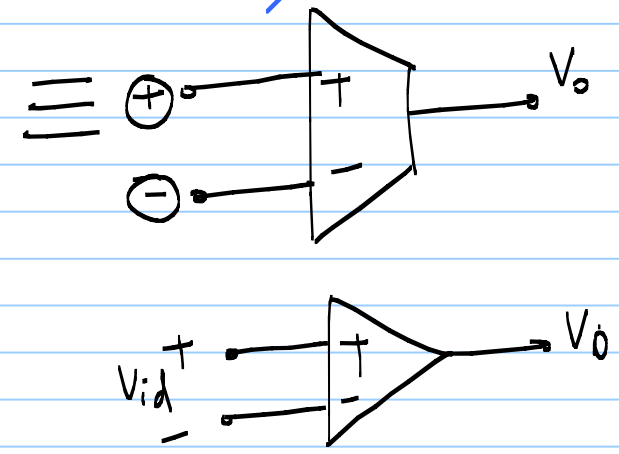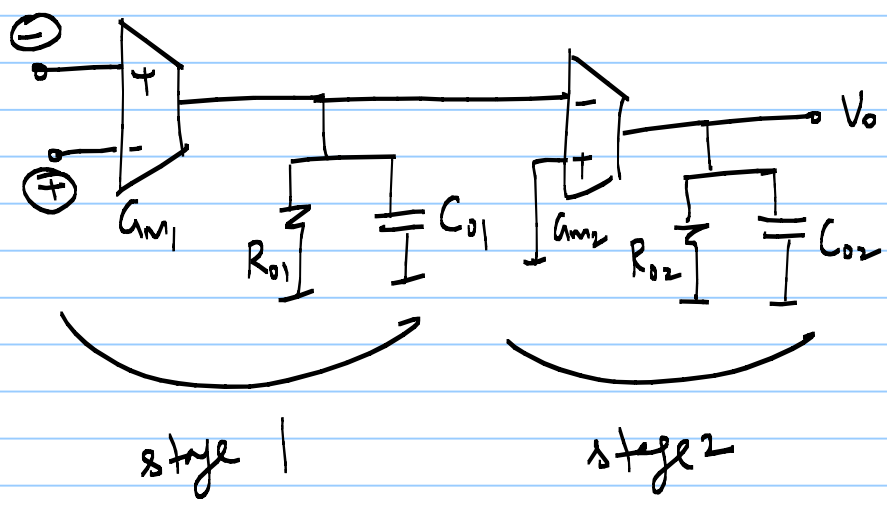

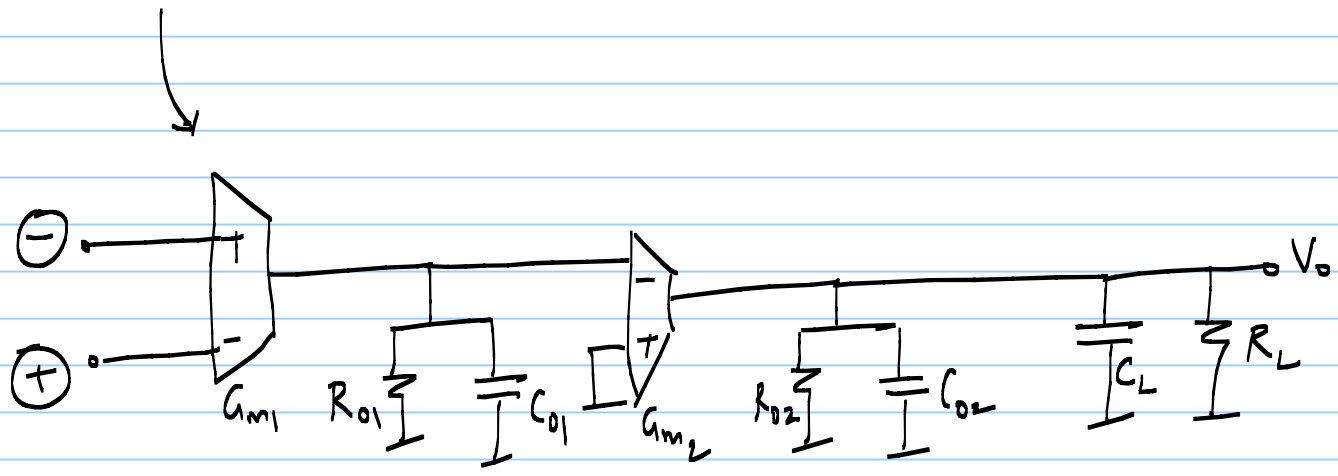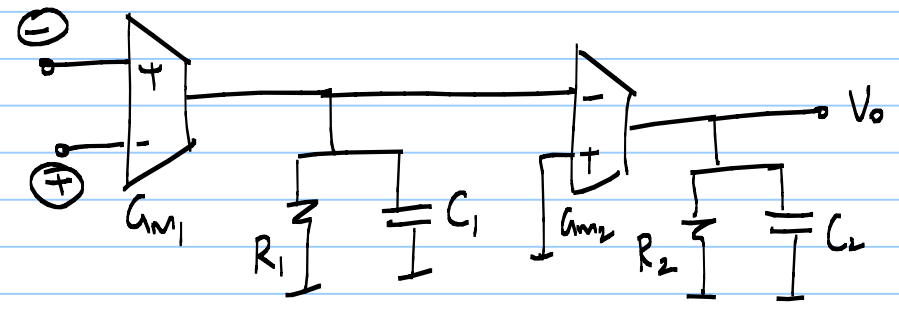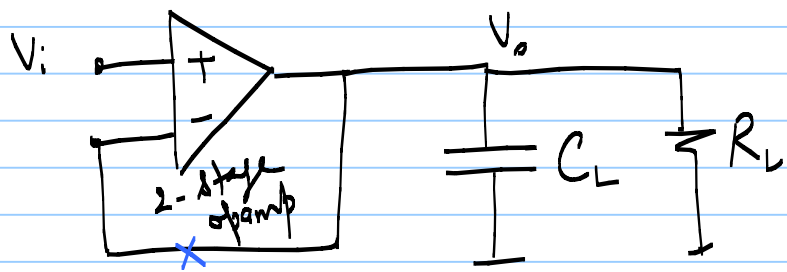


$$R_2 = R_{o2} \parallel R_L$$

$$C_2 = C_{o2} \parallel C_L$$

$$R_1 = R_{o1}$$

$$C_1 = C_{o1}$$

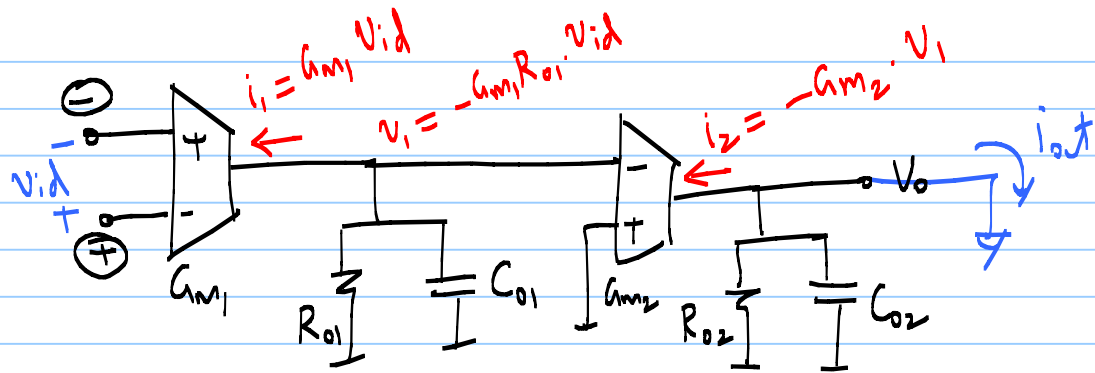



$$DC \text{ gain} = (G_{m1} R_{o1}) \cdot (G_{m2} R_{o2})$$

can be close to $(g_m r_{ds})^2$

$$R_{out} = R_{o2} \quad (\text{large})$$
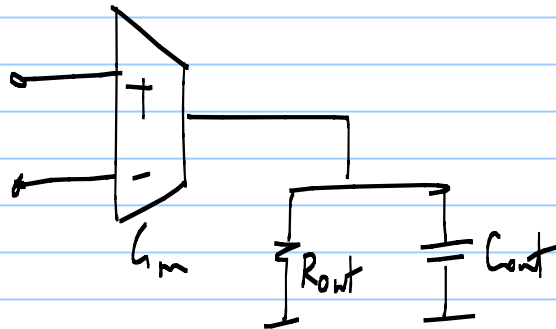
$$G_m = \frac{i_{out}}{V_{id}} = (G_{m1} R_{o1}) G_{m2}$$




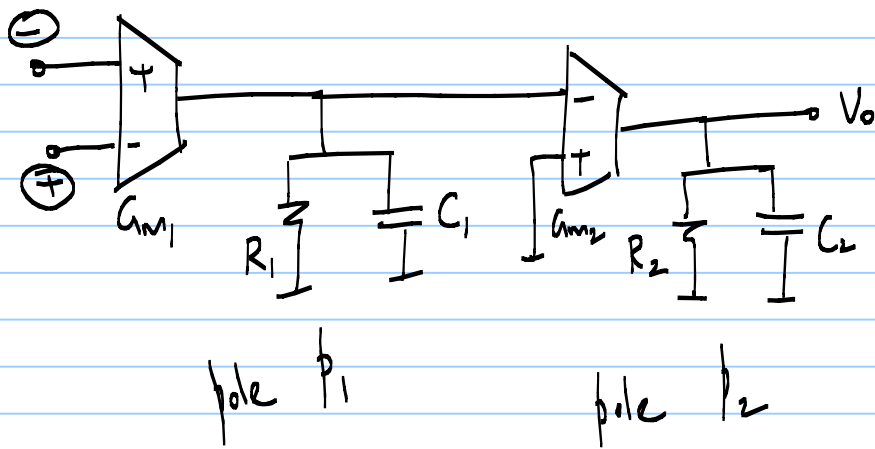

2-pole system

↳ technically "unconditionally" stable

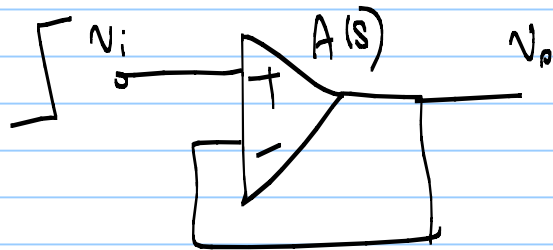↳ If p_1 & p_2 are close to each other, ringing




$A = \text{DC gain}$

$$A(s) = \frac{A}{(1+s/p_1)(1+s/p_2)}$$

$$CL(s) = \frac{A(s)}{1+A(s)} = \frac{N(s)}{D(s)}$$
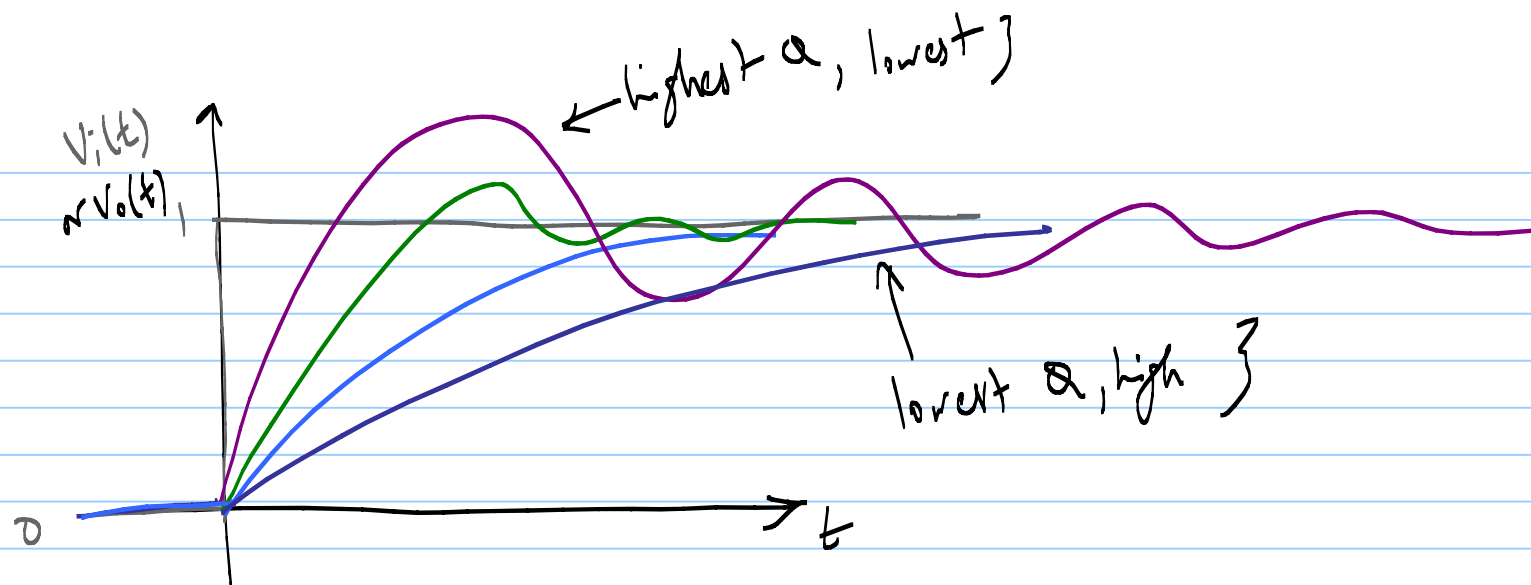
$$\begin{aligned}
 D(s) &= 1 + (1+s/p_1)(1+s/p_2) \\
 &= (1+A) + s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}
 \end{aligned}$$



$$\begin{aligned}
 D(s) = \frac{D(s)}{1+A} &= 1 + \frac{s}{1+A} \left(\frac{1}{p_1} + \frac{1}{p_2} \right) + \frac{s^2}{(1+A)p_1 p_2} \\
 &= 1 + 2\zeta \left(\frac{s}{\omega_n} \right) + \left(\frac{s}{\omega_n} \right)^2 \quad \text{or} \quad 1 + \frac{s}{Q\omega_n} + \frac{s^2}{\omega_n^2}
 \end{aligned}$$

* try $p_1 = p_2 = p$ { identical stages 1 & 2 }

$$D'(s) = 1 + \frac{s}{\frac{1}{2}p(1+A)} + \frac{s^2}{p^2(1+A)}$$

$$\omega_n = p \sqrt{1+A}$$

$$Q = \frac{\sqrt{1+A}}{2}$$

$A = \text{high}$ (DC gain)

⇓

$Q = \text{high}$

⇓

ringing in step response



$$CLG = \frac{A(s)}{1+A(s)} = \frac{A / (1+s/p_1)(1+s/p_2)}{1 + \frac{A}{(1+s/p_1)(1+s/p_2)}}$$

$$= \frac{A}{A + (1+s/p_1)(1+s/p_2)} = \frac{N(s)}{D(s)}$$

$$= \frac{A}{A + 1 + s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}} = \frac{\frac{A}{(1+A)}}{1 + \frac{s}{1+A}\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{(1+A)p_1 p_2}}$$



$N'(s)$
 $D'(s)$

$$A(s) = \frac{A}{(1 + s/p)}$$

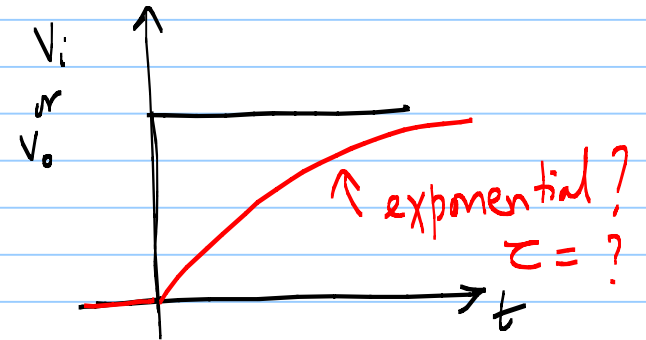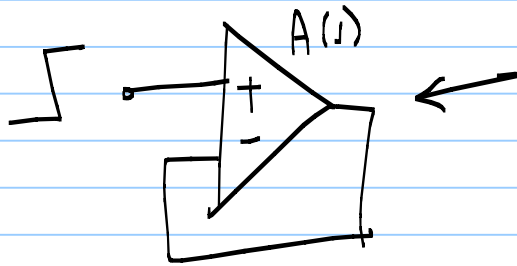

2/11/2023

Lec 17

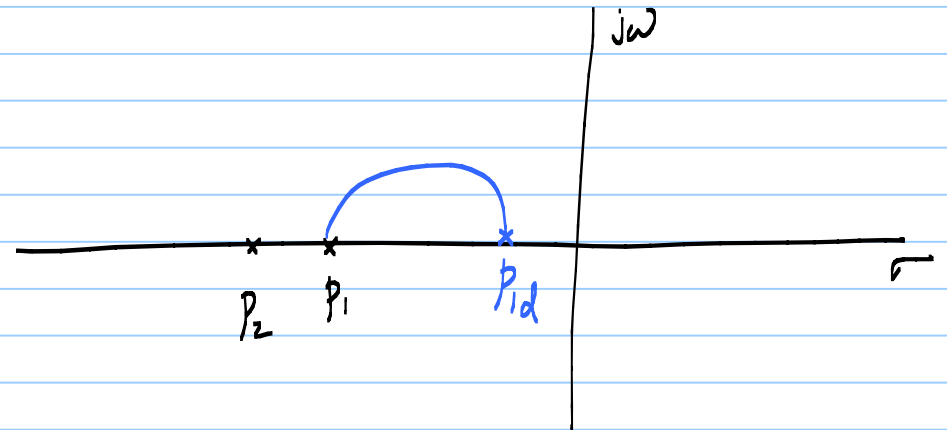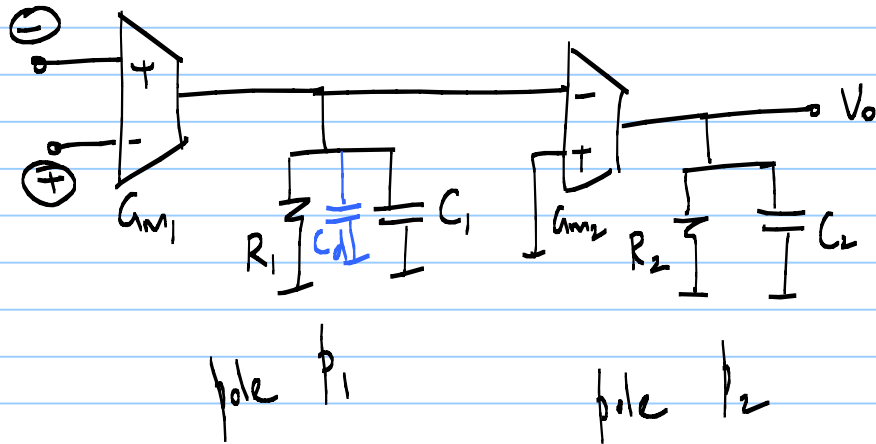


perform freq. compensation \rightarrow 1) Dominant pole comp. \rightarrow add cap C_d

$p_{id} \ll \omega_n$ (high A_0)

$p_2 > \omega_n$ (high PM)

$p_1 \rightarrow p_{id}$

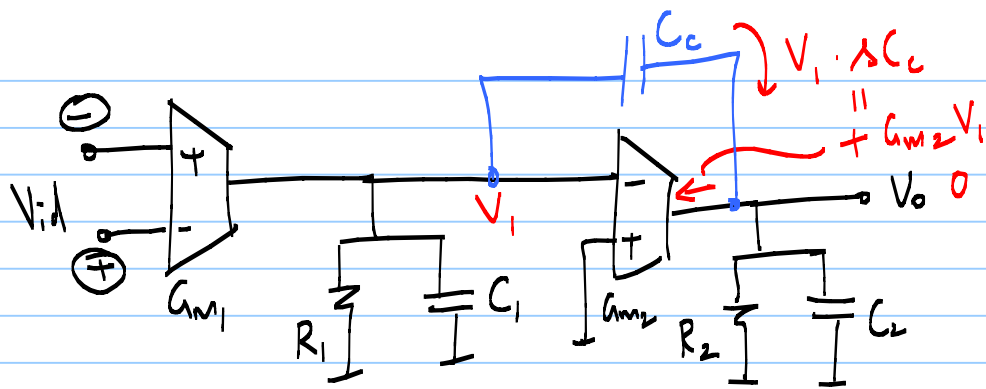need $C_d \gg C_1$, because $p_{id} \ll p_2$ is required




pole p_1

pole p_2

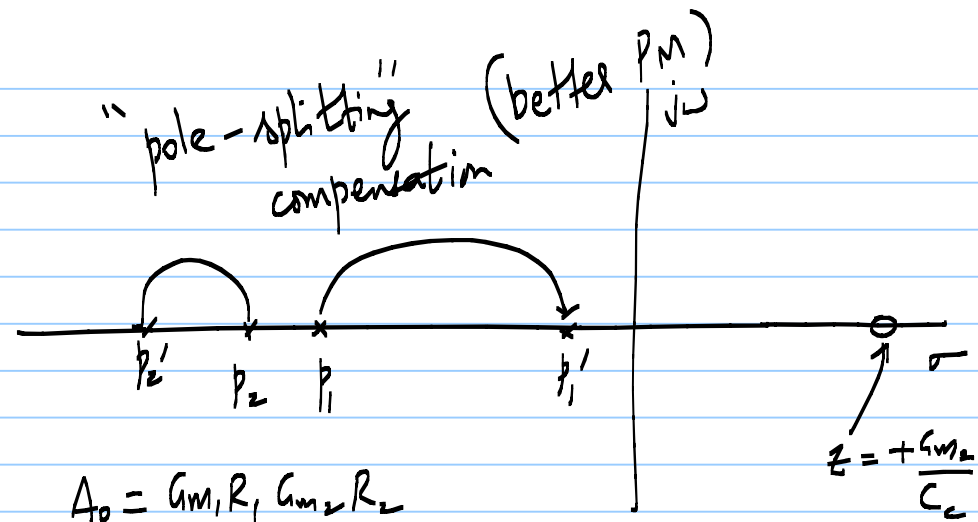2) Miller Compensation

$$\frac{V_o}{V_{id}}(s) = \frac{A_0 (1 - s/z)}{\left(1 + \frac{s}{p_1'}\right) \left(1 + \frac{s}{p_2'}\right)}$$

$$C_{eff} \approx C_2 + \frac{C_1 C_c}{C_1 + C_c}$$



$$A_0 = G_{m1} R_1 G_{m2} R_2$$




$$z = \frac{G_{m2}}{C_c}$$


$$p_1' \approx \frac{1}{R_1 \cdot C_{eff}} ; C_{eff} \approx C_1 + (G_{m2} R_2) C_c$$

$$p_2' = \frac{1}{R_{2eff} \cdot C_{2eff}} ; C_{2eff} = C_2 + f(C_1, C_c)$$

(HW)

$$R_{2eff} = R_2 \parallel R_{ox}$$

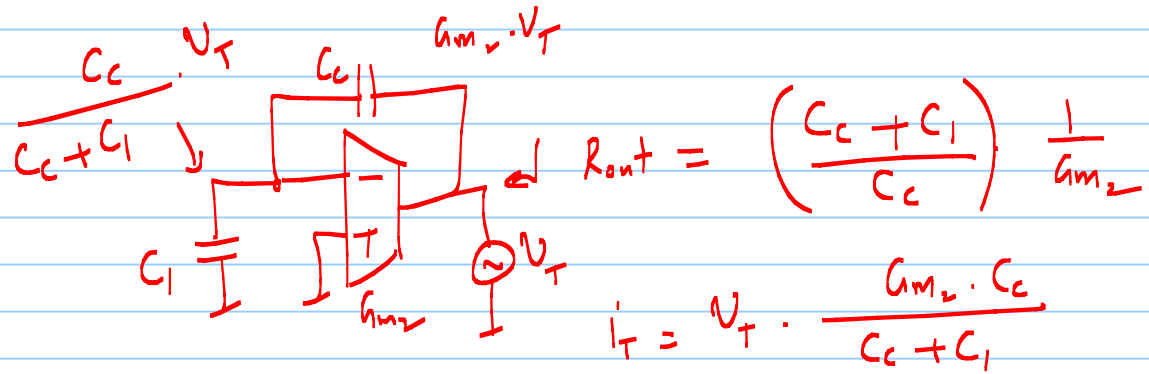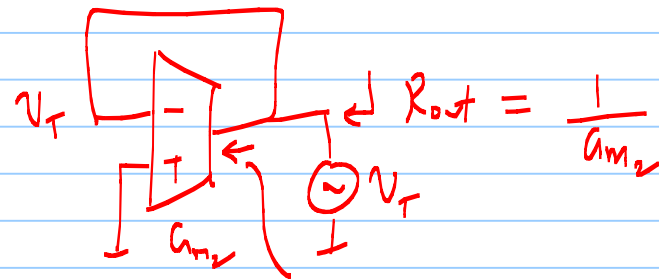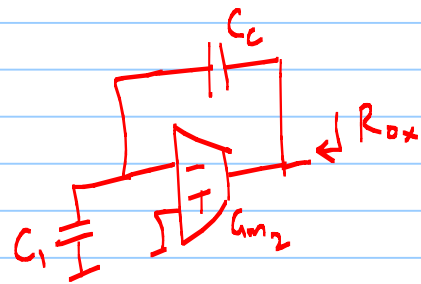


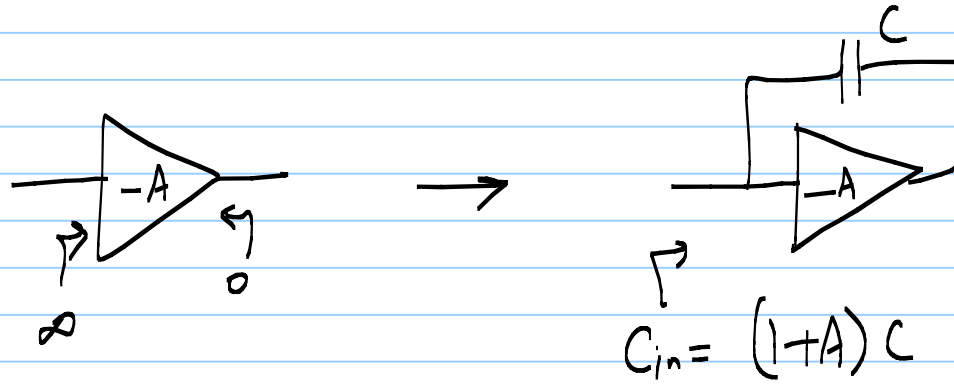

Miller Effect

Miller Compensation :

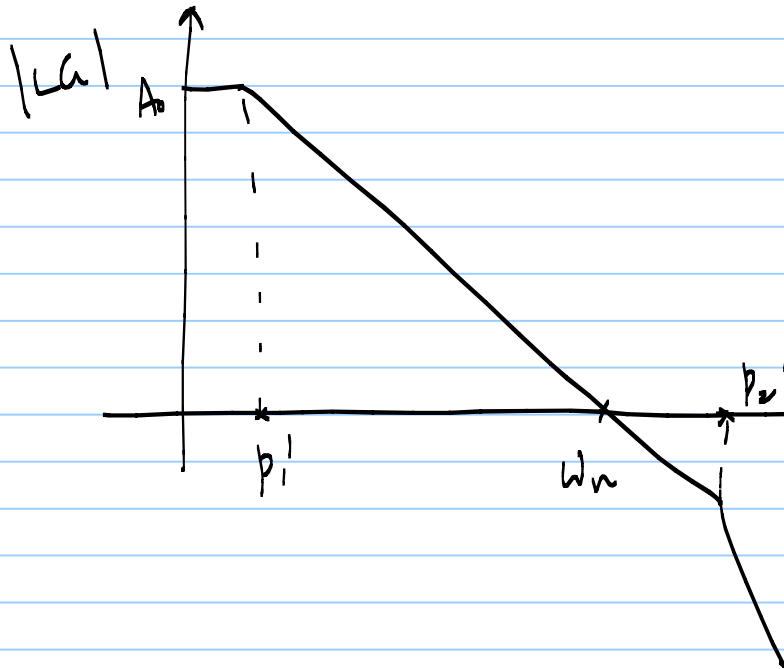ω_u after compensation = $\frac{G_{m1}}{C_c}$




$$\omega_u = A_0 \cdot p_1'$$

$$\approx G_{m1} R_1 \cdot G_{m2} R_2 \cdot \frac{1}{R_1 \cdot G_{m2} R_2 C_c}$$


$$\approx \frac{G_{m1}}{C_c}$$

$\Rightarrow \omega_u$
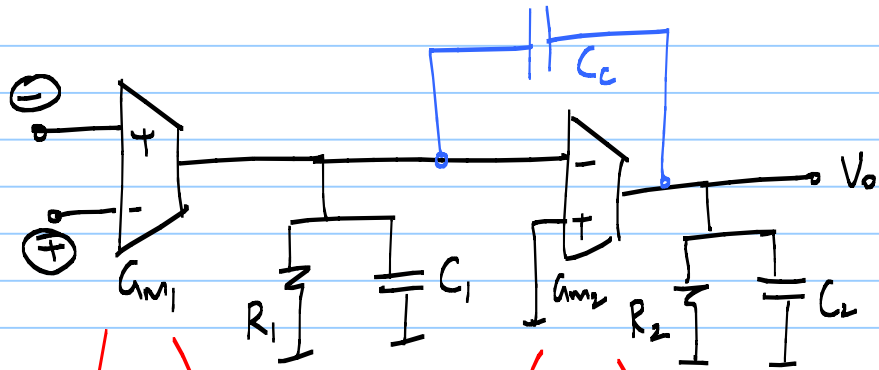
$$\frac{G_{m2}}{C_c} \Rightarrow \frac{G_{m1}}{C_c} \Rightarrow \boxed{G_{m2} \gg G_{m1}}$$



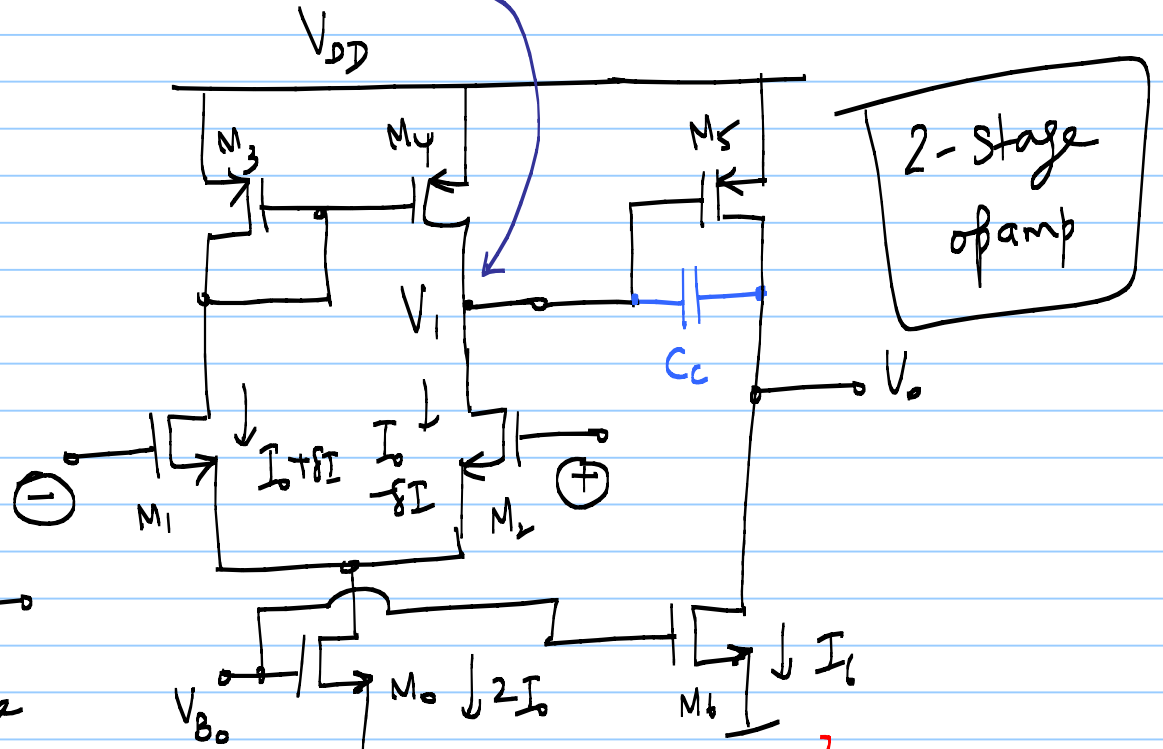
expected DC voltage = $V_{DD} - V_{S_{3,4}}$



2-stage opamp

looks like S-T OTA

CSA with active load

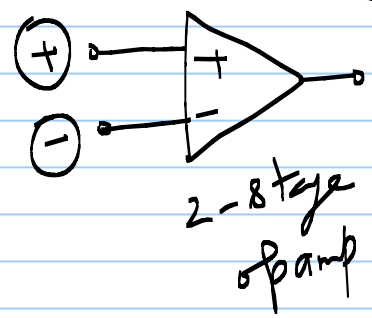

2-stage opamp

$G_{m1} = g_{m_{1,2}}$

$G_{m2} = g_{m5} \gg g_{m_{1,2}}$

$$R_{o1} = r_{ds4} \parallel r_{ds2}$$

$$R_{o2} = r_{ds5} \parallel r_{ds6}$$

$$C_{o1} = C_{db4} + C_{db2} + C_{gs5}$$

$$C_{o2} = C_{db5} + C_{db6}$$

$$1) \quad G_{m1} = g_{m1} \quad ; \quad G_{m2} = g_{m5}$$

$$2) \quad Z \gg \omega_c \Rightarrow \frac{G_{m2}}{C_c} \gg \frac{G_{m1}}{C_c} \Rightarrow G_{m2} \gg G_{m1} \Rightarrow \boxed{g_{m5} \gg g_{m1}}$$



$$3) \quad V_{DD} - V_{S_{g_{3,4}}} \Big|_{I_D} = V_{DD} - V_{S_{g_5}} \Big|_{I_6}$$

$$V_{S_{g_{3,4}}} \Big|_{I_D} = V_{S_{g_5}} \Big|_{I_6} \Rightarrow V_{ov_{at_{3,4}}} \Big|_{I_D} = V_{ov_{at_5}} \Big|_{I_6}$$

$$\sqrt{\frac{2 I_0}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{3,4}}} = \sqrt{\frac{2 I_b}{\mu_p C_{ox} \left(\frac{W}{L}\right)_5}}$$


$$\Rightarrow \boxed{\frac{I_0}{\left(\frac{W}{L}\right)_{3,4}} = \frac{I_b}{\left(\frac{W}{L}\right)_5}}$$

$$4) L_{3,4} = L_5$$

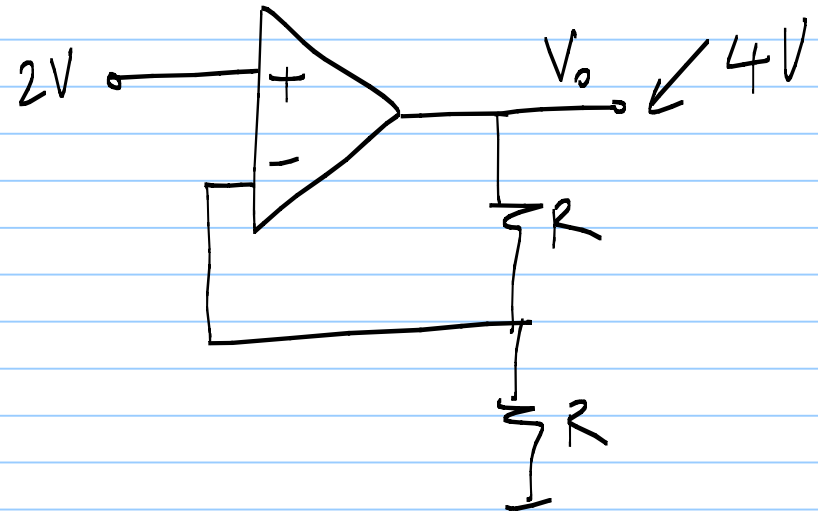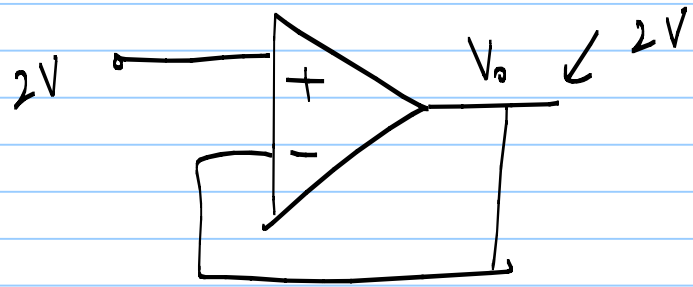

9/11/2023

Lec 18

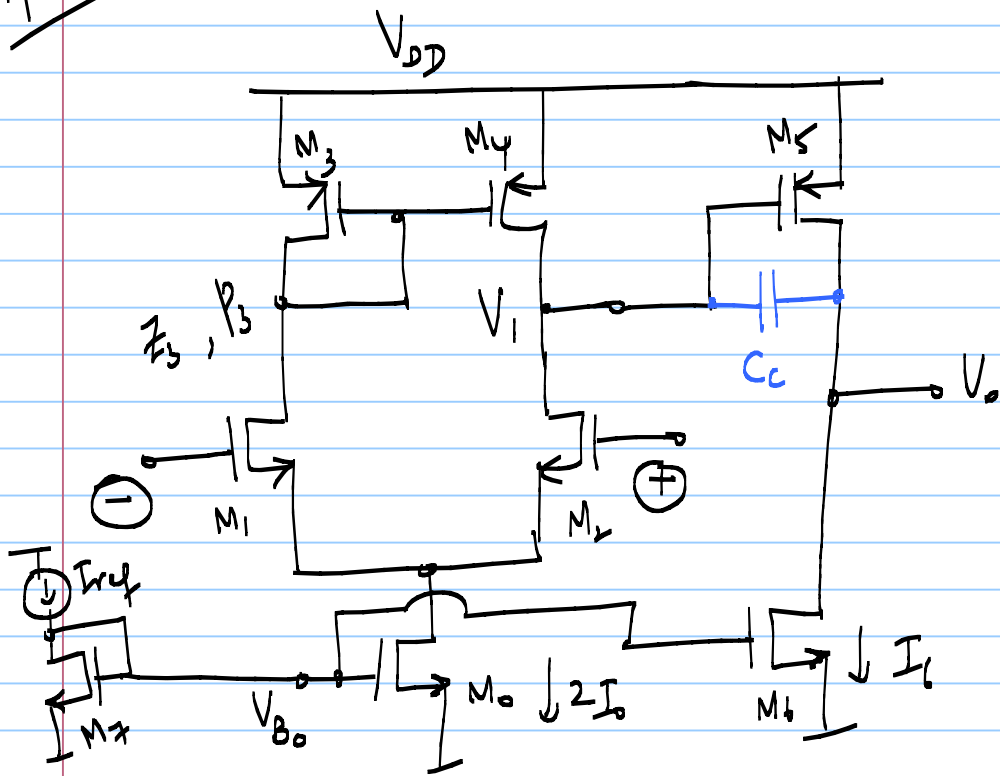

$$L_7 = L_0 = L_6$$

$$W_7 : W_0 : W_6 = I_{ref} : 2I_0 : I_0$$

2-stage opamp datasheet

1) DC gain = $g_{m1} R_{i1} \cdot g_{m5} r_{e2}$
 $= g_{m1} \cdot (r_{ds2} \parallel r_{ds4}) \cdot g_{m5} \cdot (r_{ds5} \parallel r_{ds6})$

2) $G_m = g_{m1} (r_{ds2} \parallel r_{ds4}) \cdot g_{m5}$

3) $\omega_u = \frac{g_{m1}}{C_c}$; $\omega_d = \frac{\omega_u}{DC \text{ gain}}$


4) ND poles & zeroes : poles: p_2' ; p_3

Zeroes: z ; z_3

5) ICMR : $\left\{ V_{GS1} \Big|_{I_0} + V_{DSAT0} \Big|_{2I_0}, V_{DD} - V_{GS3} \Big|_{I_0} + V_{T1} \right\}$

6) OCMR : $\left\{ V_{DSAT4}, V_{DD} - V_{DSAT5} \right\}$

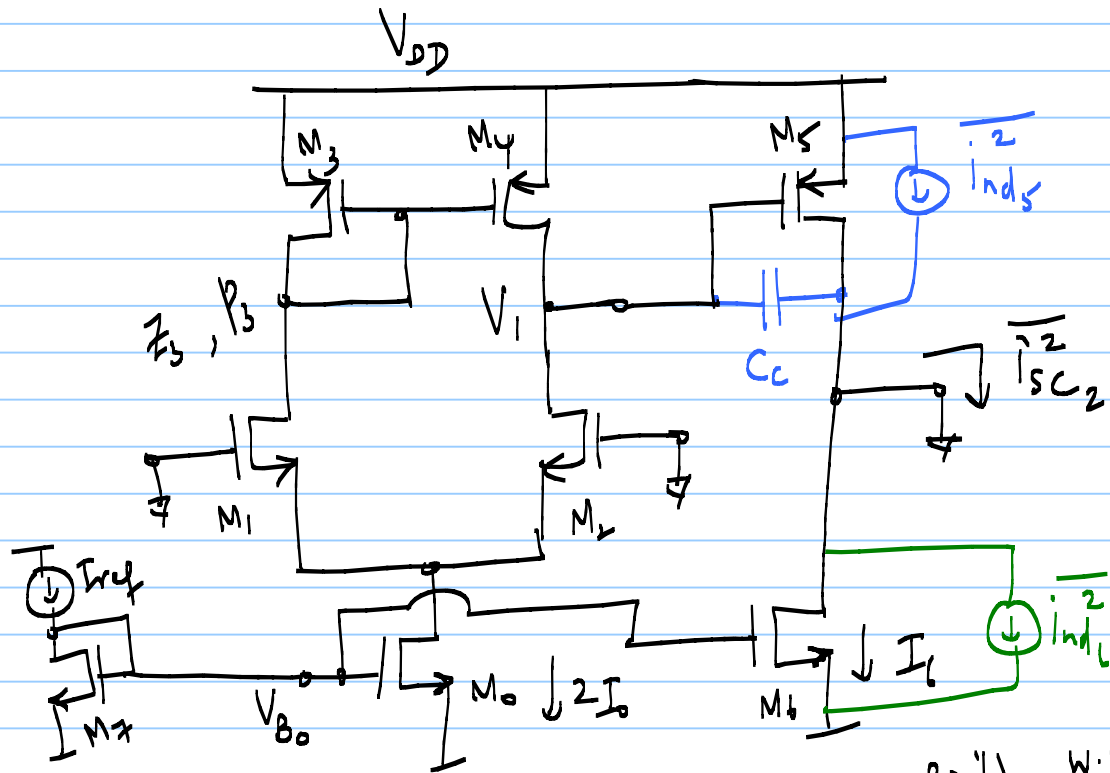7) Noise : $\frac{\overline{e_n^2}}{\Delta f} = \frac{16kT}{3g_{m1}} + \frac{16kT \cdot g_{m3}}{3g_{m1}^2}$



$$\overline{e_n^2} = \overline{e_{n1}^2} + \overline{e_{n2}^2}$$


↑ 1st stage ↑ 2nd stage

$$\overline{i_{sc2}^2} = \overline{i_{nd5}^2} + \overline{i_{nd6}^2} + \overline{i_{nd7}^2}$$

$$\overline{e_{n2}^2} = \frac{\overline{i_{nd5}^2} + \overline{i_{nd6}^2} + \overline{i_{nd7}^2}}{G_m^2}$$

negligible w.r.t. $\overline{e_{n1}^2}$
 due to large gain
 of stage 1


$$= \left[g_{m1} (r_{ds2} || r_{ds4}) \cdot g_{m5} \right]^2$$

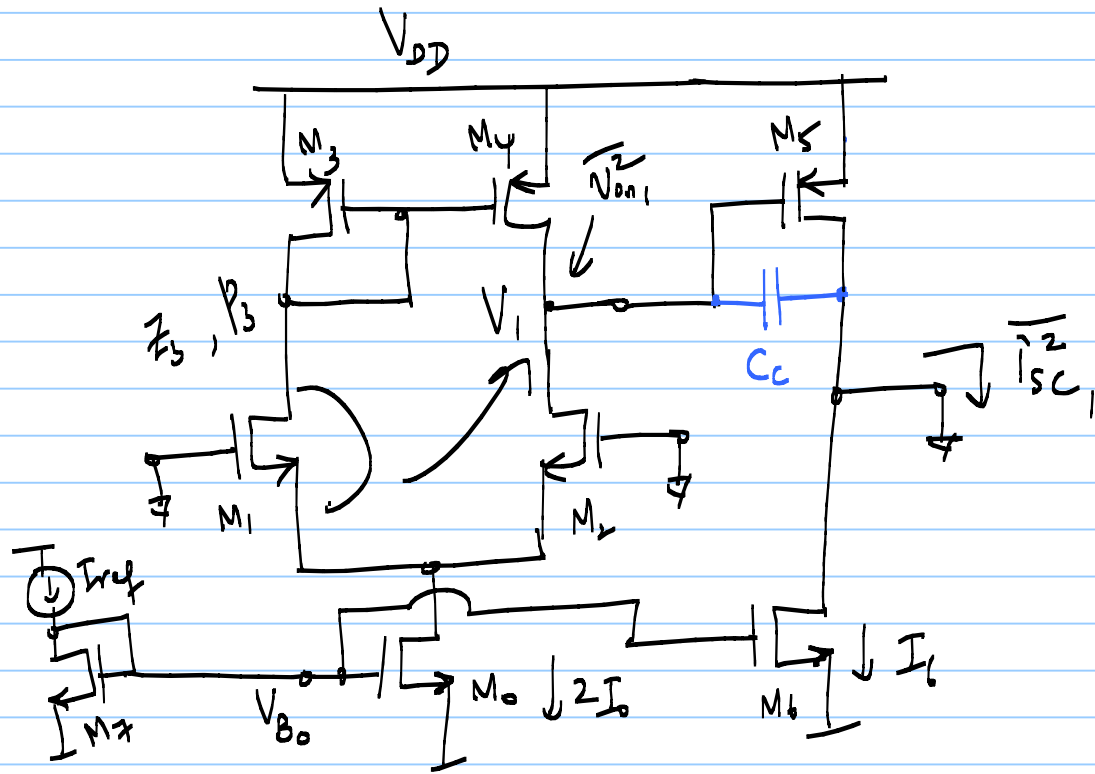

$$\overline{V_{on1}^2} = \left[\frac{8kT}{3} g_{m1} + \frac{8kT}{3} g_{m2} + \frac{8kT}{3} g_{m3} + \frac{8kT}{3} g_{m4} \right] \cdot (r_{ds2} \parallel r_{ds4})^2$$

$$\overline{i_{sc1}^2} = \overline{V_{on1}^2} \cdot g_{m5}^2$$
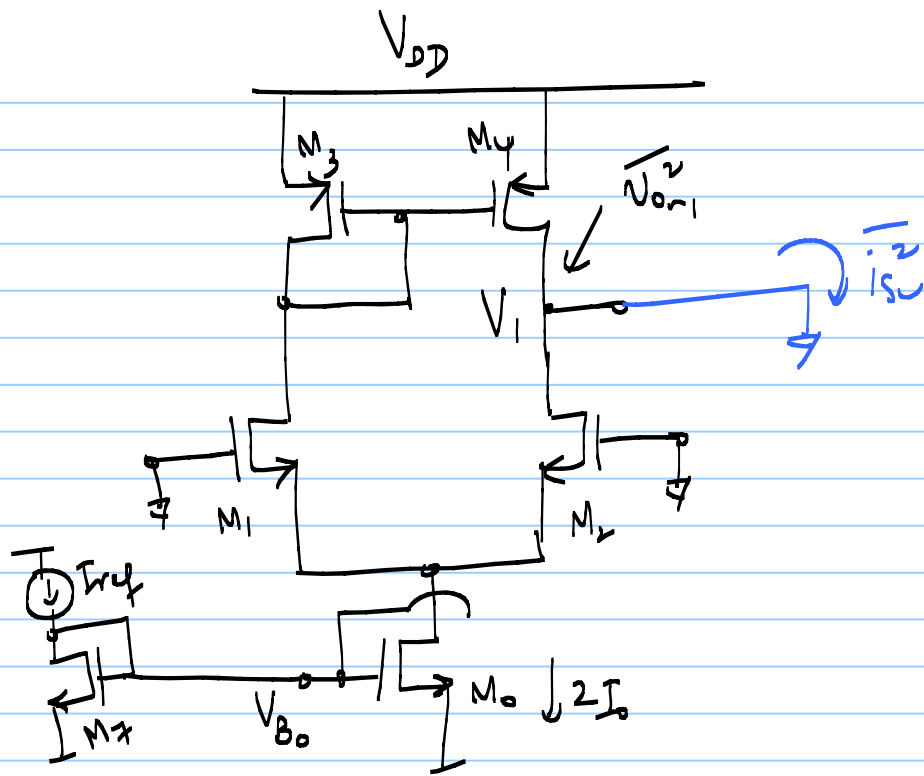
$$\overline{en_1^2} = \frac{\overline{i_{sc1}^2}}{G_m^2}$$





$$\overline{e_n^2} = \frac{\overline{i_{s2}^2}}{G_m^2}$$

$$\overline{e_n^2} = \frac{\overline{V_{on1}^2}}{A^2}$$

$$\frac{e_{n1}^2}{\Delta f} = \frac{\left[\frac{8kT}{3} g_{m1} + \frac{8kT}{3} g_{m2} + \frac{8kT}{3} g_{m3} + \frac{8kT}{3} g_{m4} \right] \cdot (r_{ds2} \parallel r_{ds4})^2 \cdot g_{m5}^2}{\left[g_{m1} (r_{ds2} \parallel r_{ds4}) \cdot g_{m5} \right]^2}$$

$$\frac{e_{n1}^2}{\Delta f} = \frac{16kT}{3g_{m1}} + \frac{16kT g_{m3}}{3g_{m1}^2}$$

Cascaded stage noise

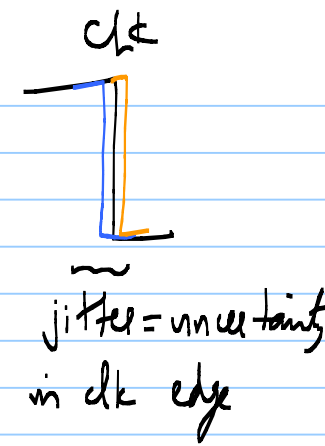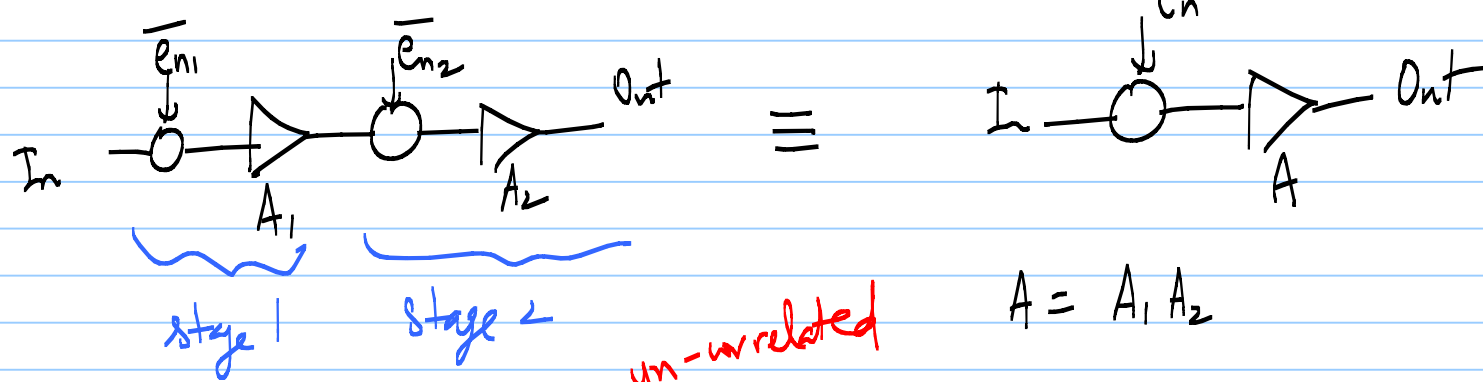

Noise @ Out

$$= \overline{e_{n1}^2} \cdot (A_1 A_2)^2 + \overline{e_{n2}^2} \cdot A_2^2$$


$= \overline{e_n^2} \cdot A^2 = \overline{e_n^2} (A_1 A_2)^2$

$$\overline{e_n^2} (A_1 A_2)^2 = \overline{e_{n1}^2} (A_1 A_2)^2 + \overline{e_{n2}^2} \cdot A_2^2$$

$$\overline{e_n^2} = \overline{e_{n1}^2} + \overline{e_{n2}^2} / A_1^2$$


voltage
density

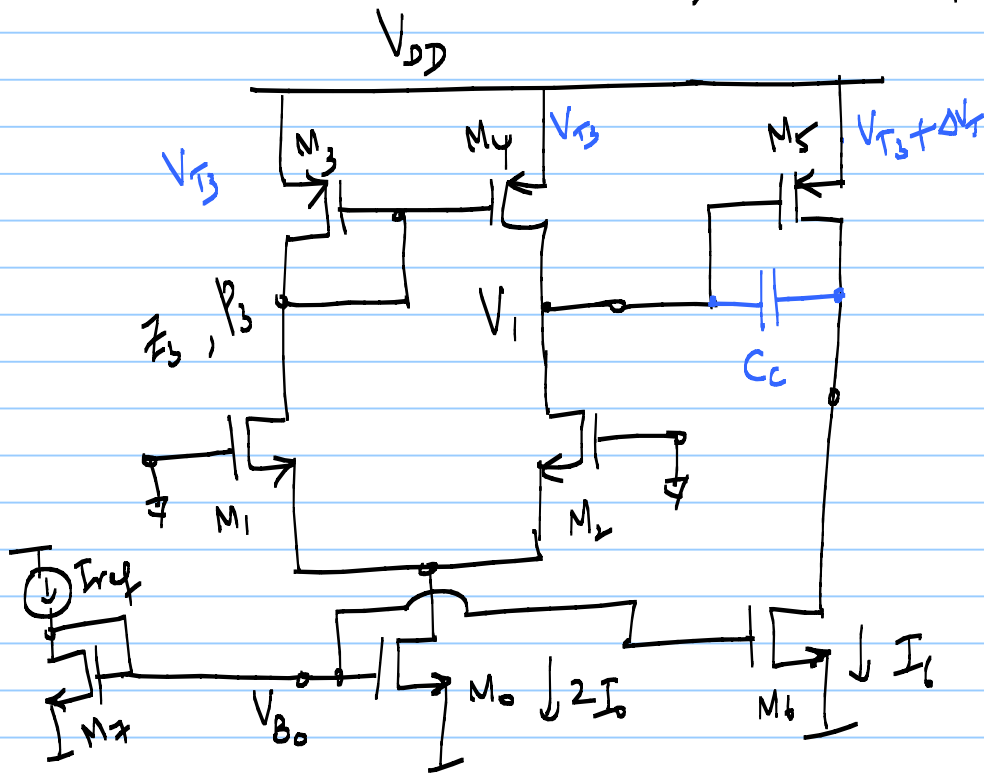8) Offset
$$V_{OS}^2 \approx \sqrt{V_{T1,2}^2} + \sqrt{V_{T3,4}^2} \left(\frac{\mu_{n2}}{\mu_{n1}} \right) + (\dots)$$



a) Slew rate



$$SR \approx \pm \frac{2I_0}{C_c}$$

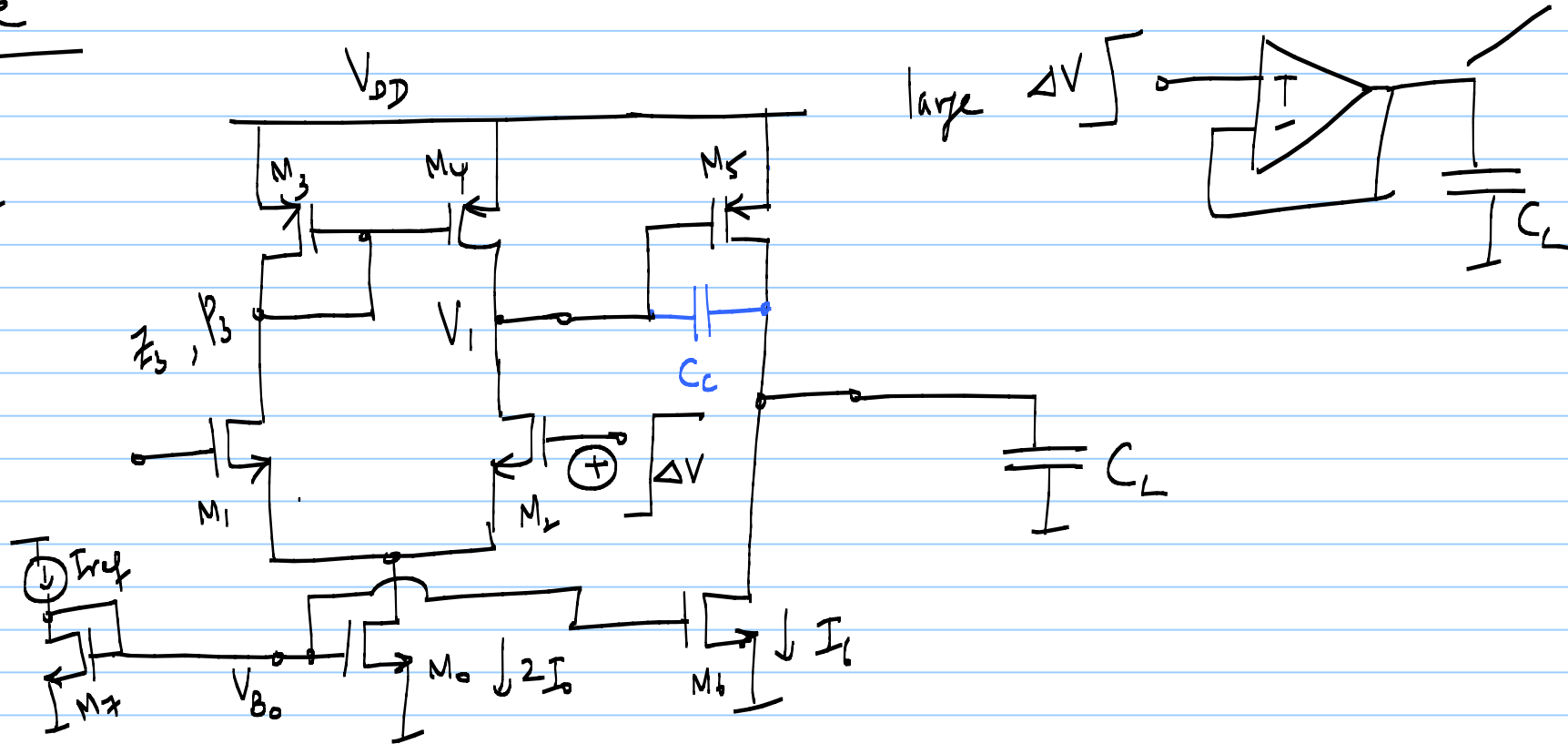


10/11/23

Lec 19

Slew Rate
of 2-stage
opamp

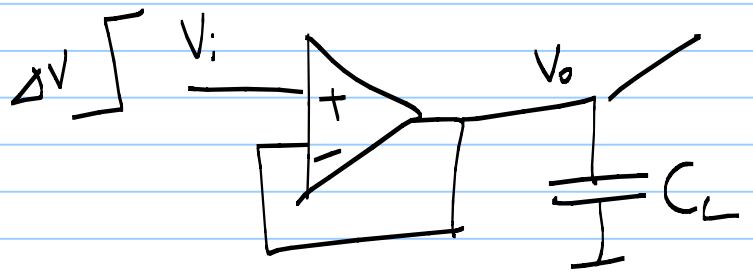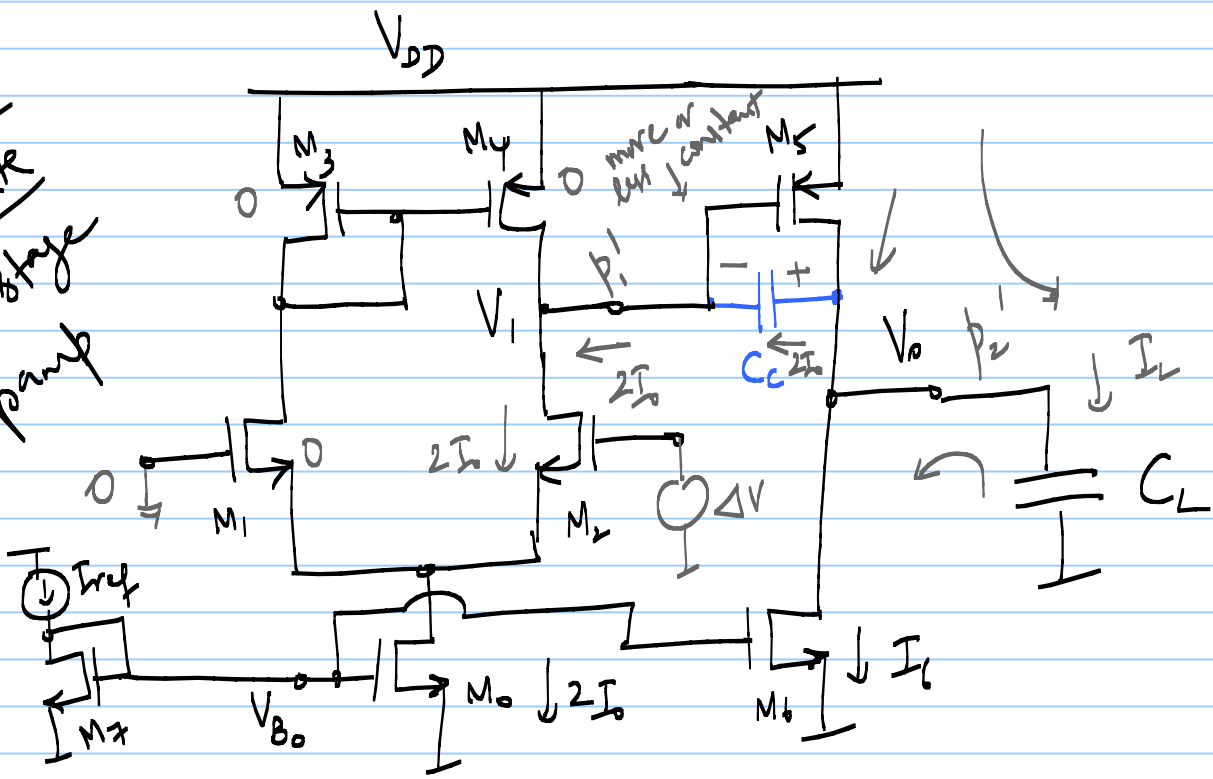

$$2I_o = C_c \frac{dV_o}{dt}$$

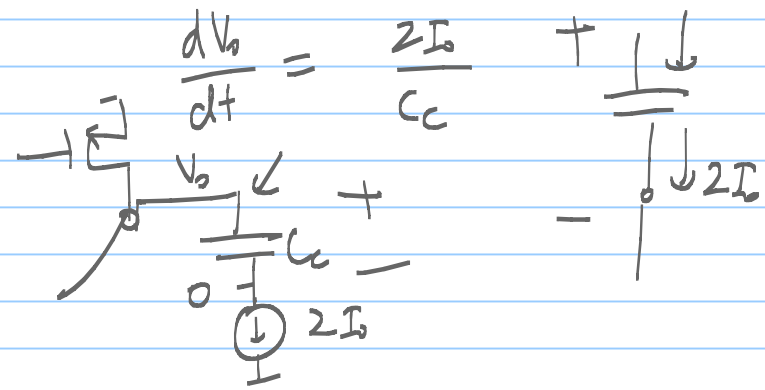

$$\frac{dV_o}{dt} = \frac{2I_o}{C_c}$$

$$I_L = C_L \underbrace{\frac{dv}{dt}}_{\frac{2I_0}{C_C}} \leftarrow \text{from } M_5$$

* Assume C_L is not too large

* Assume $\epsilon \gg \omega_u$


$$\Rightarrow \frac{g_{m2}}{C_C} \gg \frac{g_{m1}}{C_C} \Rightarrow g_{m2} \gg g_{m1} \Rightarrow \boxed{g_{m5} \gg g_{m1}}$$

$$\Rightarrow I_6 \gg I_0; \left(\frac{v}{L}\right)_5 \gg \left(\frac{v}{L}\right)_1$$

* $2I_0$ is small enough
so that $SR \approx \frac{2I_0}{C_C}$
is valid

* Cross check via simulation

Design Example

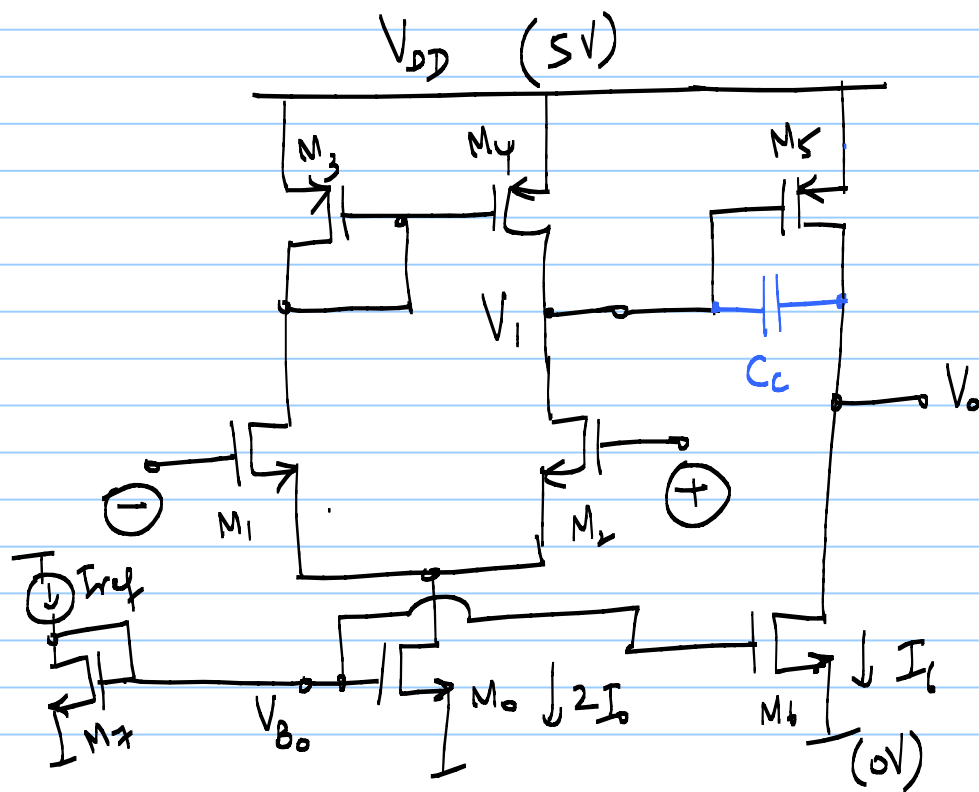

Specs

- 1) $A_o \geq 80 \text{ dB}$ ($= 10^4 \text{ V/V}$)
- 2) $V_{o\text{p-p}} \geq 4 \text{ V}$
- 3) $f_u \geq 5 \text{ MHz}$
- 4) $SR \geq 10 \text{ V}/\mu\text{s}$
- 5) Unity gain $PM \geq 60^\circ$
- 6) $C_L = 10 \text{ pF}$

MOSFET parameters: $\mu_n C_{ox} = 50 \mu A/V^2$; $\mu_p C_{ox} = 25 \mu A/V^2$

$$V_{Tn} = V_{Tp} = 1V \quad ; \quad V_{DD} = 5V$$

$$L_{min} = 2 \mu m \quad ; \quad C_{ox} = 1.5 \text{ fF}/\mu m^2$$

$$(\lambda L_{min})_p = 0.1 \mu m/V \quad ; \quad (\lambda L_{min})_n = 0.04 \mu m/V$$

$$\left. \begin{array}{l} * (\lambda L) = \text{constant} \\ r_{ds} = \frac{1}{\lambda I} \end{array} \right)$$

$$L \uparrow \Rightarrow \lambda \downarrow \Rightarrow r_{ds} \uparrow$$

* Assume I_{CMR} is large enough e.g. $> 1.5V \Rightarrow$ NMOS input pair

$$1) f_u = \frac{g_{m1}}{2\pi C_c}$$

$$2) SR = \frac{2I_0}{C_c}$$

$$3) A_{v0} = (g_{m1} R_{o1}) \cdot (g_{m5} R_{o2})$$

$$4) PM > 60^\circ \Rightarrow \tan 60^\circ = \sqrt{3} = \frac{p_2}{\omega_u}$$

$$p_2 = \sqrt{3} \omega_u$$

$$5) L_3 = L_4 = L_5$$


$$L_1 = L_2$$

$$L_0 = L_6 = L_7$$


$$6) V_{sat5} = V_{sat6} = 0.5V$$

$$7) g_{m5} \gg g_{m1} \quad \{z \gg \omega_u\}$$

$$\text{say, } g_{m5} = 10 g_{m1}$$

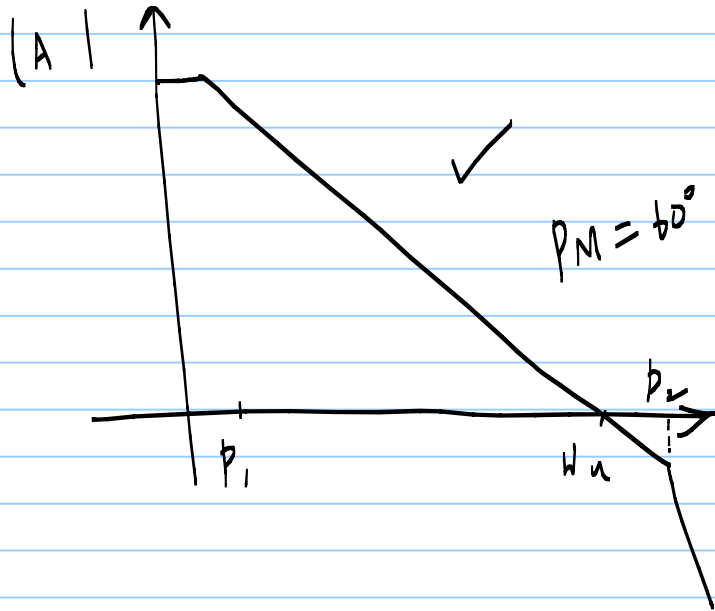


w

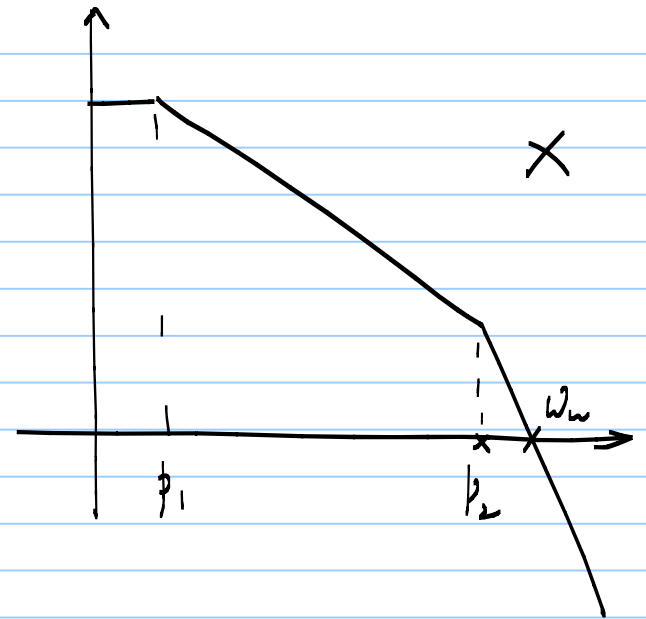

* Assume C_1 is small (negligible)

* $C_L \gg C_c$

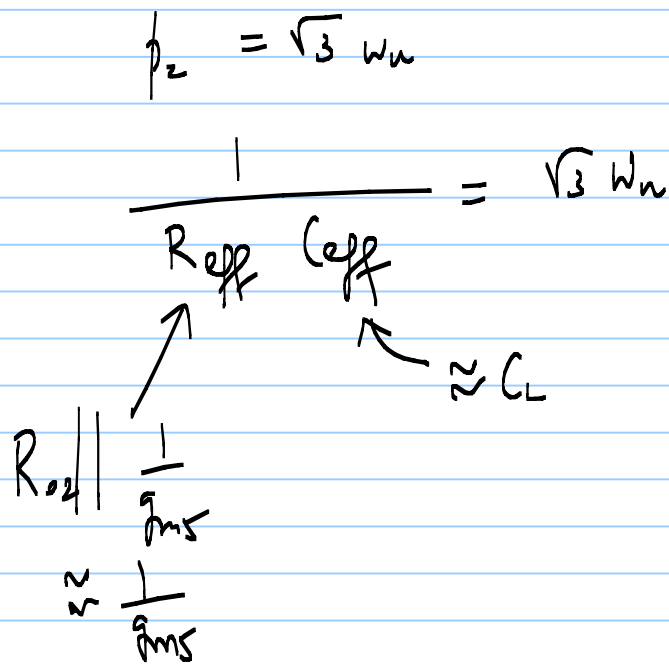

$$\Rightarrow \frac{g_{m5}}{C_L} \approx \sqrt{3} \omega_n$$

$$\omega_{m5} = \sqrt{3} \times 2\pi \times 5 \times 10^6 \times 10 \times 10^{-12}$$

$$g_{m5} = 540 \mu S$$

$$\Rightarrow g_{m1} = 54 \mu S$$

$$\omega_u = \frac{g_{m1}}{C_c}$$

$$C_c = \frac{g_{m1}}{\omega_u} = \frac{54 \mu S}{2\pi \times 5 \times 10^6} = 1.72 \text{ pF}$$

$$SR = \frac{2I_b}{C_c}$$

$$2I_b = SR \times C_c = 10 \text{ V}/\mu\text{s} \times 1.72 \text{ pF}$$

$$2I_b = 10 \times 10^6 \times 1.72 \times 10^{-12} = 17.2 \mu\text{A}$$

$$I_{D1} = I_{D2} = 8.6 \mu\text{A}$$

$\left(\frac{W}{L}\right)_{1,2}$ from I_{D1} & g_{m1}

$$g_{m1,2} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{1,2} \cdot I_{D1,2}}$$

$$\left(\frac{W}{L}\right)_{1,2} = 3.4$$

for M_5 : $g_{m5} = \frac{2I_{D5}}{V_{sat5}}$

$$540\mu S = \frac{2I_{D5}}{0.5} \Rightarrow I_{D5} = I_6 = 135\mu A$$

$$I_{D5} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_5 \cdot I_{D5}}$$

$$\left(\frac{W}{L}\right)_5 = 43.2$$

$$V_{Dsat6} = \sqrt{\frac{2 I_{D6}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_6}}$$

$$0.5V = \sqrt{\frac{2 \times 135 \mu A}{50 \mu A/V^2 \times \left(\frac{W}{L}\right)_6}}$$

$$\Rightarrow \left(\frac{W}{L}\right)_6 = 21.6$$

$$\frac{2I_0}{(W/L)_0} = \frac{I_6}{(W/L)_6}$$

$$\Rightarrow \boxed{\left(\frac{W}{L}\right)_0 = 2.75}$$

$$\frac{2I_{3,4}}{(W/L)_{3,4}} = \frac{2I_5}{(W/L)_5} \Rightarrow \boxed{\left(\frac{W}{L}\right)_{3,4} = 2.75}$$

HW

find

$L_1 - L_6$

↳ assume L_{min}


↳ calculate $r_{ds\ 's}$

↳ calculate R_{o1}, R_{o2}

↳ calculate A_0


↳ if $A_0 < 10^4$,

↑ L of device
limiting R_{o1}/R_{o2}

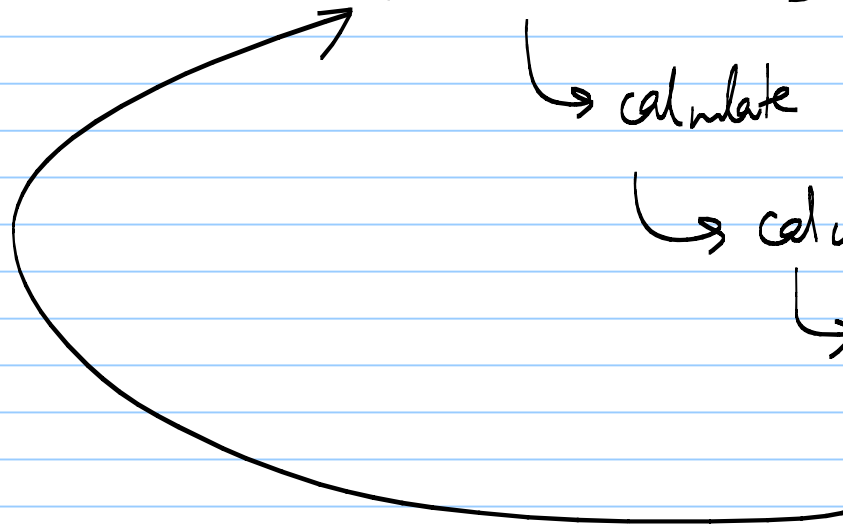

14/11/23

Lec 20

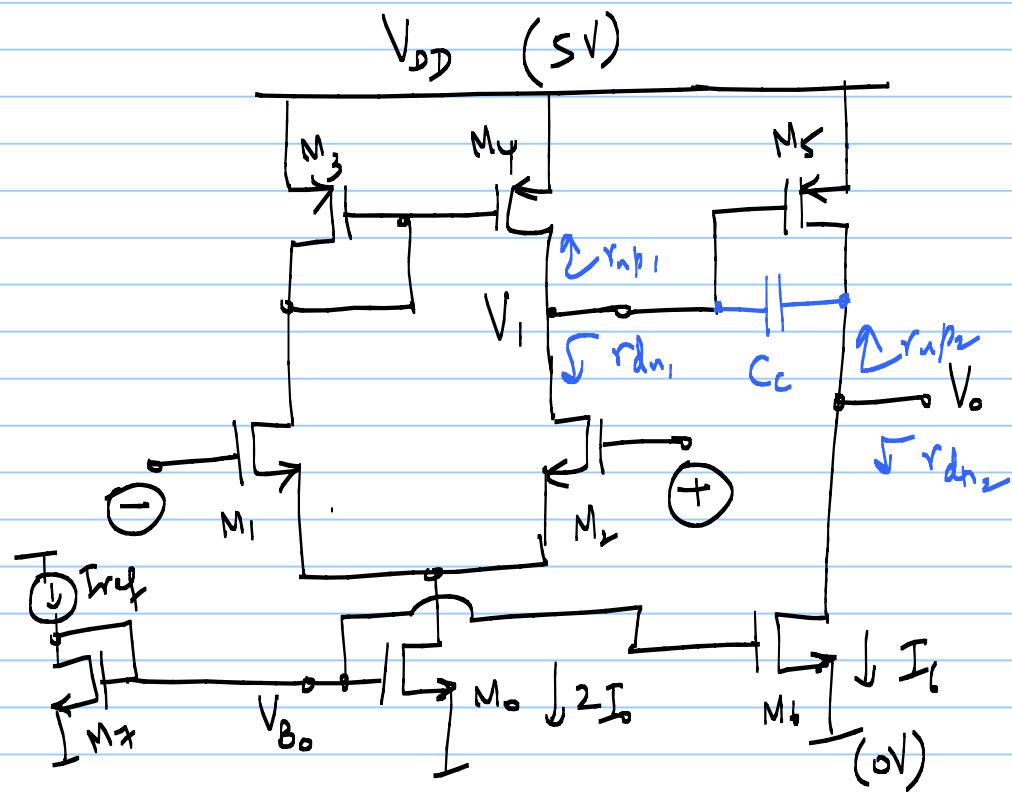

Assume all $L's = L_{min}$

$$A_o = g_{m1} r_{out1} \cdot g_{m5} r_{out2} \quad ? \quad ?$$

$$r_{out1} = r_{np1} \parallel r_{dn1}$$

$$r_{out2} = r_{np2} \parallel r_{dn2}$$

$$r_{up1} = r_{ds4} = \frac{1}{\lambda_4 \cdot I_{D4}} = \frac{1}{\frac{0.1 \text{ mm/V}}{2 \mu\text{m}} \times 8.6 \mu\text{A}} = 2.33 \text{ M}\Omega$$

$$r_{dn1} = r_{ds2} = \frac{1}{\lambda_2 \cdot I_{D2}} = \frac{1}{\frac{0.04 \text{ mm/V}}{2 \mu\text{m}} \times 8.6 \mu\text{A}} = 5.81 \text{ M}\Omega$$

$$r_{out1} = 1.66 \text{ M}\Omega$$

$$\Rightarrow A_1 = g_{m1} \cdot r_{out1} = 54 \mu\text{S} \times 1.66 \text{ M}\Omega$$

$$A_1 = 89.8 \text{ V/V}$$

$$r_{up2} = r_{ds5} = \frac{1}{\lambda_5 \cdot I_{D5}} = 148.4 \text{ k}\Omega ; r_{dn2} = \frac{1}{\lambda_6 \cdot I_{D6}} = 371 \text{ k}\Omega$$

$$r_{out2} = 105.71 \text{ k}\Omega$$

$$A_2 = g_{m5} r_{out2} = 540 \mu\text{S} \times 105.71 \text{ k}\Omega$$

$$A_2 = 57.1 \text{ V/V}$$


$$A_0 = A_1 \cdot A_2 = 5127.58 \text{ V/V} < 10^4 \text{ V/V}$$

* \uparrow L of PMOS devices so that $r_{up1} = r_{dn1}$ & $r_{up2} = r_{dn2}$

$$\Rightarrow r_{out1} = \frac{r_{dn1}}{2} \approx 2.9 \text{ M}\Omega ; r_{out2} = \frac{r_{dn2}}{2} \approx 185.5 \text{ k}\Omega$$


$$\Rightarrow A_1 = 156.6 ; A_2 = 100.2 \Rightarrow A_0 = 15,686 \text{ V/V} \quad \checkmark$$
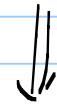
$$L_{3,4,5} = \frac{(\lambda L_{min})_p}{(\lambda L_{min})_n} \cdot L_{min} = \frac{0.1}{0.04} \times 2 = 5 \mu m$$




$$A_0 = 15,186 \text{ V/V}$$



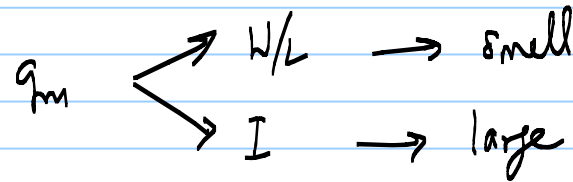
* Choose slightly shorter $L_{3,4,5}$ if parasitic cap is a concern.




Body Effect

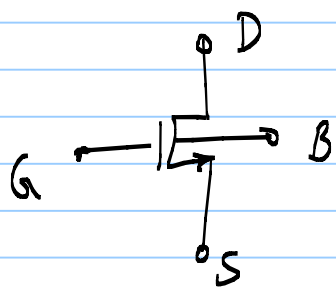
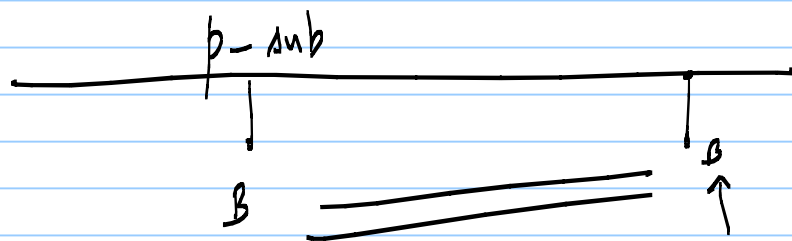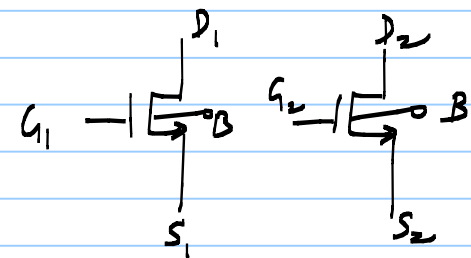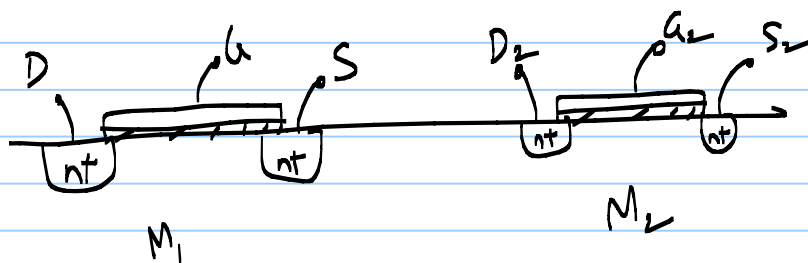
$$V_T = V_{T_0} + \gamma \left[\sqrt{2\phi_F + V_{sb}} - \sqrt{2\phi_F} \right]$$





lowest potential possible e.g. gnd

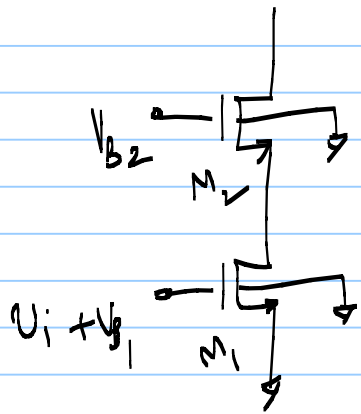


$$V_{T1} = V_{T0}$$

$$V_{T2} > V_{T0} \quad (V_{S2B} > 0)$$

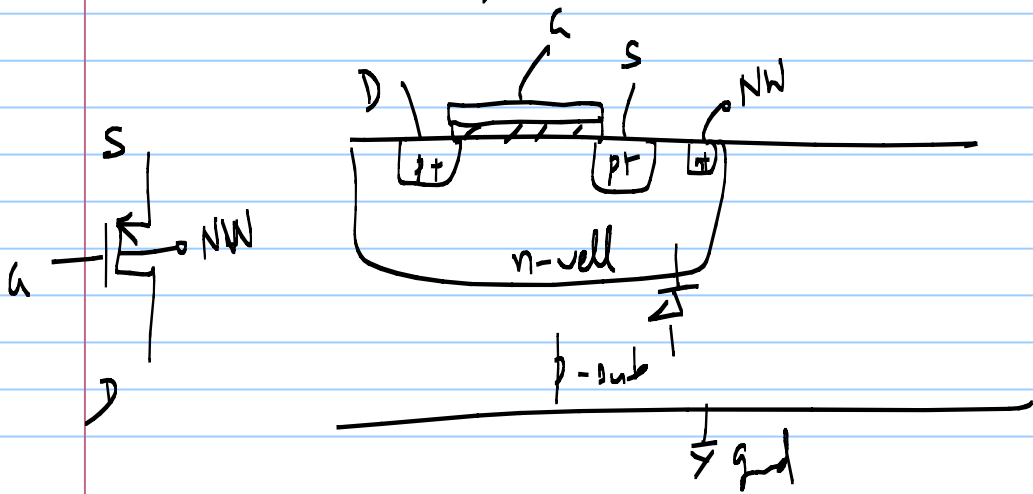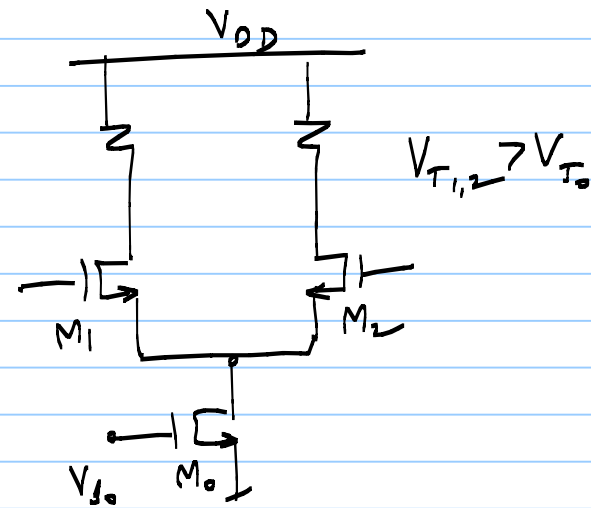

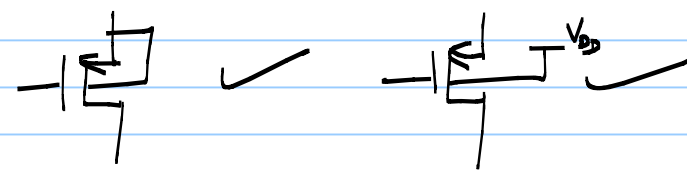$V_{nwell} > 0V \rightarrow$ well-sub diode is reverse biased.




$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

\uparrow
 g_m
 \uparrow
 r_{ds}

$$\frac{\partial I_D}{\partial V_{SB}} = -g_m \cdot \frac{\partial V_T}{\partial V_{SB}} = -\alpha g_m$$


$\alpha \ll 1$
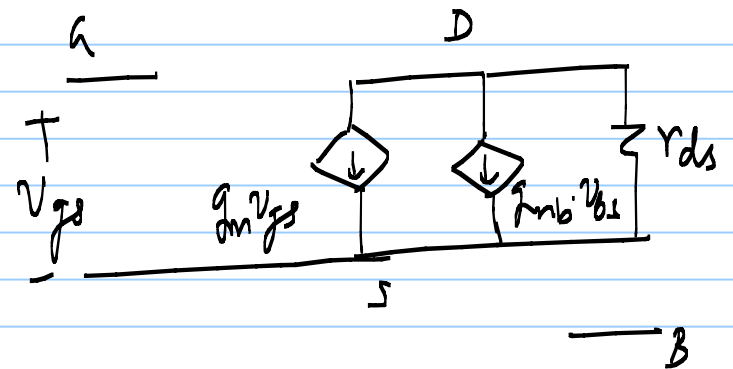
$$\frac{\partial I_D}{\partial V_{BS}} = \alpha g_m = g_{mb} \text{ or } g_{mbs}$$



Transition Frequency (ω_T or f_T)

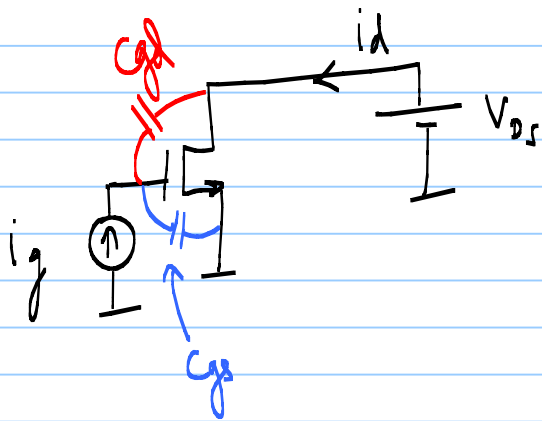* freq. at which "current gain" of device = 1 or 0 dB



freq. at which $\left| \frac{i_d}{i_g} \right| = 1$

$$v_{gs} = \frac{i_g}{sC_{gs}} ; \quad i_d = g_m v_{gs} = \frac{g_m i_g}{sC_{gs}}$$

$$\frac{i_d}{i_g}(\omega) = \frac{g_m}{j\omega C_{gs}} \Rightarrow \boxed{\omega_T = \frac{g_m}{C_{gs}}} = \frac{g_m}{C_{gs} + C_{gd}}$$



$$W_T \approx \frac{g_m}{C_{gs}} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_T)}{\frac{2}{3} W \cdot L \cdot C_{ox}}$$

$$W_T \approx \frac{3}{2} \frac{\mu_n \cdot (V_{gs} - V_T)}{L^2}$$

→ keep $L = L_{min}$. (low intrinsic gain)

→ keep $(V_{gs} - V_T) = \text{large}$ } low swing limits
 i.e. $\frac{I_D}{W} = \text{large}$

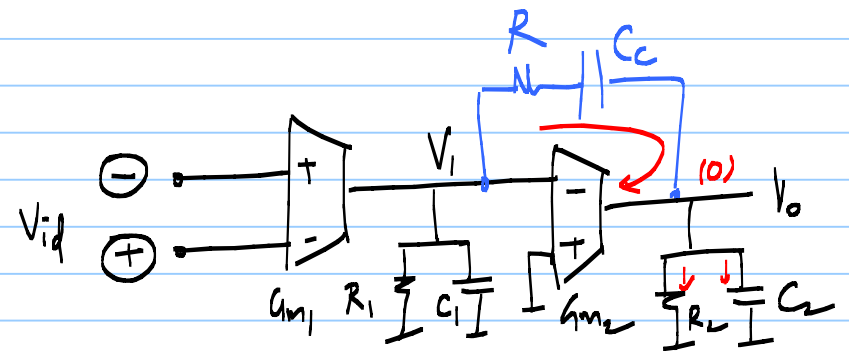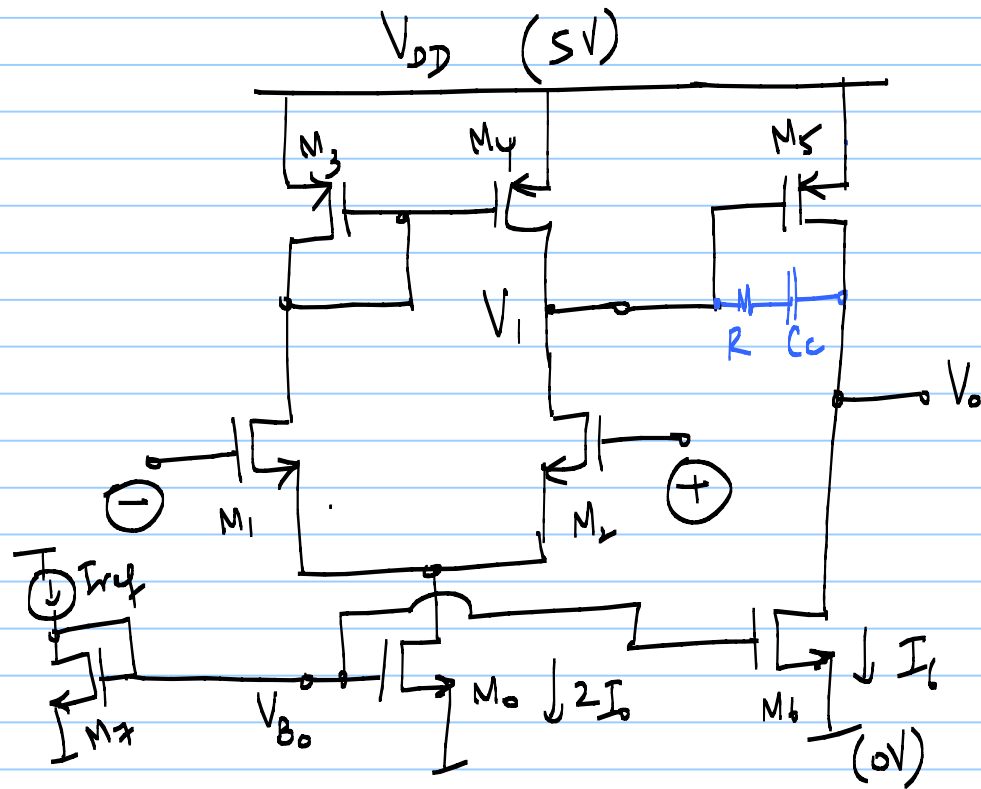
$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_T)$$



$$Z = \frac{gm_2}{C_c} \rightarrow f(R)$$

$$\omega_n = \frac{gm_1}{C_c}$$

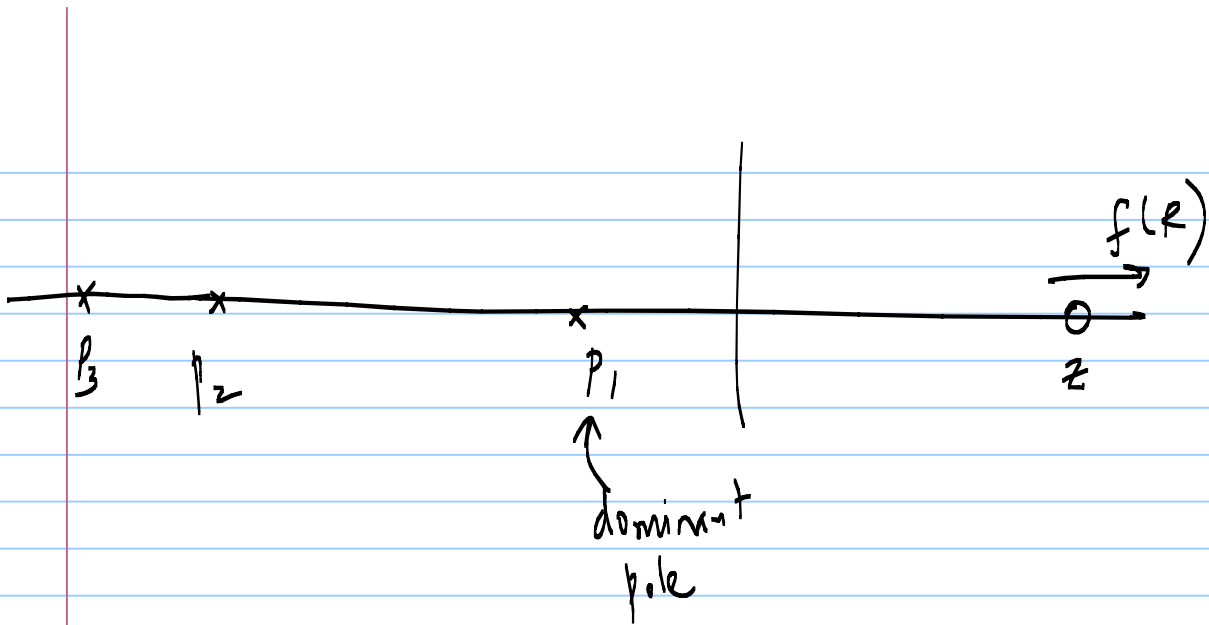\downarrow
 R changes
 phase/freq. resp.
 $\neq I_{C_c}$



HW: find out $\frac{V_o}{V_{id}}(s)$

$$\frac{V_o}{V_{id}}(s) = \frac{N(s) \leftarrow \text{degree 1}}{D(s) \leftarrow \text{degree 3}}$$

$$p_1 \approx \frac{-1}{R_1 (G_{m2} R_2) C_c}$$

$$p_2 = ?$$

$$p_3 = ?$$

(HW)


$$z = ?$$

$$G_{m2} V_1 = V_1 \cdot \frac{1}{R + \frac{1}{s C_c}}$$

$$z = \frac{1}{C_c \left(\frac{1}{G_{m2}} - R \right)}$$

16/11/23

Lec 21

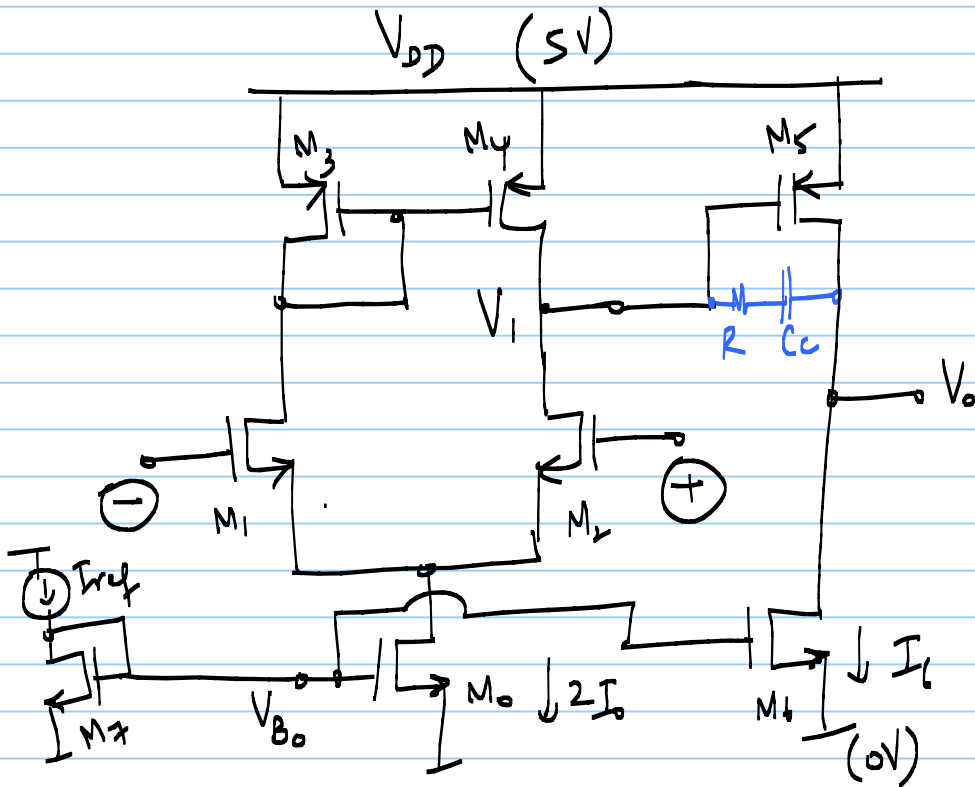


$$p_1 \approx \frac{-1}{R_1 \cdot (G_{m2} R_L) C_c} = p_d$$

$$z = \frac{+1}{C_c \left(\frac{1}{G_{m2}} - R \right)} = f(R)$$

$$p_2 \approx \frac{-G_{m2}}{(C_1 + C_2 + \dots)} = f(G_{m2})$$

$$p_3 \approx \frac{-1}{R(C_1 || C_2)}$$

$$\omega_u = \frac{G_{m1}}{C_c}$$

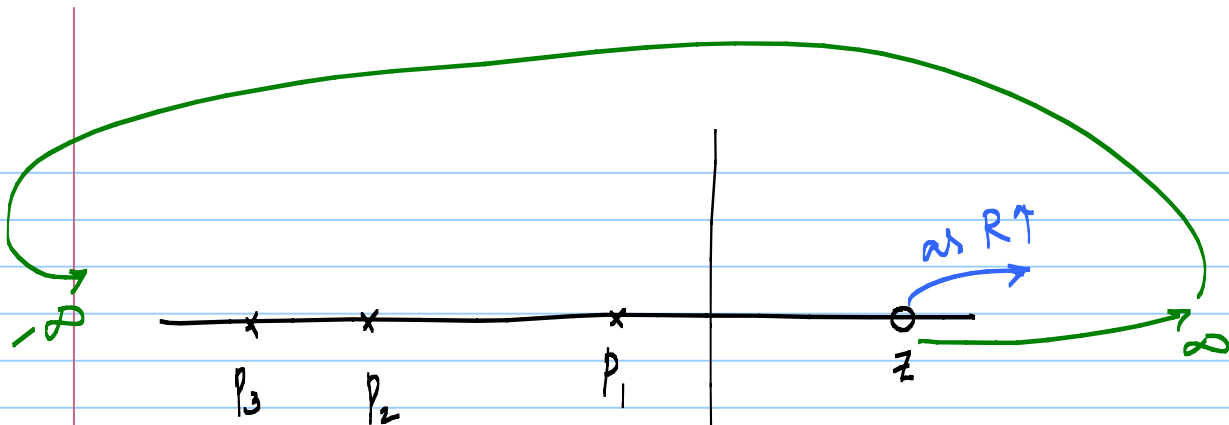


as $R \uparrow \rightarrow \left(\frac{1}{G_{m2}} - R \right)$ reduces

1) Set $R = \frac{1}{G_{m2}} \Rightarrow z = \infty$

$\hookrightarrow p_3$ limits phase margin
(apart from p_2)

2) Set $R > \frac{1}{G_{m2}} \rightarrow z$ moves into LHP

(from $-\infty$)

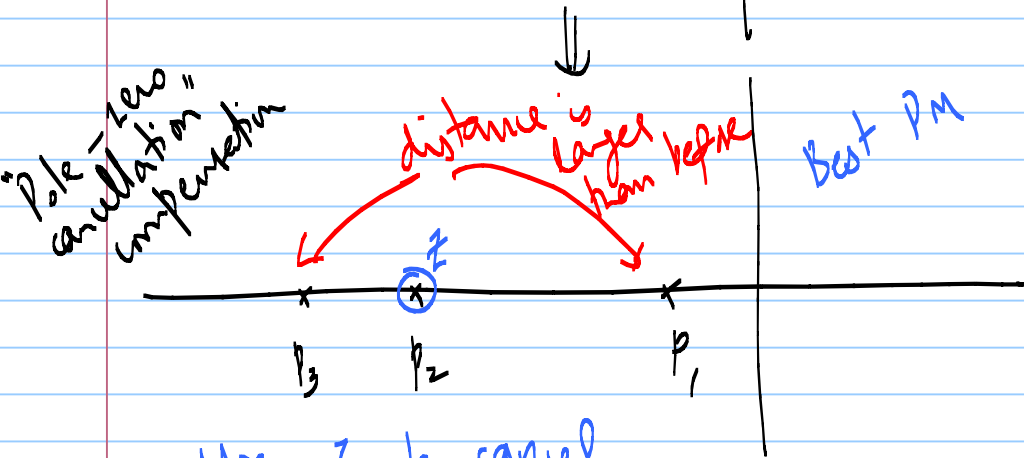

Pole-zero cancellation = imperfection

distance is larger than before


Best PM

Use z to cancel first ND pole


$R = f(G_{m2}) = f(g_{ms})$


$$p_z = f(g_{ms})$$

You want $R = f(g_{ms})$

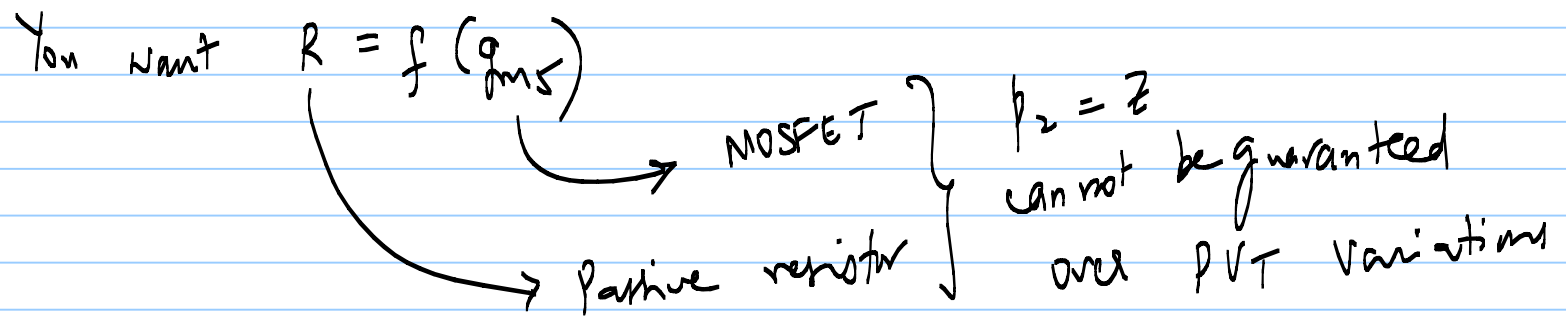

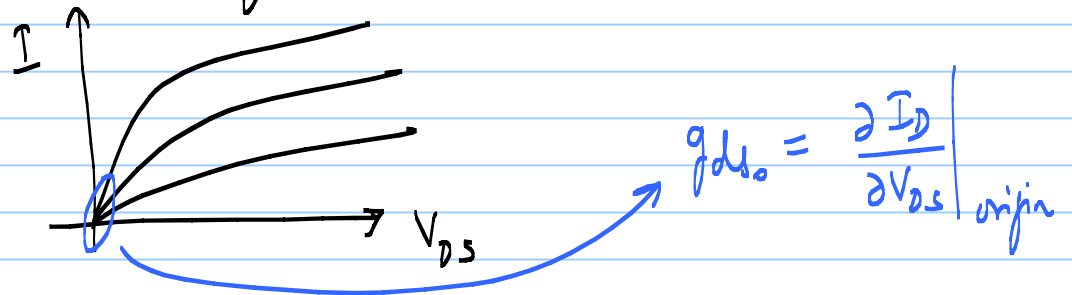1) Use a MOSFET in triode region to create R



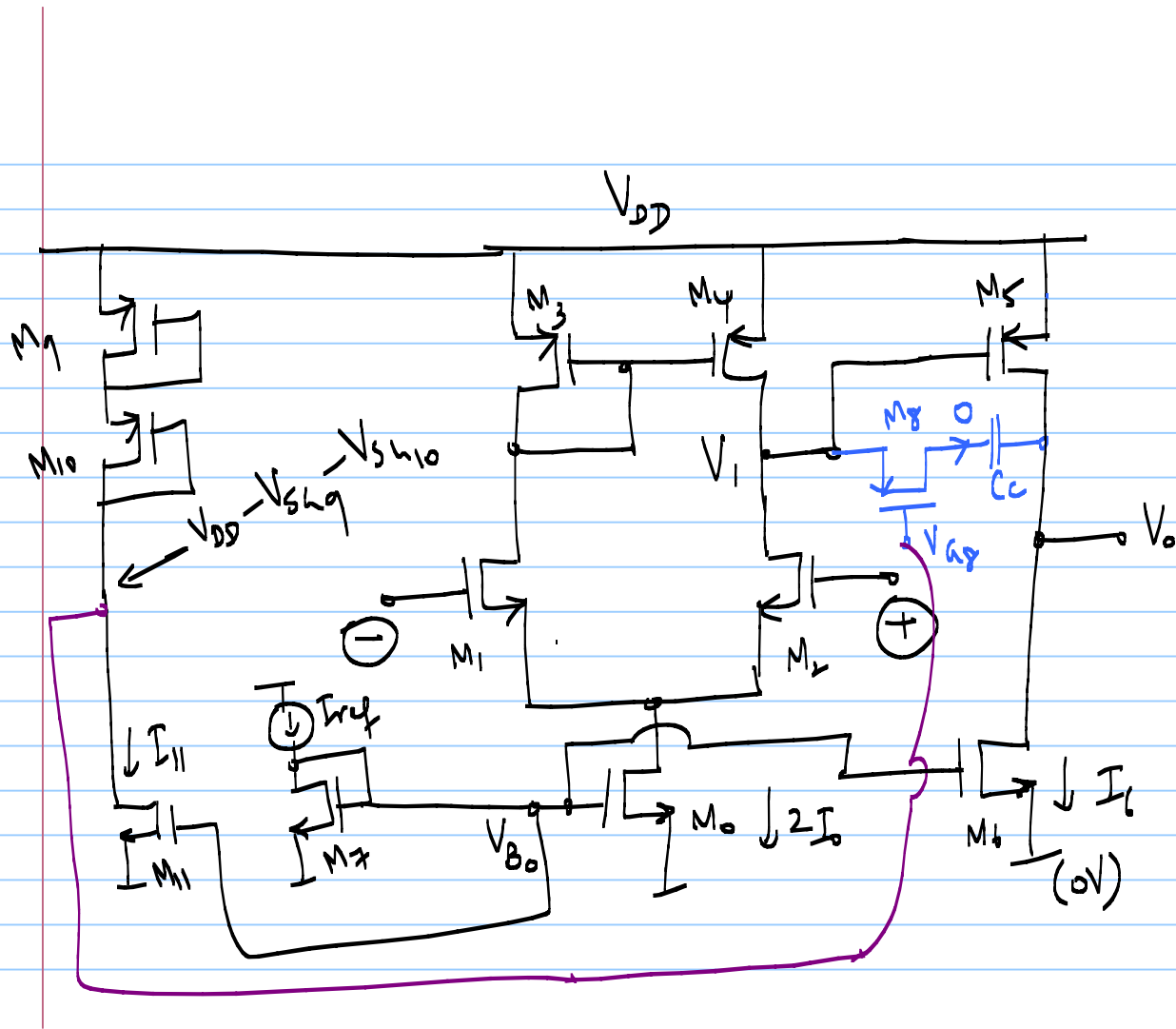

$$I_{D_{S_8}} = 0$$

Need: $V_{G_8} = V_{DD} - V_{S_{G_5}} - V_{S_{G_8}}$

Set $V_{G_8} = V_{DD} - V_{S_{G_9}} - V_{S_{G_{10}}}$

* Set $\frac{I_{D_1}}{(W/L)_9} = \frac{I_{D_6}}{(W/L)_5}$

$$\Rightarrow V_{S_{G_9}} = V_{S_{G_5}}$$

$$\Rightarrow \boxed{V_{S_{G_8}} = V_{S_{G_{10}}}$$

Issue: $M_g \Rightarrow$ linear
 $M_{i0} \Rightarrow$ saturation


$$I_{Dg} = \mu_p C_{ox} \left(\frac{W}{L}\right)_g \left[(V_{SGg} - V_{Tp})(V_{SDg}) - \frac{V_{SDg}^2}{2} \right]$$

$$g_{ds_g} \Big|_{V_{SD}=0} = \mu_p C_{ox} \left(\frac{W}{L}\right)_g \left[V_{SGg} - V_{Tp} - V_{SDg} \right] \Big|_{V_{SD}=0}$$

$$g_{ds_g} = \mu_p C_{ox} \left(\frac{W}{L}\right)_g (V_{SGg} - V_{Tp}) = \underbrace{\mu_p C_{ox} \left(\frac{W}{L}\right)_g (V_{SGi0} - V_{Tp})}_{\propto g_{m_{i0}}}$$

$$\Rightarrow g_{ds} \propto g_{m10}$$
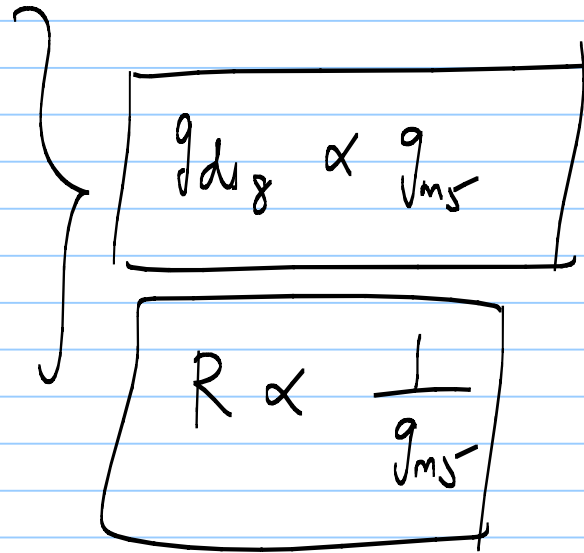
$$g_{m10} \propto g_{m5} \left\{ I_{11} \propto I_0 \right\}$$



Set R

so that
 $z = 1/2$


2) Use a passive Resistor R

Ensure that g_{m5} tracks $\frac{1}{R}$

$$g_{m5} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_5 I_{D5}}$$

$$g_{m5} \begin{cases} \rightarrow I_{D5} \leftarrow \propto \frac{1}{R^2} \\ \rightarrow \left(\frac{W}{L}\right)_5 \leftarrow \text{fixed} \end{cases}$$

"constant g_m "
reference

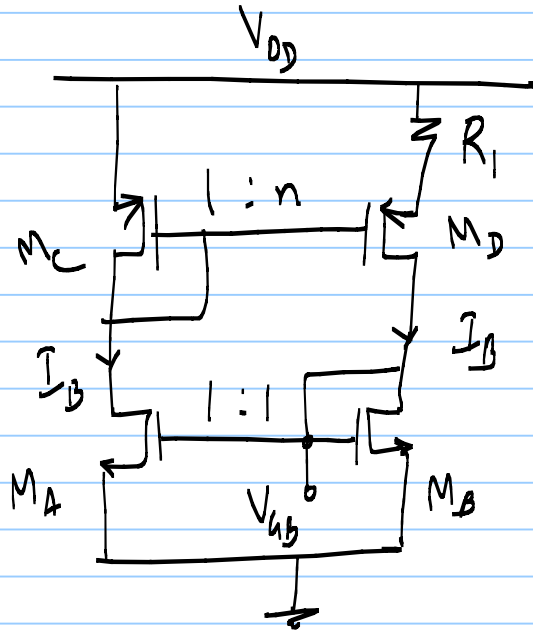

$$M_A : M_B = 1 : 1 \Rightarrow I_{DA} = I_{DB} = I_B \\ = I_C = I_D$$

$$\left(\frac{W}{L}\right)_D = n \left(\frac{W}{L}\right)_C$$

$$(V_{SGC} - V_{TP}) = \sqrt{n} (V_{SGD} - V_{TP})$$

$$V_{SGC} = V_{SGD} + I_B \cdot R_1$$

$$\rightarrow (V_{SGC} - V_{TP}) = (V_{SGD} - V_{TP}) + I_B R_1$$

$$\frac{2I_B}{g_{mc}} = \frac{1}{\sqrt{n}} \cdot \frac{2I_B}{g_{mc}} + I_B R_1 \quad \rightarrow \quad I_B = 0 \text{ is one solution}$$

This circuit needs a startup circuit

$$\underline{I_f \quad I_B \neq 0:}$$

$$\frac{2}{g_{mc}} = \frac{2}{\sqrt{n} g_{mc}} + R_1$$


$$\frac{2}{g_{mc}} \left(1 - \frac{1}{\sqrt{n}}\right) = R_1 \Rightarrow$$

$$g_{mc} = \frac{2}{R_1} \left(1 - \frac{1}{\sqrt{n}}\right)$$

$$g_{mc} \propto \frac{1}{R_1}$$

* Use this to bias the opamp

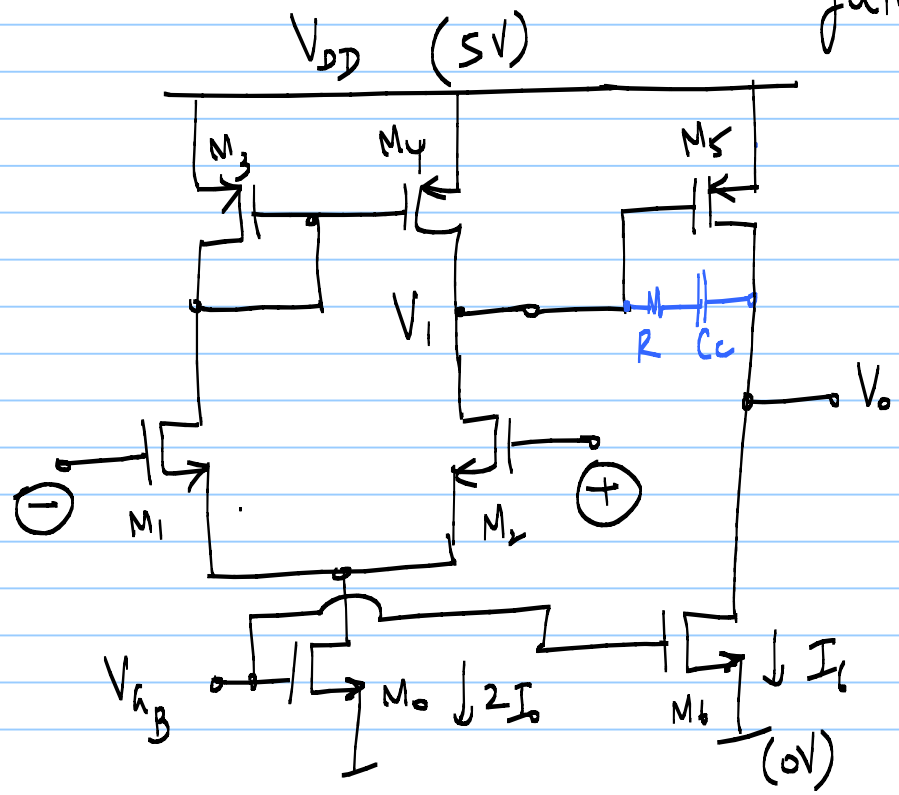gate of $M_3 \rightarrow$ biases M_0 & M_6
 \nearrow 1st stage \nearrow 2nd stage



$$I_b \propto I_B \propto \frac{1}{R_1^2}$$




$$I_{MS} \propto \frac{1}{R_1}$$


set R & R_1 to be same type of resistor

21/11/2023

Lec 22


Fully Differential Opamps

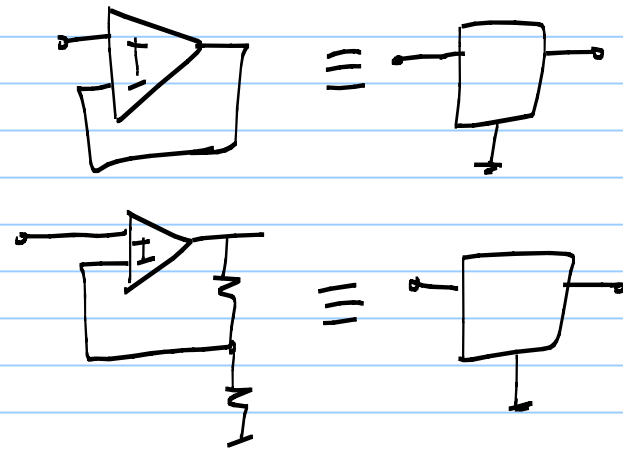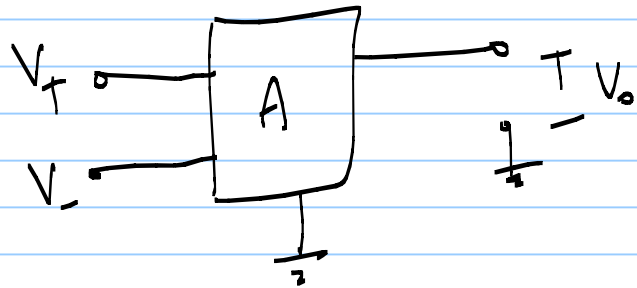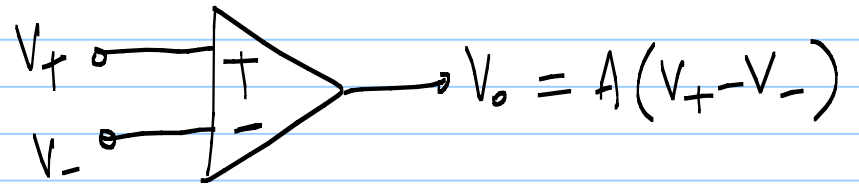

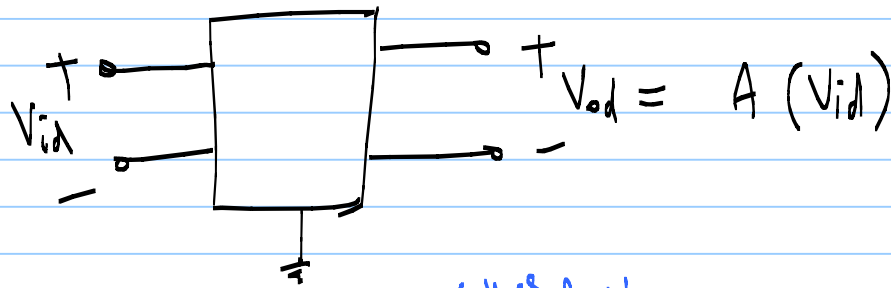


$$V_{od} = A (V_{id})$$

1)



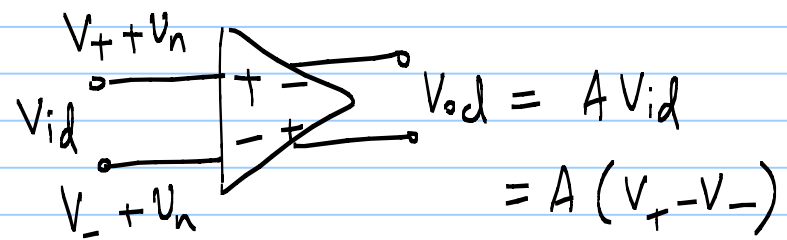




CM noise immunity


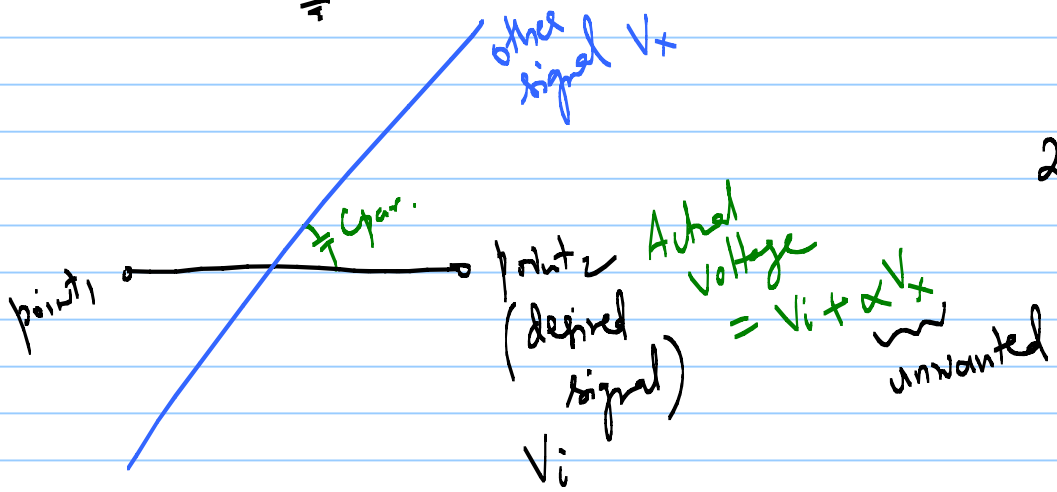


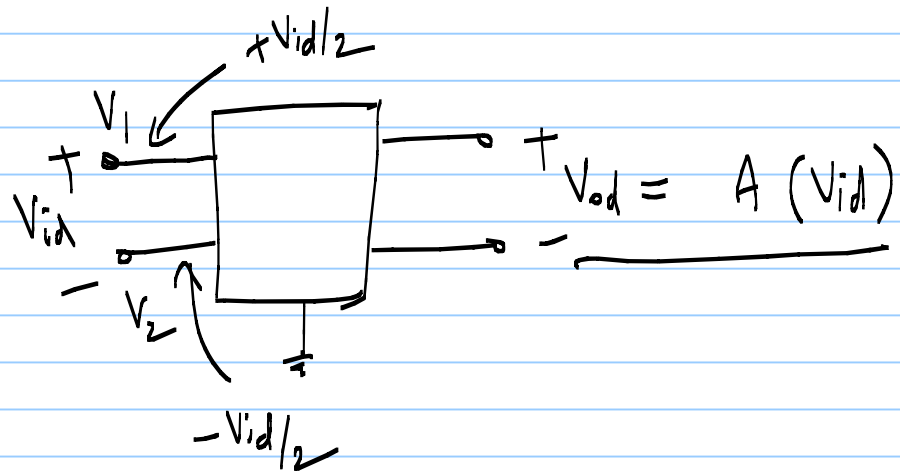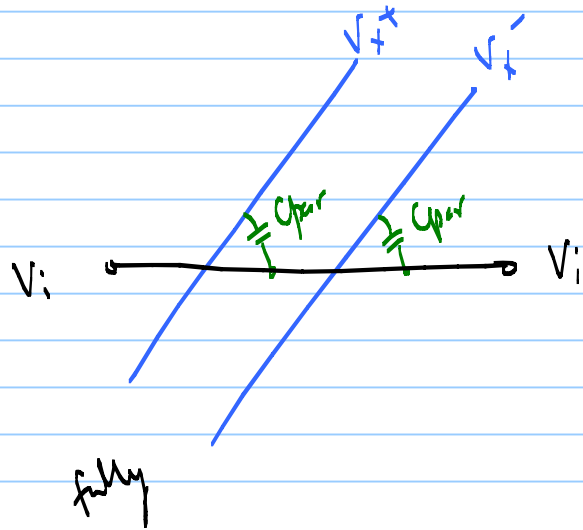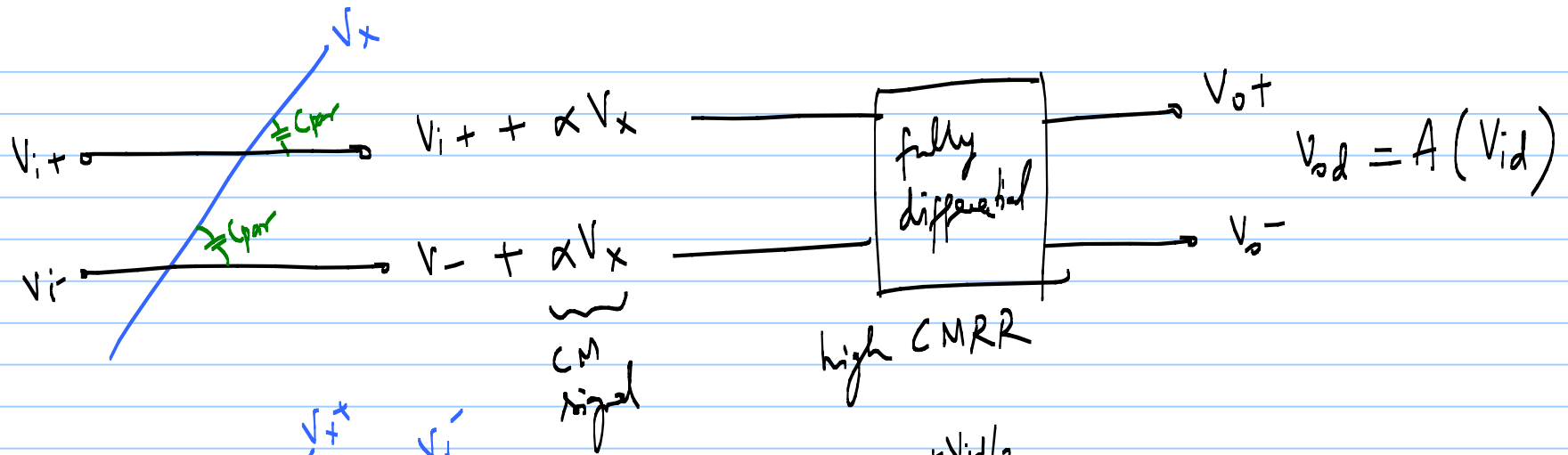2)

Not referred explicitly to gnd
 $(V_+, V_-, V_{o+}, V_{o-})$
 (processed differentially)




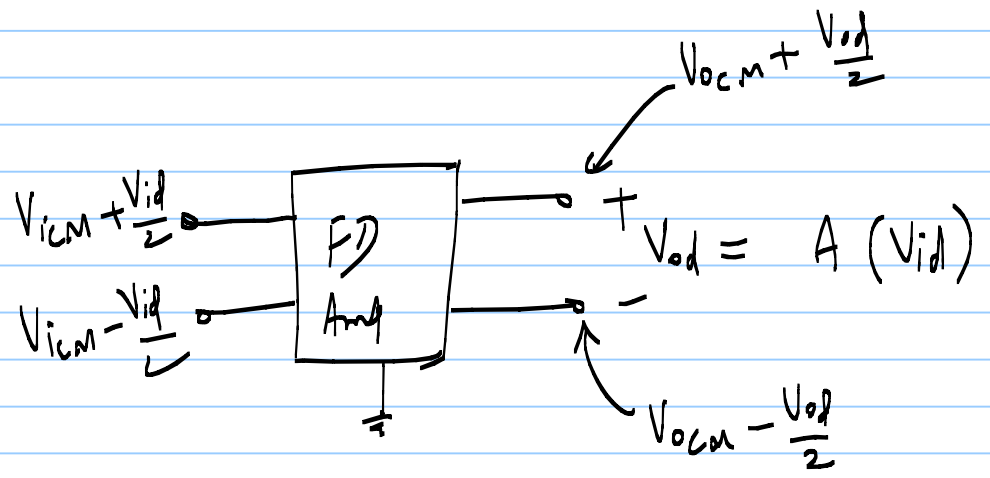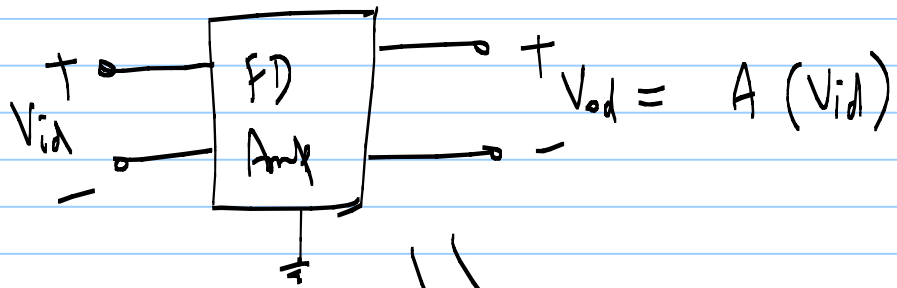



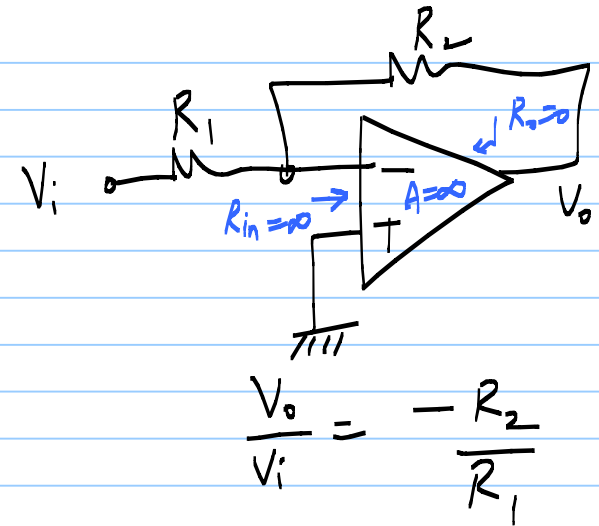
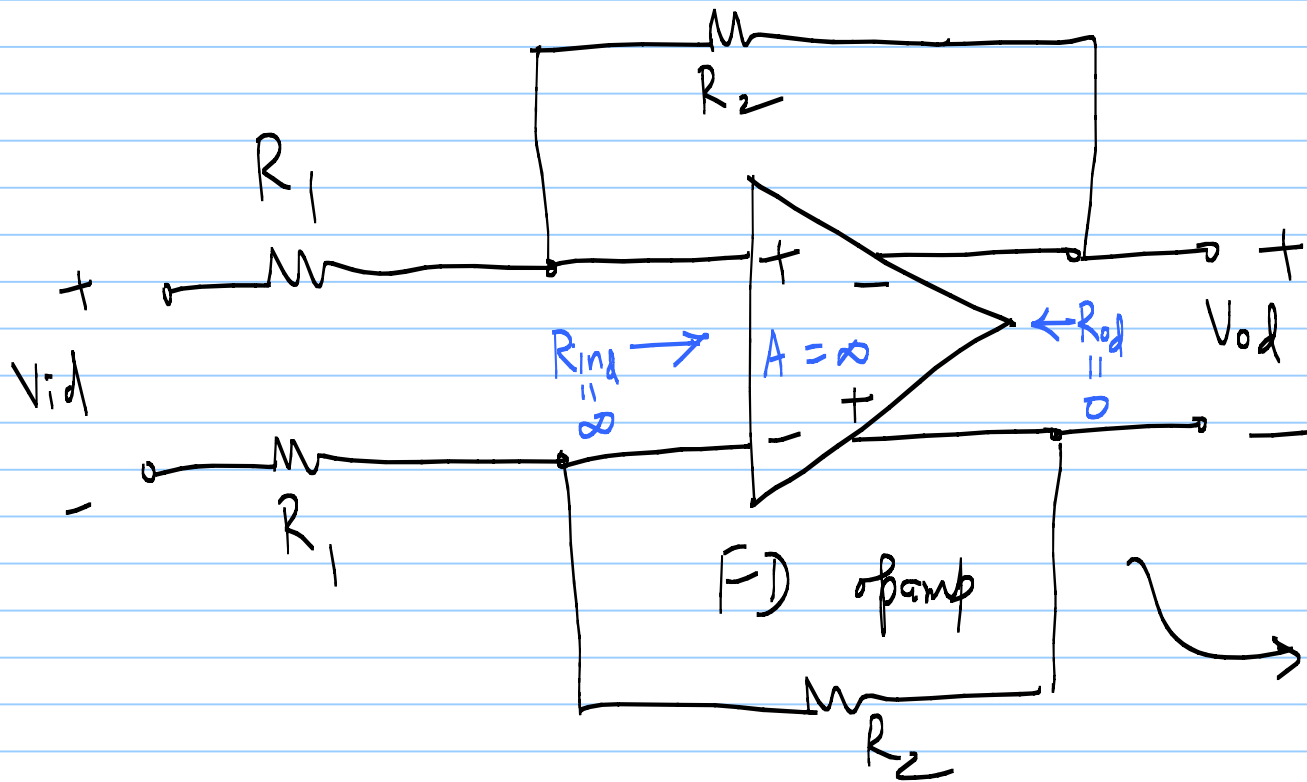


$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$


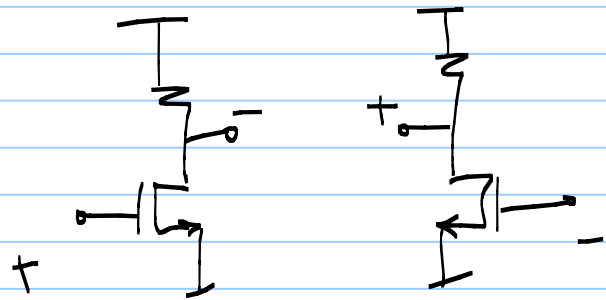
$$\frac{V_{od}}{V_{id}} = -\frac{R_2}{R_1}$$



pseudo differential amplifier

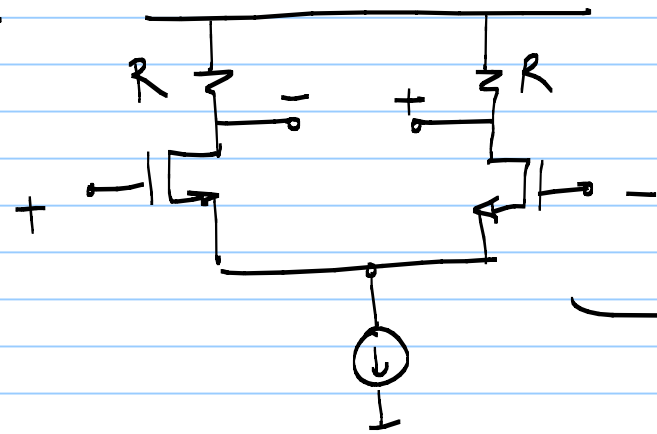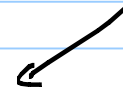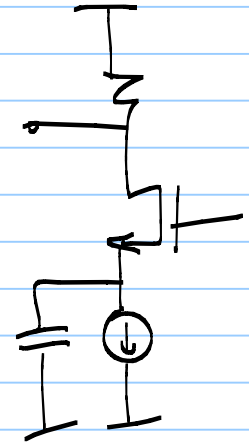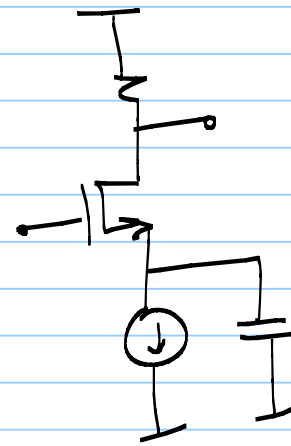


active load

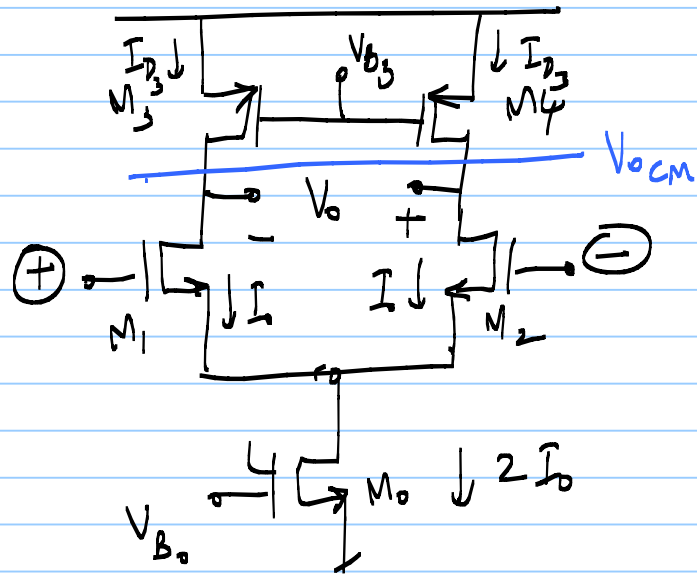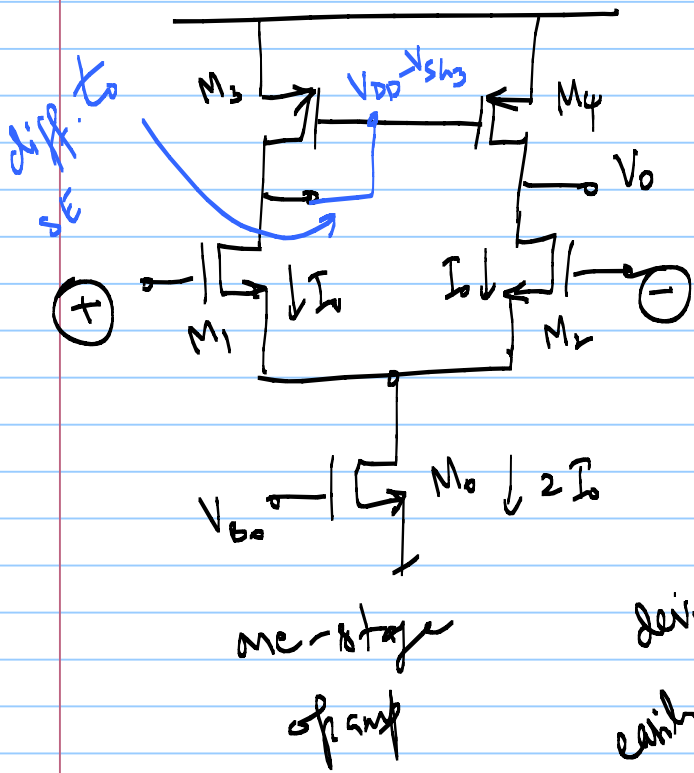

devices can
easily move out of
saturation

fully differential
one-stage op-amp

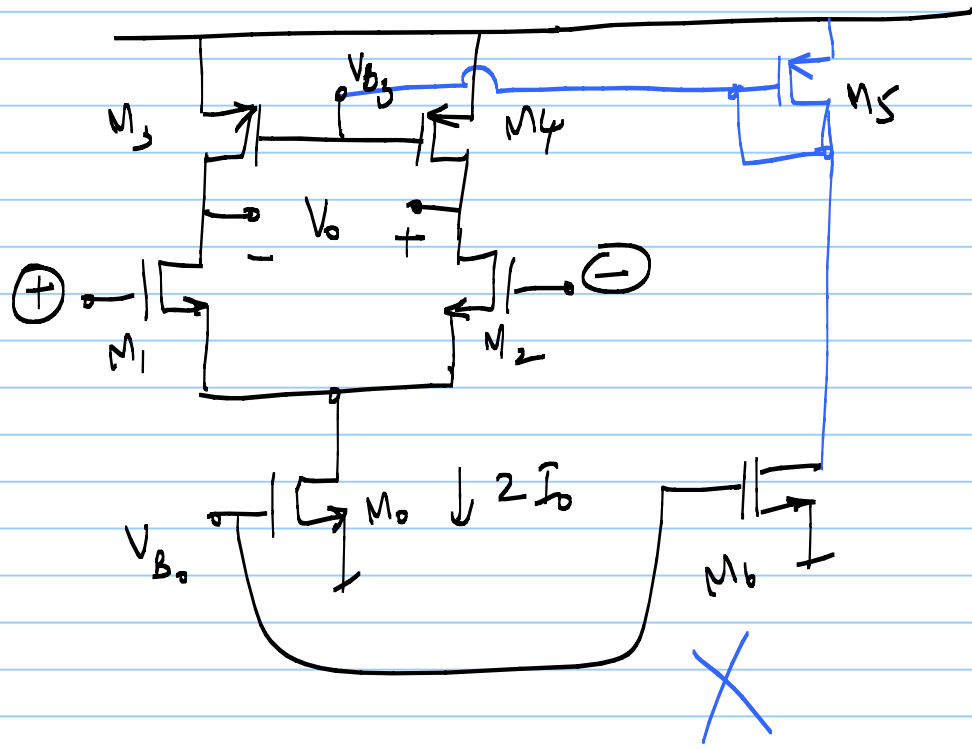- 1) Set V_{B3} so that $I_{D3} = I_0$
- 2) $V_{ocm} = ?$
undefined
- 3) What happens if V_{b3} varies, or $V_{T3,4}$ changes etc.?
 $\Rightarrow I_{D3} \neq I_0$
 $I_{D3} > I_0 \Rightarrow V_{ocm} \uparrow$
 $I_{D3} < I_0 \Rightarrow V_{ocm} \downarrow$




* V_{DS} mismatches are still an issue

* $V_{O,cm}$ is still ill-defined

⇒ Set $V_{O,cm}$ so that all devices are in saturation

↳ Negative f.b. → 1) Sense $V_{O,cm}$
 2) Compare w/ $V_{O,cm}$ desired

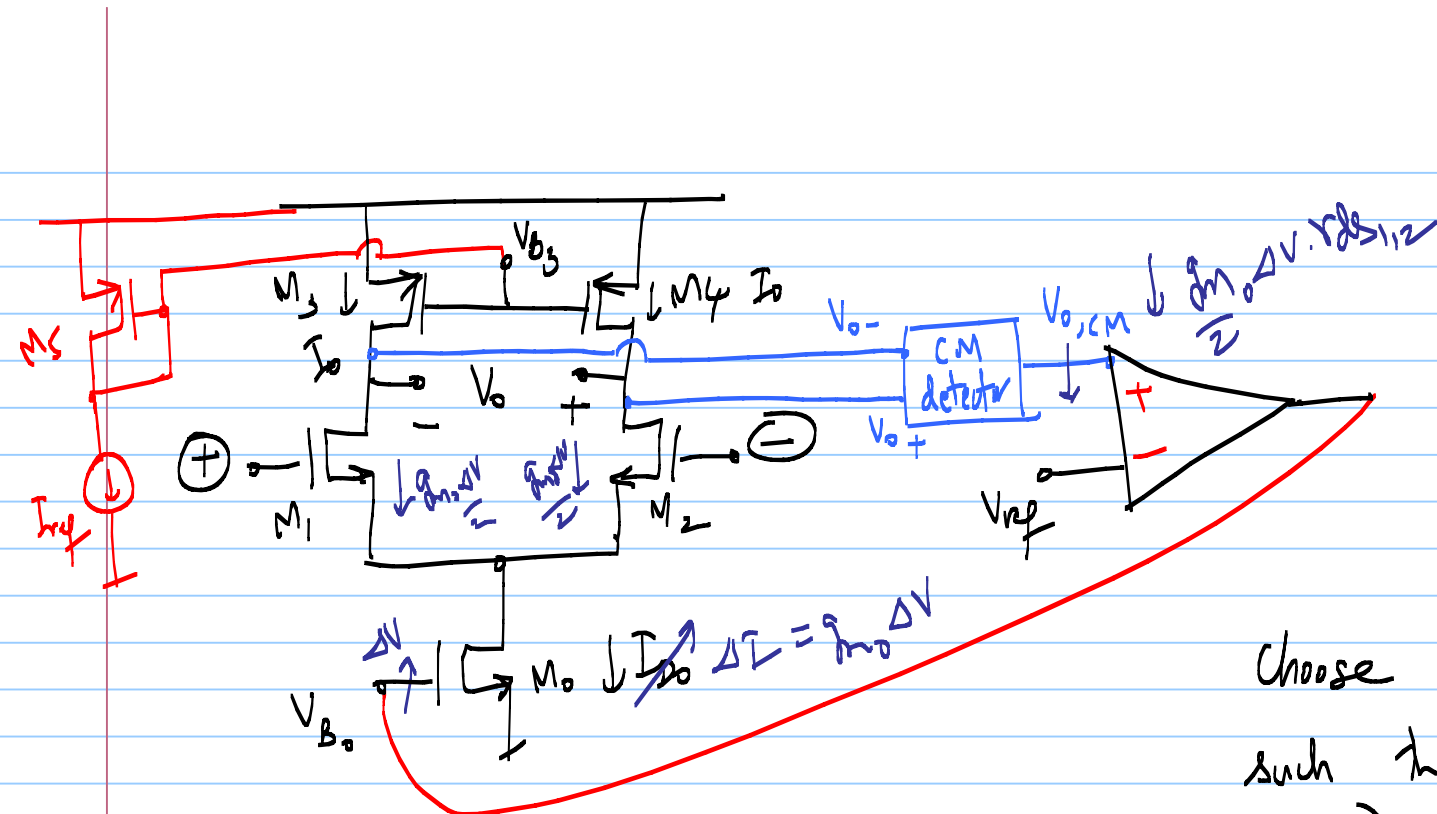3) Drive actual $V_{O,cm} \rightarrow V_{O,cm}$ (desired)



Set V_{b3} independently }
 Set V_{b0} via neg. f.b. }

$\Delta I = g_{m0} \Delta V$

$$V_{o+} = V_{0,cm} + \frac{V_{od}}{2}$$



$$V_{o-} = V_{0,cm} - \frac{V_{od}}{2}$$

Choose $V_{0,cm}$ (desired) = V_{ref}
 such that all devices are in sat. AND
 e.g. 1) Max output signal swing
 2) Set by V_{icm} of next stage

23/11/2023

Lec 23

Circuit # 1

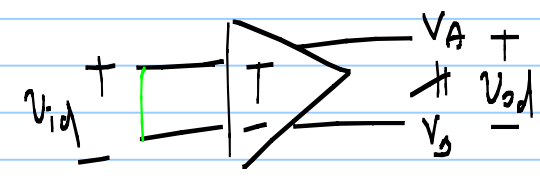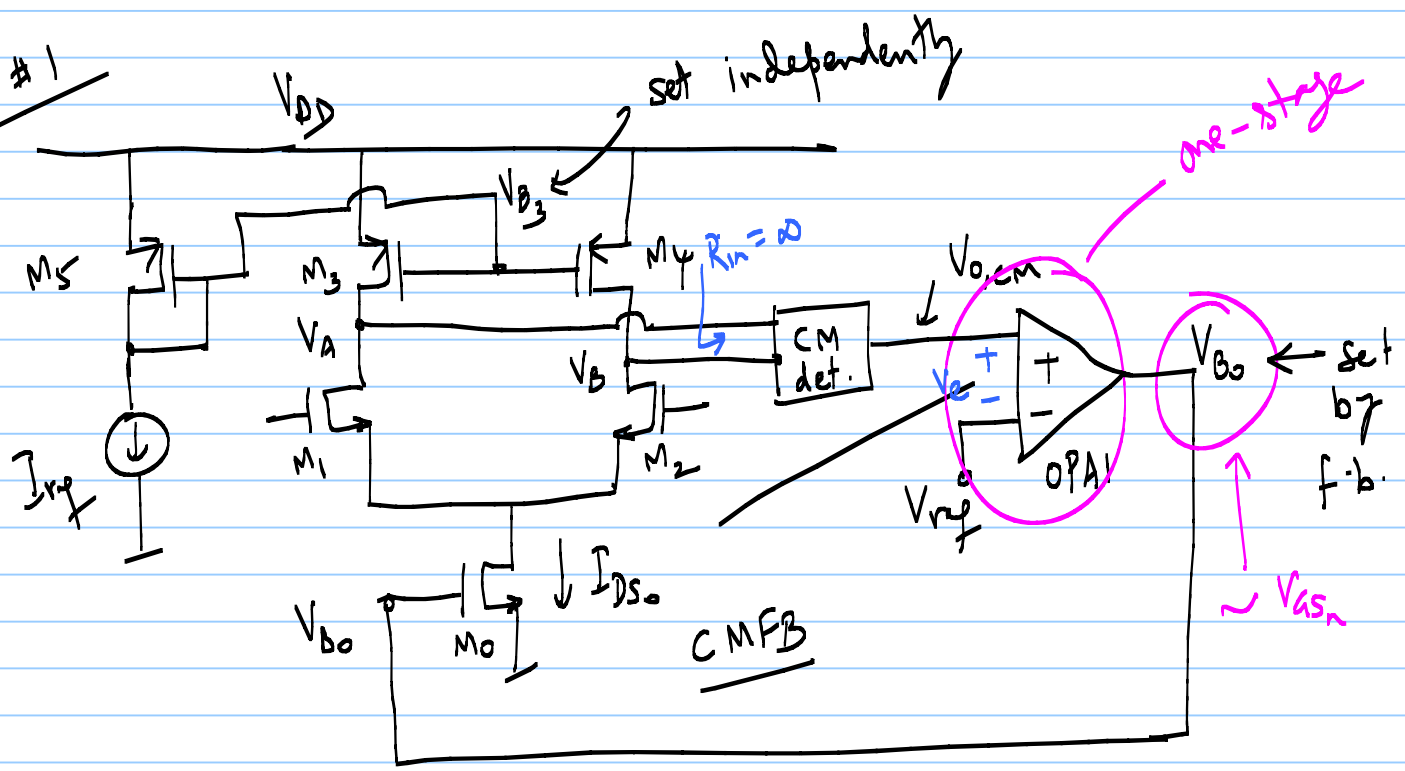

* CMFB
 = common-mode
 feedback

* Steady State:

$$V_{o,cm} = V_{ref}$$

* errors \rightarrow finite A_o
 finite V_{os}

* ICMR of OPA1 needs to include V_{ref} by design

→ $V_{Bo} \sim V_{Asn}$

→ OPA1 OCMR needs to cover $\sim V_{Asn}$ (low)



* OPA1 → one stage opamp → 2-stage loop → adequate gain in most cases

* OCM_{low} of OPA1 \Leftrightarrow ICM of OPA1

OPA1 with NMOS input pair → $OCM_{low} = ICM - V_{Tn}$
 $= V_{o,icm} - V_{Tn}$

OPA1
with PMOS
pair input

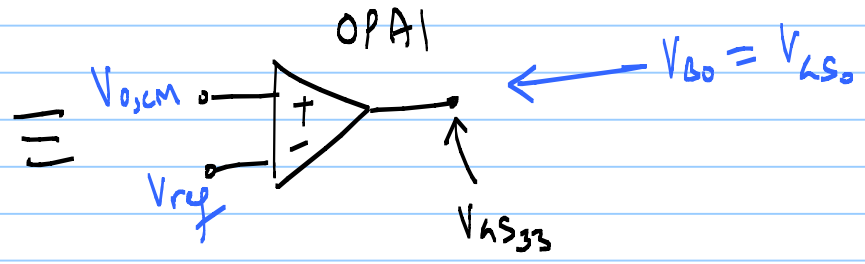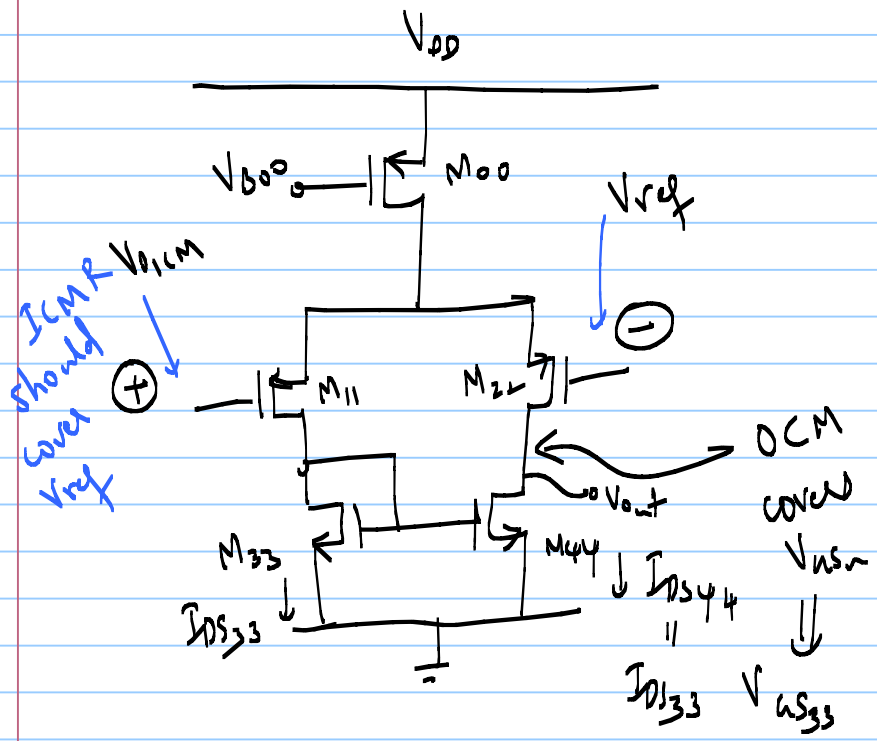← { may not be low
enough to cover V_{Bo}



If $V_{LS33} \neq V_{DD}$

e.g. $V_{LS33} < V_{DD} \Rightarrow$ mismatch inside OPA1


* Design OPA1

so that: $V_{LS33} = V_{LS0} = V_{DD}$

$$L_{33} = L_{44} = L_0$$

$$\frac{I_{D33}}{(W/L)_{33}} = \frac{I_{D50}}{(W/L)_0}$$

* CM detector

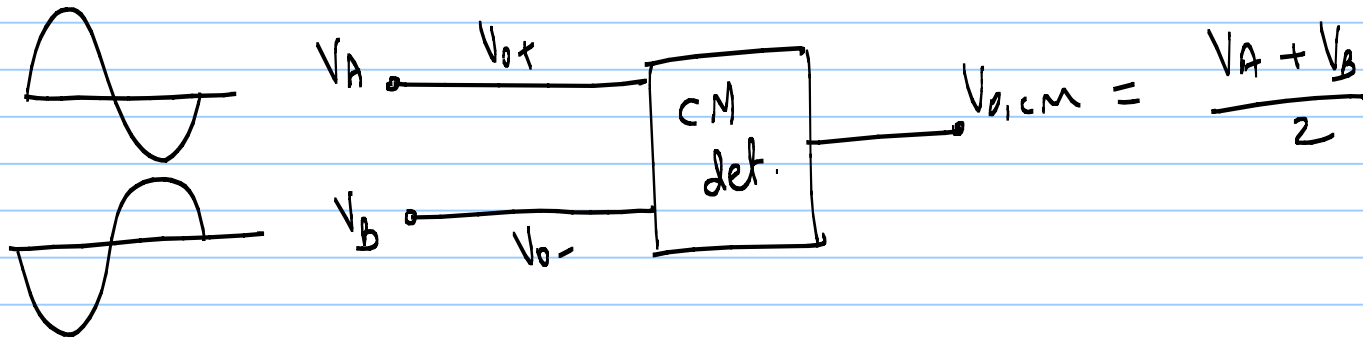

- 1) $Out = \text{avg. of inputs}$
 2) Linear in the presence of FD swings @ V_A & V_B


Circuit #1 : FD one-stage opamp

- * $\frac{V_{od}}{V_{id}}$ = gain for 1-stage
- * Don't want resistive loads ✓
- * V_A & V_B have large swings ✓

- active circuit with MOSFETs
- 3) $R_{in,CM} = \infty$
 So that $\frac{V_{od}}{V_{id}}$ of FD opamp is not affected

For circuit #1

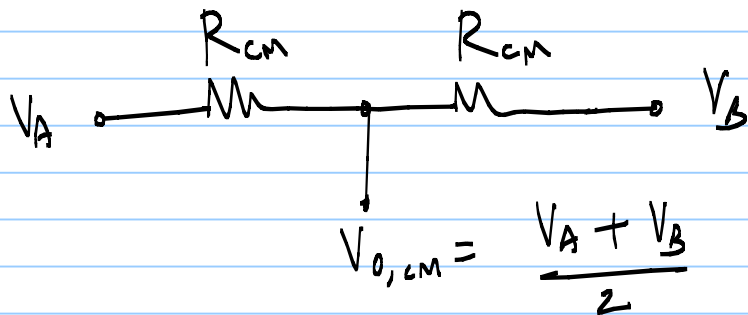- 1) Choose fully passive CM det.
- 2) Choose R_{in} as high as possible
- 3) Deal with effects of large R_{in}




\Rightarrow Resistive CM detector
perfectly linear
(if R's are linear)

$\rightarrow R_{CM}$ as high as possible

e.g. $R_{CM} = 10 \times R_{out}$ of FD op-amp

28/11/23

Lec 24

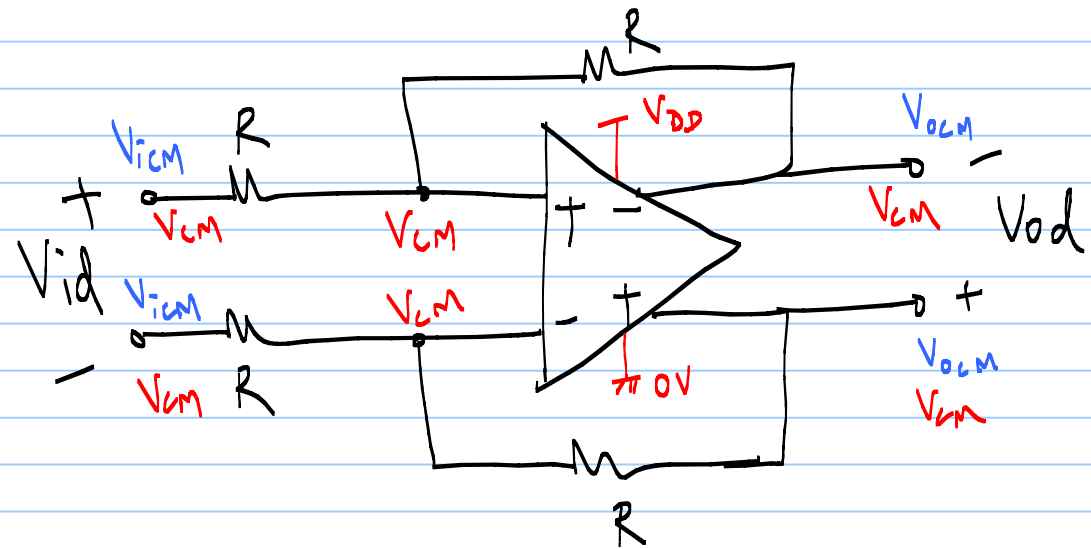


* V_{icm} , V_{ocm} etc. need to be set carefully

* Need to have all devices in saturation

* Need to satisfy the opamp $ICMR$ & $OCMR$


e.g. choose $V_{icm} = V_{ocm} = V_{cm}$

V_{cm} needs to satisfy $ICMR$ & $OCMR$

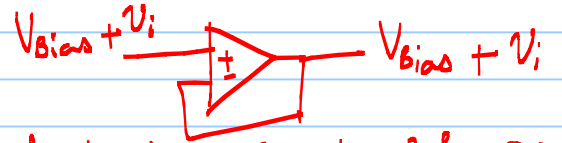

V_{bias} needs to be in $ICMR$ & $OCMR$



Circuit # 1

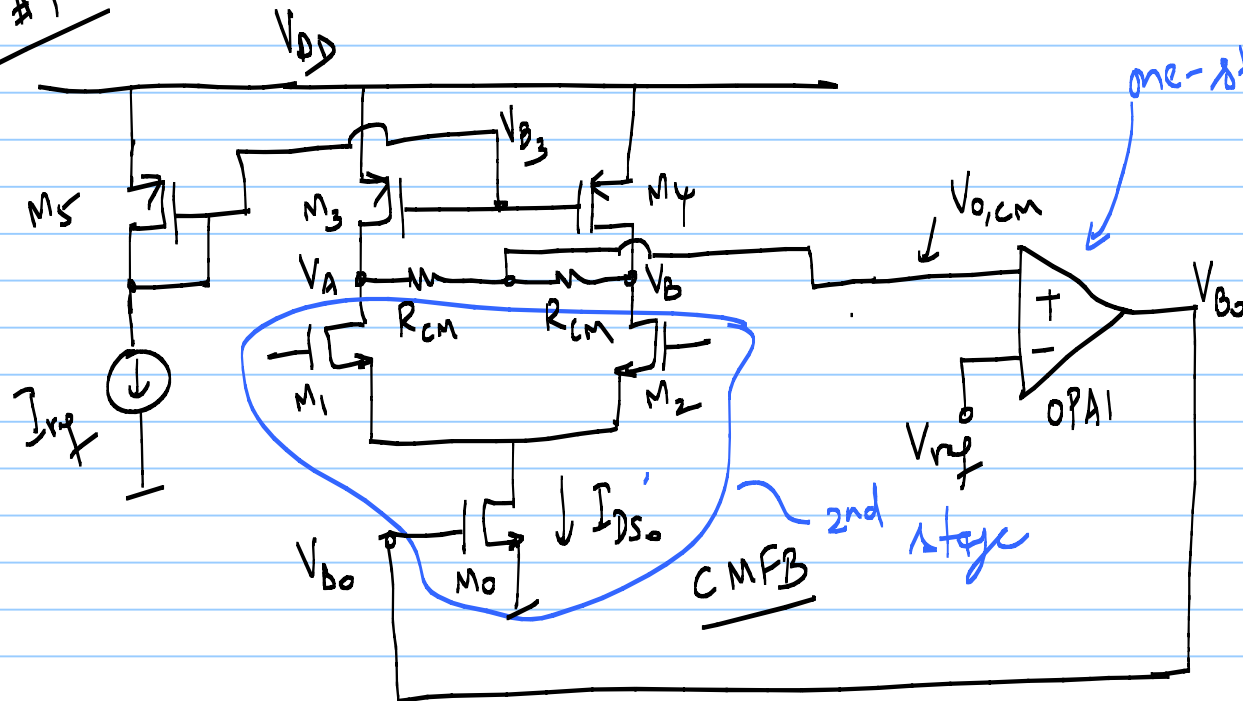


one-stage opamp


* 2-stage loop

CMFB 2nd stage

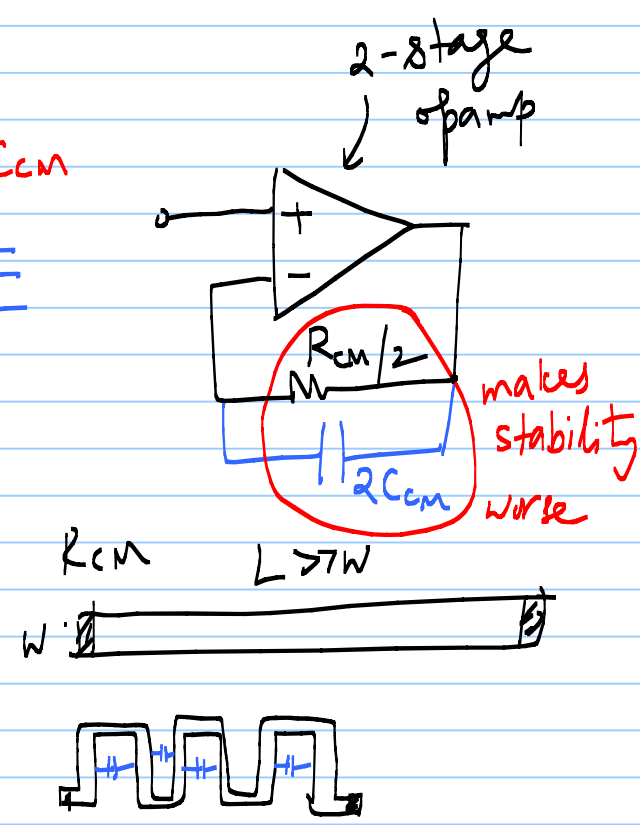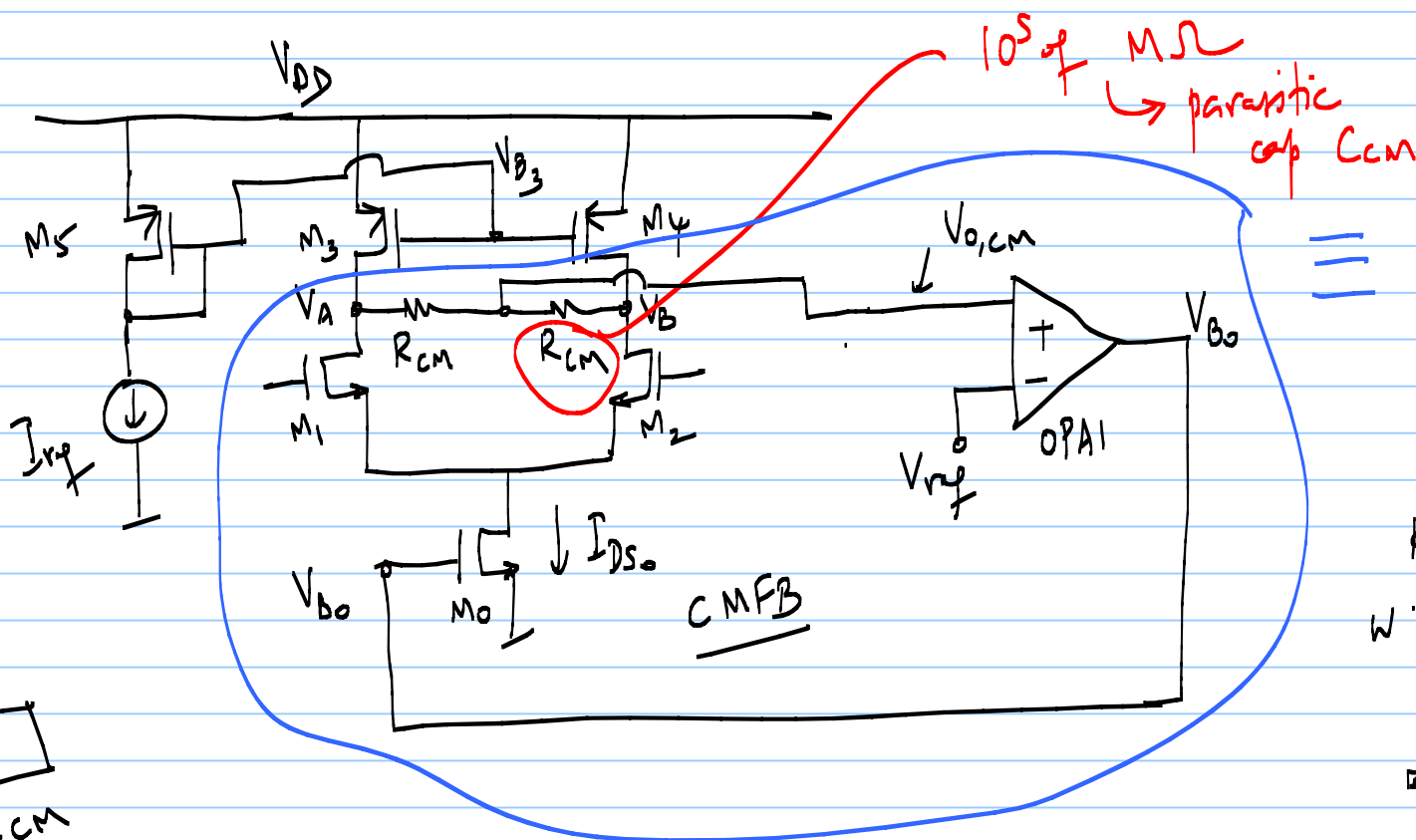

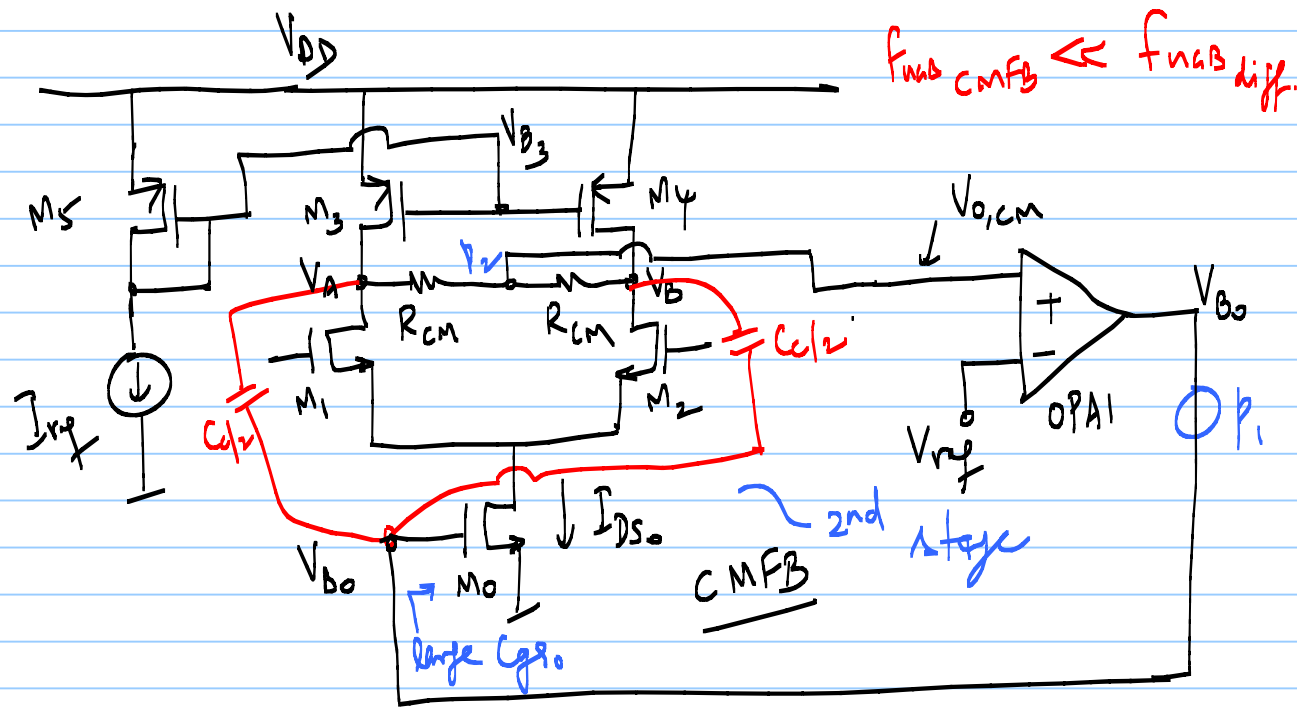

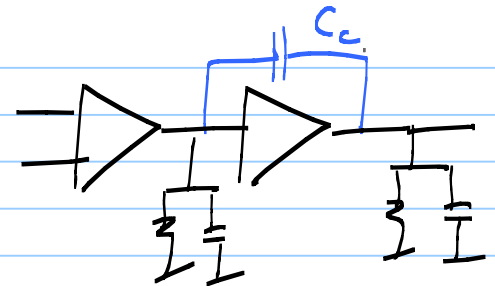$f_{\text{stab CMFB}} \ll f_{\text{stab diff.}}$




$p_1 \ll p_2$

$M_0 \rightarrow$ large L
 due to 1) good CMRR
 2) $I_{D_{S0}}$ indep of V_{icm}
 \rightarrow large w/L to achieve low $V_{icm_{min}}$

Choose C_c so that CMFB loop has good PM

Circuit #2

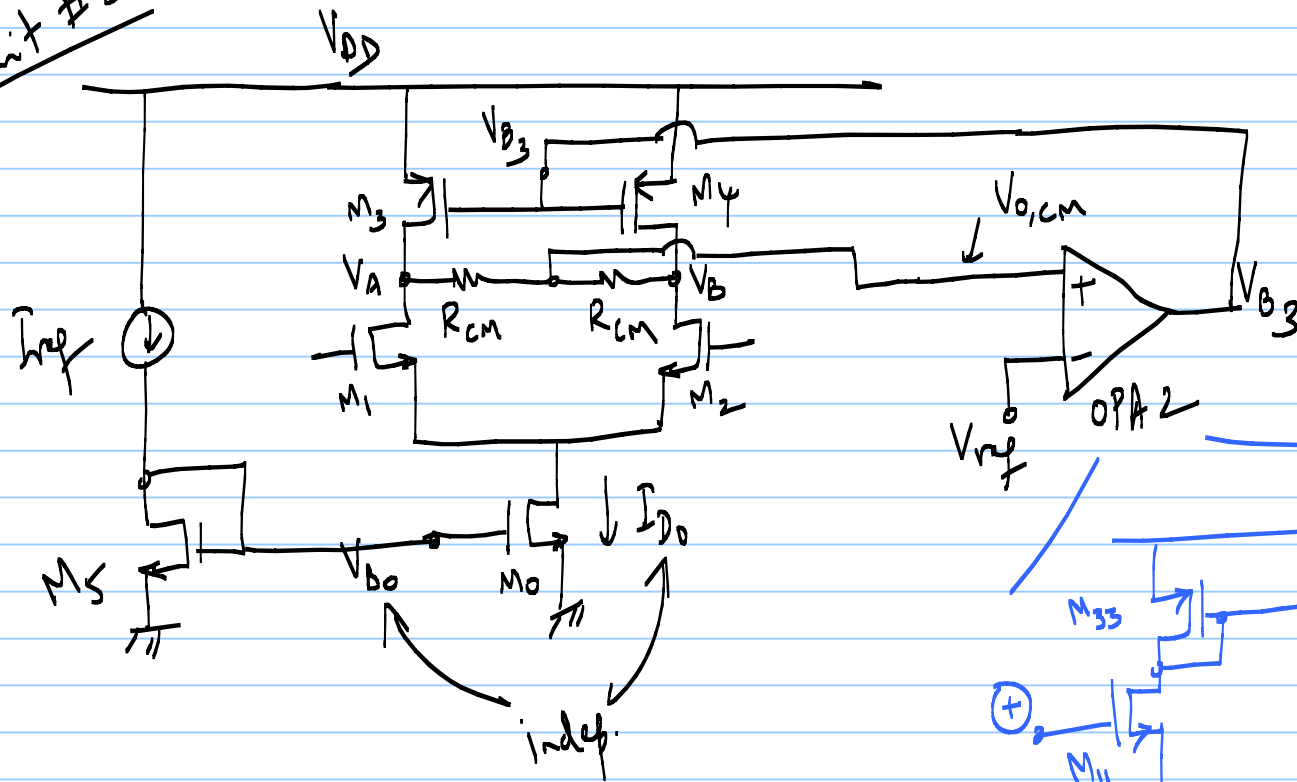


$$* V_{o,cm} = V_{ref}$$


$$\hookrightarrow I_{D3} = I_{D4} = \frac{1}{2} I_{D0}$$

$$* V_{S_{f33}} = V_{S_{f3,4}}$$

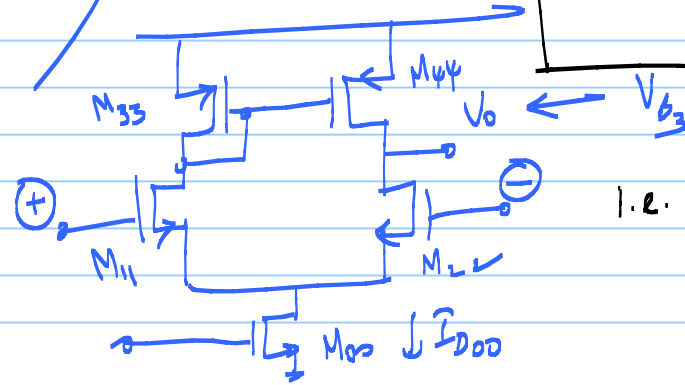
$$\hookrightarrow \frac{I_{D33}}{(W/L)_{33}} = \frac{I_{D3,4}}{(W/L)_{3,4}}$$




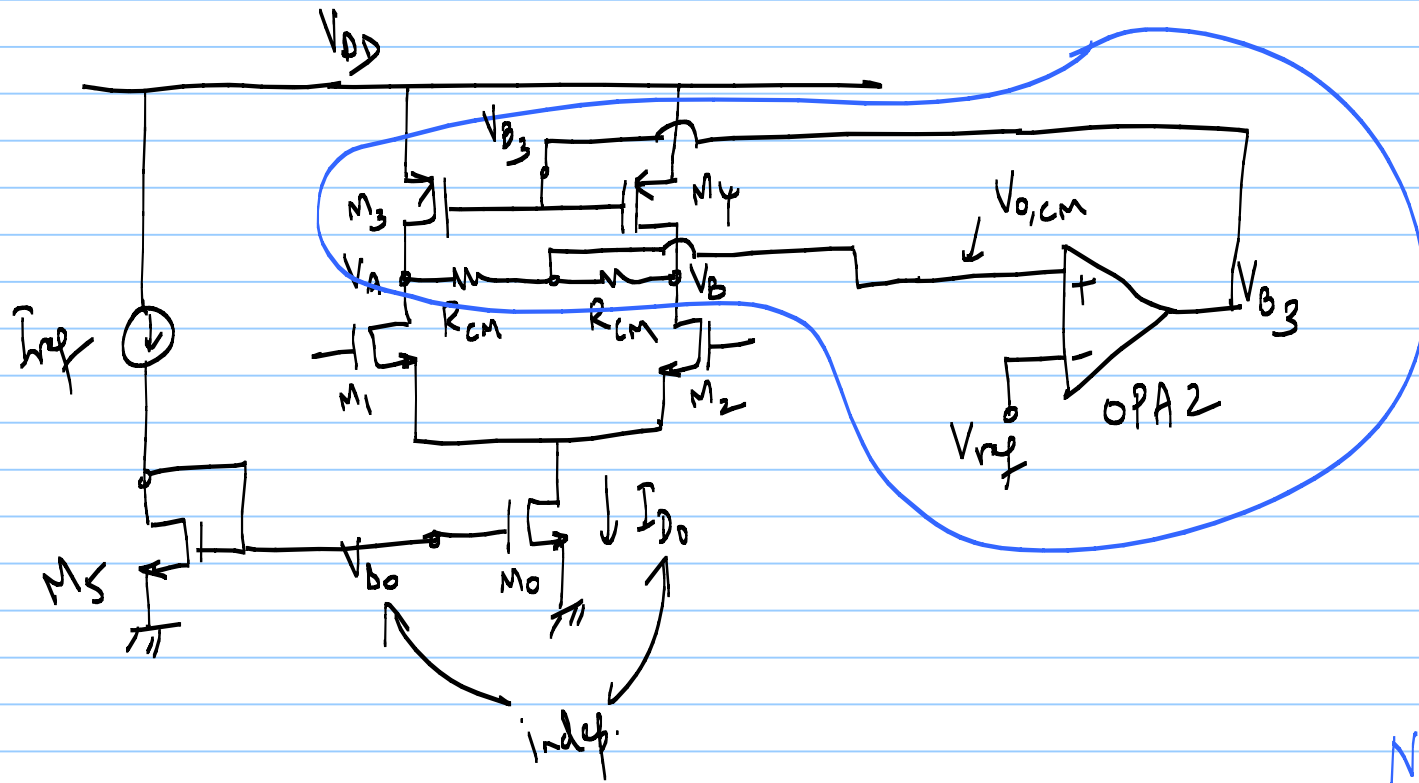
$$\text{i.e. } V_{DD} - V_{S_{f33}} = V_{b3}$$




2-stage
CMFB loop

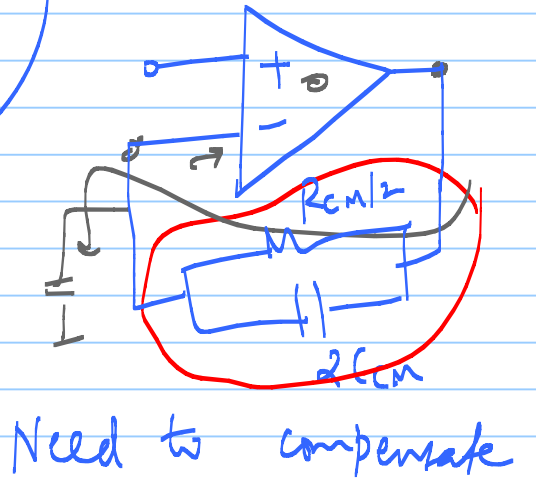

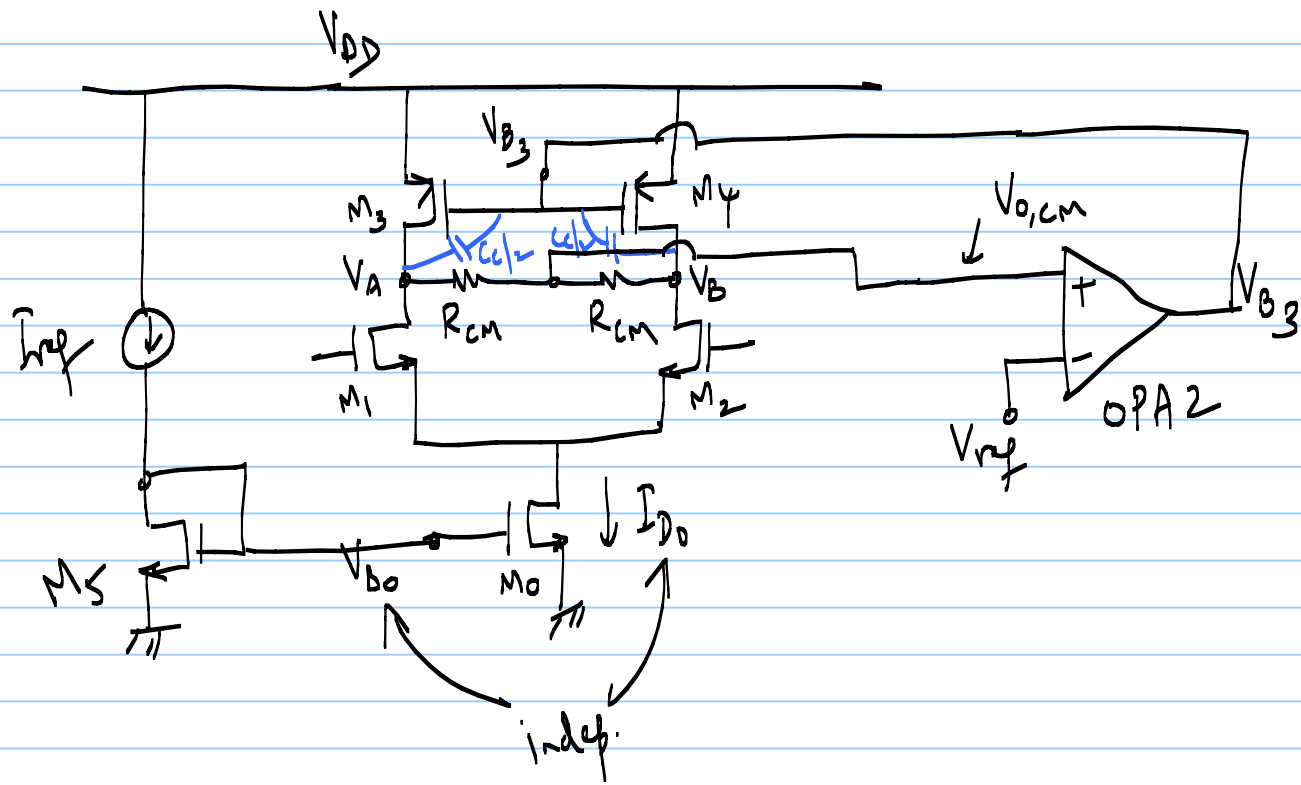

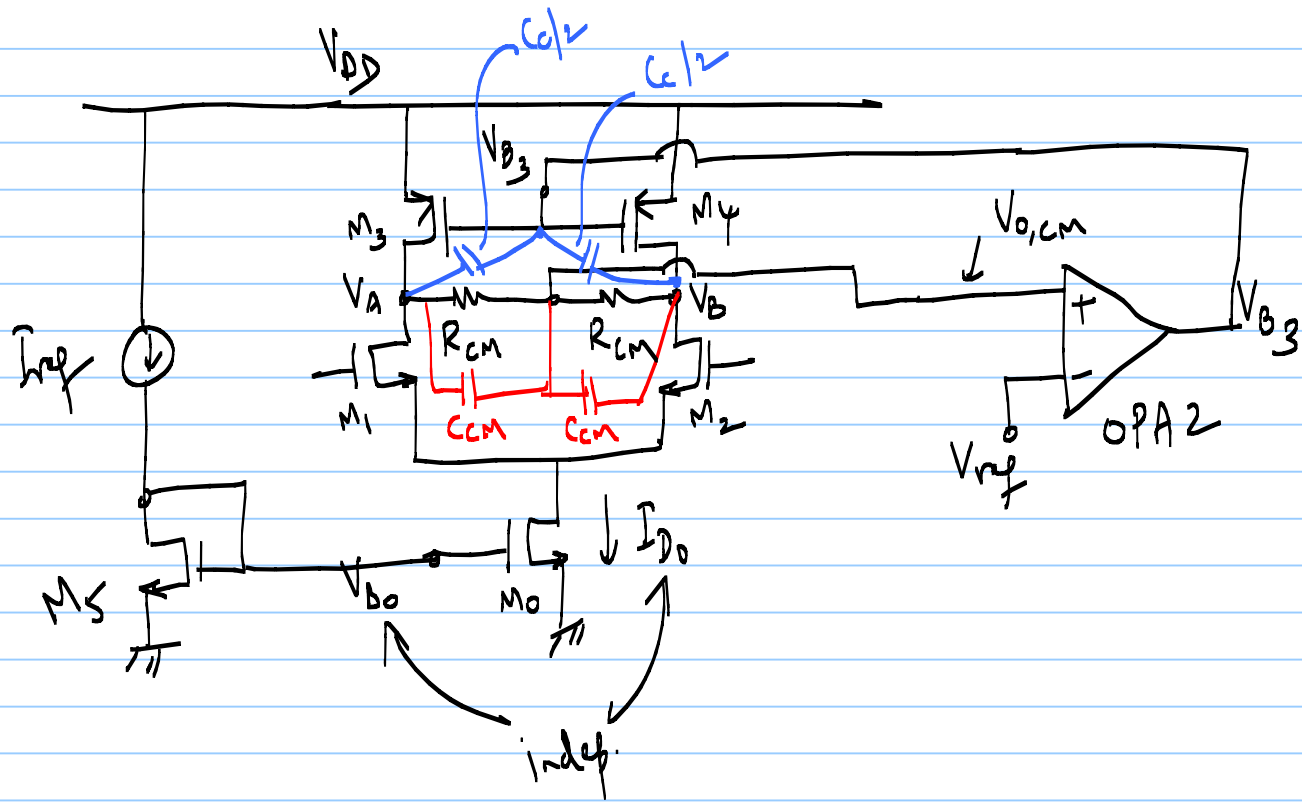

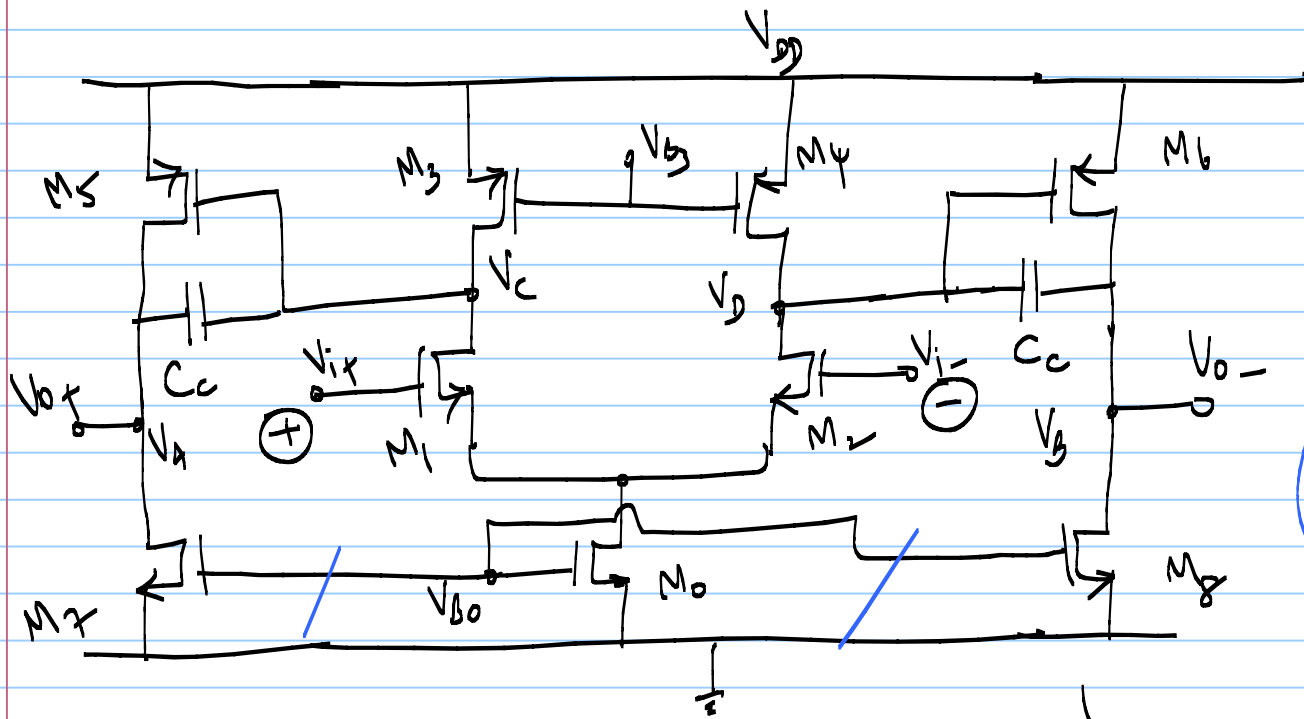


* disconnect V_{A7} & V_{B7} from V_{B0} ?

1) $C_c \rightarrow$ compensation cap for FD mode

2) Set $\frac{V_A + V_B}{2}$ i.e. V_{OCM}

3) Set $\frac{V_C + V_D}{2}$ i.e. V_{ICM}


\rightarrow 2 v CMFB loops independent

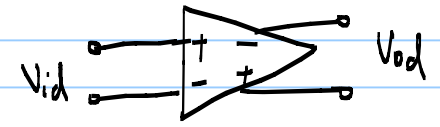

30/11/2023

Lec 25

CMFB for two-stage FD opamp

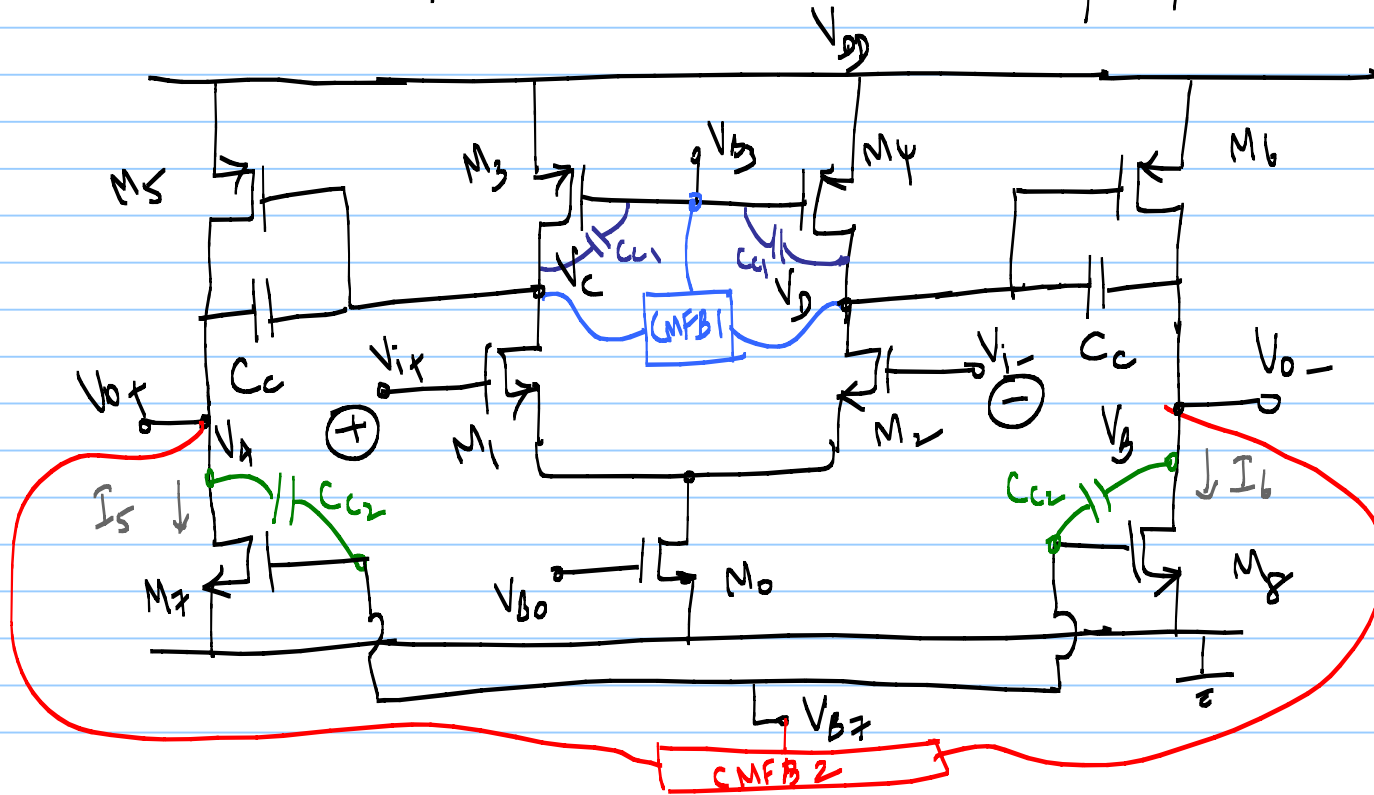

C_c - compensation cap for \rightarrow path


$$V_{o1,cm} = \frac{V_c + V_D}{2}$$

$$V_{o,cm} = \frac{V_A + V_B}{2}$$

Simple: Set $V_{o1,cm}$ & $V_{o,cm}$ independently


Setting $V_{o,CM} = \frac{V_C + V_D}{2} = V_{ref1}$



* Setting $V_{o,CM}$

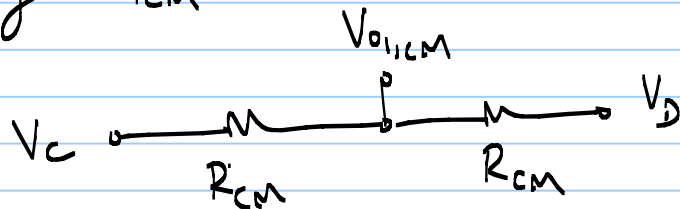


* V_C & V_D swings are low (output swing \div gain of 2nd stage)
 \hookrightarrow (Resistive) CM detector is not mandatory
 linear

* If driving resistive loads \rightarrow most of the gain comes from 1st stage \leftarrow don't use R_{CM}
 @ opamp of $(R_L || C_L)$

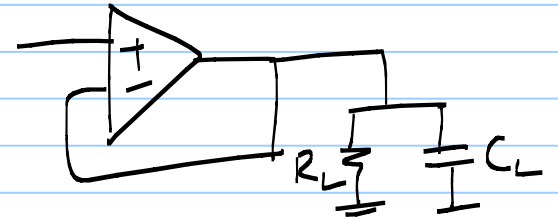

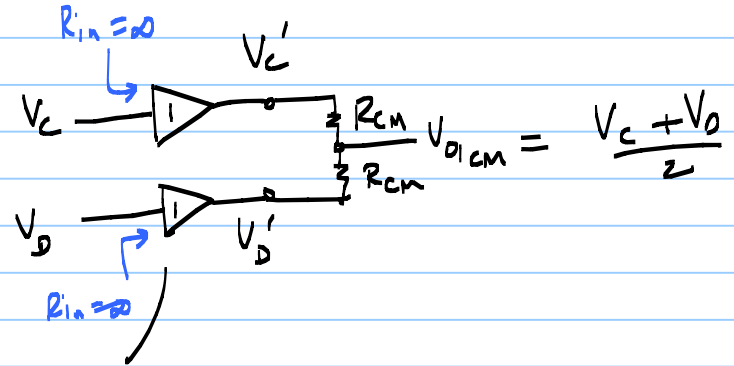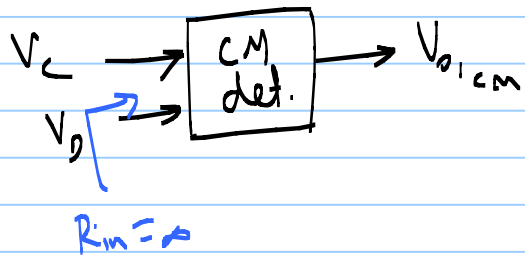


small-signal VCVS of gain = 1

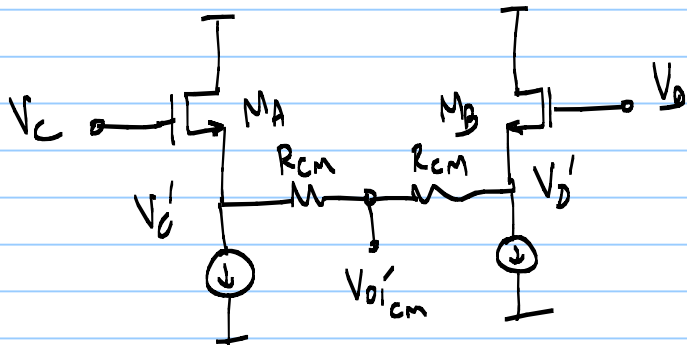

$$V_{c'} = V_c - V_{asA}$$



$$V_{d'} = V_d - V_{asB}$$
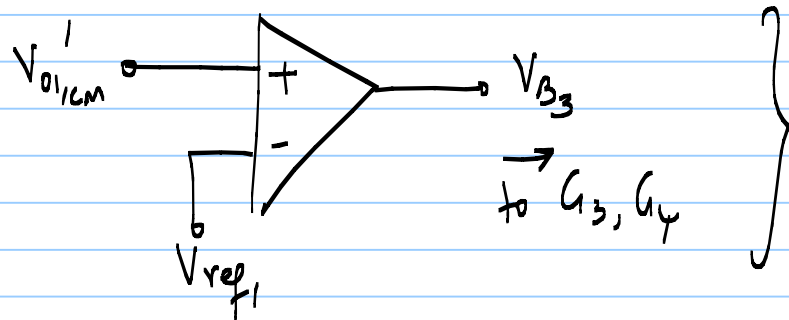
$$V_{o1cm}' = \frac{V_c + V_d}{2} - V_{asAB} = V_{o1cm} - V_{asA,B}$$



\Rightarrow sets $V_{o1,cm}' = V_{ref1}$

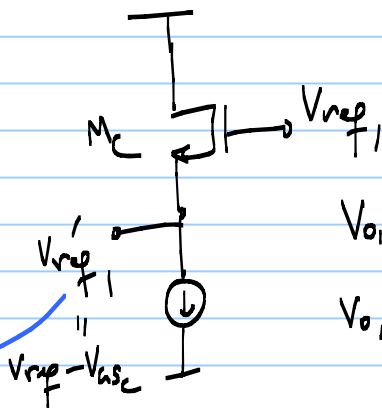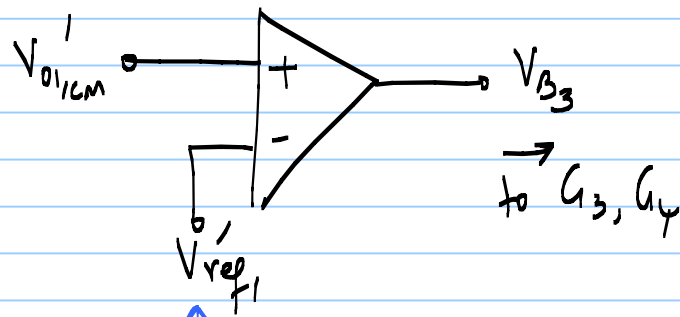
$V_{o1,cm} = V_{ref1} + V_{ASA,B} \times$



set $V_{ASA} = V_{ASs} = V_{ASc}$

$V_{o1,cm}' = V_{ref1}$

$V_{o1,cm} = V_{ref1}$

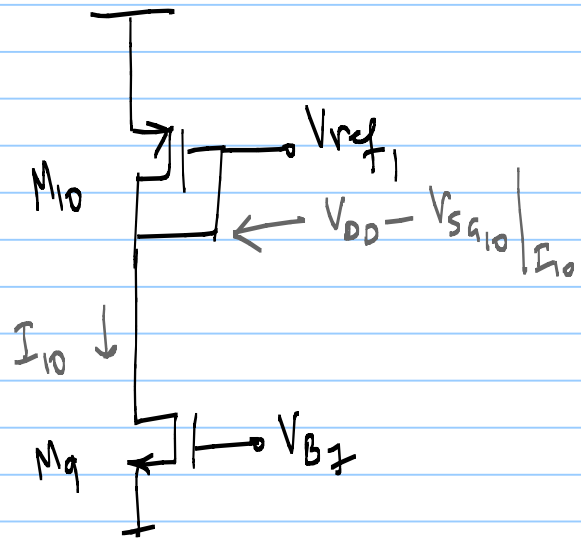


$$V_{o1,cm} = V_{ref1} \rightarrow \text{need this to be } = V_{DD} - V_{th_{5,6}} \Big|_{I_{5,6}}$$


$$* \text{ Set } V_{DD} - V_{th_{10}} \Big|_{I_{10}} = V_{DD} - V_{th_{5,6}} \Big|_{I_{5,6}}$$

$$\Rightarrow \boxed{\frac{I_{10}}{(W/L)_{10}} = \frac{I_{5,6}}{(W/L)_{5,6}}}$$

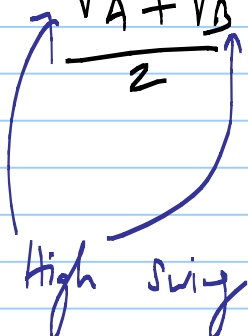
Set $\frac{V_A + V_B}{2} = V_{o,cm} = V_{ref}$



High swing \rightarrow we res. CM det.

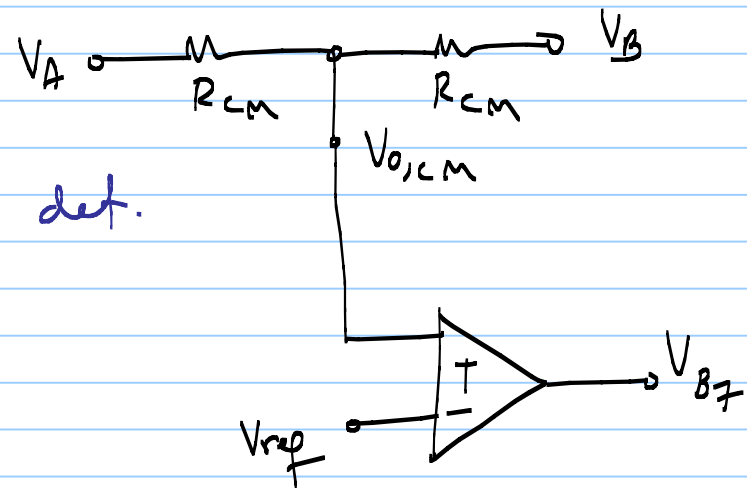


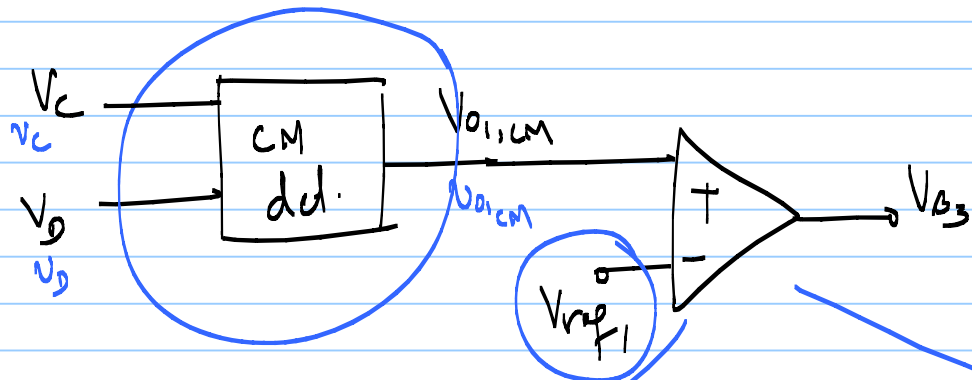
Setting $V_{o1,cm} = \frac{V_c + V_D}{2} = V_{ref1}$ - circuit 2




$$i_{d11} = g_{m11} \cdot \frac{V_{o1,cm}}{2} = g_{m11} \left(\frac{V_c + V_D}{4} \right)$$
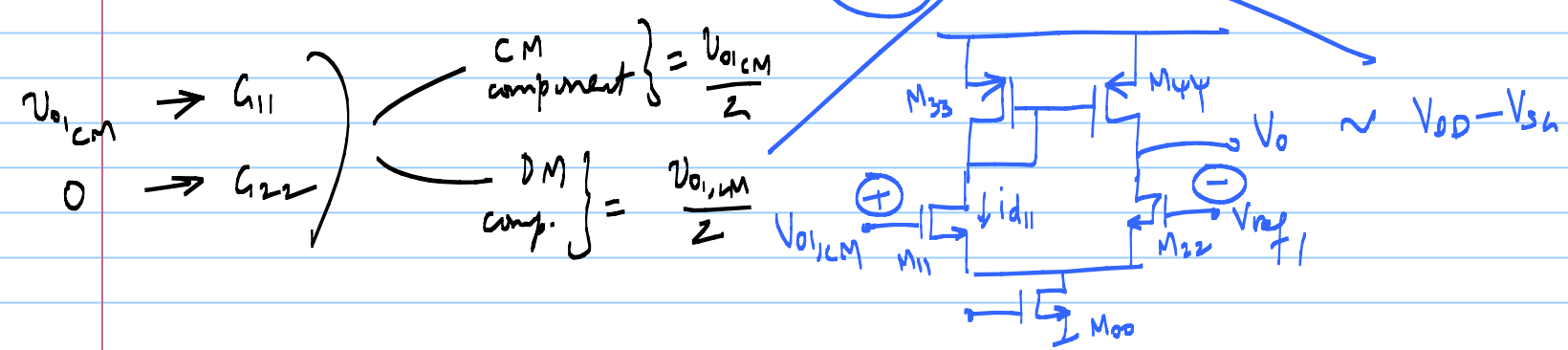
$$= \frac{g_{m11}}{4} \cdot V_c + \frac{g_{m11}}{4} \cdot V_D$$



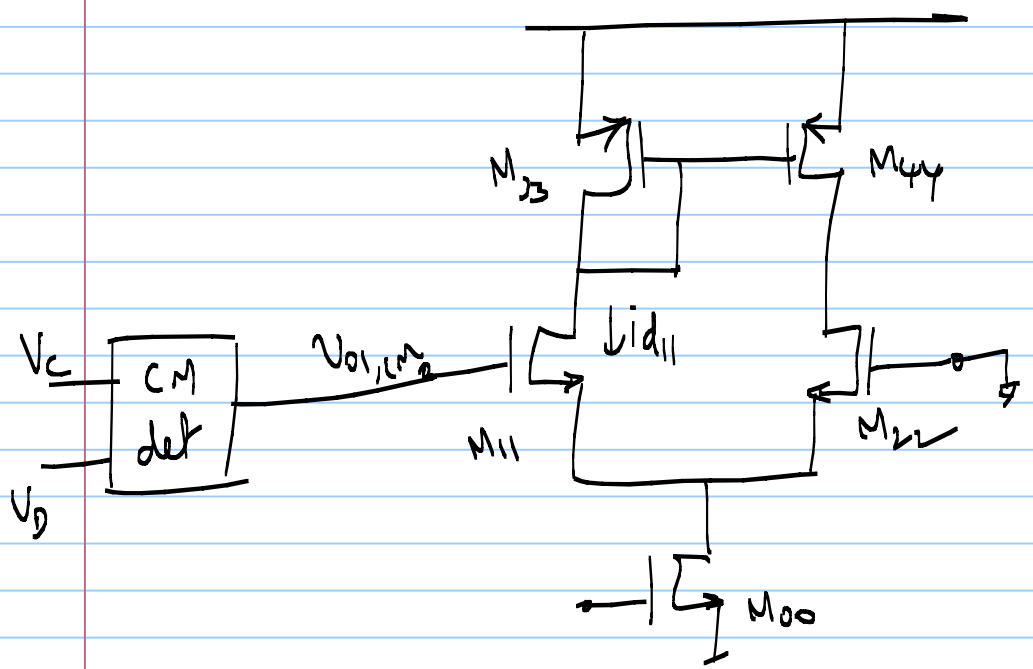
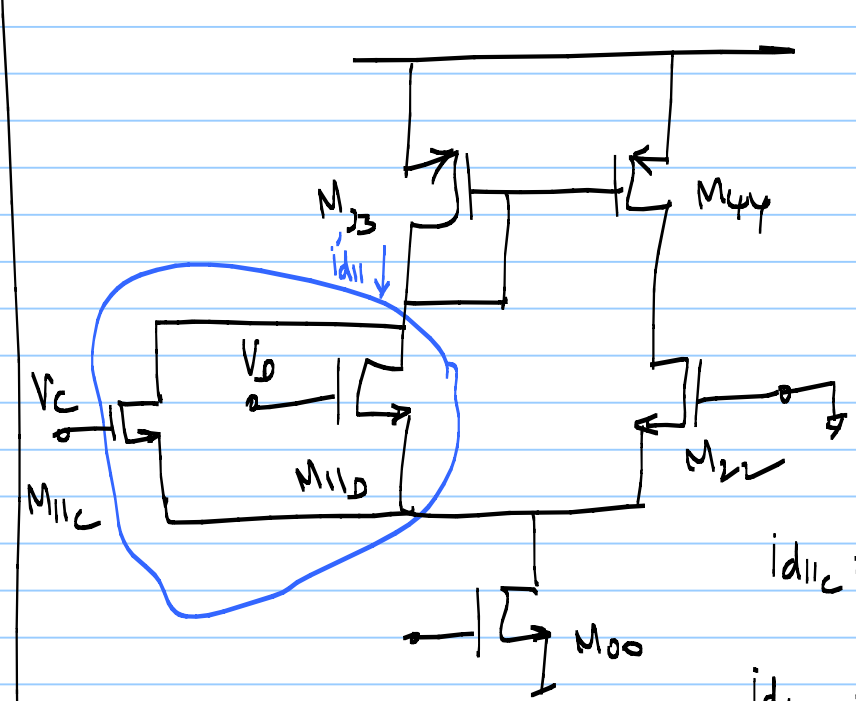
$$i_{d11} = \frac{g_{m11}}{4} \cdot V_c + \frac{g_{m11}}{4} \cdot V_D$$




$$M_{11C} = M_{11D} = M_{11}/2$$

$$i_{d11}' = i_{d11C} + i_{d11D} = g_{m11}/2 \cdot (V_{01CM})$$

$$i_{d11C} = g_{m11C} \cdot \frac{V_c}{2}$$

$$i_{d11D} = g_{m11D} \cdot \frac{V_D}{2}$$

$$g_{m11}/2$$

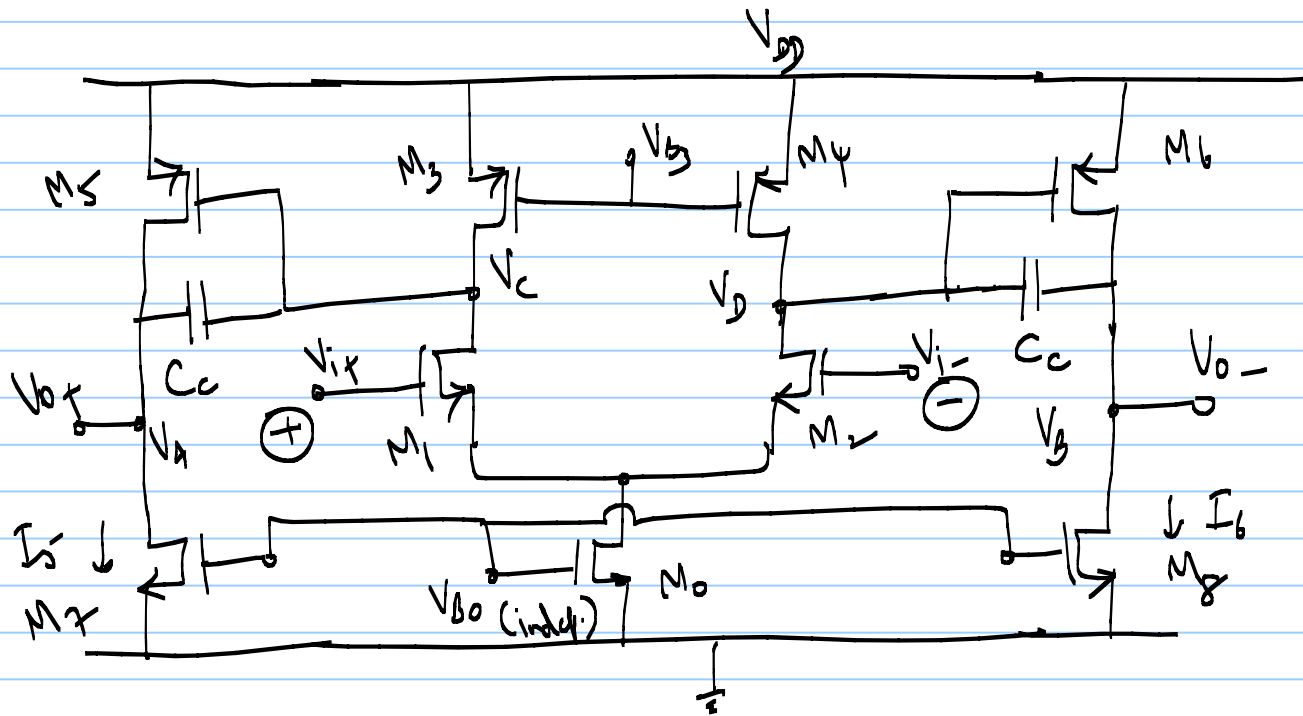

V_{B3} sets $V_{O1,CM}$


$$\text{Set } \frac{V_A + V_B}{2} = V_{O1,CM}$$

via M_5, M_6


* M_5 & M_6 are pseudo-differential amplifiers

↳ they have CM gain

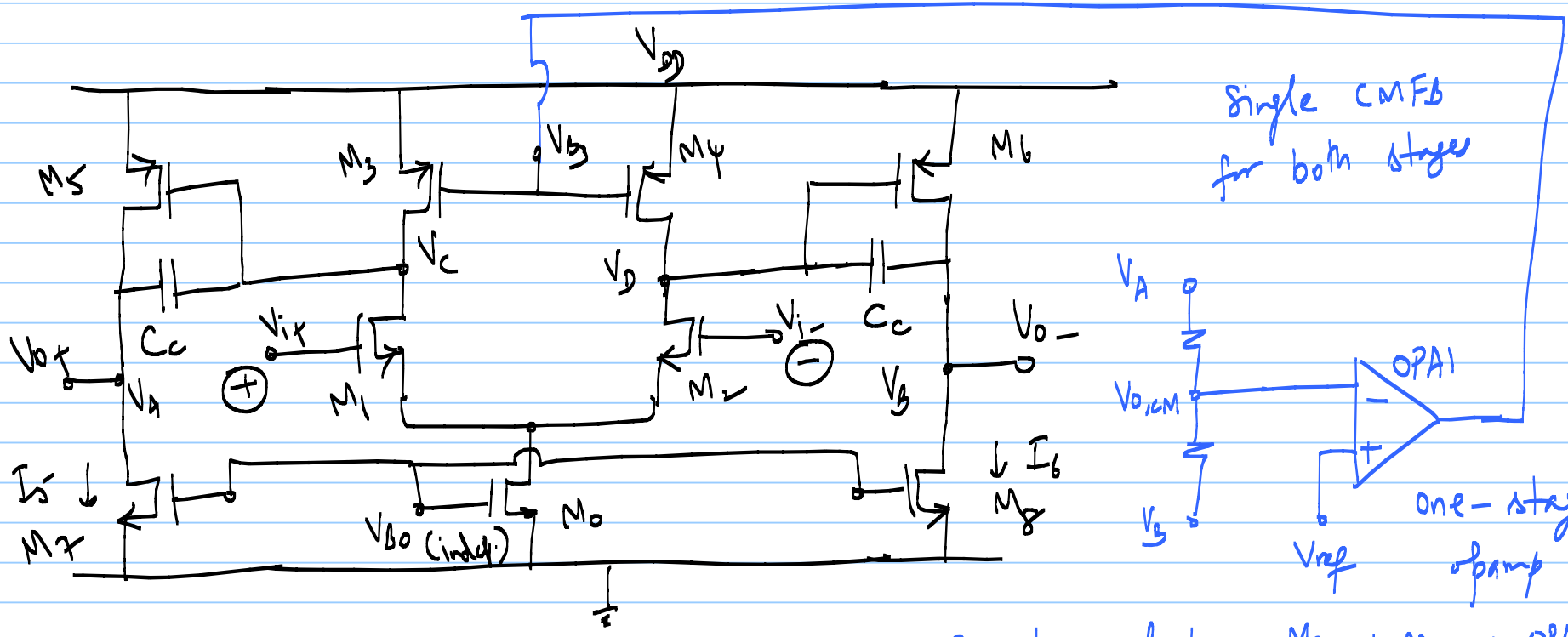↳ $\frac{V_C + V_D}{2}$ controls $\frac{V_A + V_B}{2}$
 $(V_{O1,CM})$ $(V_{O2,CM})$




single CMFB
for both stages

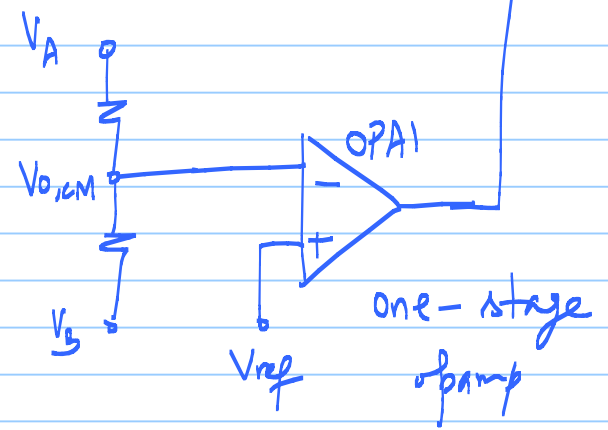

3-stage loop \rightarrow $M_{5,4}$; $M_{5,6}$; OPA1
needs to be compensated

Compensation
Scheme # 1

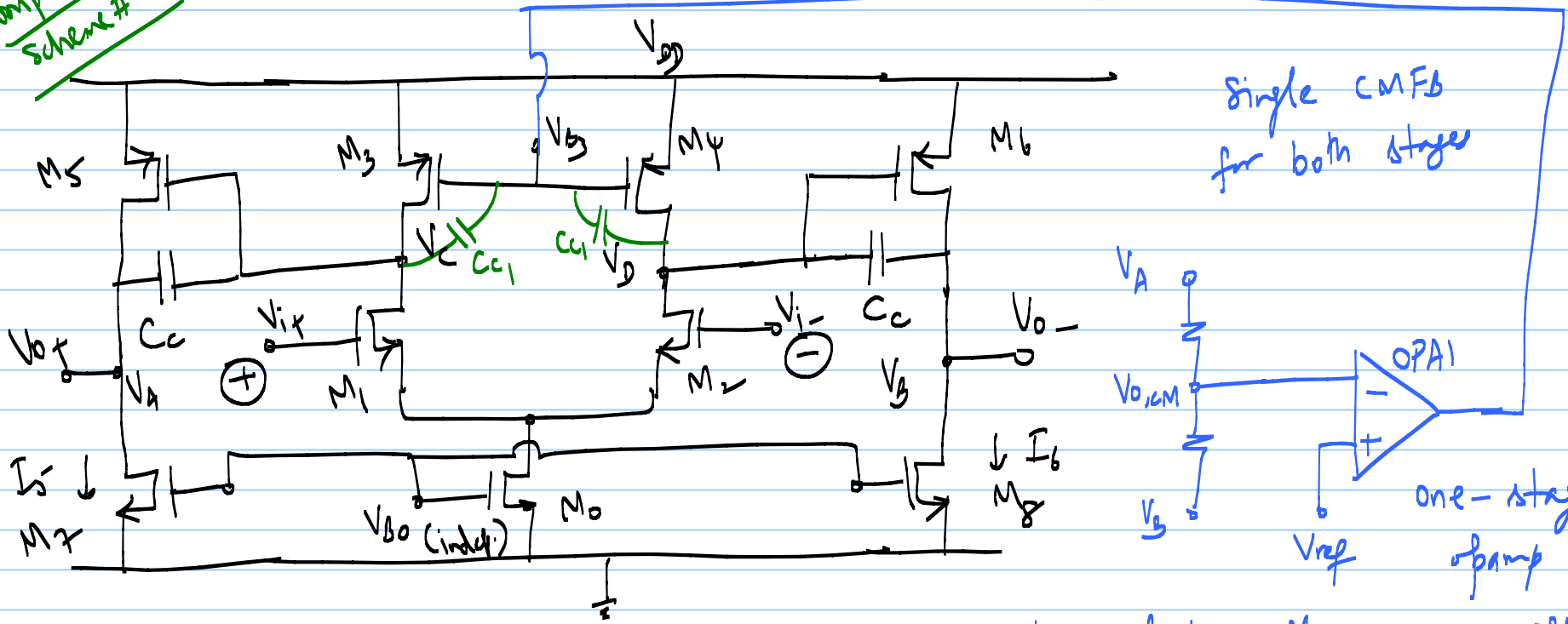


Single CMFB
for both stages

one-stage
opamp

3-stage loop \rightarrow $M_{3,4}$; $M_{5,6}$; OPA1
needs to be compensated

Compensation
scheme #2

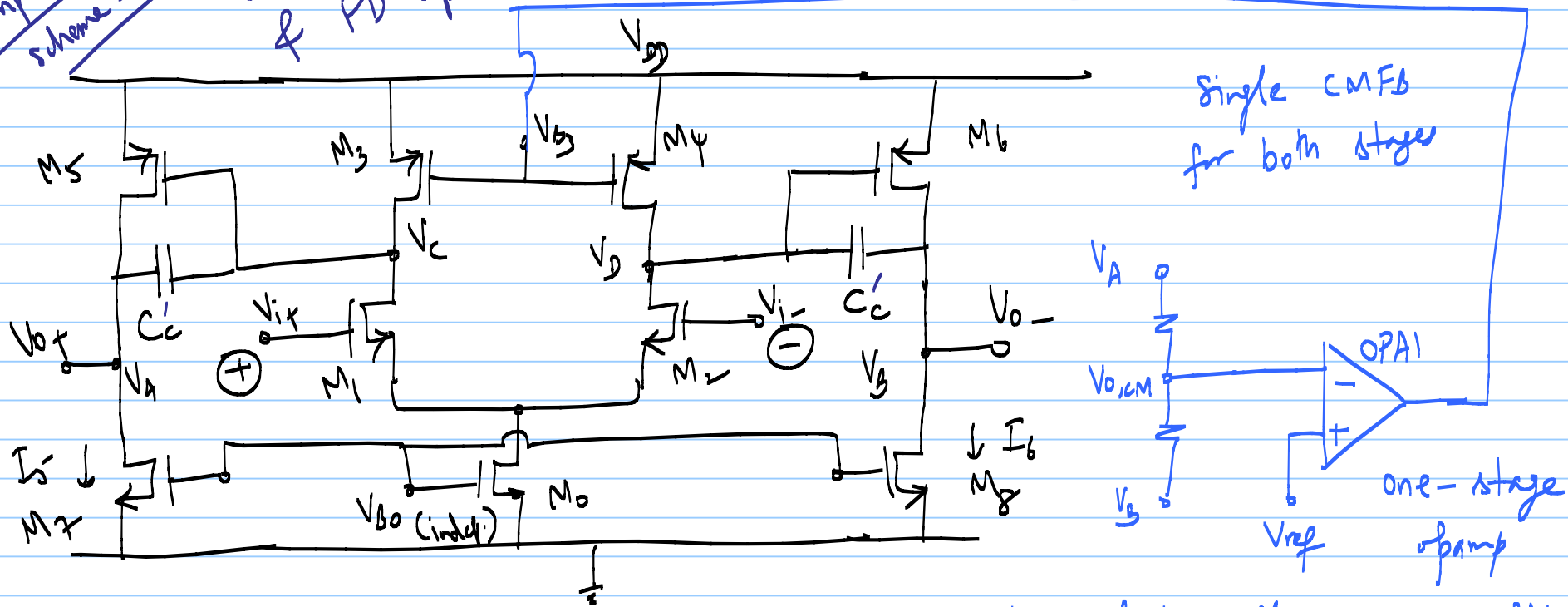
combine CMFB compensation
& FD opamp compensation into a single cap C_c




3-stage loop \rightarrow $M_{3,4}$; $M_{5,6}$; OPA1
needs to be compensated

Compensation
scheme #3

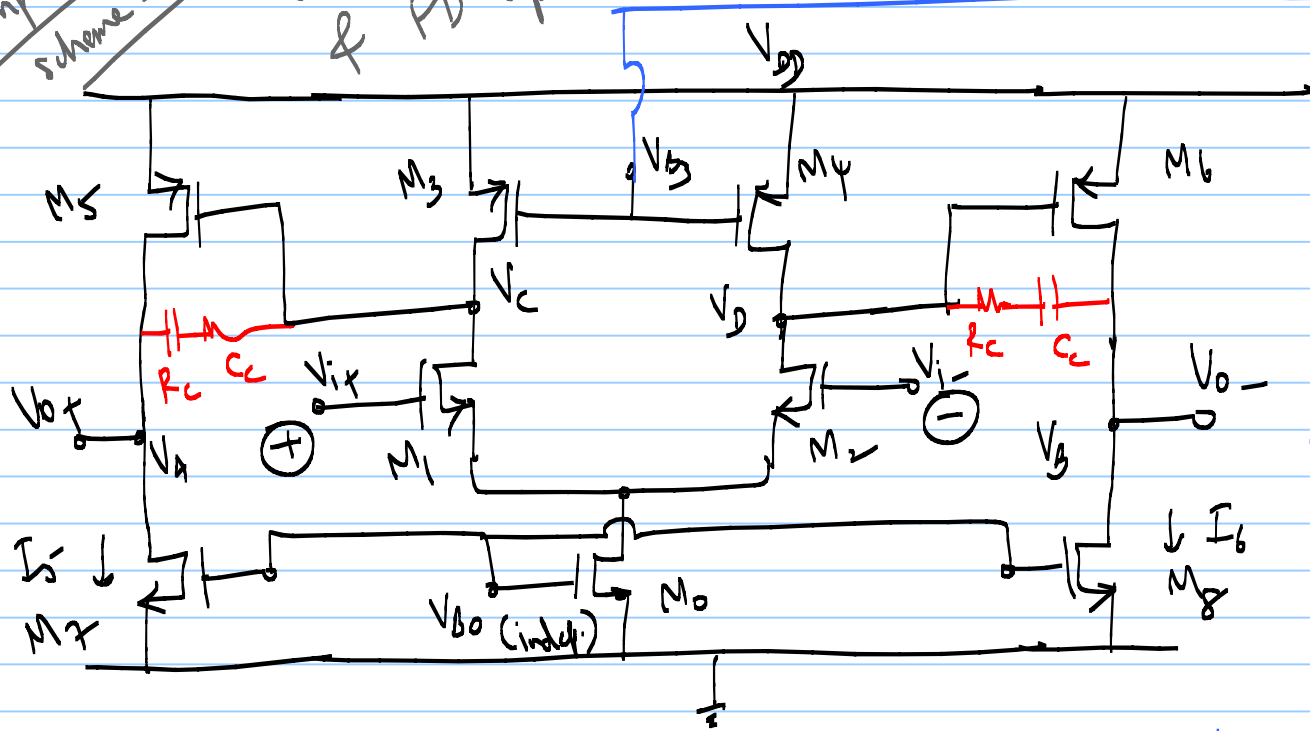combine CMFB compensation
& FD opamp compensation into a single cap $C_c + R_c$ for pole-zero
cancellation





single CMFB
for both stages

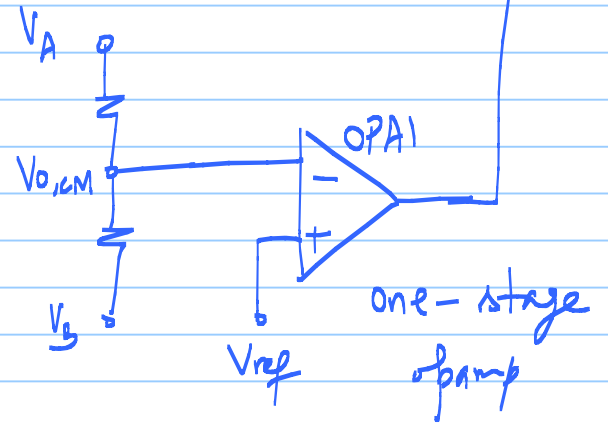

3-stage loop \rightarrow $M_{3,4}$; $M_{5,6}$; OPA1
needs to be compensated

8/12/2023


Lec 26

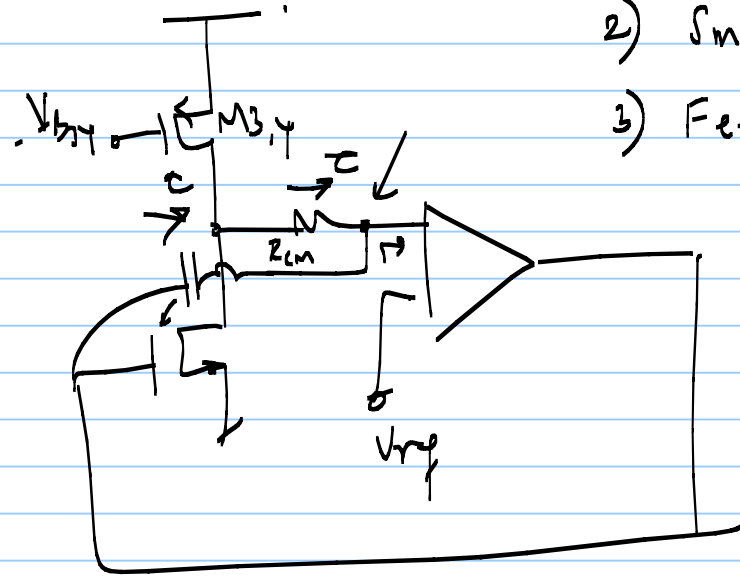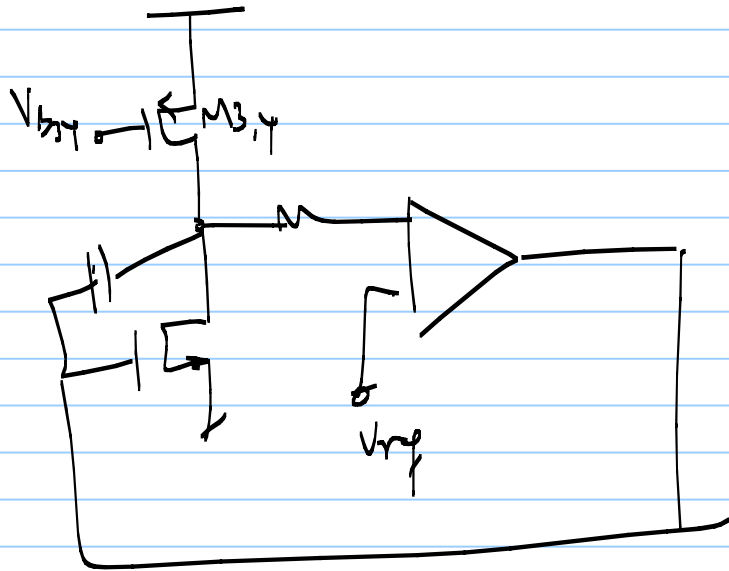

- 1) 3-stage opamps
- 2) Small R-loads
- 3) Feed forward op-amps

Phase Locked Loop \rightarrow set phase based on a negative fdb. loop


Voltage Amplifier

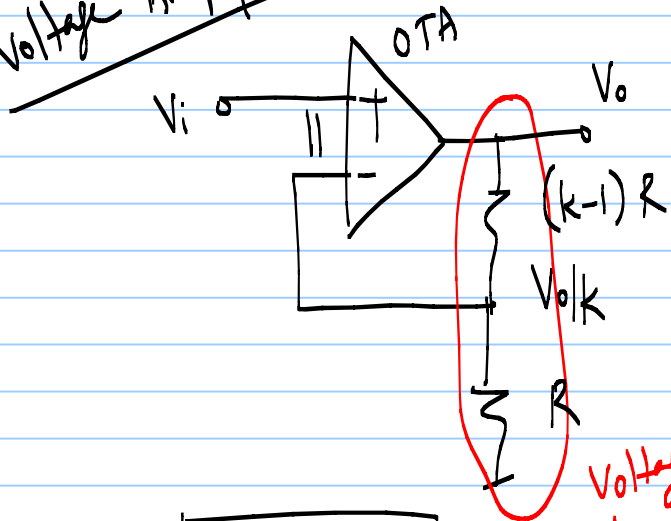

Want

$$V_o = k V_i$$


Voltage divides

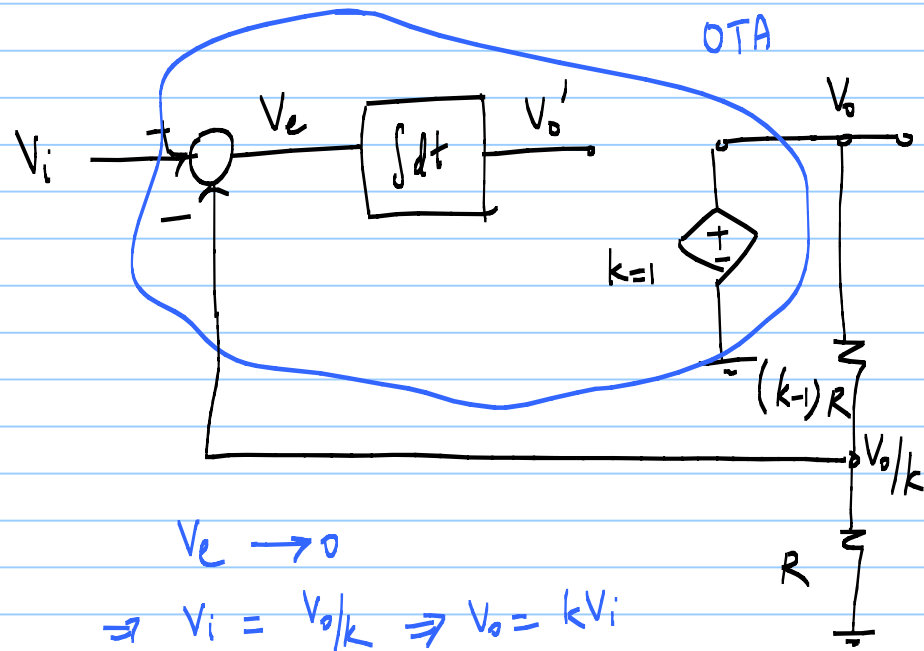

$$V_e \rightarrow 0$$

$$\Rightarrow V_i = V_o/k \Rightarrow V_o = k V_i$$

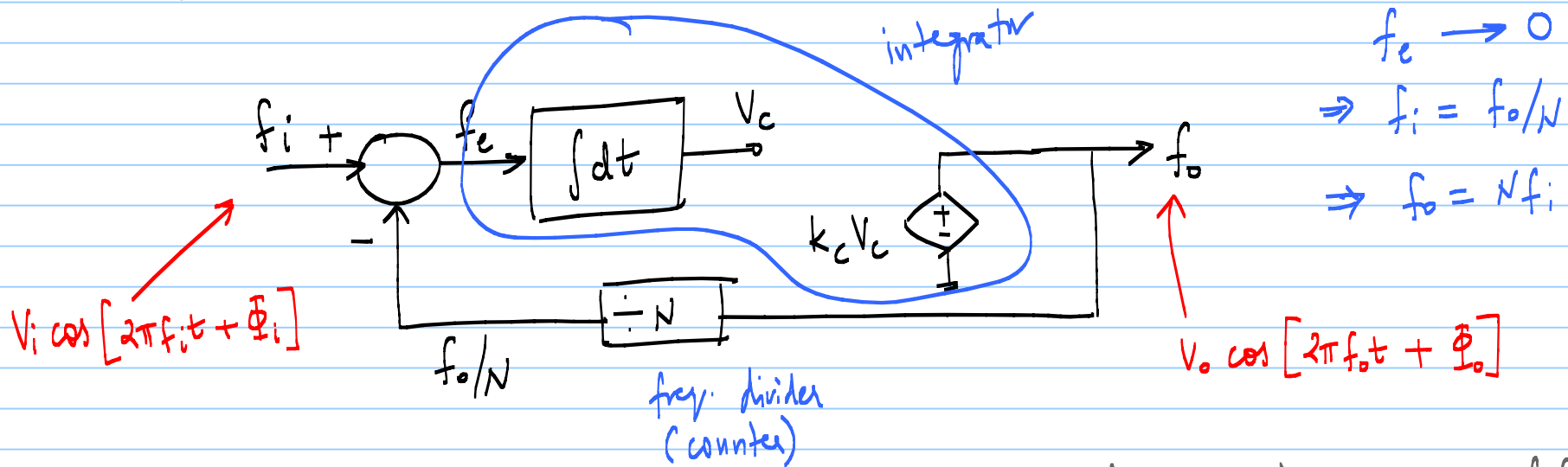Frequency Multiplier : Want $f_o = N f_i$





$$A \cos (\omega_o t + \phi_o)$$

$$\text{phase} = \omega_o t + \phi_o = 2\pi f_o t + \phi_o$$


$$\text{angular freq.} = \frac{d}{dt} (\text{phase}) = \omega_o + \frac{d\phi_o}{dt}$$

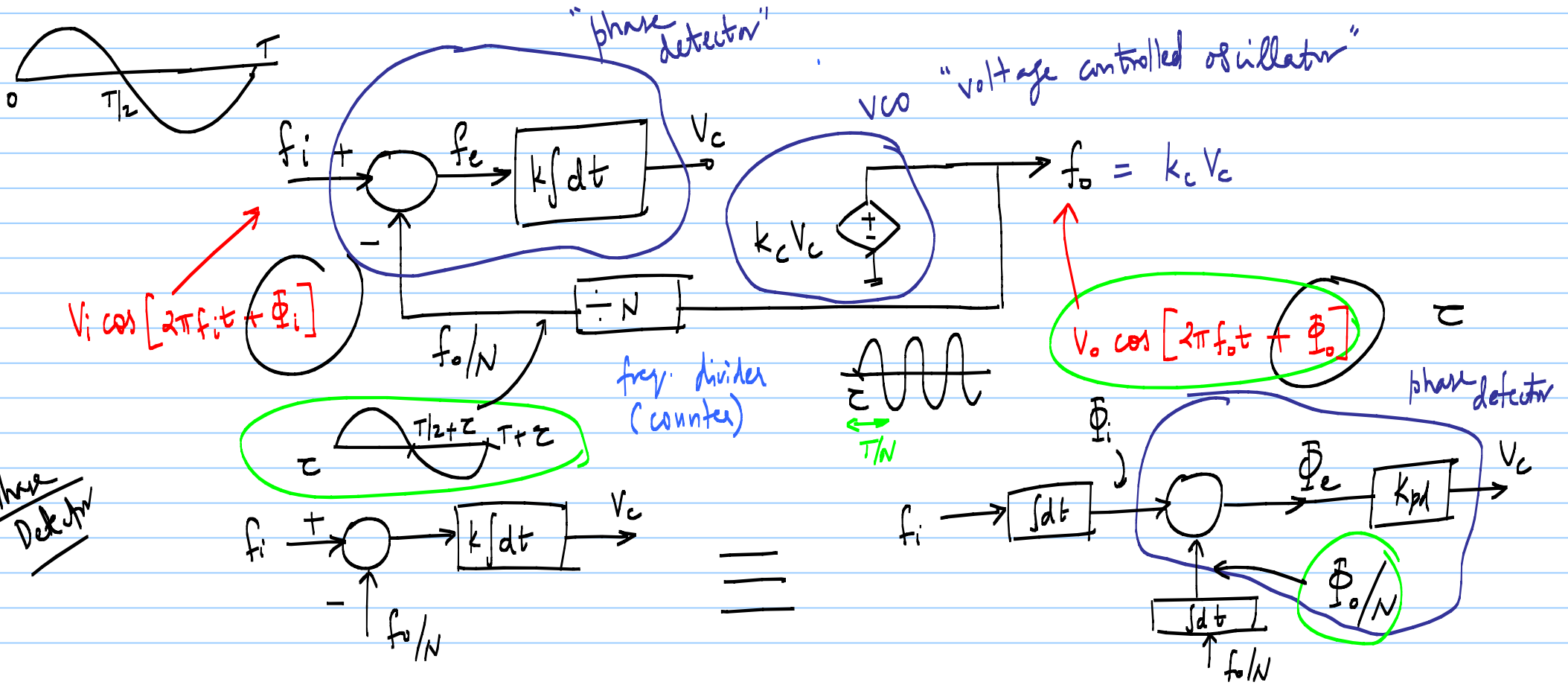
$$\text{freq. (Hz)} = \frac{1}{2\pi} \frac{d}{dt} (\text{phase}) = \frac{\omega_o}{2\pi} + \frac{1}{2\pi} \frac{d\phi_o}{dt}$$



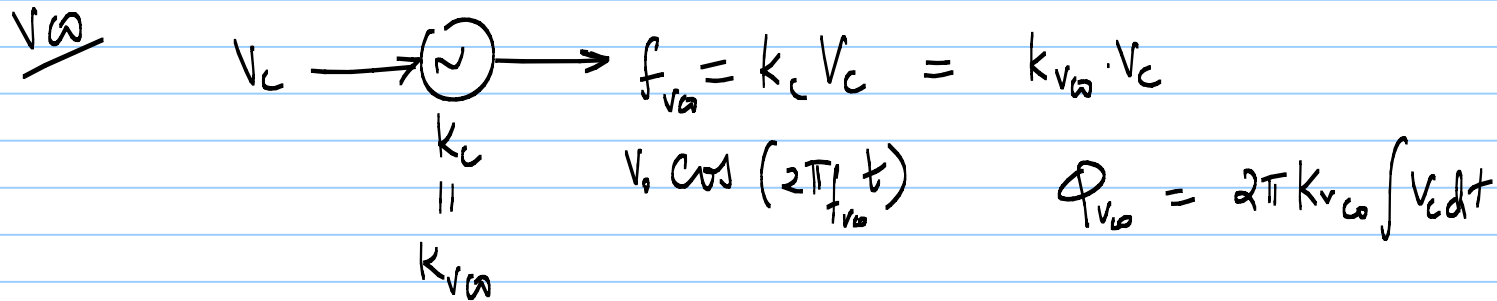


Phase domain model gain = N

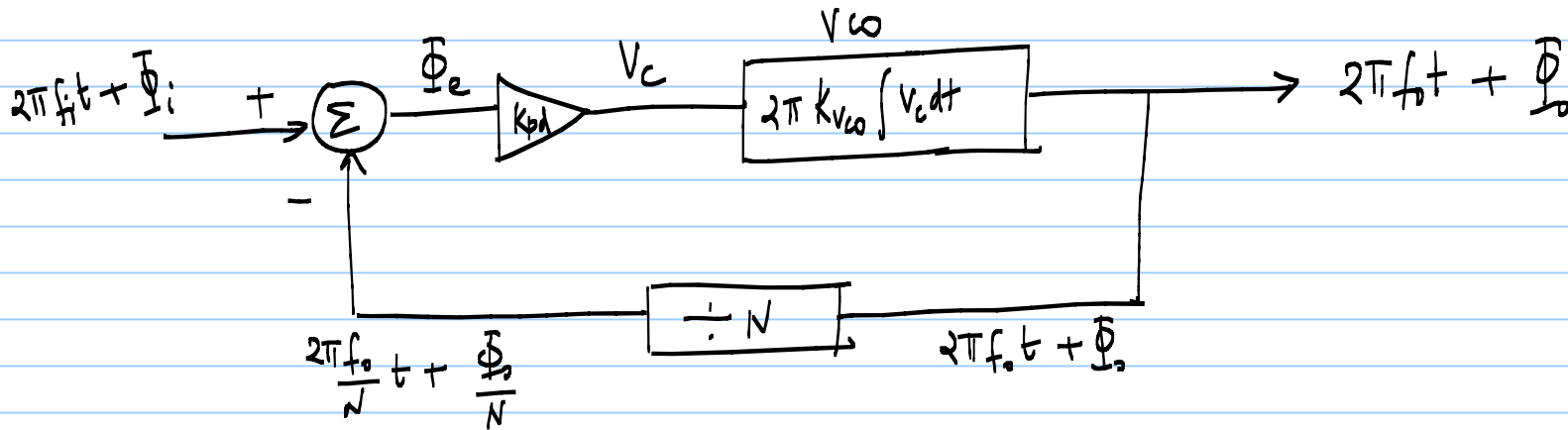

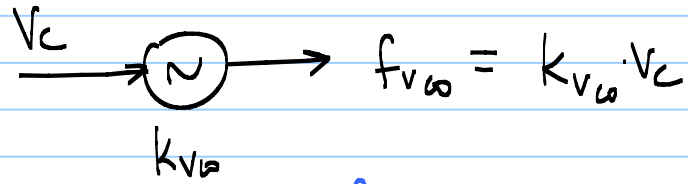


$$f_{VCO} = f_{free} + K_{VCO} \cdot V_c$$

↑
free running
freq. of VCO ($V_c=0$)

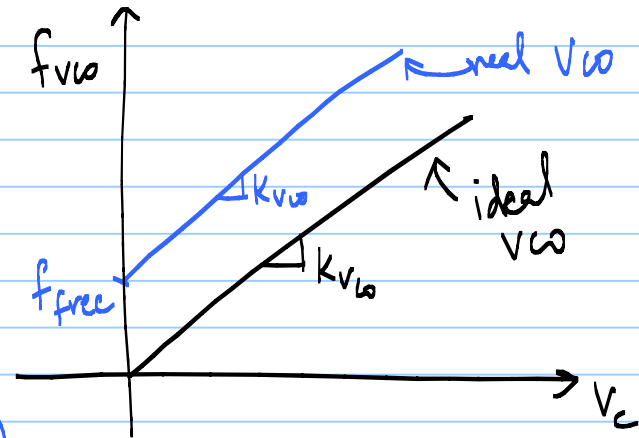

Phase domain model

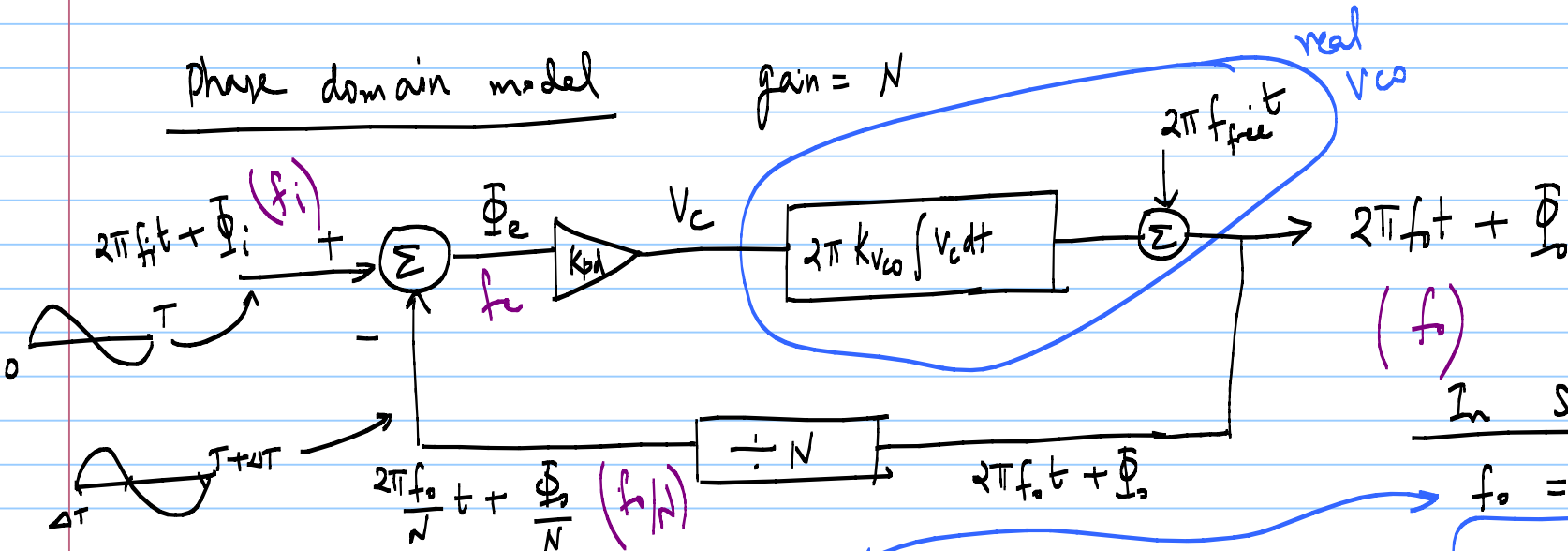

gain = N

In Steady State

$f_o = f_i \cdot N$ ← $f_e = 0$

$$\Phi_e = (2\pi f_i t + \Phi_i) - (2\pi f_o t + \frac{\Phi_o}{N}) = \Phi_i - \frac{\Phi_o}{N}$$


$$V_c = K_{pd} \cdot \Phi_e = K_{pd} (\Phi_i - \frac{\Phi_o}{N})$$

$$f_o = f_{free} + K_{vco} \cdot V_c = N f_i \Rightarrow V_c = \frac{N f_i - f_{free}}{K_{vco}}$$


$\frac{f_i}{f_{free}} N f_i > f_{free} \rightarrow$ nm-zero V_c
 nm-zero Φ_e

14/12/23


Lec 27

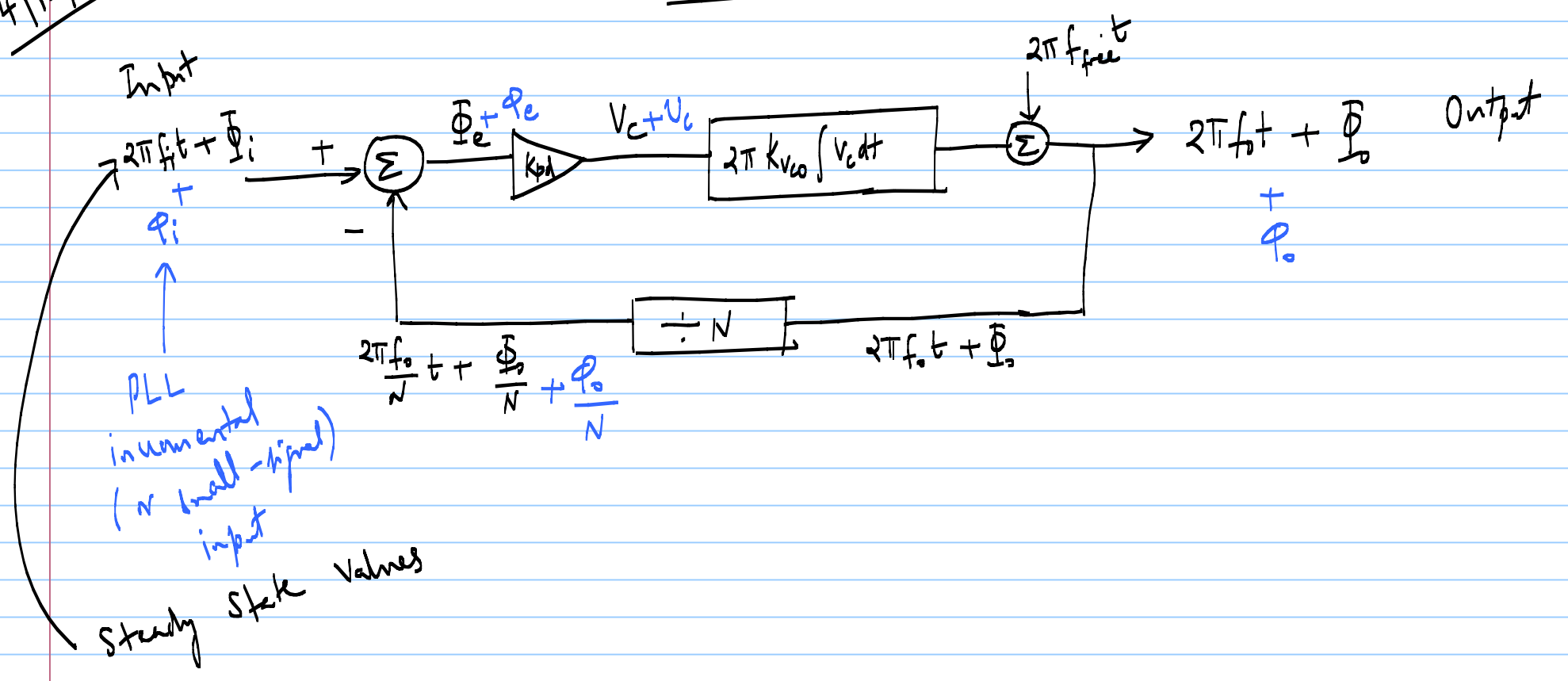


Steady State Values

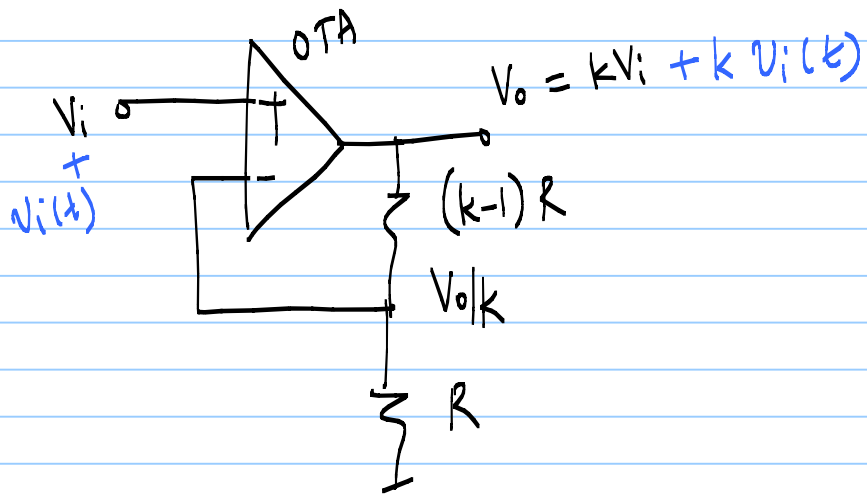


→ incremental eq. det.

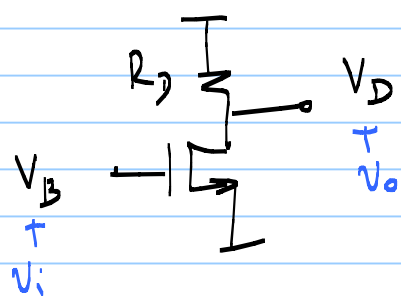

→

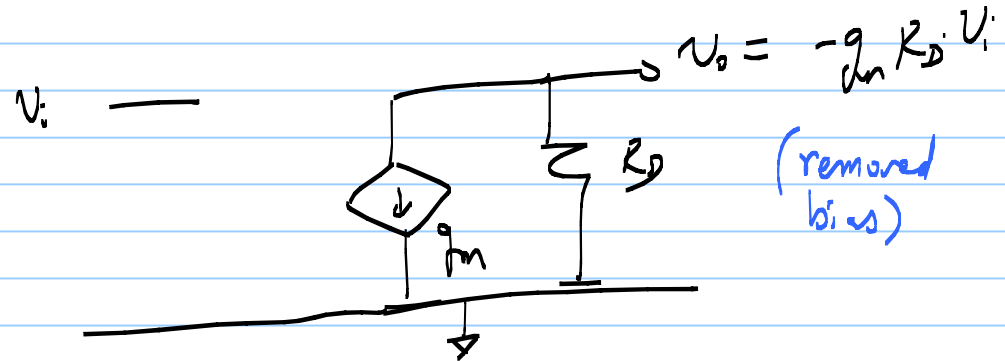

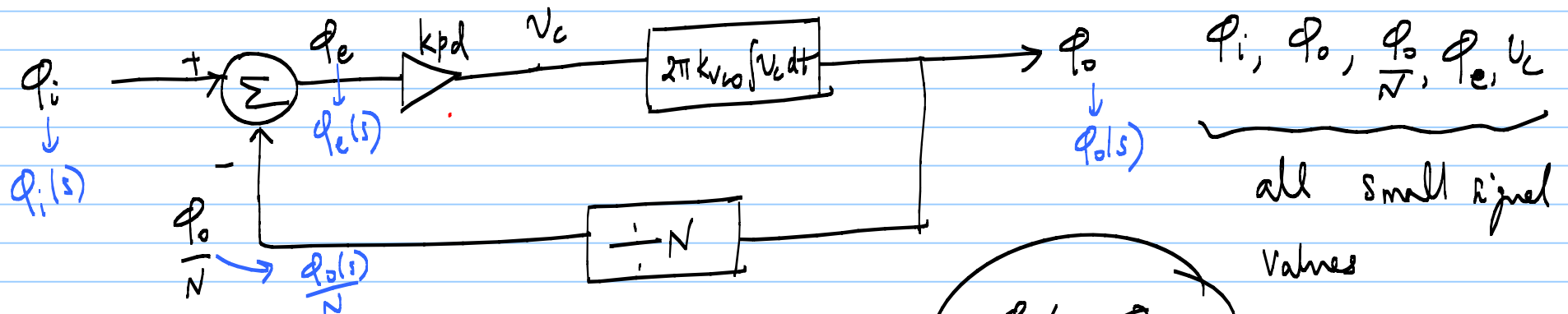Incremental Phase Domain Model of PLL ← phase locked loop



Type-I phase locked loop

$$\phi_o/N = \phi_{fb}$$

- 1) Closed loop gain as a function of freq.
- 2) $LG(s) \rightarrow PM, GM$ from Bode plots
- 3) Step response
- 4) $-3dB BW, ULB$

...


$$1) \quad \frac{\text{Loop Gain}}{L_G(s)} = \frac{2\pi K_{pA} K_{V\omega}}{Ns}$$

$$2) \quad \frac{\text{Closed loop gain}}{CL_G(s)}$$


$$= \frac{Q_o}{Q_i}(s) = N \cdot \frac{L_G(s)}{1 + L_G(s)}$$

$$= N \cdot \frac{1}{1 + \frac{Ns}{2\pi K_{pA} K_{V\omega}}} = N \cdot \frac{1}{1 + \frac{s}{\omega_{3dB}}}$$
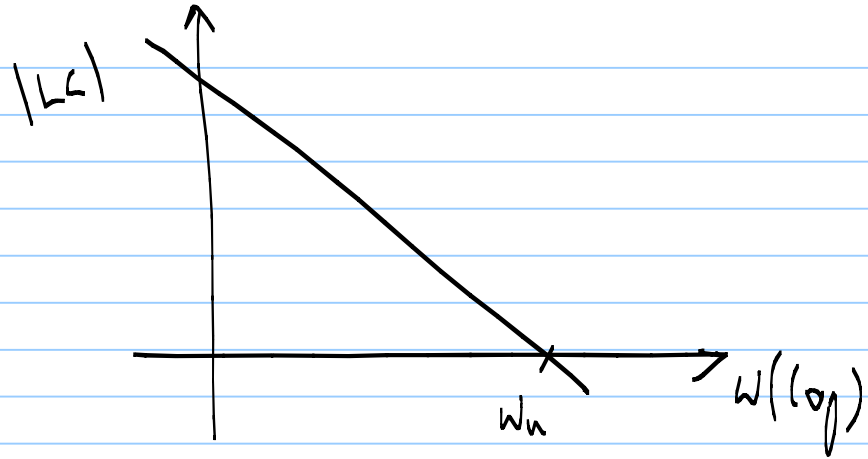
$$3) \quad \omega_{-3dB}^{(CL)} = \frac{2\pi K_{pA} K_{V\omega}}{N} \quad ; \quad f_{-3dB}^{(CL)} = \frac{K_{pA} K_{V\omega}}{N}$$




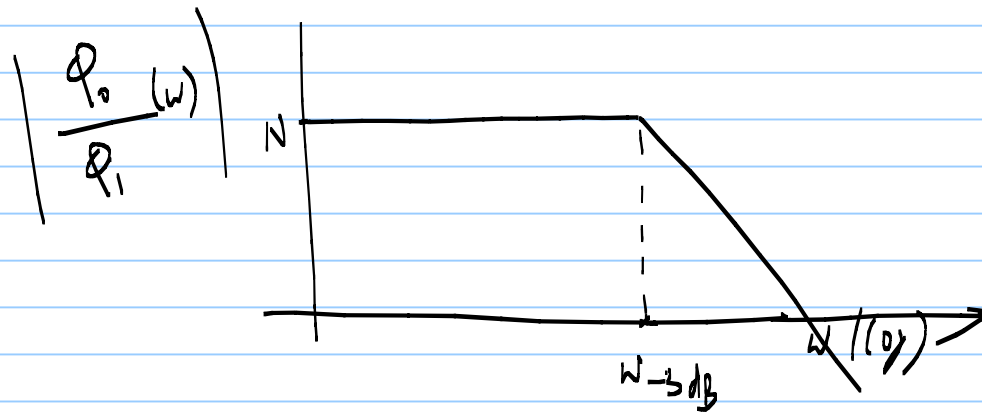
$$\omega_n = \frac{2\pi K_p \Lambda K_{vco}}{N}$$



HW: step response

Phase Detector (Tristate Phase-frequency Detector)




(PFD) (very common)

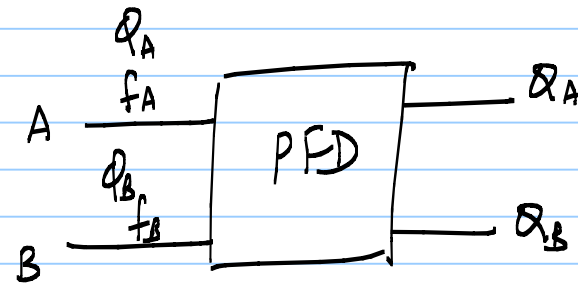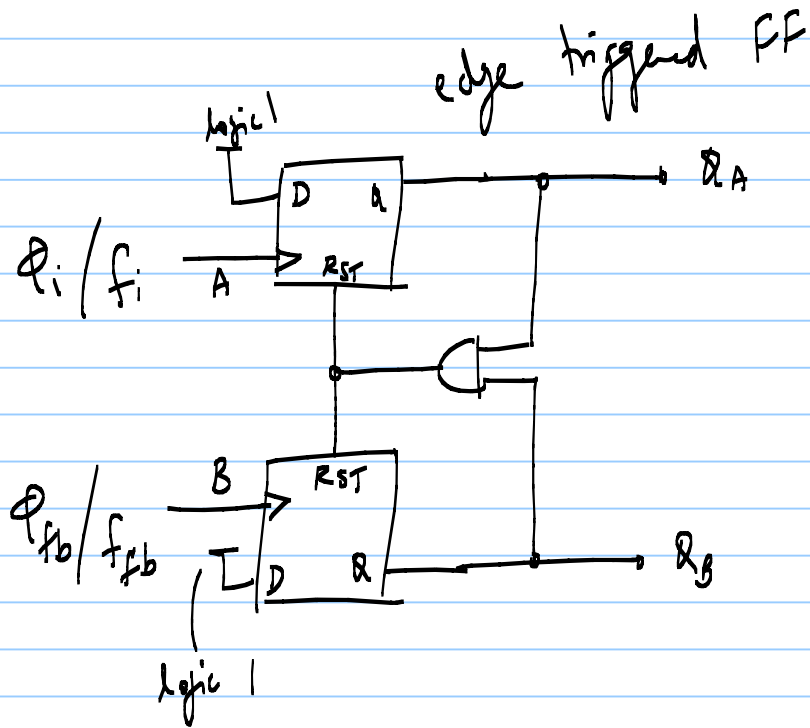

$$\frac{1}{N} \cdot \phi_o = \phi_{fb}$$


Desired output PFD } = $\text{avg.} (Q_A - Q_B)$ "V_c"
 in volts

Q_A	Q_B	State
0	0	0
0	1	-1
1	0	+1
1	1	Reset

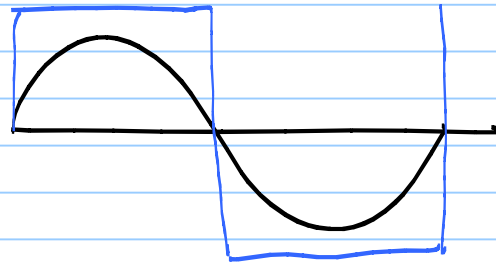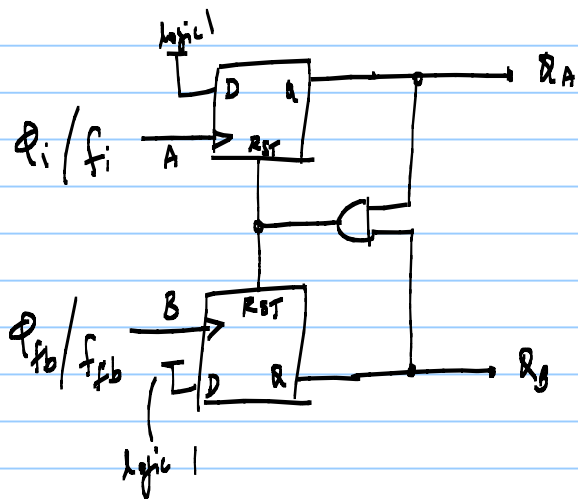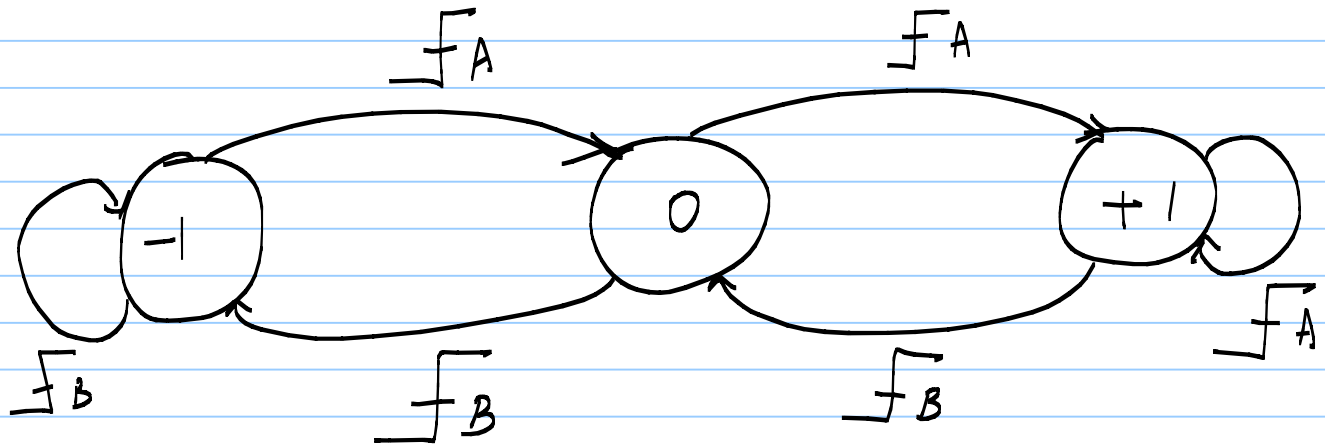

+ve edge triggered
DFFs
No gate delays

$f_A = f_B$
 $\phi_A \neq \phi_B$

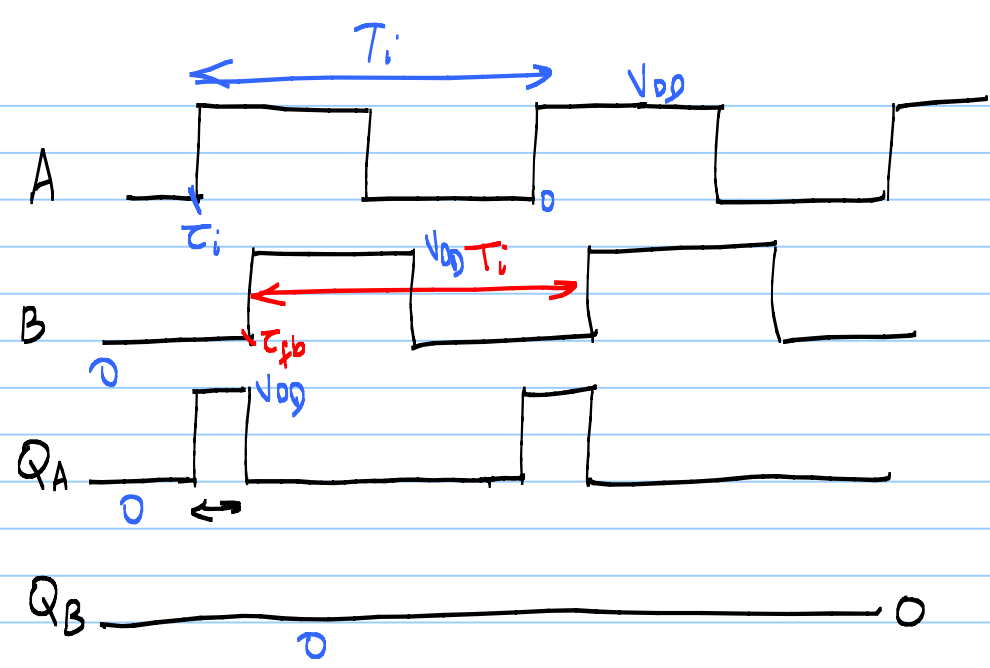

$\tau_{fb} < \tau_i$

\Downarrow
 Q_A remains @ zero


Q_B goes high for $(\tau_i - \tau_{fb})$

PFD characteristic plot

\hookrightarrow plot $avg. (Q_A - Q_B)$ \leftarrow output voltage

$\phi_A - \phi_B$ \leftarrow input phase diff.

PF-D
characteristics

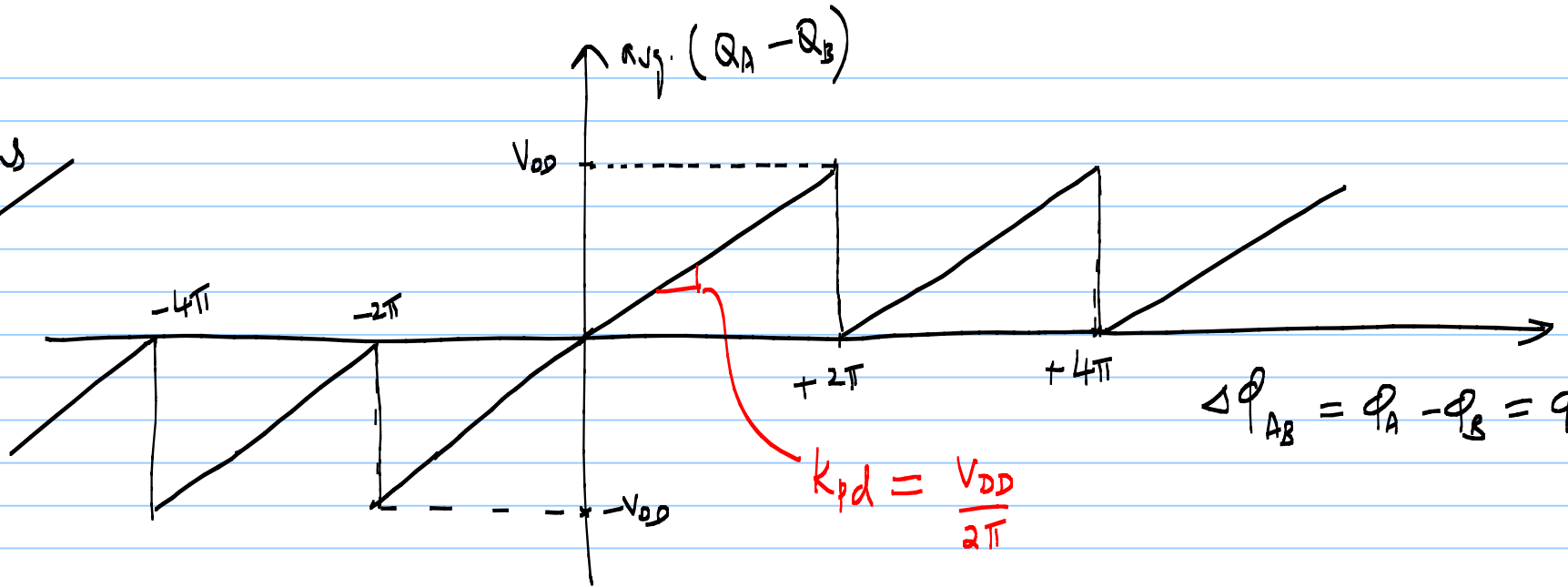


$(Q_A - Q_B)$




DC value
avg. $(Q_A - Q_B)$

fundamental $\frac{1}{T_i} (= f_i)$

harmonics $\frac{k}{T_i} (= k f_i)$

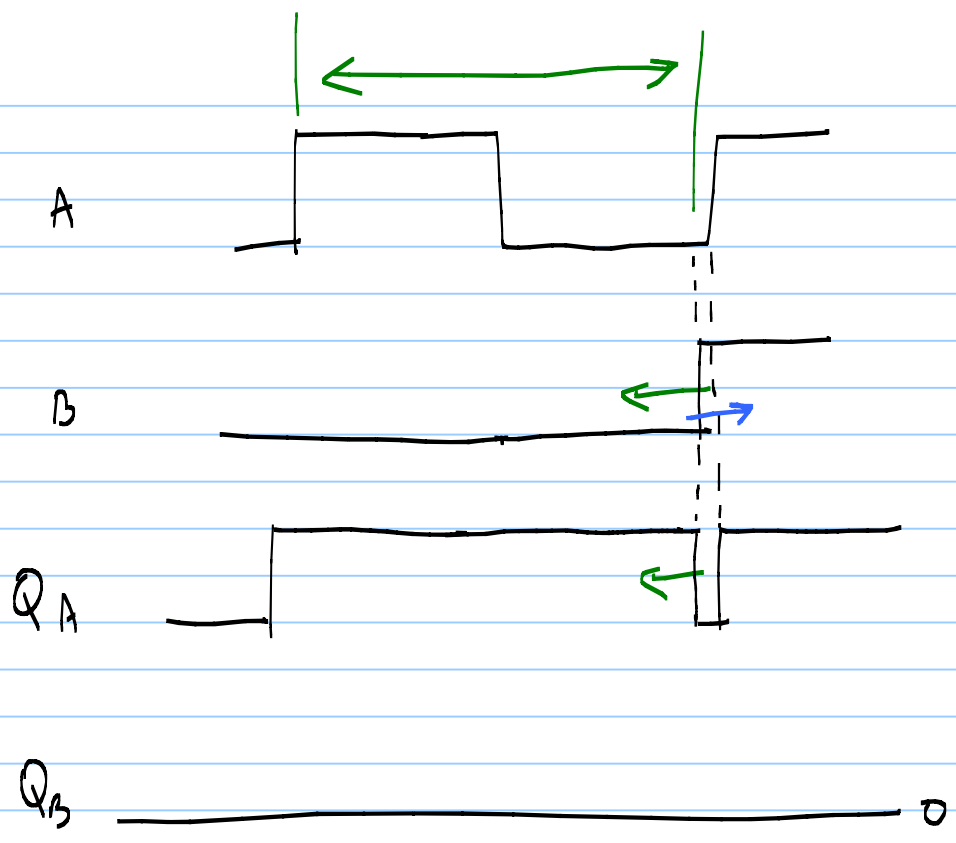



$f_A \gg f_B$

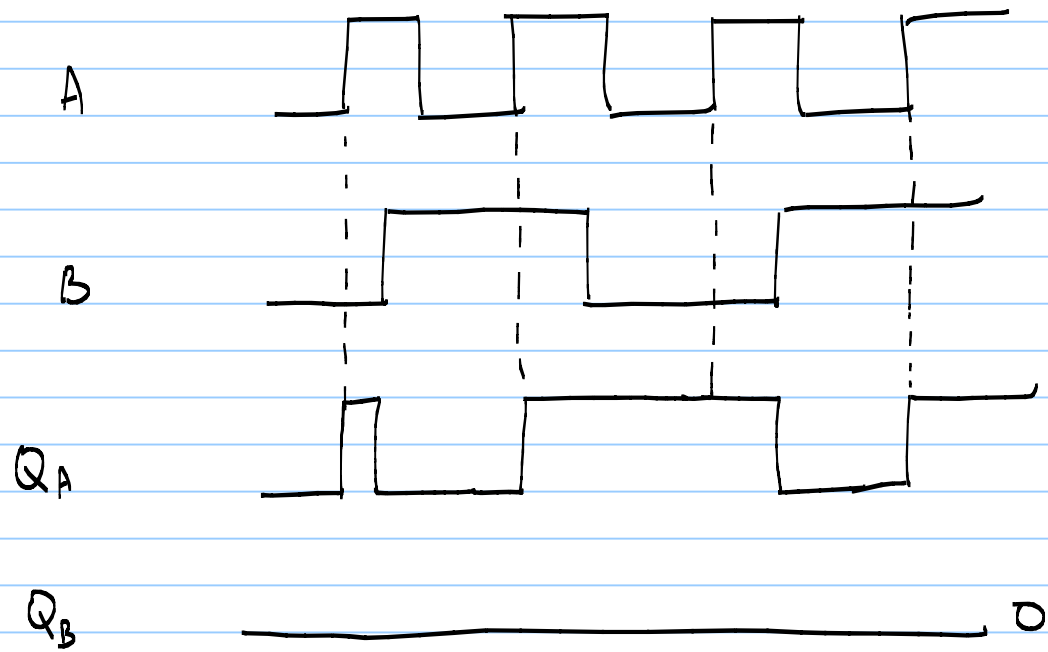

$$V_c(t) = V_{c0} + \text{fundamental } V_{c1}(t) + \text{harmonics } V_{cF}(t)$$


(DC)

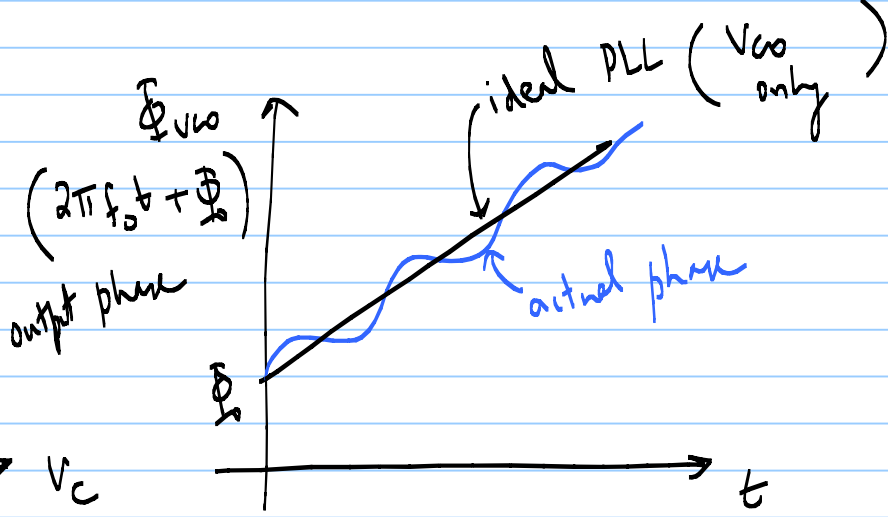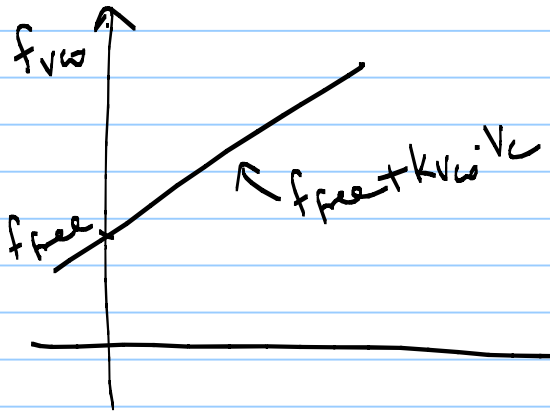→ output freq. will have avg. value = $f_{free} + K_{VCO} \cdot V_{c0}$



instantaneous freq. - dep. on $V_c(t)$
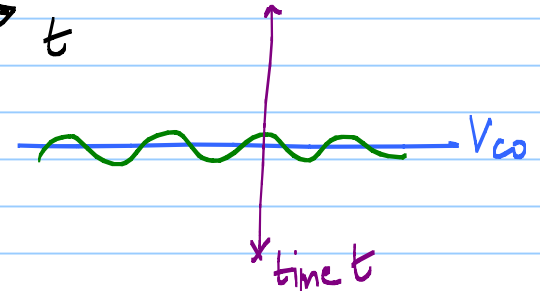
$$\Phi_{VCO} = 2\pi f_{VCO} t + \Phi_0 = \Phi_{out}$$



assume only fundamental exists

$$V_c(t) = V_{co} + v_c(t)$$

$$f_o = f_{vco} = f_{free} + K_{vco} \cdot V_{co} + K_{vco} \cdot v_c(t)$$

PLL output

$$V_o(t) = A \cos(2\pi f_o t + \Phi_o)$$
$$= A \cos \left[2\pi \left(\underbrace{f_{free} + K_{vco} \cdot V_{co}}_{N \cdot f_i} + \int_{-\infty}^t \underbrace{K_{vco} \cdot v_c(t)}_{FM} dt \right) + \Phi_o \right]$$

- e.g. $v_c(t) = a \cos(2\pi f_i t)$


$a = \text{small}$

$$v_o(t) = A \cos\left(2\pi N f_i t + 2\pi K_{VCO} \cdot a \sin(2\pi f_i t) + \Phi_0\right)$$

output components @ $N f_i$; $(N \pm 1) f_i$; $(N \pm k) f_i$

← desired component

VCO
Spectrum

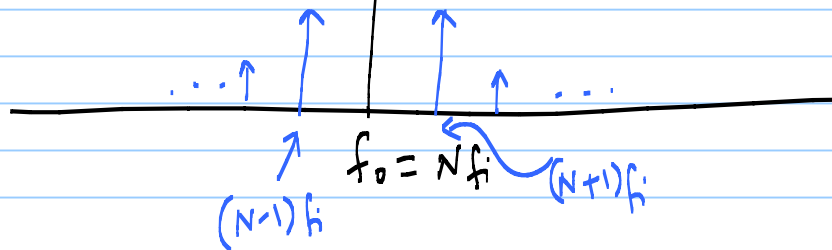

Type-I PLL

output

$(N \pm k) f_i$
 $(k \neq 0)$

} reference
feed through

* filter $V_c(t)$ to give V_{cs} \leftarrow affects ω_n , PM, ...


* Reduce ω_n of loop \leftrightarrow tradeoff loop speed/BW vs. ref. feed through.

* Type I loop is simple, stable

* find use in clocks of digital systems

19/12/23


Lec 28

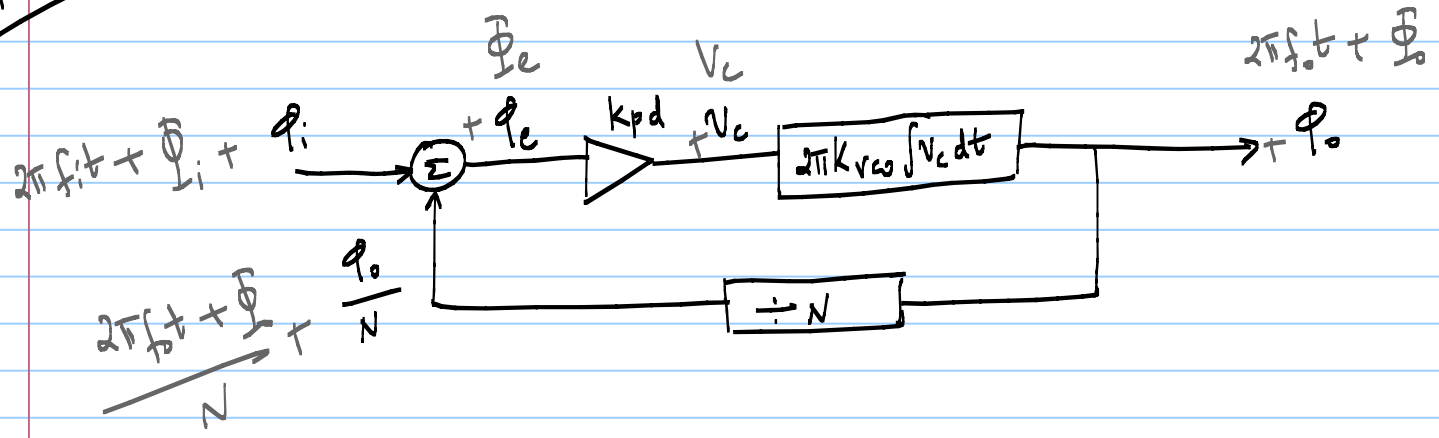

$f_o \neq f_{free}$
 \Downarrow
 $V_c \neq 0$
 \Downarrow
 $\Phi_e \neq 0$
 \Downarrow

$$2\pi f_i t + \Phi_i \neq \frac{2\pi f_i t}{N} + \frac{\Phi_o}{N}$$

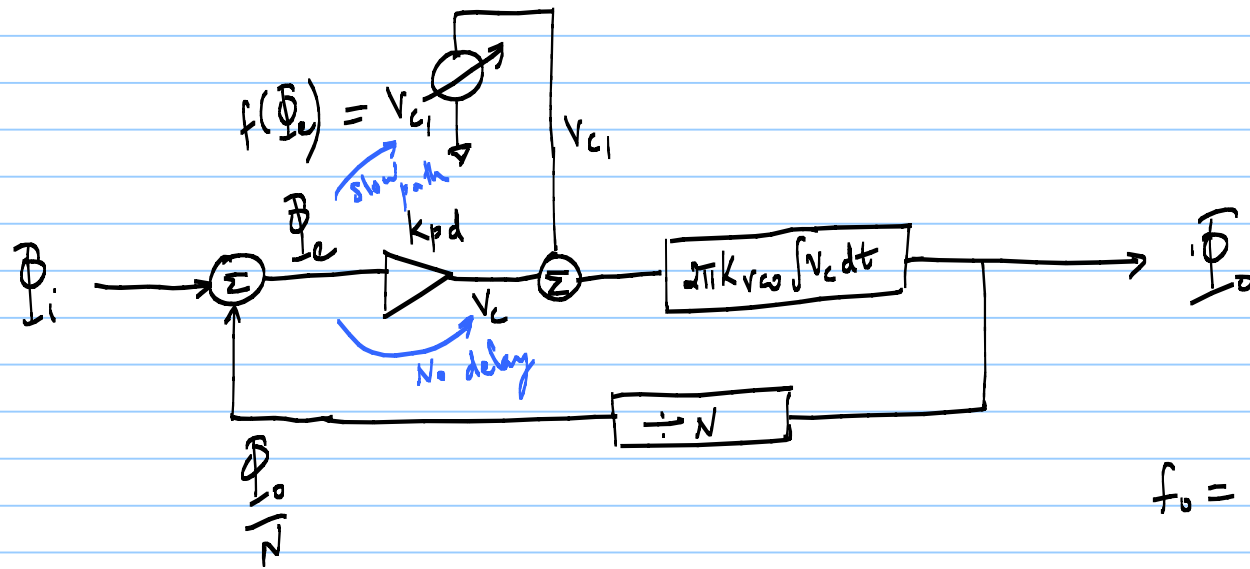
$$\Phi_e = \frac{N f_i - f_{free}}{K_{vco} k_{pd}} \Rightarrow \Phi_e = 0 \text{ only when } N f_i = f_{free}$$




Set V_{c1} so that
 $V_c = 0$ in steady state
 \Downarrow
 $\Phi_e = 0$


$$f_o = f_{free} + K_{vo} \cdot V_{c1} + K_{vo} \cdot V_c$$
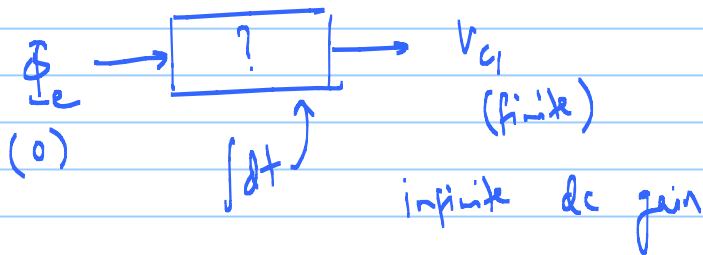
$$V_{c1} = \frac{f_o - f_{free}}{K_{vo}}$$





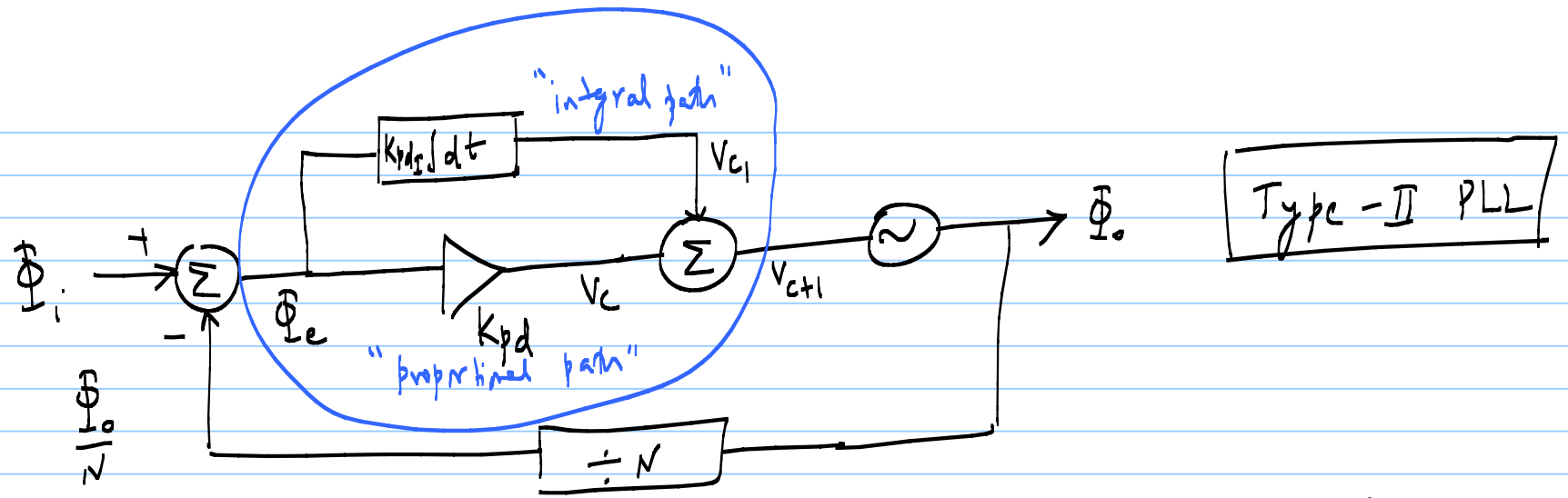


Type-II PLL

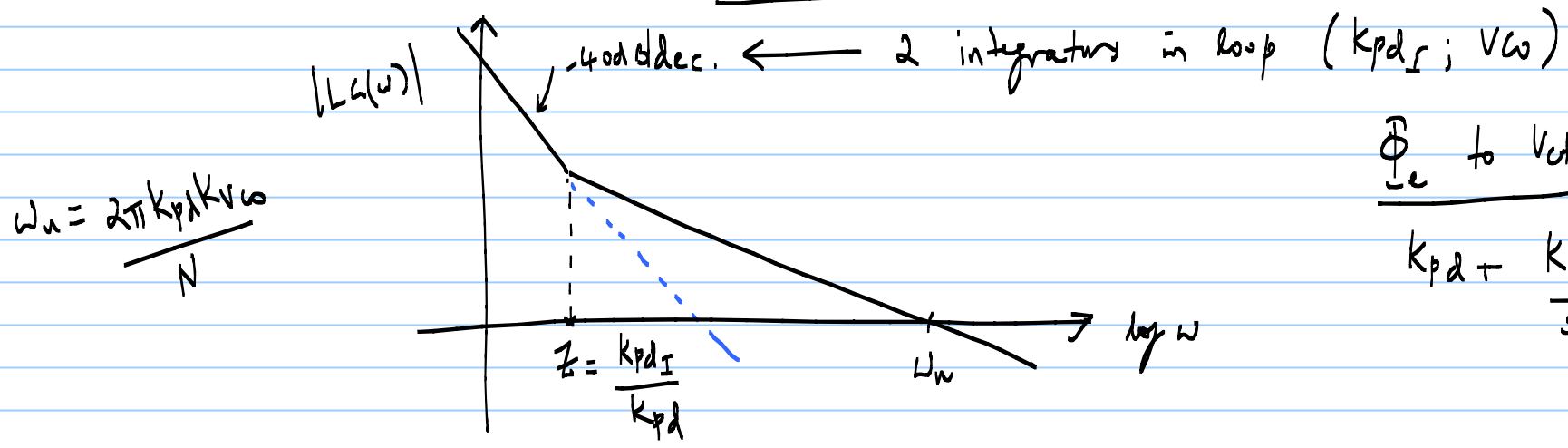
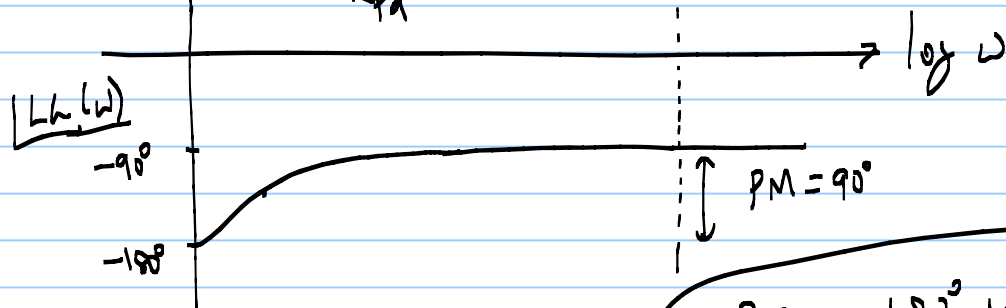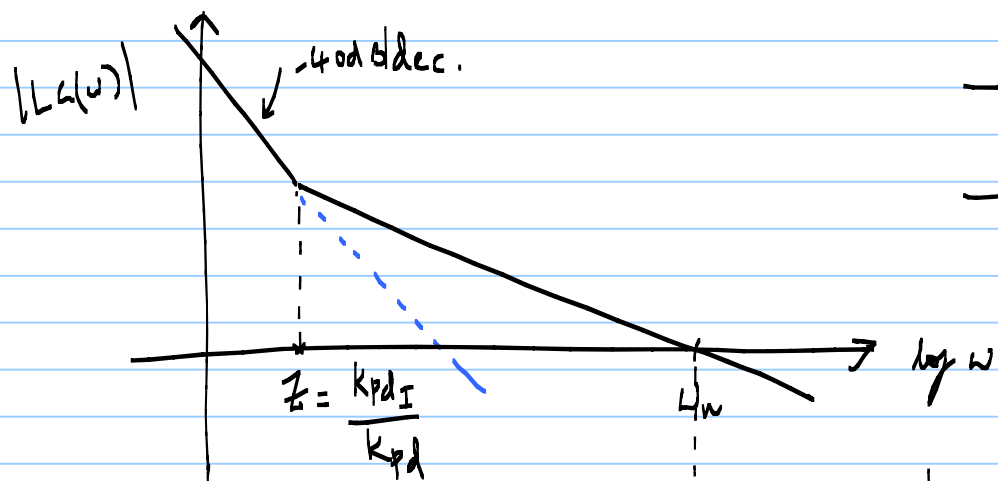
$$\frac{\Phi_e \text{ to } V_{c+I}}{K_{pd} + \frac{K_{pdI}}{s}} = \frac{sK_{pd} + K_{pdI}}{s}$$





$$PM = 180^\circ + |Lh(\omega_n)|$$

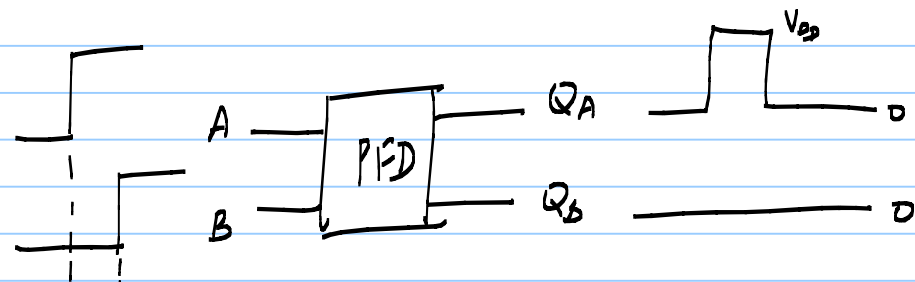





$(Q_A - Q_B) \rightarrow$ represents Φ_e

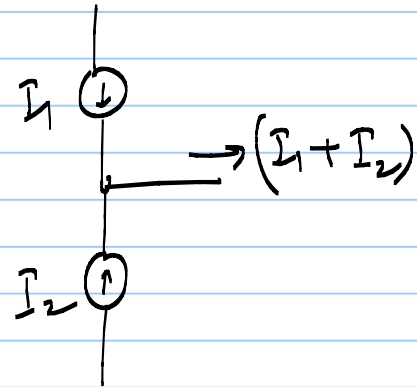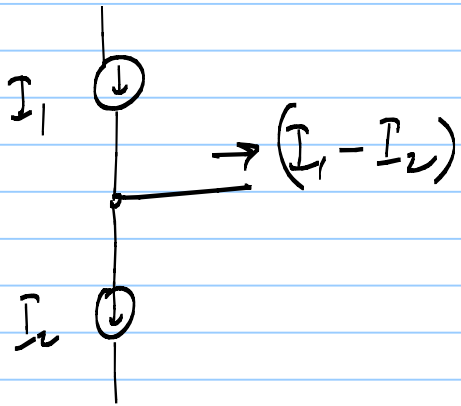
addition & subtraction are most easily done using currents



charge pump




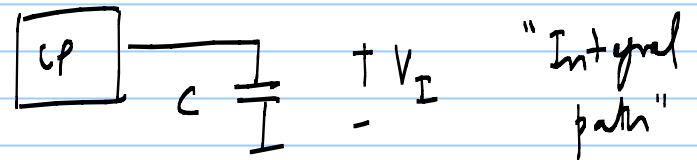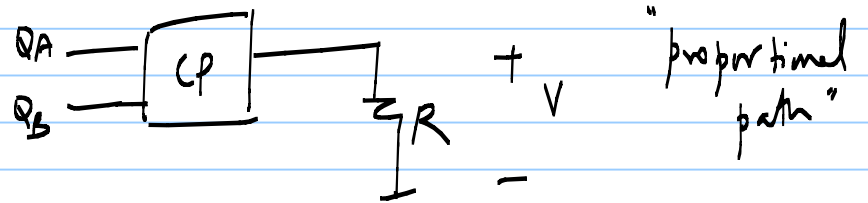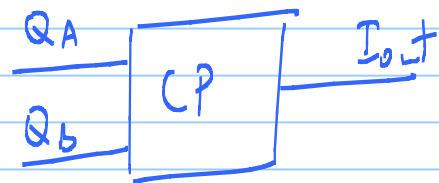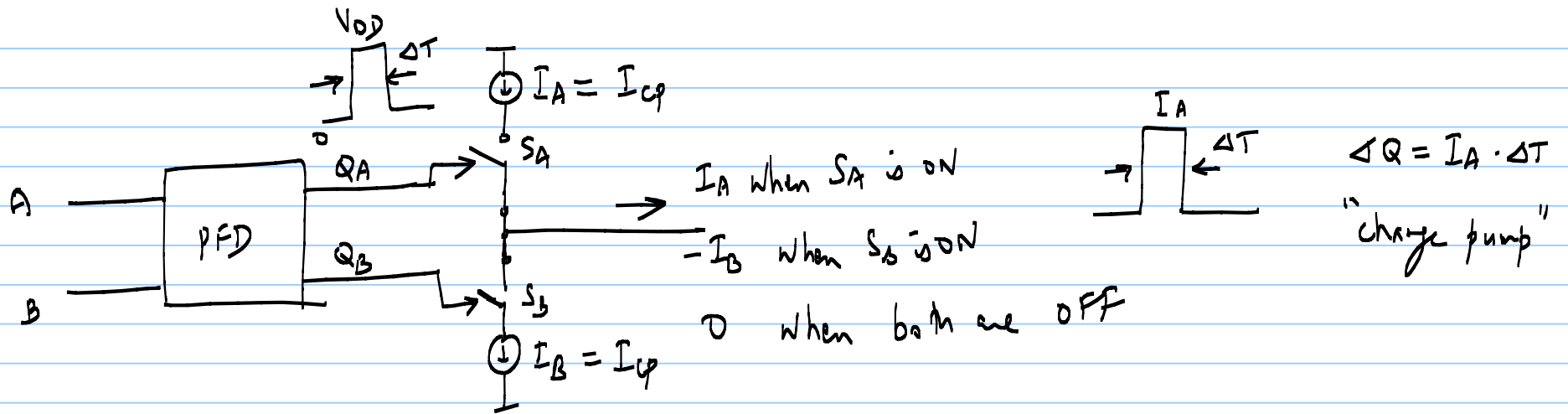

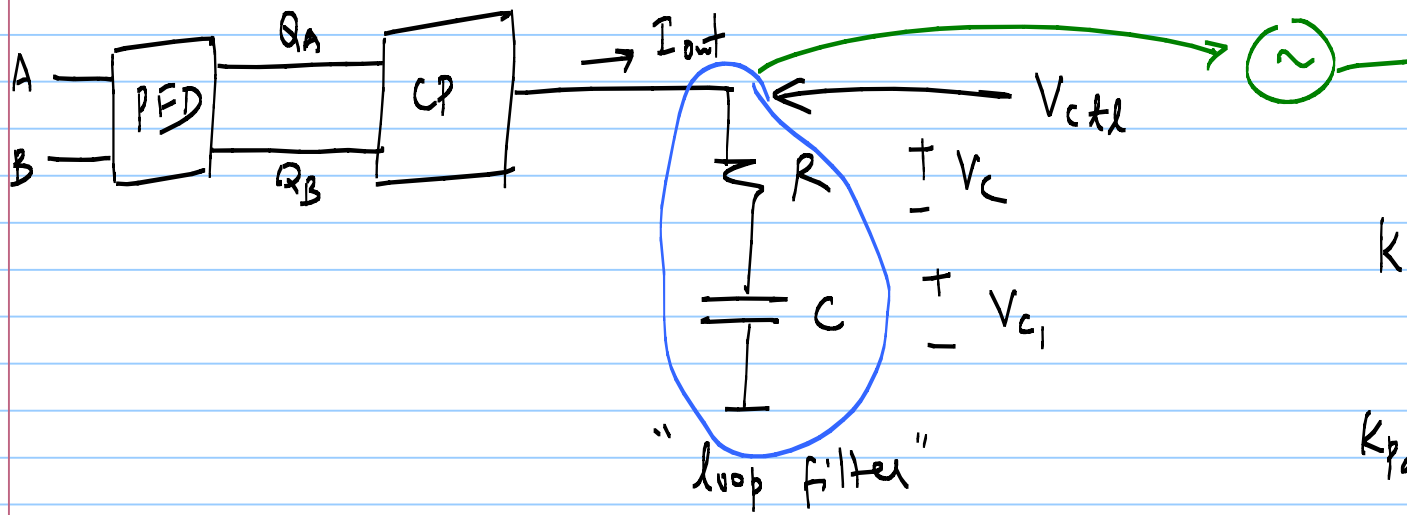



$$K_{pd} = \frac{V_{DD}}{2\pi} \times \frac{I_{cp}}{V_{DD}} \times R = \frac{I_{cp} \cdot R}{2\pi}$$

$$K_{pdI} = \frac{I_{cp}}{2\pi C}$$

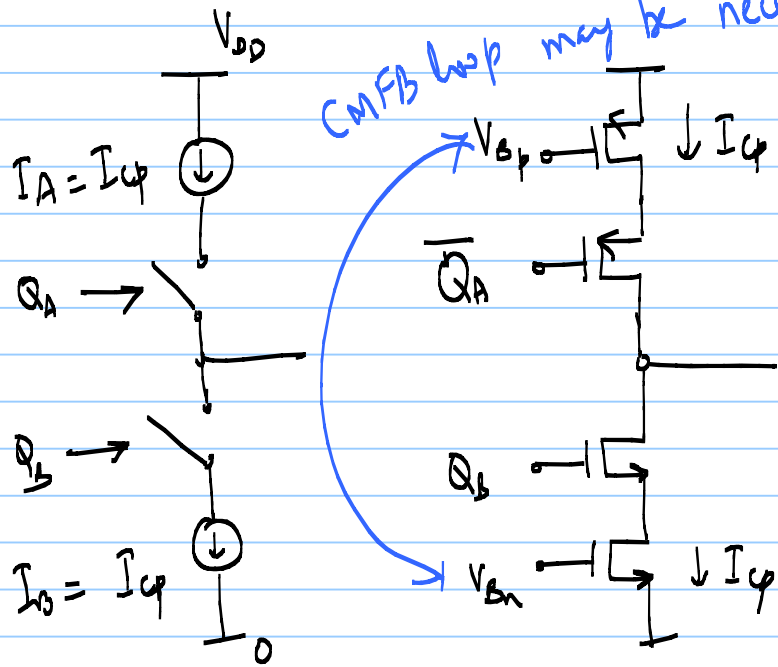

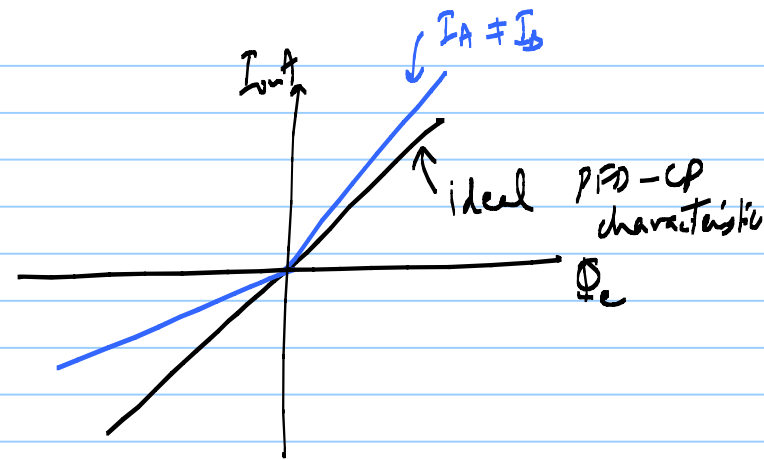CMFB loop may be necessary to set V_{on} & V_{op} properly



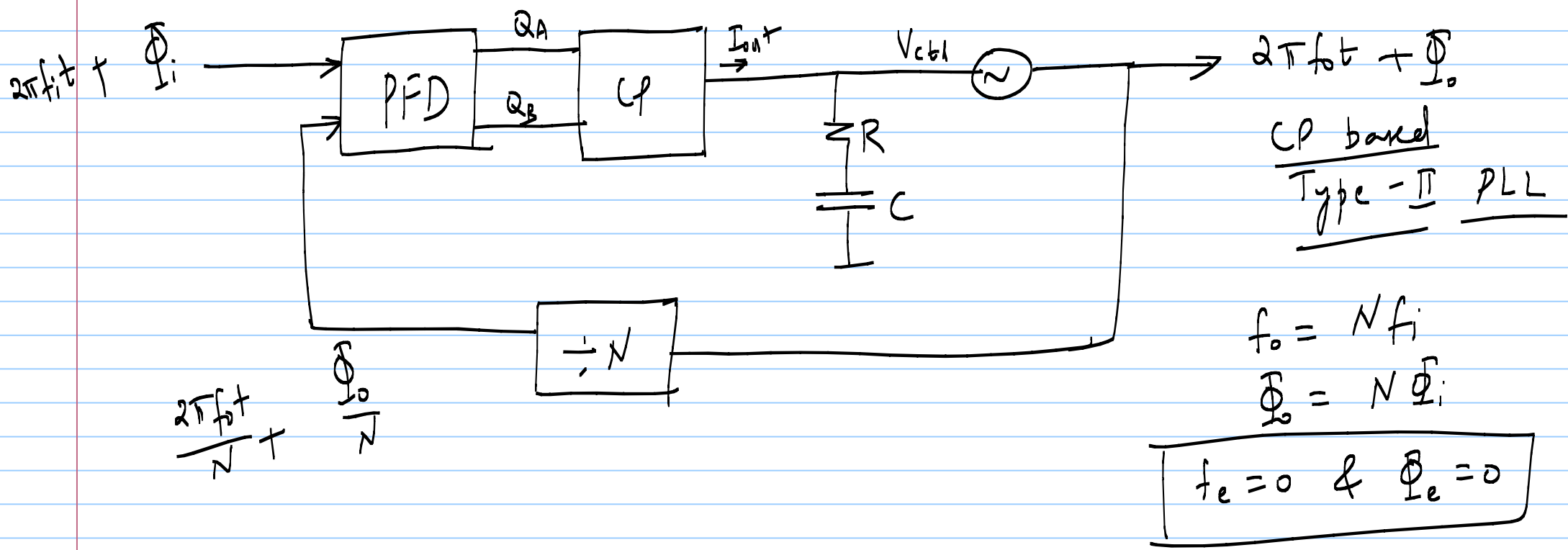

$$f_o = N f_i$$

$$\Phi_o = N \Phi_i$$

$f_e = 0 \ \& \ \Phi_e = 0$

Type-II PLL design example

$$\begin{array}{l} * f_i = 10 \text{ kHz} \\ * f_o = 1 \text{ MHz} \end{array} \quad N = 100$$

$$* \text{Loop BW} = 500 \text{ Hz} \quad \leftarrow f_{-3\text{dB}}$$

$$* K_{VCO} = 500 \text{ kHz/V}$$

$$* \zeta = \frac{1}{\sqrt{2}} = 0.707 \quad \leftarrow ? \text{ PM, settling response}$$

$$L_G(s) = \frac{I_{cp}}{2\pi} \left[R + \frac{1}{sC} \right] \times \frac{2\pi K_{v\omega}}{s} \times \frac{1}{N}$$

$$= \frac{I_{cp} \cdot K_{v\omega} (1 + sCR)}{s^2 NC}$$

$$CL_G(s) = N \times \frac{L_G(s)}{1 + L_G(s)} = N \cdot \frac{I_{cp} \cdot K_{v\omega} (1 + sCR) / s^2 NC}{1 + I_{cp} \cdot K_{v\omega} (1 + sCR) / s^2 NC}$$

$$= N \cdot \frac{I_{cp} \cdot K_{v\omega} (1 + sCR)}{s^2 NC + s \cdot I_{cp} \cdot K_{v\omega} \cdot CR + I_{cp} \cdot K_{v\omega}}$$

$$CLG(s) = N \cdot \frac{\frac{I_{cp} \cdot K_{v\omega}}{NC} (1 + sCR)}{s^2 + s \cdot \frac{I_{cp} \cdot K_{v\omega} \cdot R}{N} + \frac{I_{cp} \cdot K_{v\omega}}{NC}}$$

$$D(s) = s^2 + 2\zeta\omega_n s + \omega_n^2$$

$$\omega_n = \sqrt{\frac{I_{cp} \cdot K_{v\omega}}{NC}} \quad \leftarrow ?$$

$$\zeta = \frac{R}{2} \sqrt{\frac{I_{cp} \cdot K_{v\omega} \cdot C}{N}}$$

$$\omega_{-3dB} = 2\pi \times 500 \text{ rad/s}$$

for a second order system:

$$\omega_{-3dB}^2 = \omega_n^2 \left[(2\zeta^2 + 1) + \sqrt{(2\zeta^2 + 1)^2 + 1} \right]$$

find out ω_n from here

$$(2\pi \times 500)^2 = \omega_n^2 \times (2 + \sqrt{5})$$

$$\omega_n = 1.527 \text{ k rad/s}$$

$$\omega_n = \sqrt{\frac{I_{cp} \cdot K_{vco}}{NC}}$$

K_{vco}, N are known

set I_{cp} via noise constraint

sets $\frac{I_{cp}}{C} = 466.1 \text{ A/F}$

here set $I_{cp} = 10 \mu\text{A} \Rightarrow \boxed{C = 21.5 \text{ nF}}$

$$\xi = \frac{1}{\sqrt{2}}$$

$$\xi = \frac{R}{2} \sqrt{\frac{I_{cp} \cdot K_{vw} \cdot C}{N}} = \frac{1}{\sqrt{2}}$$

$$R = \sqrt{\frac{2N}{I_{cp} \cdot K_{vw} \cdot C}} = 43.1 \text{ k}\Omega$$